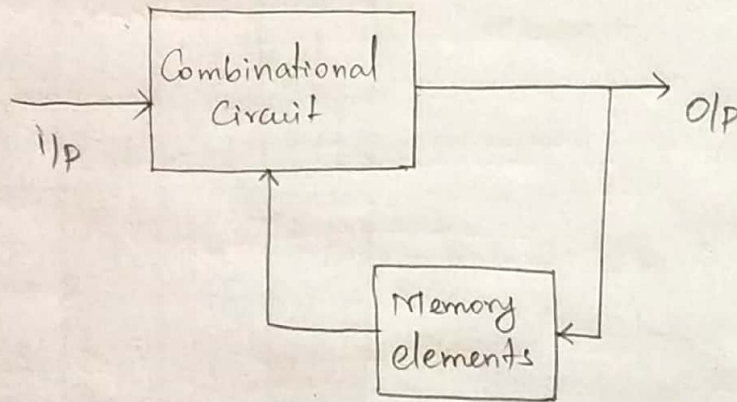


UNIT - III

SYNCHRONOUS SEQUENTIAL CIRCUITS

SEQUENTIAL LOGIC CIRCUITS

The output of a combinational logic depends on the input levels whereas the output of a sequential logic depends on stored levels and also the input levels. A sequential circuit consists of a combinational circuit and a memory element.



The information stored in the memory elements at any given time defines the Present State of the Sequential Circuits. The present State and the inputs determine the next State and the output of the Sequential circuit.

Combinational Circuit

- 1) The output depends on input only.
- 2) Memory elements are not required.
- 3) Combinational Circuits are easy to design.
- 4) These circuits are faster in speed.
- 5) Ex: Parallel adder
Half Adder

Sequential Circuit

- 1) The output depends on Present ip & Past o/p.
- 2) Memory elements are required to store the past outputs.
- 3) These circuits are harder to design.
- 4) These circuits are slower than combinational circuits.
- 5) Ex: Counters
Shift Registers.

There are 2 types of Sequential Circuits.

Asynchronous Sequential Circuits.

In asynchronous sequential circuit the outputs depend upon the order in which its input variables change and can be affected at any instant of time.

Synchronous Sequential Circuits.


In synchronous sequential circuit the outputs depend upon the order in which its input variables change and can be affected at discrete instants of time.

FLIP-FLOPS


It is a sequential device that normally samples its inputs and changes its output only at times determined by clocking signal.

Flip Flops are bistable elements. The main difference between latches and Flip Flops is in the method used for changing their states.


SR FLIP-FLOPS

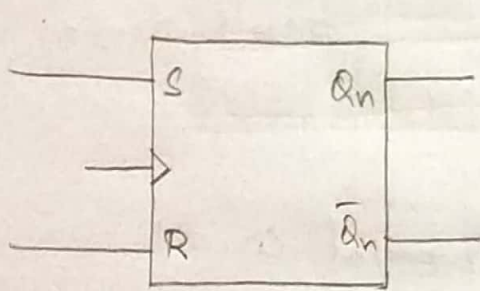

Positive edge triggered

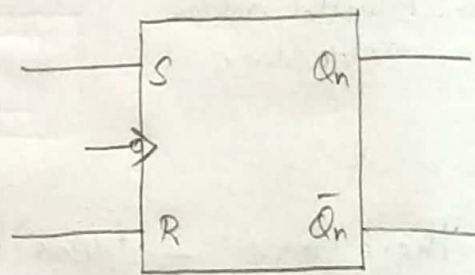

Negative edge triggered

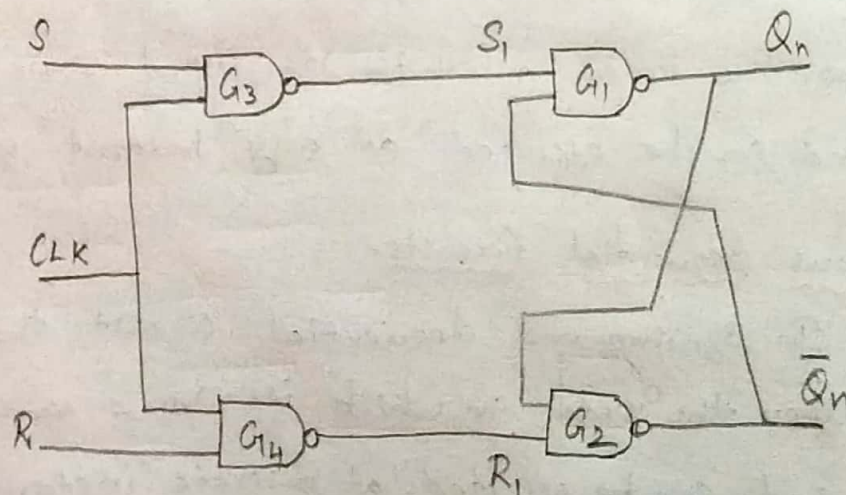

CLK	S	R	Q_n	Q_{n+1}	State
0	x	x	0	0	Nochange
0	x	x	1	1	
↑	0	0	0	0	Nochange
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	x	Indeterminate
↑	1	1	1	x	

S	R	Q_{n+1}	State
0	0	Q_n	Nochange
0	1	0	Reset
1	0	1	Set
1	1	x	Indeterminate

Case(1) when $S=0$ and $R=0$, CLK is +ve.

Assume $Q_n = 1$ $\bar{Q}_n = 0$

So the inputs G_2 are $Q_n = 1$ and $R_1 = 1$

Hence the o/p of G_2 is 0.

Similarly

Input of G_1 are $S_1 = 1$ and $\bar{Q}_n = 0$

Hence the output of G_1 is 1.

\therefore When S & R both are low the output state does not change.

Case(2) when $S=0$ and $R=1$, CLK is +ve.

Assume $Q_n = 1$ $\bar{Q}_n = 0$

$G_2 = 1$ $G_1 = 0$

Case (3): $S=1, R=0$ CLK is +ve
 Assume $Q_n=1, \bar{Q}_n=0$.


$\therefore G_1=1, G_2=0$.

Case (4): $S=1, R=1$ CLK is +ve
 Assume $Q_n=1, \bar{Q}_n=0$


$\therefore G_1=1, G_2=1$.

		Q_{n+1}			
	RQ_n	00	01	11	10
S	0	0	1	0	0
	1	1	1	X	X


$$Q_{n+1} = S + \bar{R}Q_n$$

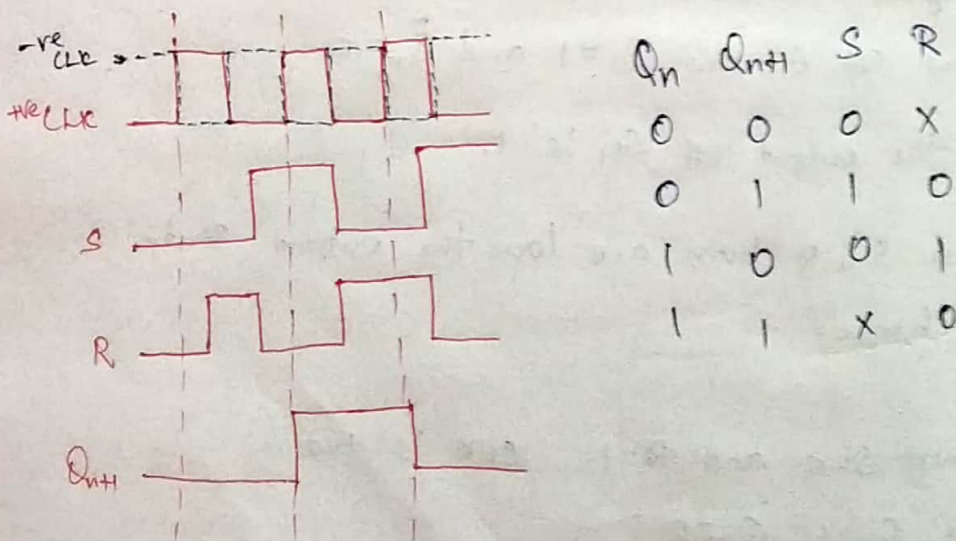

D-FLIP FLOP

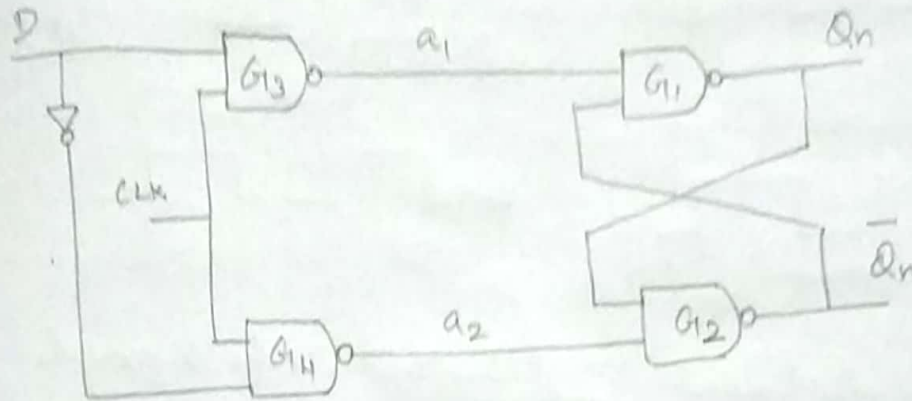

CLK	D	Qn	Qn+1	State
0	x	0	0	Nochange
0	x	1	1	
↑	0	0	0	Reset
↑	0	1	0	
↑	1	0	1	Set
↑	1	1	1	

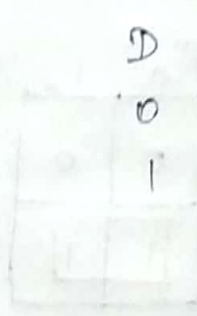

Case 1: When $D=0$, CLK is +ve

Assume $Q_n=1$ $\bar{Q}_n=0$

$$G_1 = Q_n = 0 \quad G_2 = \bar{Q}_n = 1$$

Case 2: When $D=1$, CLK is +ve


Assume $Q_n=1$ $\bar{Q}_n=0$

$$G_1 = Q_n = 1 \quad G_2 = \bar{Q}_n = 0$$


Negative Edge Triggered

Same Truth table.

Qn	Qn+1	D
0	0	0
0	1	1
1	0	0
1	1	1

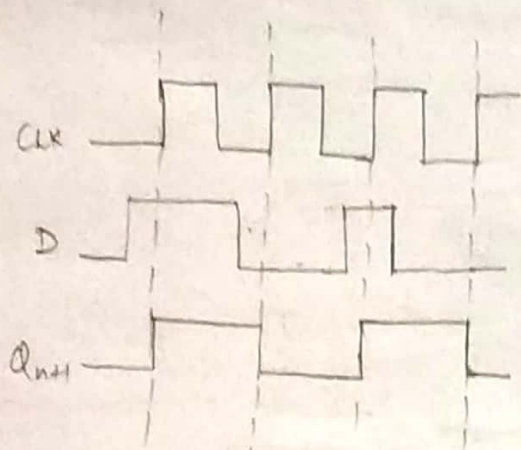

Positive edge triggered

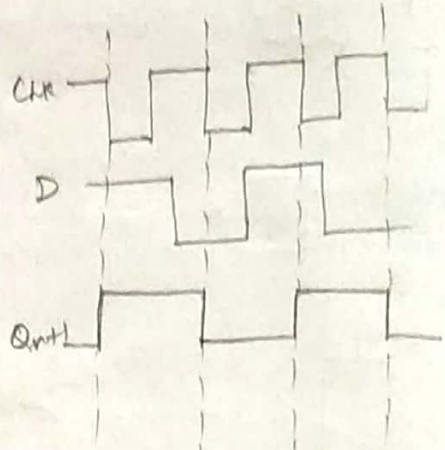


Negative edge triggered.

	Q_n	0	1
D	0	0	0
	1	1	1

$Q_{n+1} = D.$


JK FLIP FLOP

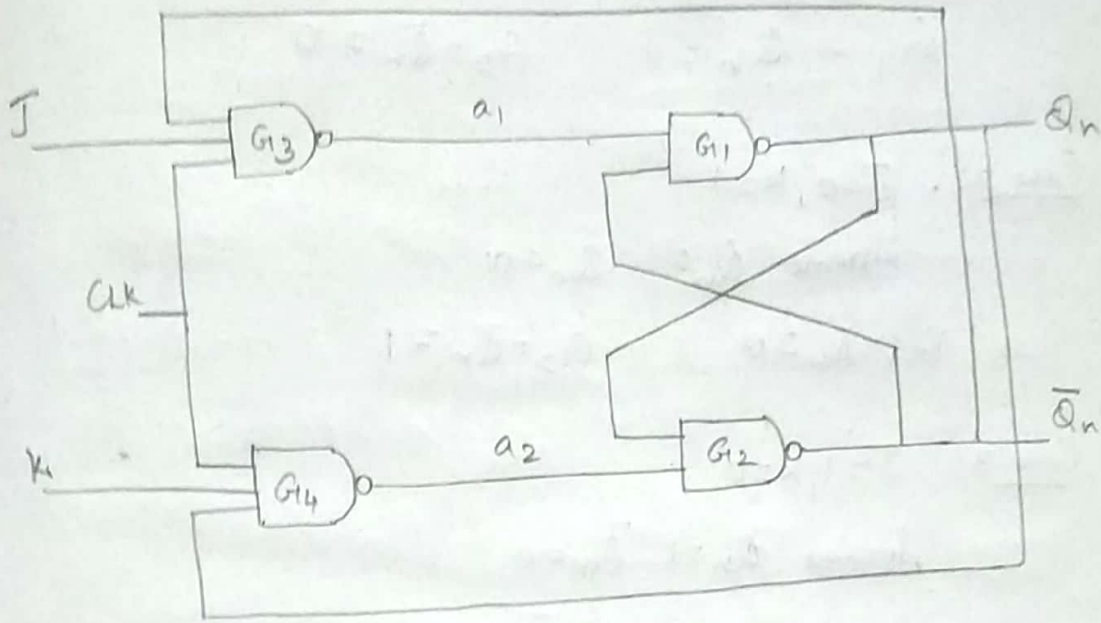

CLK	J	K	Qn	Qn+1	State
0	x	x	0	0	No change
0	x	x	1	1	
↑	0	0	0	0	No change
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	1	Toggles
↑	1	1	1	0	

J	K	Qn+1	State
0	0	Qn	No change
0	1	0	Reset
1	0	1	Set
1	1	\bar{Q}_n	Toggles

K-map: Qn+1

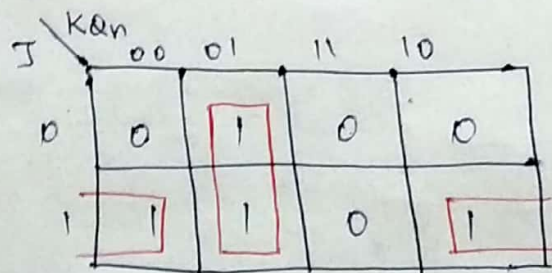

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

Case 1: $J=0, k=0$
Assume $Q_n=1, \bar{Q}_n=0$.

$$G_1 = Q_n = 1 \quad G_2 = \bar{Q}_n = 0$$

Case 2: $J=0, k=1$
Assume $Q_n=1, \bar{Q}_n=0$.

$$G_1 = Q_n = 0 \quad G_2 = \bar{Q}_n = 1$$


Case 3: $J=1, k=0$
Assume $Q_n=1, \bar{Q}_n=0$

$$G_1 = Q_n = 1 \quad G_2 = \bar{Q}_n = 0$$


Case 4: $J=1, k=1$
Assume $Q_n=1, \bar{Q}_n=0$

$$G_1 = Q_n = 0 \quad G_2 = \bar{Q}_n = 1$$

Q_n	Q_{n+1}	J	k
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

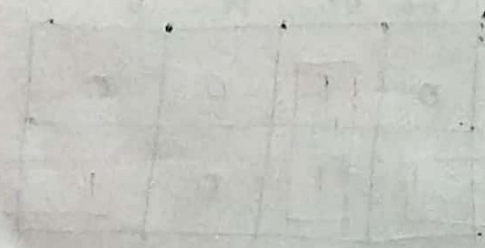

T-FLIP FLOP

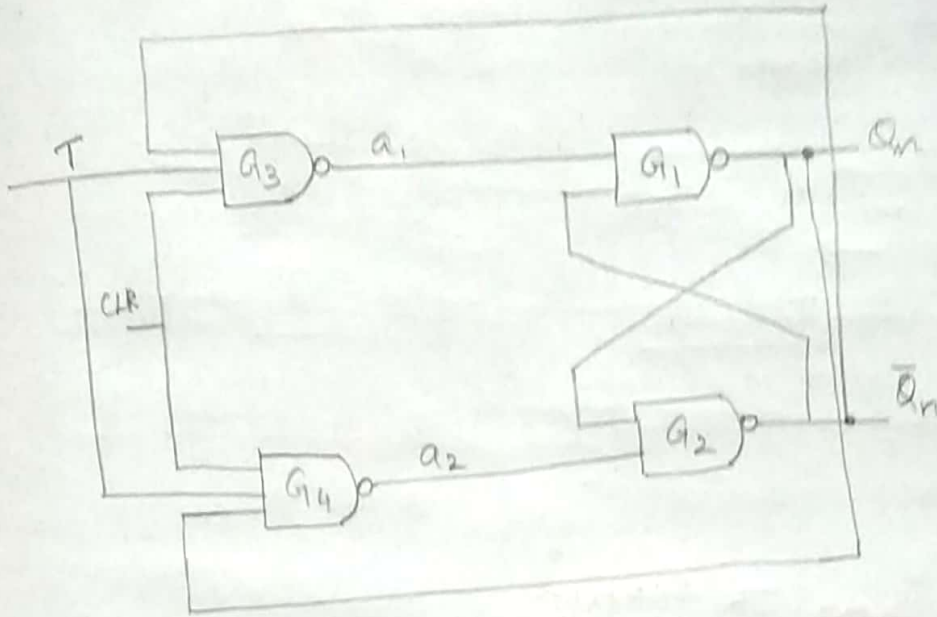

CLK	T	Qn	Qn+1	State
0	x	0	0	No change
0	x	1	1	
↑	0	0	0	No change
↑	0	1	1	
↑	1	0	1	Toggle
↑	1	1	0	

T	Qn+1	State
0	Qn	Nochange
1	\bar{Q}_n	Toggle

T \ Qn	0	1
0	0	1
1	1	0

$$Q_{n+1} = T\bar{Q}_n + \bar{T}Q_n$$

Case (1): $T=0, Q_n=1, \bar{Q}_n=0$

$$G_1 = Q_n = 1$$

$$G_2 = \bar{Q}_n = 0$$

Case (2): $T=1, Q_n=1, \bar{Q}_n=0$

$$G_1 = Q_n = 0$$

$$G_2 = \bar{Q}_n = 1$$

Negative Edge triggered - Same table

Qn	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0