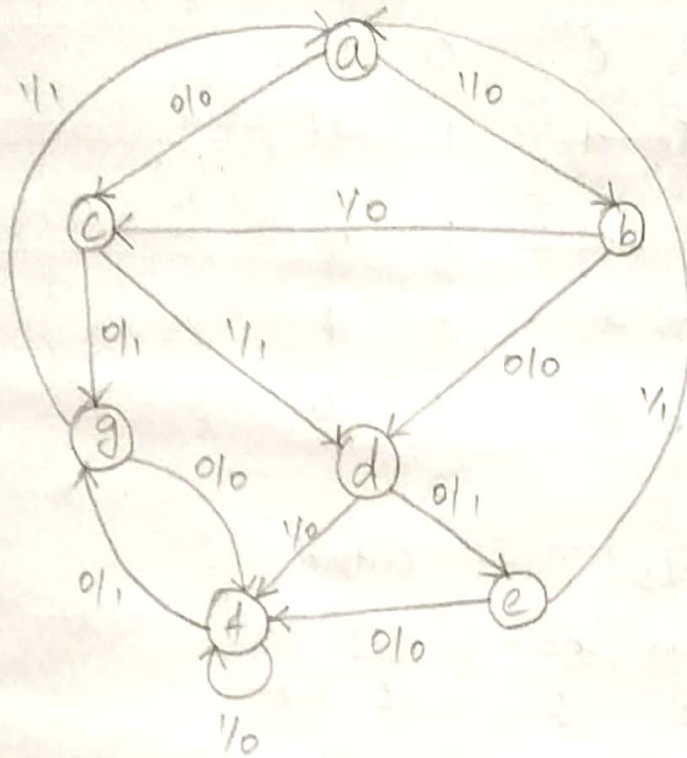


Analysis & Design of clocked Sequential Circuit.

- 1) Design a clocked sequential circuit using D Flip flop for the diagram



Solu:

Let x be the input z be the output

State table

Ps	NS		Output	
	$x=0$	$x=1$	$z=0$	$z=1$
a	c	b	0	0
b	d	c	0	0
c	g	d	1	1
d	e	f	1	0
e	f	a	0	1
f	g	f	1	0
g	f	a	0	1

} Equivalent States

Ps	Ns		Output	
	x=0	x=1	x=0	x=1
a	c	b	0	0
b	d	c	0	0
c	e	d	1	1
d	e	d	1	0
e	d	a	0	1
d	e	d	1	0

Ps	Ns		Output	
	x=0	x=1	x=0	x=1
a	c	b	0	0
b	d	c	0	0
c	e	d	1	1
d	e	d	1	0
e	d	a	0	1

No. of bits required to assign each state must contain 3 bit ($2^3 \geq 5$)

∴ Assign a=000 b=001 c=010 d=011 e=100

Use D Flip Flop excitation table.

A	A'	D _A
0	0	0
0	1	1
1	0	0
1	1	1

PS			Input	NS			FF inputs.			Output
A	B	C	x	A'	B'	C'	D _A	D _B	D _C	Z
0	0	0	0	0	1	0	0	1	0	0
0	0	0	1	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0	1	1	0
0	0	1	1	0	1	0	0	1	0	0
0	1	0	0	1	0	0	1	0	0	1
0	1	0	1	0	1	1	0	1	1	1
0	1	1	0	1	0	0	1	0	0	1
0	1	1	1	0	1	1	0	1	1	0
1	0	0	0	0	1	1	0	1	1	0
1	0	0	1	0	0	0	0	0	0	1

	Cx	D _A			
AB		00	01	11	10
00		0	0	0	0
01		1	0	0	1
11		X	X	X	X
10		0	0	X	X

$D_A = B\bar{x}$

	Cx	D _B			
AB		00	01	11	10
00		1	0	1	1
01		0	1	1	0
11		X	X	X	X
10		1	0	X	X

$D_B = Bx + Cx + \bar{B}\bar{x}$

D_c

$AB \backslash Cx$				
	0	1	0	1
	0	1	1	0
	X	X	X	X
	1	0	X	X

Z

$AB \backslash Cx$				
	0	0	0	0
	1	1	0	1
	X	X	X	X
	0	1	X	X

$$D_c = A\bar{C}\bar{x} + Bx + \bar{A}\bar{C}x + \bar{B}Cx$$

$$Z = Ax + B\bar{x} + B\bar{C}$$

