

# **SNS COLLEGE OF ENGINEERING**

**Coimbatore**

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC  
with 'A' Grade

Approved by AICTE, New Delhi & Affiliated to Anna  
University, Chennai

## **DEPARTMENT OF ELECTRONICS & ELECTRONICS ENGINEERING**


### **ELECTRICAL ENGINEERING & INSTRUMENTATION**

II YEAR/ III SEMESTER

#### **UNIT 2 – TRANSFORMERS**

#### **TOPIC 4 – EQUIVALENT CIRCUIT OF TRANSFORMER**

# IDEAL TRANSFORMER ON NO LOAD

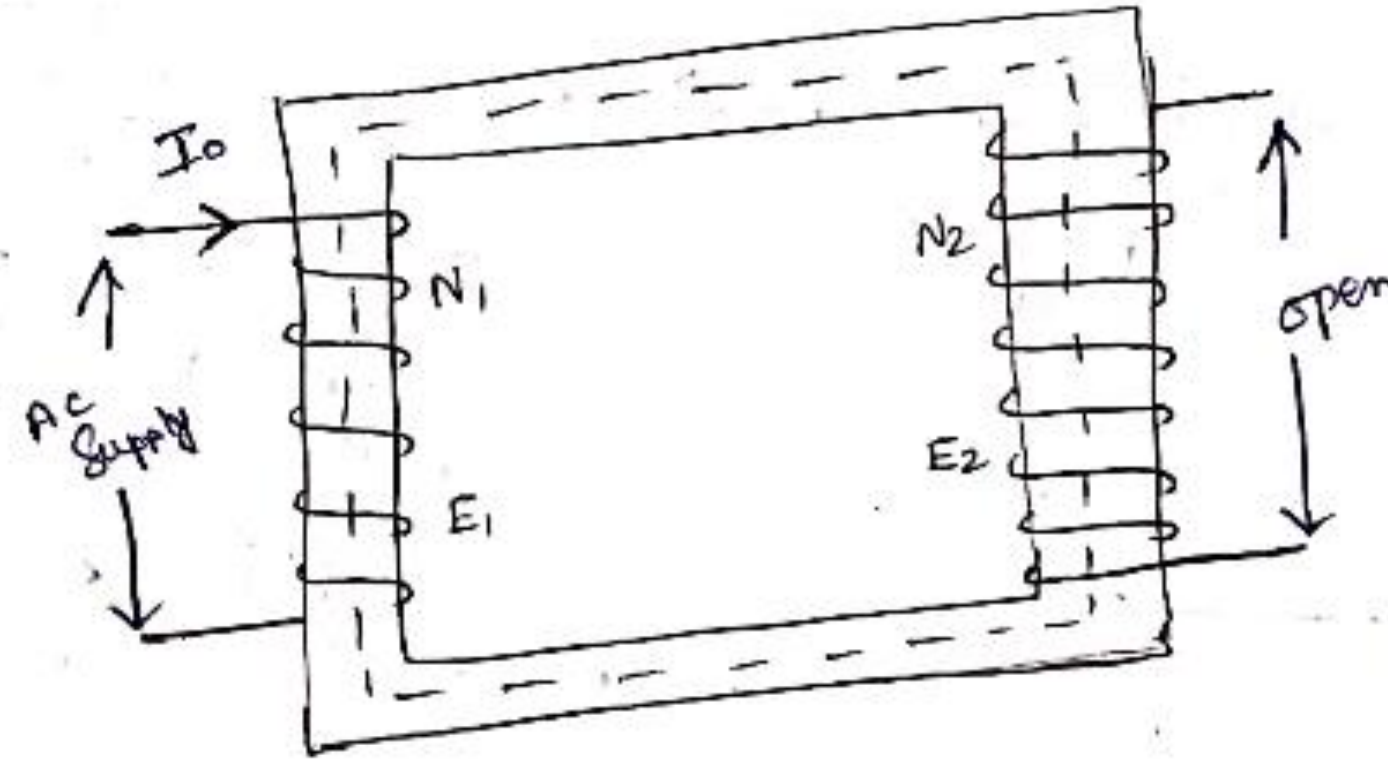

No load current  
2 to 10% of  
rated current

$I_0$  - No load current

Losses:

- \* Core loss

- \* Copper loss

In secondary - 0  
 $\Phi$  will be lesser  
in primary winding

$I_0$  is divided as

$I_w$  - Working Component Current or Active Current.


$I_M$  - Magnetizing Current or reactive Current.

$V_1$  - Supply voltage

$E_1, E_2$  = Rms value of primary & Secondary voltage.

# IDEAL TRANSFORMER ON NO LOAD

PHASOR DIAGRAM:-

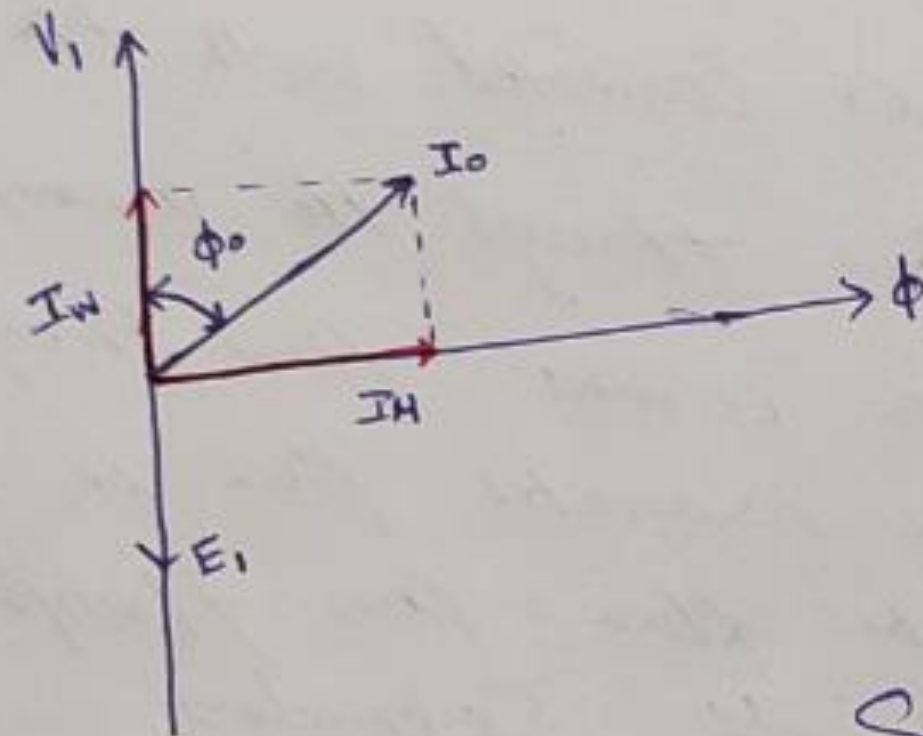

From the phasor diagram

$$\cos \phi_0 = \frac{I_w}{I_0}$$

$$I_w = I_0 \cos \phi_0 \rightarrow (1)$$

$$\sin \phi_0 = \frac{I_H}{I_0}$$

$$I_H = I_0 \sin \phi_0 \rightarrow (2)$$

Square and add eqn (1) & (2)


$$I_w^2 + I_H^2 = I_0^2 \cos^2 \phi_0 + I_0^2 \sin^2 \phi_0$$

$$= I_0^2 (\cos^2 \phi_0 + \sin^2 \phi_0)$$


$$= I_0^2$$

$$\therefore I_0 = \sqrt{I_w^2 + I_H^2}$$

# IDEAL TRANSFORMER ON LOAD

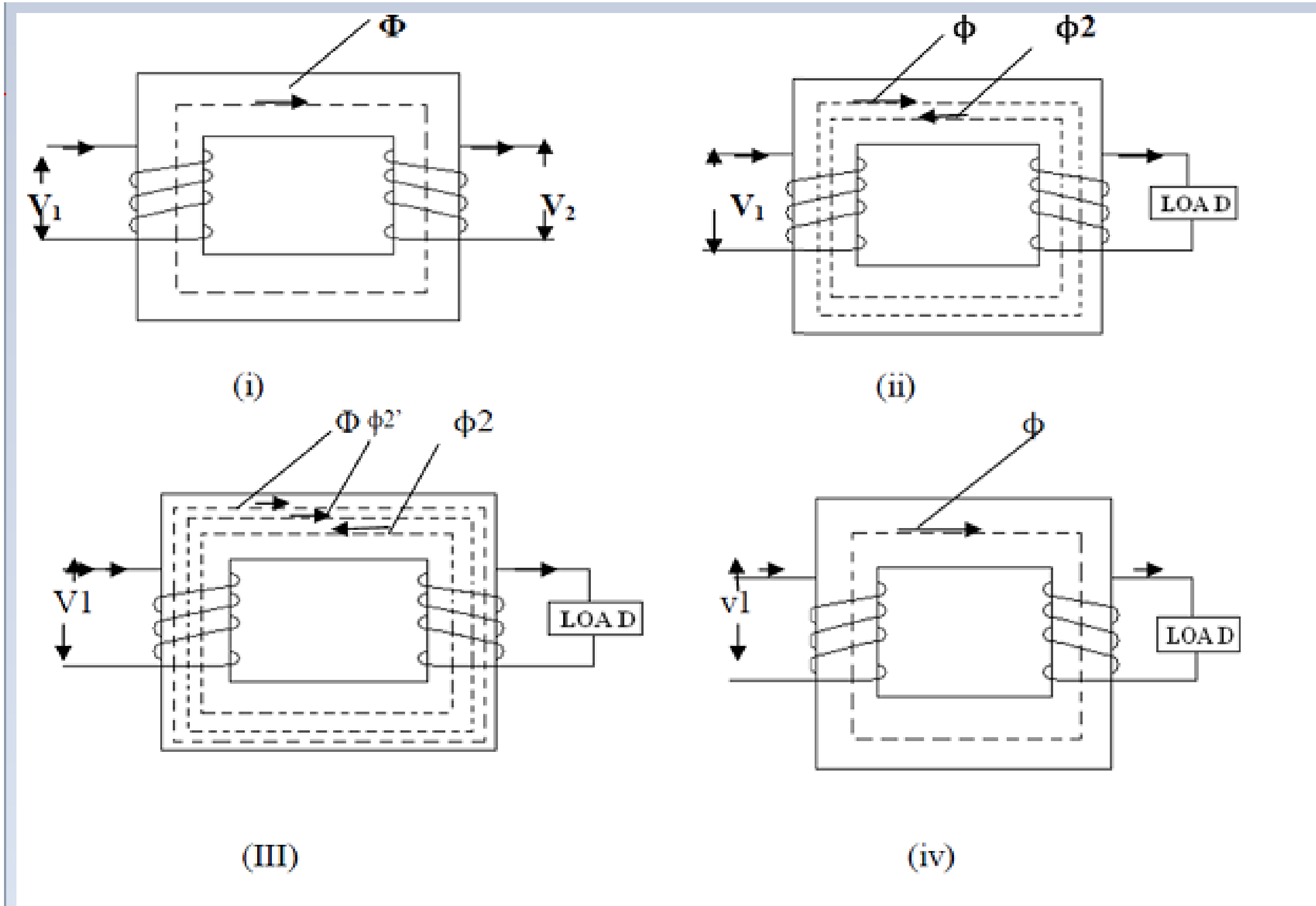

# EQUIVALENT CIRCUIT OF TRANSFORMER

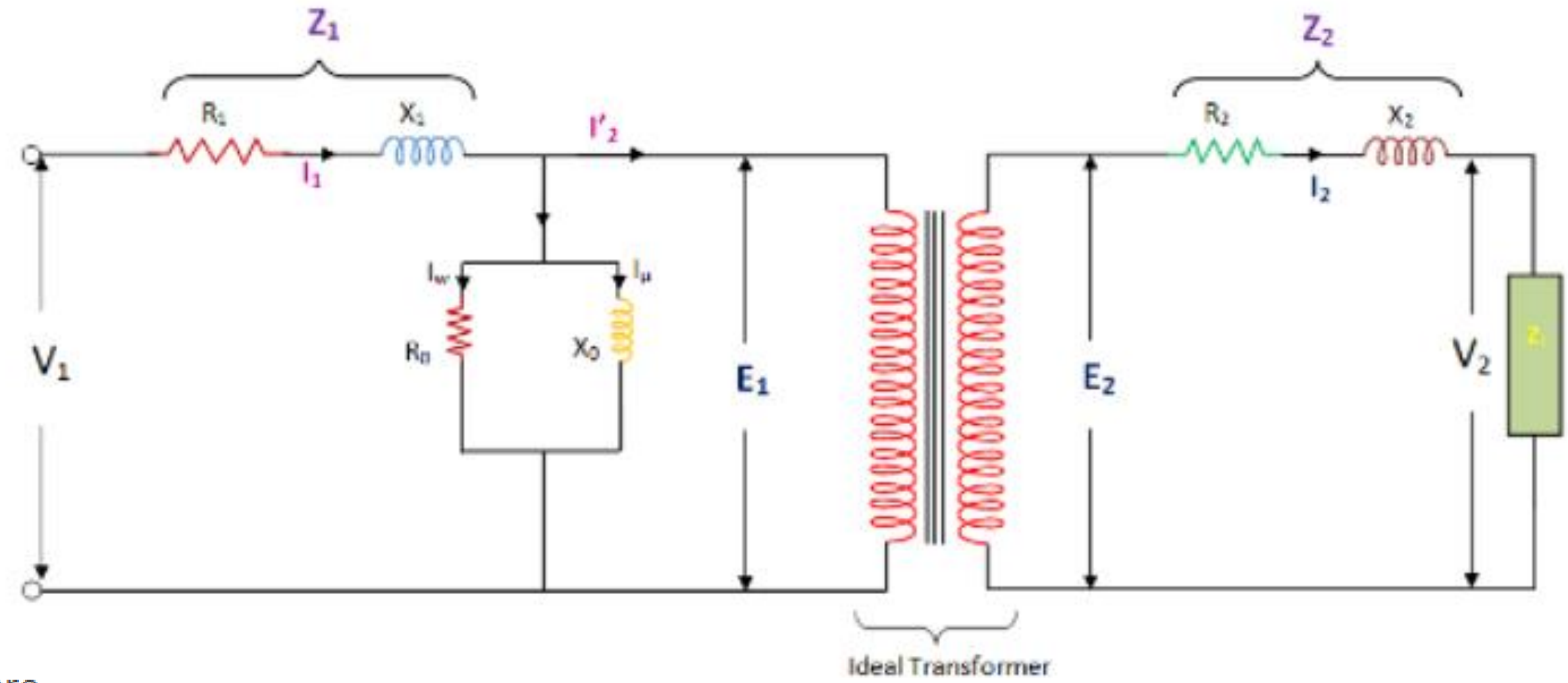

Where,

$R_1$  = Primary Winding Resistance.


$R_2$  = Secondary winding Resistance.

$I_0$  = No-load current.


$I_\mu$  = Magnetizing Component,

$I_w$  = Working Component,

# EQUIVALENT CIRCUIT OF TRANSFORMER

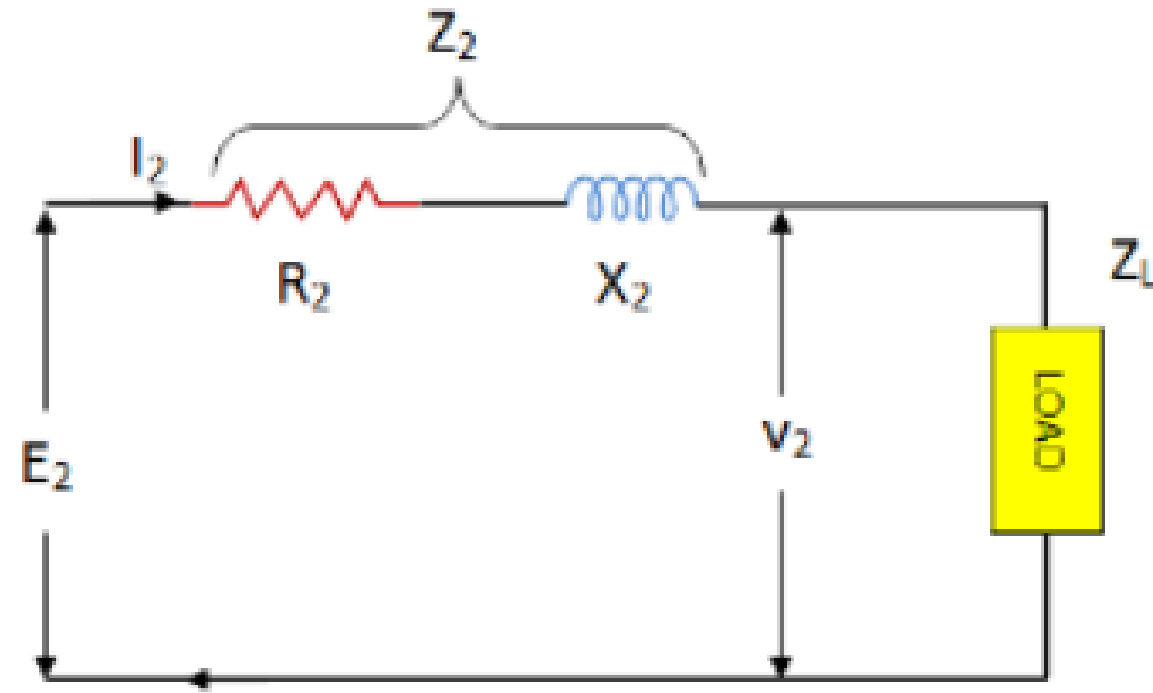

**SECONDARY CIRCUIT**

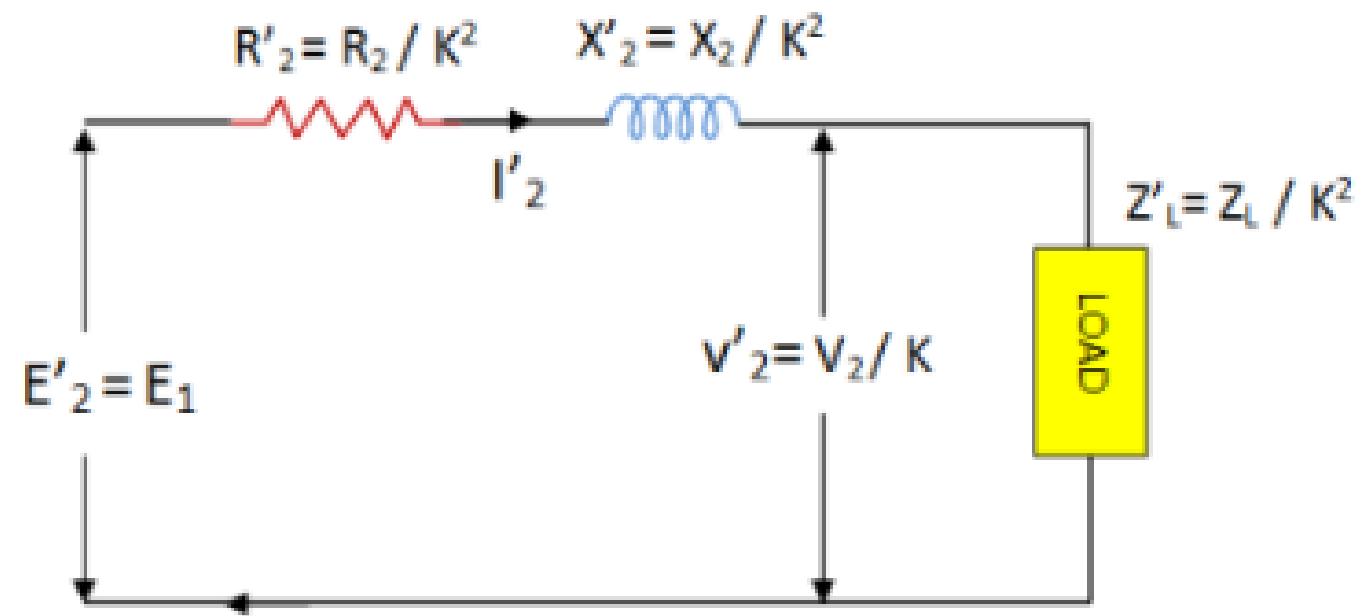

**SECONDARY CIRCUIT EQUIVALENT PRIMARY VALUE**


- Transferring resistance or reactance from primary to secondary, multiply it by  $K^2$
- Transferring resistance or reactance from secondary to primary, divide it by  $K^2$
- Transferring voltage or current from one winding to other, only  $K$  is used By EMF Eqn

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$


$$E_1 = 4.44 f N_1 \Phi_m$$

$$E_2 = 4.44 f N_2 \Phi_m$$

# EQUIVALENT CIRCUIT OF TRANSFORMER

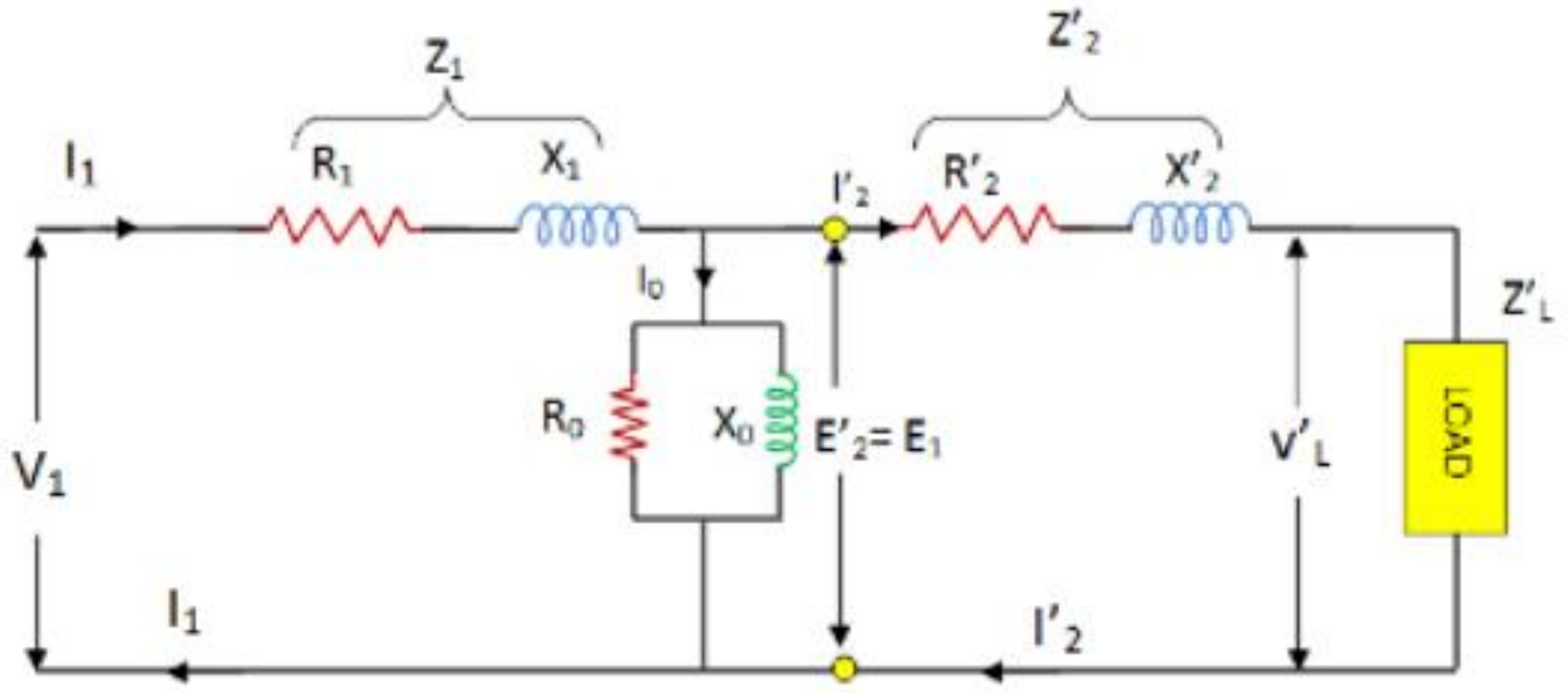


# EQUIVALENT CIRCUIT OF TRANSFORMER

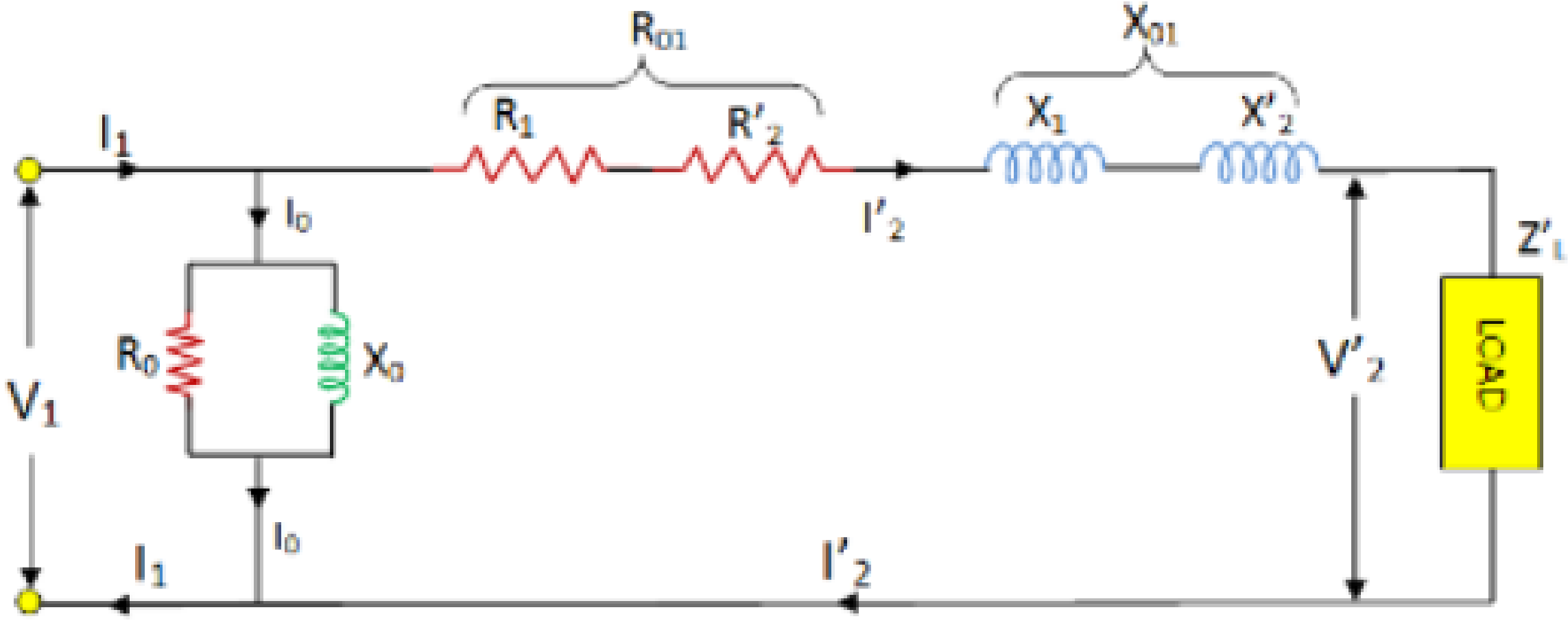


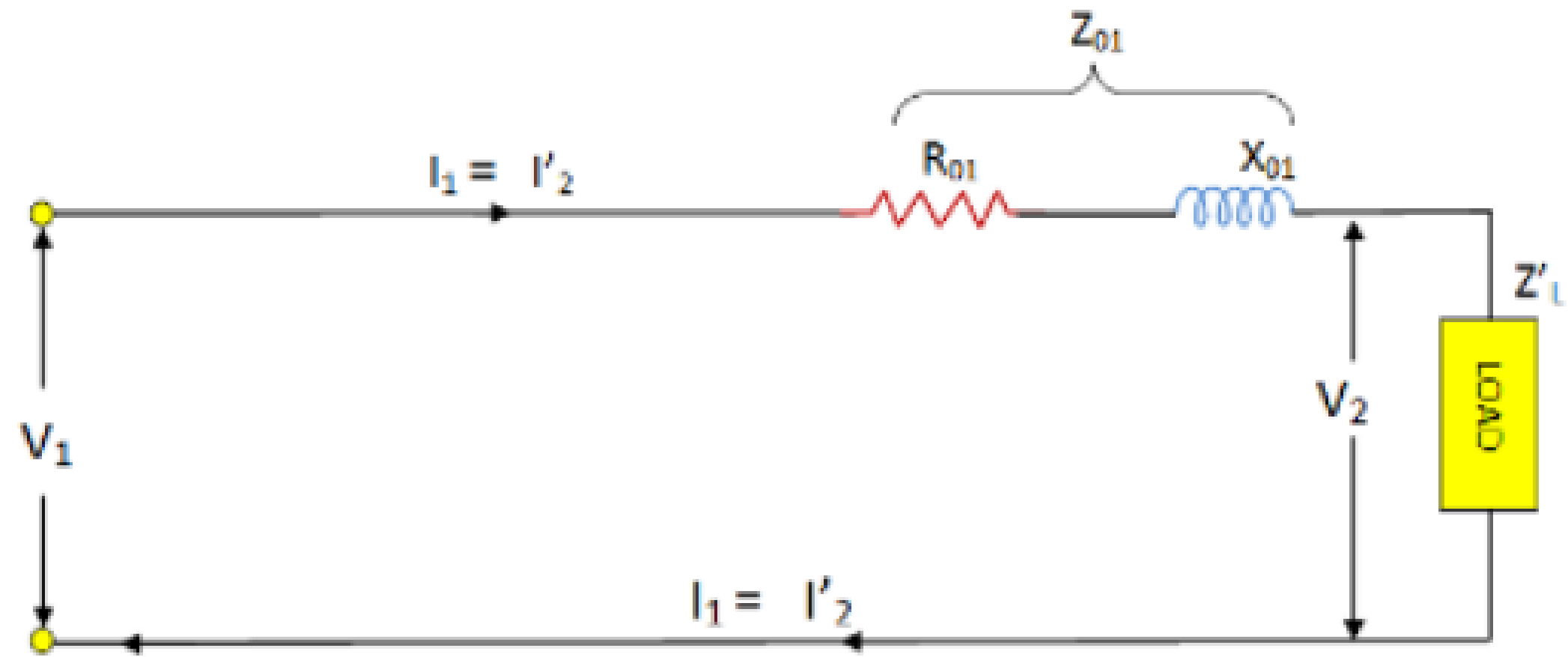
# SIMPLIFIED EQUIVALENT CIRCUIT OF TRANSFORMER



# VOLTAGE REGULATION OF TRANSFORMER

The voltage regulation of a transformer is the arithmetic difference between the no – load secondary voltage ( $E_2$ ) and the secondary voltage on load expressed as percentage of no – load voltage.

$$\% R = \frac{E_2 - V_2}{V_2} \times 100$$

The ratio  $(E_2 - V_2)/V_2$  is called per unit regulation.

$E_2 =$  no load secondary voltage =  $KV_1$

$V_2 =$  secondary voltage on load

The secondary voltage also depends on the power factor of the load

$V_2 < E_2$  - lagging power factor - '+ve Regulation

$E_2 < V_2$  - leading power factor - '-ve Regulation


## EXPRESSION FOR VOLTAGE REGULATION

$$\% R = \frac{E_2 - V_2}{V_2} \times 100 = \frac{\text{Total voltage drop}}{V_2} \times 100$$

By using the expression of voltage drop from approximate voltage drop

$$\text{Total voltage drop} = I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi.$$

Substitute in above we get

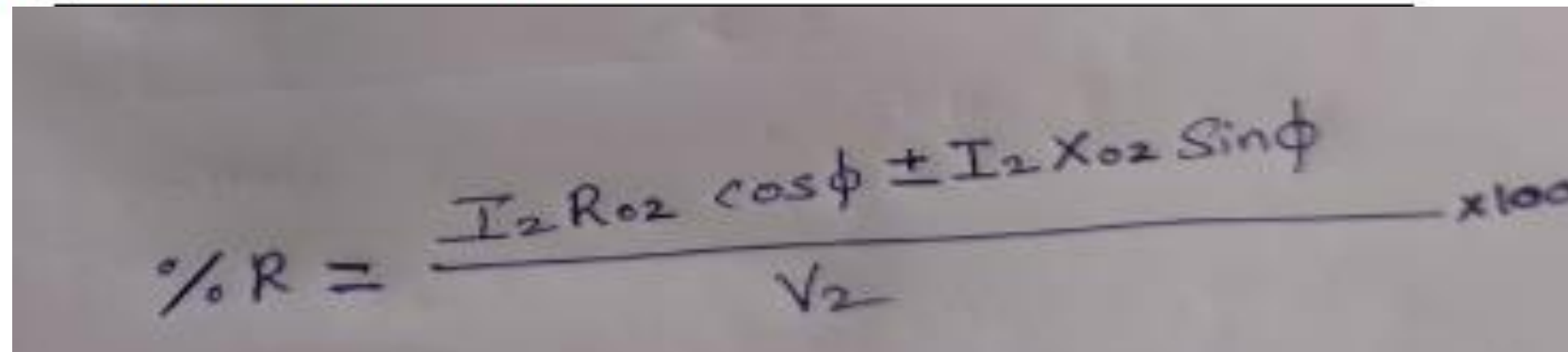

$$\% R = \frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \times 100$$

Note:

‘+’ve – sign for lagging power factor

‘-’ve - sign for leading power factor

# EFFICIENCY OF TRANSFORMER

## Efficiency of a Transformer

Like any other electrical machine, the efficiency of a transformer is defined as the ratio of output power (in watts or kW) to input power (watts or kW) i.e.,

$$\text{Power output} = \text{power input} - \text{Total losses}$$

$$\begin{aligned} \text{Power input} &= \text{power output} + \text{Total losses} \\ &= \text{power output} + P_i + P_{cu} \end{aligned}$$

$$\text{Efficiency} = \frac{\text{power output}}{\text{power input}}$$

$$\text{Efficiency} = \frac{\text{power output}}{\text{power input} + P_i + P_{cu}}$$

Power output =  $V_2 I_2 \cos \phi$ ,  $\cos \phi$  = load power factor

Transformer supplies full load of current  $I_2$  and with terminal voltage  $V_2$

$P_{cu}$  = copper losses on full load =  $I_2^2 R_{2e}$

➤ **IN ELECTRICAL MACHINE EFFICIENCY:99% IS COMMON AT SAFER OPERATING CONDITIONS**

# EFFICIENCY OF TRANSFORMER

$$\text{EFFICIENCY} = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_i + I_2^2 R_{02}}$$

$V_2 I_2 = \text{VA rating of a transformer}$

$$\text{EFFICIENCY} = \frac{(\text{VA rating}) \times \cos \phi}{(\text{VA rating}) \times \cos \phi + P_i + I_2^2 R_{02}}$$

This is full load efficiency and  $I_2 = \text{full load current}$ .

We can now find the full-load efficiency of the transformer at any p.f. without actually loading the transformer.

➤ **TRANSFORMER FAILURE RATE IN INDIA IS 20% .WERE IT SHOULD BE ONLY 4%**

*Thank  
You*