

## UNIT - II

### TRANSISTORS

Transistor is a three terminal semiconductor device.

#### Bipolar Junction Transistor (BJT):-

- \* BJT is a three terminal semiconductor device.
- \* It will operate depend on the interaction of both majority and minority carriers.
- \* Hence the name Bipolar.
- \* It is used in amplifier circuits.



Construction :-

Two types of BJT.

- \* NPN transistor
- \* PNP "



Three terminals are

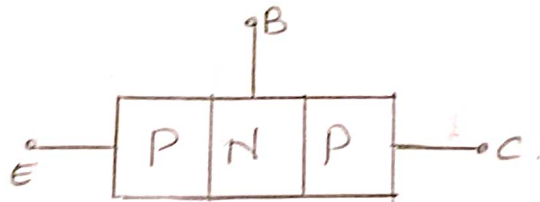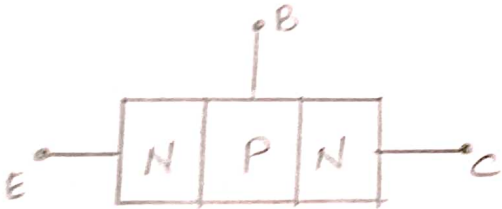- \* Emitter (E)
- \* Base (B)
- \* Collector (C).



- \* Emitter is heavily doped, so that it can inject large number of charge carriers into the base.
- \* Base is lightly doped and very thin.
- \* Collector is moderately doped.



Circuit Symbol :-

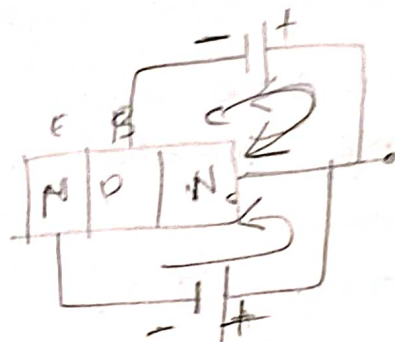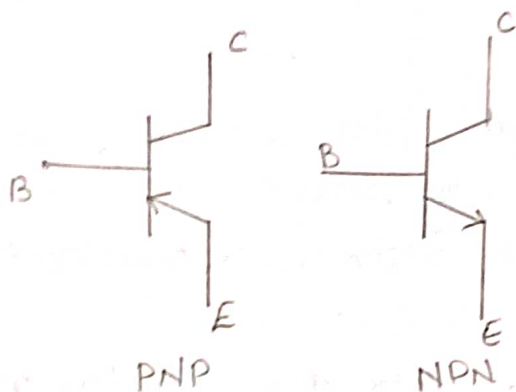

Transistor Biasing :-

There are two types of biasing they are

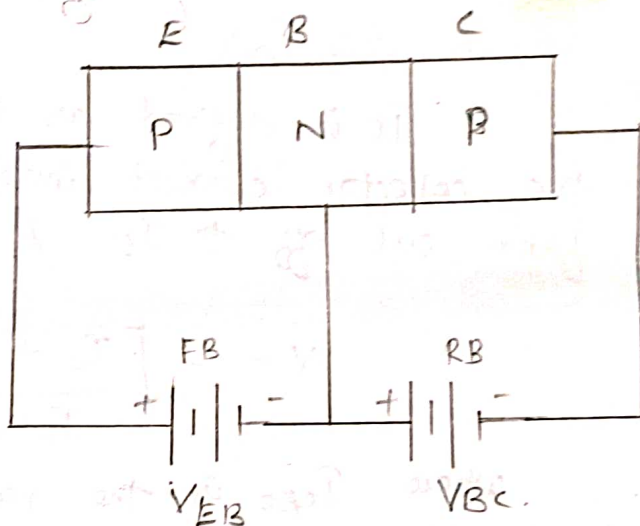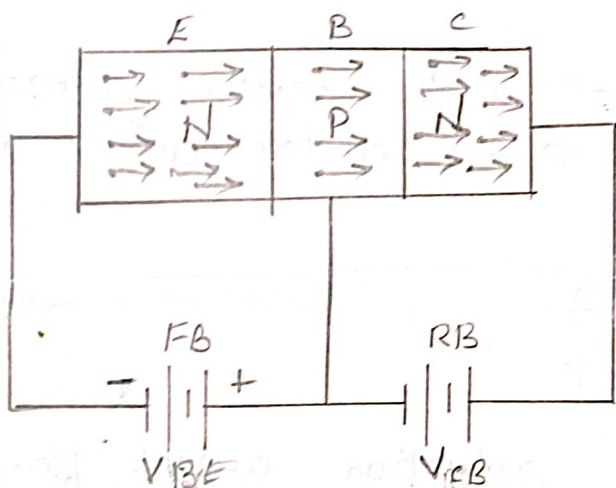- \* Forward biasing
- \* Reverse biasing



Operation of NPN :-

The forward bias is applied to the emitter base junction of NPN transistor. causes lot of electrons from the emitter region to cross over to the base region.

As the base is lightly doped, the number of holes in base region is very small and hence electron combine will also be small.

The remaining electrons cross over to the collector region to constitute a collector current  $I_c$ .

$$I_E = I_B + I_C$$



PNP Operation:  
 The forward bias is applied to emitter-base junction of PNP transistor causes lot of holes from the emitter region to the base region.

The base region is lightly doped with electrons, so the holes combined will also be very slow.

Hence a few holes combined with electrons to constitute the base current. ( $I_B$ ).

The remaining holes crossover into the collector region.

$$I_E = I_C + I_B.$$

This equation gives the fundamental relationship between the bipolar transistor circuit.

Current gain ( $\alpha$ )

It is defined as the ratio of the negative feedback of the collector current increment to the emitter current change from cut off to  $I_E$  i.e.

$$\alpha = - \left[ \frac{I_C - I_{CBO}}{I_E - 0} \right].$$

where  $I_{CBO}$  is the reverse saturation current flow through the reverse biased collector base junction.

$I_{CBO}$  is negligible.

$$\alpha = - \frac{I_C}{I_E}.$$

$I_C$  &  $I_E$  will be in opposite directions,  $\alpha$  will always be +ve

$\alpha$  will be approx 0.90 to 0.995.

$$I_C = -\alpha I_E + I_{CBO} (1 - e^{V_C/V_T})$$

current amplification factor.

$$\beta = \frac{\alpha}{1 - \alpha}.$$

if  $V_C$  is large  $I_C = -\alpha I_E + I_{CBO}$   
 $\therefore I_C$  &  $I_E$  flow in opp directions  
 $I_E = -(I_C + I_B)$

$$\therefore I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{I_{CBO}}{1 - \alpha}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

## Types of Configuration:

When a transistor is connected in a circuit, one terminal is used as input, the other terminal as output and third terminal is common to input and output.



Depending upon the input and output terminal, transistor can be connected in three configurations. They are

- \* Common Base (CB)
- \* Common Emitter (CE)
- \* Common Collector (CC).

When device switched ON  
 $V \downarrow I \uparrow$   
 Switched OFF  $V \uparrow I \downarrow$

## CB (Common Base) :-

Circuit diagram is.

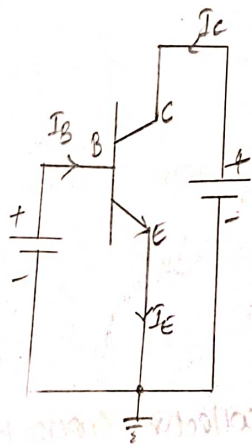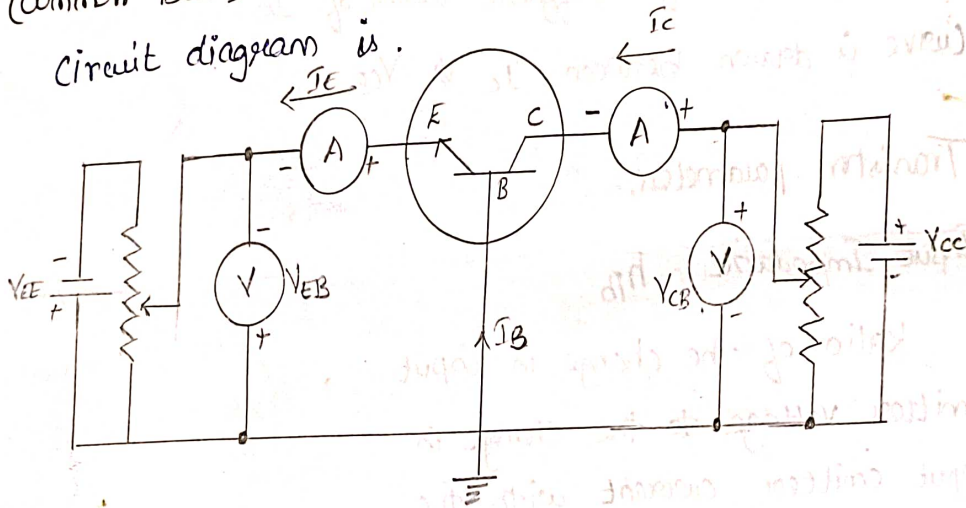


## Input characteristics:-

- \* Collector base Voltage  $V_{CB}$  is kept at 0V.
- \* Emitter current  $I_E$  should be increased in equal steps by increasing  $V_{EB}$ .
- \* This is repeated for maximum values of  $V_{CB}$ .
- \* A curve is drawn between emitter current and emitter base Voltage. at constant  $V_{CB}$ .

\* When  $V_{CB} = 0$ , Emitter base junction is forward biased, junction behaves as forward biased diode so that  $I_E \uparrow$  rapidly.

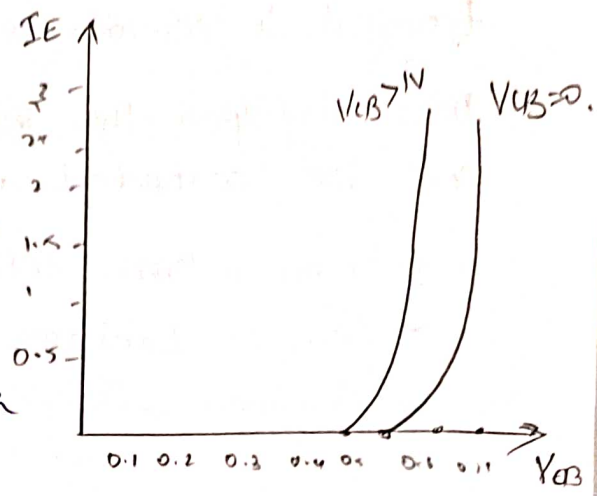\* When  $V_{CB} \uparrow$  keeping  $V_{EB}$  constant, width of the base region will decrease.




Output characteristics:

\* Emitter current  $I_E$  is kept constant by adjusting  $V_{EB}$ .

\*  $V_{CB}$  is  $\uparrow$  and  $I_C$  is noted for each value of  $I_E$ .

\* This is repeated for different values of  $I_E$ .

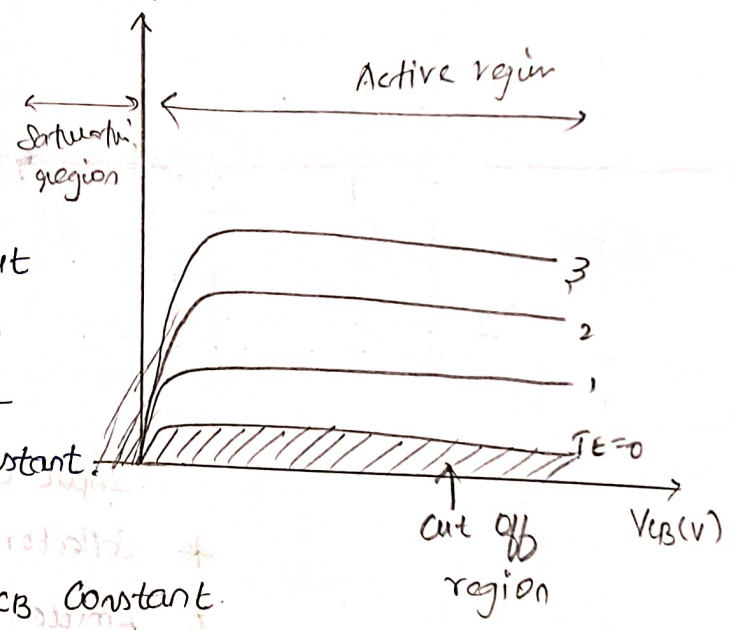\* Curve is drawn between  $I_C$  vs  $V_{CB}$ .  $I_C(\text{mA})$



Transistor parameters:-

Input Impedance :-  $h_{ib}$ .

Ratio of the change in input emitter voltage to the change in input emitter current with the output collector voltage kept constant.

$$h_{ib} = \frac{\Delta V_{EB}}{\Delta I_E}, V_{CB} \text{ constant.}$$

Output Admittance :-  $h_{ob}$ .

Ratio of change in the output collector current to the corresponding change in the output collector voltage with  $I_E$  kept constant.

$$h_{ob} = \frac{\Delta I_C}{\Delta V_{CB}}, I_E \text{ constant.}$$

Forward current gain ( $h_{fb}$ ).

Ratio of change in the output collector current to the change in the input emitter current keeping  $V_{CB}$  constant.


$$h_{fb} = \frac{\Delta I_c}{\Delta I_e}, V_{CB} \text{ constant.}$$

Reverse voltage gain ( $h_{rb}$ ):-

Ratio of change in the input emitter voltage to change in output collector voltage with  $I_E$  constant.

$$h_{rb} = \frac{\Delta V_{EB}}{\Delta V_{CB}}, I_E \text{ constant.}$$


CE configuration:-

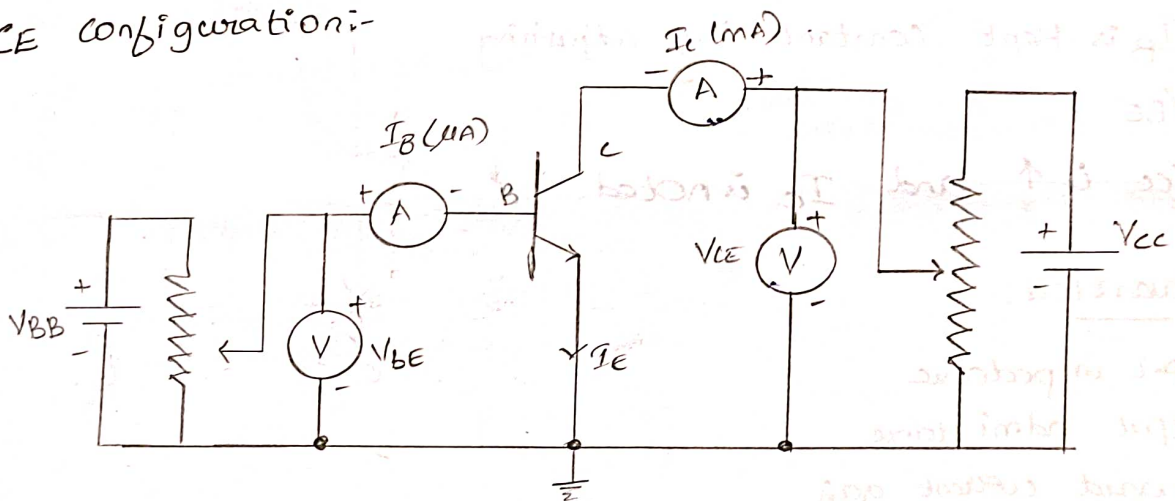

Input characteristics.

- \*  $V_{CE}$  is kept constant at 0 VOLT and base current  $I_B$  is increased from 0 by increasing  $V_{BE}$ .
- \* The value of  $V_{BE}$  is noted for each setting of  $I_B$ .

Connection diagram

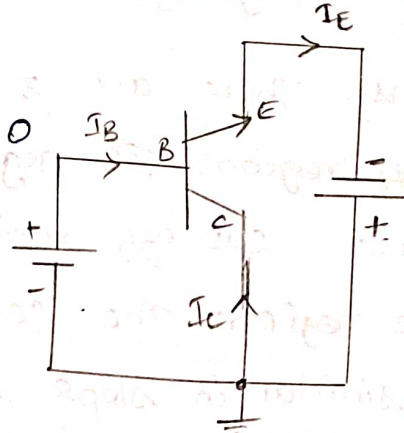

This procedure is repeated for higher fixed values of  $V_{CE}$ .


\*  $V_{CE} = 0$ , Emitter base junction is forward biased.

\*  $V_{CE} \uparrow$  width of the depletion region at collector base junction will increase.

\* Width of the base will decrease  $I_B$  will  $\downarrow$

\* To get same value of  $I_B$  at  $V_{CE} = 0$ , we should increase  $V_{BE}$


\* The curve shifts to right.

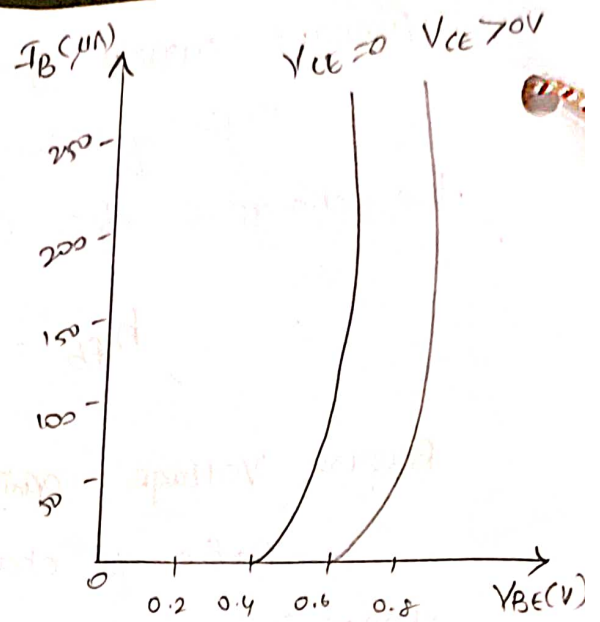

Output characteristics:-

\*  $I_B$  is kept constant by adjusting  $V_{BE}$

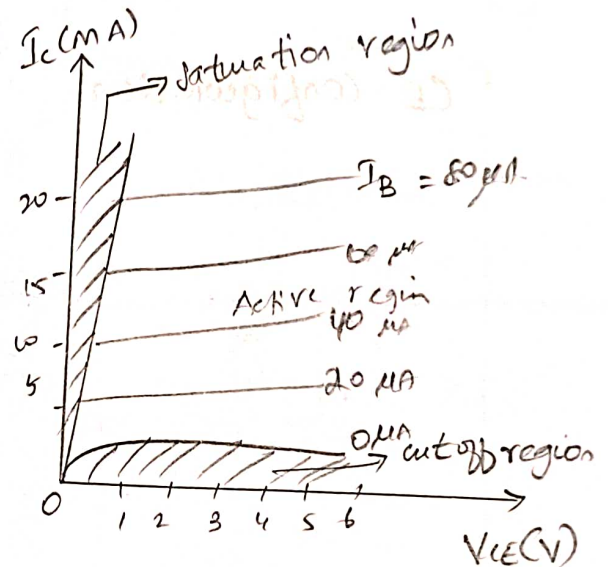\*  $V_{CE}$  is  $\uparrow$  and  $I_C$  is noted.



Parameters:

Input impedance

Output admittance

Forward current gain

Reverse voltage gain.


Regions: There are 3 regions

Cut off region: The region below the curve where the  $I_B = 0$  is called cut off region.

Active region: The central region where the curves are uniform and similar in slope is called active region.

Saturation region: Both junctions will be forward biased,  $\uparrow$  in  $I_B$  will not cause much change in the  $I_C$ . So this is called saturation region.

# CC Configuration:-

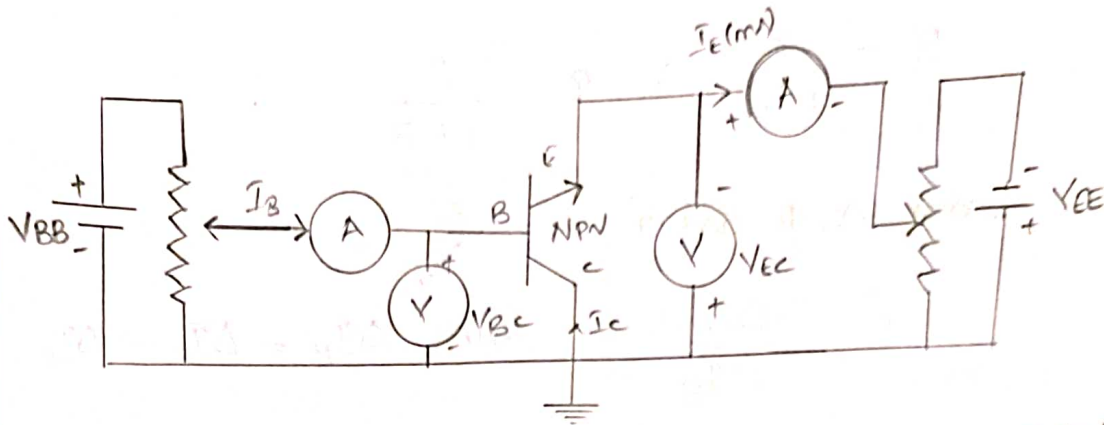


## Input characteristics:-

- \*  $V_{CE}$  is kept constant (arbitrary value)
- \*  $V_{BE} \uparrow, I_B$  not zero

## Output characteristics.

Illustr to CE characteristics.

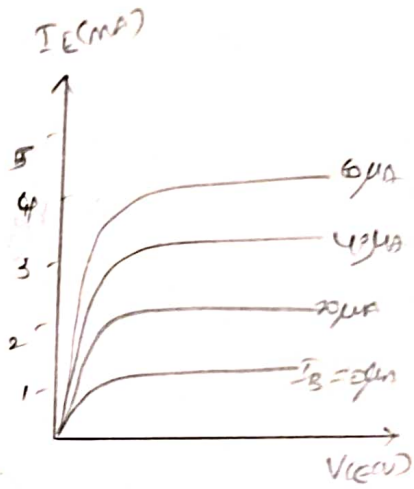

## Current Amplification factor.

CB Configuration  $\alpha = \frac{-\Delta I_C}{\Delta I_E}$

CE "  $\beta = \frac{-\Delta I_C}{\Delta I_B}$

CC "  $\gamma = \frac{-\Delta I_E}{\Delta I_B}$

$-\alpha \Delta I_E + \Delta I_C$

$\Delta I_E (1-\alpha) = \Delta I_B$

$\Delta I_C = \alpha \Delta I_E$

$-(\Delta I_E (1-\alpha))$

## Relationship b/w $\alpha$ and $\beta$ .

K.K.T  $\Delta I_E = \Delta I_C + \Delta I_B$

$\therefore \Delta I_C = \alpha \Delta I_E$

$\therefore \Delta I_E = \alpha \Delta I_E + \Delta I_B$

$\therefore \Delta I_B = \Delta I_E (1-\alpha)$

divide both sides  $\Delta I_C$

$\frac{\Delta I_B}{\Delta I_C} = \frac{\Delta I_E}{\Delta I_C} (1-\alpha)$



$$\therefore \frac{1}{\beta} = \frac{1}{\alpha} (1 - \alpha)$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad ; \quad \alpha = \frac{\beta}{1 + \beta}$$

Relation among  $\alpha$ ,  $\beta$  and  $\gamma$ .

$$\gamma = \frac{\Delta I_E}{\Delta I_B} \quad \text{and} \quad \Delta I_B = \Delta I_E - \Delta I_C$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$\div$  by  $\Delta I_E$

$$\gamma = \frac{\Delta I_E / \Delta I_E}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{1}{1 - \alpha}$$

$$\gamma = \frac{1}{1 - \alpha} = (\beta + 1)$$

**Biasing:-**

\* In order to produce distortion free output in amplifier circuits, the supply voltage and resistances in the circuit must be suitably chosen.

\* These voltages and resistance establish a dc voltage & current

\* Voltages & currents are called quiescent values which determines the operating point of transistor.

"The process of giving proper supply voltages and resistances for obtaining the desired operating point is called biasing".

The circuits used for getting desired operating point is called biasing circuits.