

Rectifier:

A rectifier is a device which converts


ac voltage
T → Temperature


to pulsating dc voltage.

Two types of rectifier

→ Half wave rectifier

→ Full wave rectifier

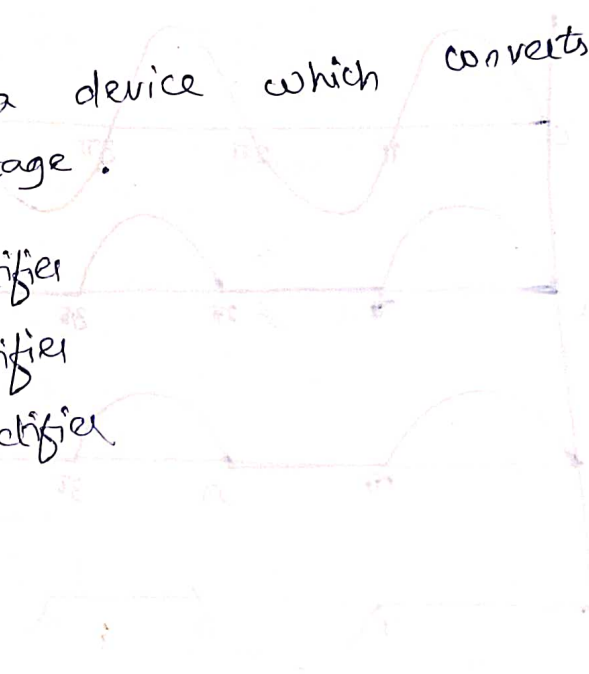

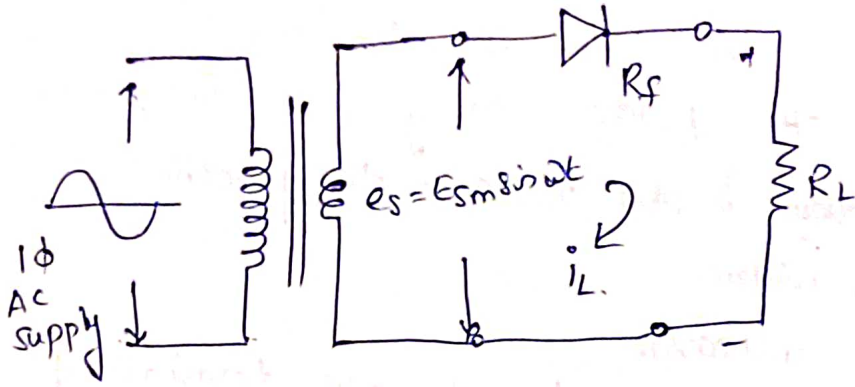

In a transformer N_1 are 1^o turns, N_2 are 2^o turns

E_{pm} → peak value of 1^o ac voltage

E_{sm} → " " " 2^o ac voltage


$$\frac{N_2}{N_1} = \frac{E_{sm}}{E_{pm}}$$

$$e_s = E_{sm} \sin \omega t$$


$$\omega = 2\pi f$$

f = supply frequency

Operation.

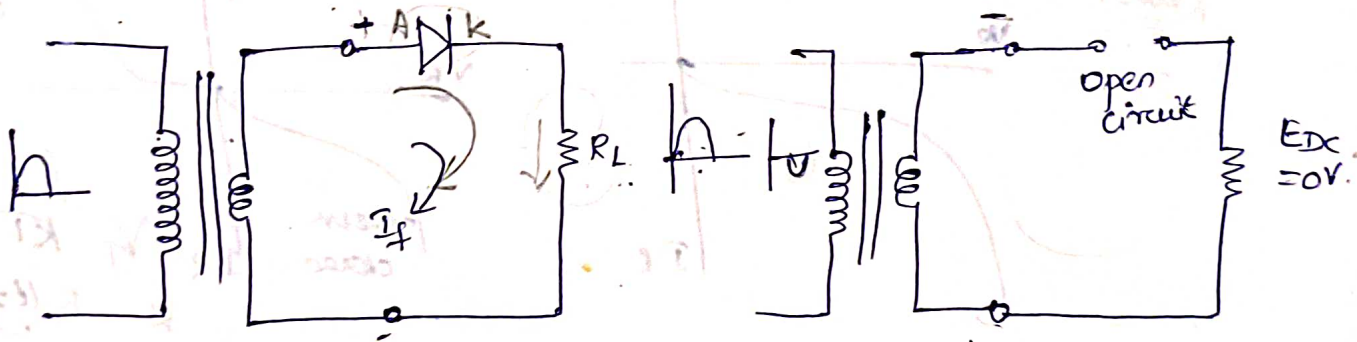

→ forward biased

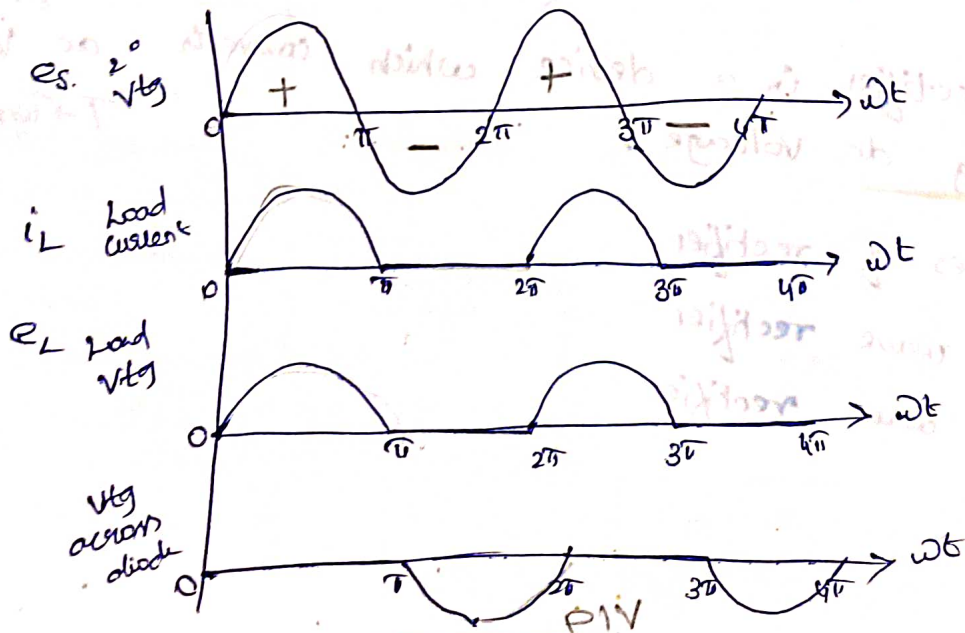


Mathematically current waveform can be described as

$$i_L = I_m \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi$$

$$i_L = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi$$

I_m is the peak value of load current.
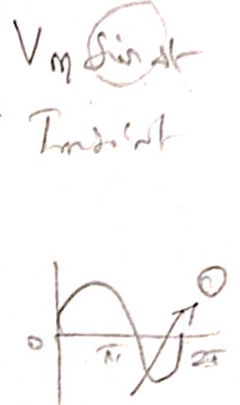
$$\begin{aligned} I_{DC} &= \frac{1}{2\pi} \int_0^{2\pi} i_L d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \cdot d\omega t \\ &= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \cdot d\omega t = \frac{I_m}{2\pi} [-\cos \omega t]_0^{\pi} \\ &= -\frac{I_m}{2\pi} [\cos \pi - \cos 0] = -\frac{I_m}{2\pi} [-1 - 1] = \frac{I_m}{\pi} \end{aligned}$$



$$I_{DC} = \frac{I_m}{\pi}$$

Apply KVL, $I_m = \frac{E_{sm}}{R_f + R_L + R_s}$

$$I = \frac{V}{R}$$

$$I_m = \frac{V_m}{R_L}$$

if R_s is not given it can be neglected.

* Average DC Load Voltage (E_{DC}).

$$\begin{aligned} E_{DC} &= I_{DC} R_L \times \frac{E_{sm}}{R_f + R_L + R_s} \\ &= \frac{I_m}{\pi} \times R_L = \frac{E_{sm}}{(R_f + R_L + R_s)\pi} \times R_L \end{aligned}$$

R_f, R_s are very small compared to R_L .

$$E_{DC} = \frac{E_{sm}}{\pi \left[\frac{R_f + R_s}{R_L} + 1 \right]}$$

is neglected.

$$E_{DC} = \frac{E_{sm}}{\pi}$$

$$V_{DC} = \frac{V_m}{\pi}$$

* RMS Value of Load current:

$$\begin{aligned}
 I_{RMS} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \omega t)^2 d(\omega t)} \\
 &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \omega t \cdot d\omega t} \\
 &= I_m \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{[1 - \cos 2\omega t]}{2} d\omega t} \\
 &= I_m \sqrt{\frac{1}{2\pi} \left[\frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right]_0^{2\pi}} \\
 &= I_m \sqrt{\frac{1}{2\pi} \left(\frac{2\pi}{2} \right)} \quad \because \sin 2\pi = \sin 0 = 0 \\
 &= \frac{I_m}{2}
 \end{aligned}$$

$$I_{RMS} = \frac{I_m}{2}$$

* RMS value of Load Voltage.

$$\begin{aligned}
 E_L (RMS) &= I_{RMS} R_L = \frac{I_m}{2} R_L \\
 &= \frac{E_{sm}}{2(R_f + R_L + R_s)} \times R_L = \frac{E_{sm}}{2 \left[1 + \frac{R_f + R_s}{R_L} \right]}
 \end{aligned}$$

$V_{RMS} = I_{RMS} R$
 $\frac{V_m}{2}$

neglected

$$E_L (RMS) = \frac{E_{sm}}{2}$$

* DC Power Output (P_{DC})

$$\begin{aligned}
 P_{DC} &= E_{DC} I_{DC} = I_{DC} R_L I_{DC} = I_{DC}^2 R_L \\
 &= \left[\frac{I_m}{\pi} \right]^2 R_L = \frac{I_m^2}{\pi^2} R_L
 \end{aligned}$$

$P_{DC} = \frac{P_{out}}{P_{in}}$
 $P_{DC} = \frac{P_{DC}}{2}$

$$P_{DC} = \frac{E_{sm}^2 R_L}{\pi^2 [R_f + R_L + R_s]^2}$$

* AC power input (P_{AC})

$$P_{AC} = I_{RMS}^2 [R_L + R_f + R_s]$$

$$I_{RMS} = \frac{I_m}{2}$$

$$P_{AC} = \frac{I_m^2}{4} [R_L + R_f + R_s]$$

$$\frac{I_m^2}{\pi^2} \times R_L$$

$$\frac{I_m^2}{4}$$

* Rectifier efficiency

$$\eta = \frac{\text{DC output power}}{\text{AC input power}} = \frac{P_{DC}}{P_{AC}}$$

$$\frac{(4/\pi^2) R_L}{(R_f + R_L + R_s)}$$

$$\eta = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{I_m^2}{4} [R_f + R_L + R_s]} = \frac{(4/\pi^2) R_L}{(R_f + R_L + R_s)}$$

$$\eta = \frac{0.406}{1 + \left(\frac{R_f + R_s}{R_L}\right)}$$

neglected.

$$\therefore \eta = 40.6\%$$

* Ripple factor

$$\gamma = \frac{\text{RMS value of ac component of output}}{\text{Average or dc component of output}}$$

$$I_{ac} = \text{RMS value of ac component present in output}$$

$$I_{dc} = \text{dc component present in output}$$

$$I_{RMS} = \text{RMS value of total output current}$$

$$I_{RMS} = \sqrt{I_{ac}^2 + I_{dc}^2}$$

$\therefore I_{ac} = \sqrt{I_{RMS}^2 - I_{DC}^2}$
 as per definition Ripple factor = $\frac{I_{ac}}{I_{DC}}$

$f = 75$
 $E_p = 230$
 $\frac{N_1}{N_2} =$

$$r = \frac{\sqrt{I_{RMS}^2 - I_{DC}^2}}{I_{DC}}$$

$$r = \sqrt{\left(\frac{I_{RMS}}{I_{DC}}\right)^2 - 1}$$

$$I_{RMS} = \frac{I_m}{2}, \quad I_{DC} = \frac{I_m}{\pi}$$


$$r = \sqrt{\left[\frac{\left(\frac{I_m}{2}\right)^2}{\left(\frac{I_m}{\pi}\right)^2} - 1\right]} = \sqrt{\frac{\pi^2}{4} - 1} = \sqrt{1.4674}$$

$$r = 1.211$$

Problem.

A half wave rectifier circuit is supplied from a 230V, 50 Hz supply with a step down ratio of 3:1 to a resistive load of 10 kΩ. The diode forward resistance is 75 Ω while transformer's resistance is 10 Ω. Calculate minimum, average, RMS value of current, DC output voltage, efficiency & ripple factor.

Solution.

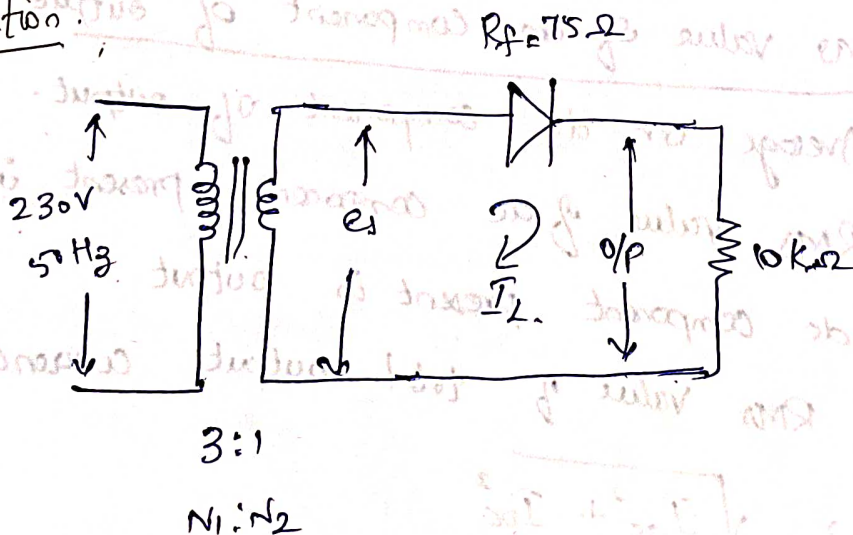

data:
 $R_f = 75 \Omega$, $R_L = 10 \text{ k}\Omega$, $R_1 = 10 \Omega$

$$E_p = 230 \text{ V}, \quad \frac{N_1}{N_2} = \frac{3}{1} \quad \text{ie} \quad \frac{N_2}{N_1} = \frac{1}{3}$$

$$\frac{N_2}{N_1} = \frac{E_s (\text{RMS})}{E_p (\text{RMS})}$$

$$\frac{1}{3} = \frac{E_s (\text{RMS})}{230}$$

$$E_s (\text{RMS}) = \frac{230}{3} = 76.667 \text{ V.}$$

$$E_{sm} = \sqrt{2} E_s (\text{RMS}) = \sqrt{2} \times 76.667 = 108.423 \text{ V}$$

$$I_m = \frac{E_{sm}}{R_s + R_f + R_L} = \frac{108.423}{10 + 75 + 10 \times 10^3} = 10.75 \text{ mA}$$

$$I_{av} = I_{DC} = \frac{I_m}{\pi} = \frac{10.75}{\pi} = 3.422 \text{ mA}$$

$$I_{RMS} = \frac{I_m}{2} = \frac{10.75}{2} = 5.375 \text{ mA}$$

$$E_{DC} = \text{dc output voltage} = I_{DC} R_L \\ = 3.422 \times 10^{-3} \times 10 \times 10^3 = 34.22 \text{ V.}$$

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100$$



$$P_{DC} = \text{dc output power} = E_{DC} I_{DC} = 34.22 \times 3.422 \times 10^{-3} \\ = 0.1171 \text{ W}$$

$$P_{AC} = I_{RMS}^2 [R_s + R_f + R_L] \\ = (5.375 \times 10^{-3})^2 [10 + 75 + 10 \times 10^3] \\ = 0.2913$$


$$\eta = \frac{0.1171}{0.2913} \times 100 = 40.19\%$$

$\eta = 1.21$ for half wave rectifier.

Full wave rectifier:

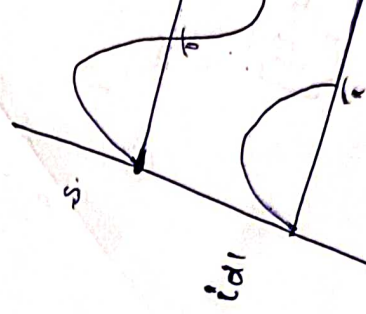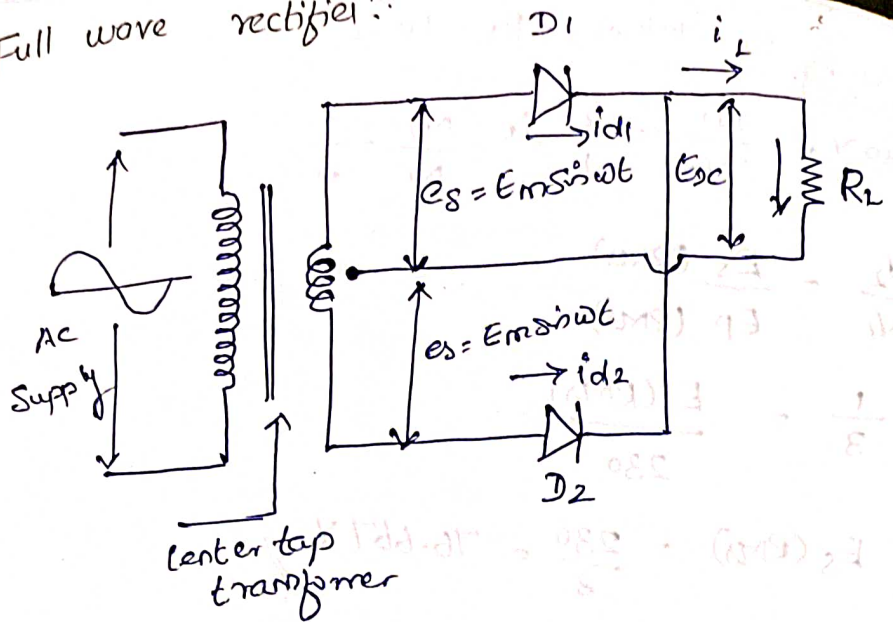

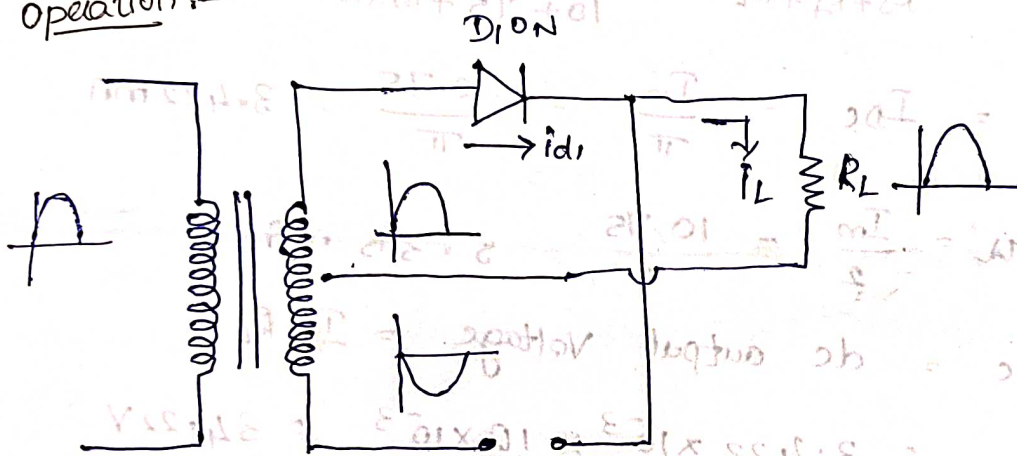It conducts during both +ve and -ve half cycle.
 In order to rectify both the half cycles, 2 diodes are used.
Operation:-




$D_1 \rightarrow$ forward biased it will conduct
 $D_2 \rightarrow$ reverse u it will be an open circuit.
 and will not conduct.


$$i_L = i_{d1}$$

$$i_L = i_{d2}$$

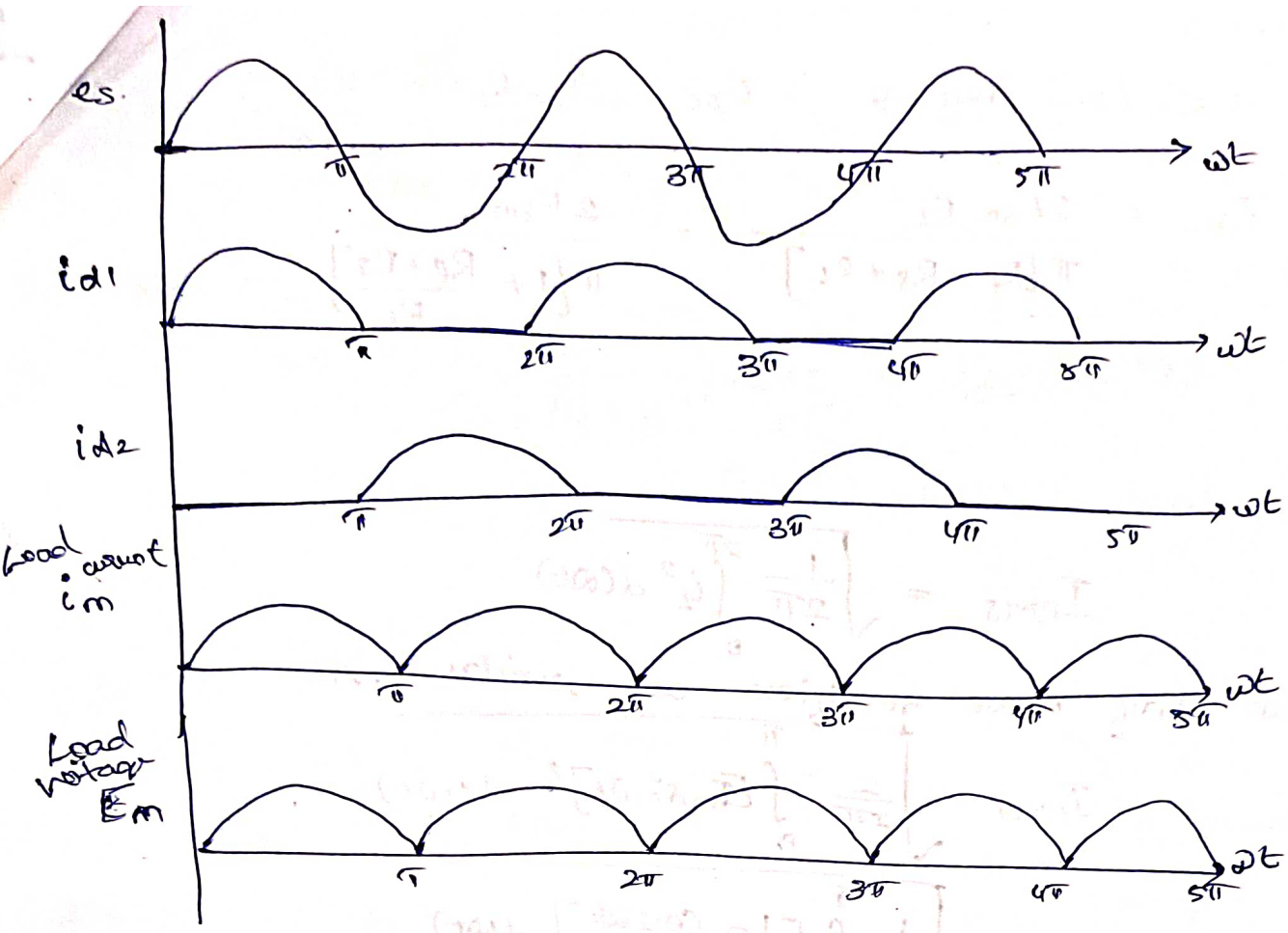The load current flows in both the half cycles of ac voltage and it will be in the same direction through load resistance.



Maximum Load Current :-

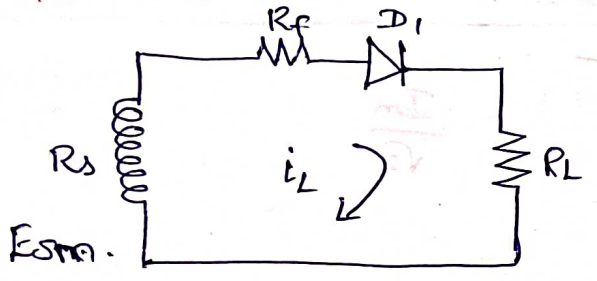

$$I_m = \frac{E_{sm}}{R_s + R_f + R_L}$$


I_m is the maximum value of load current i_L .

Average DC Load Current (I_{DC})

$$i_L = I_m \sin \omega t \quad 0 \leq \omega t \leq \pi$$

$$I_{AV} = I_{DC} = \frac{1}{\pi} \int_0^{\pi} i_L d(\omega t)$$
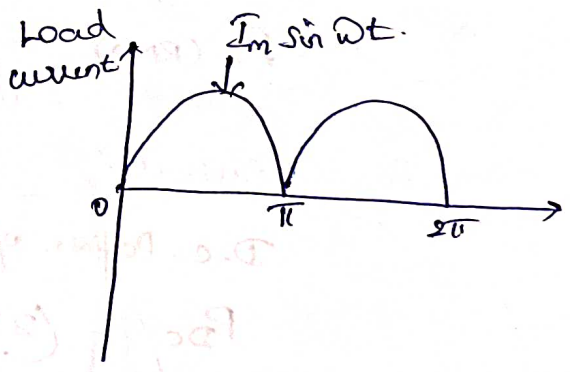
$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \cdot d\omega t$$



$$= \frac{I_m}{\pi} \left[(-\cos \omega t) \Big|_0^{\pi} \right] = \frac{I_m}{\pi} \left[-\cos \pi - (-\cos 0) \right]$$

$$= \frac{I_m}{\pi} (1 - (-1)) = \frac{2I_m}{\pi}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

Average DC Load Voltage

$$\text{d.c. Load Voltage, } E_{DC} = I_{DC} R_L = \frac{2 I_m R_L}{\pi}$$

$$E_{DC} = \frac{2 E_{sm} R_L}{\pi [R_f + R_s + R_L]} = \frac{2 E_{sm}}{\pi \left[1 + \frac{R_f + R_s}{R_L} \right]}$$

$$E_{DC} = \frac{2 E_{sm}}{\pi}$$

RMS Load Current (I_{RMS})

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_L^2 d(\omega t)}$$

Full half wave rectifiers are similar, so

$$I_{RMS} = \sqrt{\frac{2}{2\pi} \int_0^{\pi} [I_m \sin \omega t]^2 \cdot d(\omega t)}$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} \left[\frac{1 - \cos 2\omega t}{2} \right] \cdot d(\omega t)}$$

$$= I_m \sqrt{\frac{1}{2\pi} (\pi)} = \frac{I_m}{\sqrt{2}}$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

RMS Value of Load Voltage

$$E_L (RMS) = I_{RMS} R_L = \frac{I_m}{\sqrt{2}} R_L$$

DC Power Output:-

$$\text{D.c. Power o/p} = E_{DC} I_{DC} = I_{DC}^2 R_L \quad \because E_{DC} = I_{DC} R_L$$

$$P_{DC} = \left(\frac{2 I_m}{\pi} \right)^2 R_L = \frac{4 I_m^2 R_L}{\pi^2}$$

Sub I_m .

$$P_{DC} = \frac{4}{\pi^2} \frac{E_{sm}^2}{(R_s + R_f + R_L)^2} \times R_L$$

power Input (P_{AC}).

$$P_{AC} = I_{RMS}^2 (R_f + R_s + R_L) = \left(\frac{I_m}{\sqrt{2}}\right)^2 (R_f + R_s + R_L)$$

$$P_{AC} = \frac{I_m^2 (R_f + R_s + R_L)}{2}$$

Sub I_m .

$$P_{AC} = \frac{E_{sm}^2}{(R_f + R_s + R_L)^2} \times \frac{1}{2} \times (R_f + R_s + R_L)$$

$$P_{AC} = \frac{E_{sm}^2}{2(R_f + R_s + R_L)}$$

Rectifier Efficiency η .

$$\eta = \frac{P_{DC} \text{ Output}}{P_{AC} \text{ input}} = \frac{\frac{4}{\pi^2} I_m^2 R_L}{\frac{I_m^2 (R_f + R_s + R_L)}{2}}$$

$$\eta = \frac{8 R_L}{\pi^2 (R_f + R_s + R_L)} \quad R_f + R_s \ll R_L,$$

$$\eta = \frac{8 R_L}{\pi^2 (R_L)} = \frac{8}{\pi^2}$$

$$\eta = \frac{8}{\pi^2} \times 100 = 81.2\%$$

Voltage Regulation:

$$(V_{dc})_{NL} = \frac{2 E_{sm}}{\pi}$$

$$(V_{dc})_{FL} = I_{DC} R_L$$

$$\%R = \frac{(V_{dc})_{NL} - (V_{dc})_{FL}}{(V_{dc})_{FL}} \times 100$$

$$\%R = \frac{\frac{2 E_{sm}}{\pi} - I_{DC} R_L}{I_{DC} R_L} \times 100$$

$$\therefore I_m = \frac{E_{sm}}{R_f + R_L + R_s}$$

$$= \frac{\frac{2 I_m}{\pi} [R_f + R_L + R_s] - \frac{2 I_m}{\pi} R_L \times 100}{\frac{2 I_m}{\pi} R_L}$$

$$E_{sm} = I_m (R_f + R_L + R_s)$$

$$I_{DC} = \frac{2 I_m}{\pi}$$

$$\% R = \frac{R_f + R_L + R_s - R_L}{R_L} \times 100$$

$$\% R = \frac{R_f + R_s}{R_L} \times 100$$

$$\% R = \frac{R_f}{R_L} \times 100$$

neglecting

resistance

(In collector

transistors are

Amplification.

Two types of

PROBLEMS:

In a centre-tapped full wave rectifier, the rms half secondary voltage is 9V, Assuming ideal diodes and load resistance $R_L = 1k\Omega$, find: 1. peak current 2. DC load voltage 3. RMS current 4. Ripple factor 5. Efficiency

Solution: $E_s(\text{rms}) = 9V$, $R_L = 1k\Omega$.

$$i) I_m = \frac{E_{sm}}{R_L}$$

$$E_{sm} = \sqrt{2} E_s(\text{rms}) = \sqrt{2} \times 9 = \underline{12.7279V}$$

$$I_m = \frac{12.7279}{1 \times 10^3} = \underline{12.7279mA}$$

$$ii) I_{DC} = \frac{2I_m}{\pi} = \frac{2 \times 12.7279}{\pi} = \underline{8.1028mA}$$

$$E_{DC} = I_{DC} R_L = 8.1028 \times 10^{-3} \times 1 \times 10^3 = \underline{8.1028V}$$

$$iii) I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{12.7279}{\sqrt{2}} = \underline{9mA}$$

$$iv) \text{Ripple factor} = \sqrt{\left[\frac{I_{rms}}{I_{DC}}\right]^2 - 1} = \sqrt{\left(\frac{9}{8.1028}\right)^2 - 1} = \underline{0.48}$$

$$v) P_{DC} = I_{DC}^2 R_L = (8.1028)^2 \times 1 \times 10^3 = \underline{65.65mW}$$

$$P_{AC} = I_{RMS}^2 R_L = 9^2 \times 1 \times 10^3 = \underline{81mW}$$

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{65.65}{81} \times 100 = \underline{81.04\%}$$