



# **SNS COLLEGE OF ENGINEERING**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**


Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**COURSE NAME : 19EE101 BASIC ELECTRICAL AND ELECTRONICS  
ENGINEERING**

I YEAR /I SEMESTER Artificial Intelligence and Datascience

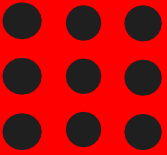Unit 1 – Electrical Circuits and Measurements





# Terminologies

**Current:** Current is just the rate of flow of electric charge (A)

**Voltage:** Voltage is the difference in electric potential between two points (V)


**Power:** The rate at which work is done is transformed into an electrical circuit (W)

**Resistance:** Is a measure of the opposition to current flow in an electrical circuit.

**Inductance:** Stores electrical energy in the form of magnetic field

**Capacitance:** Stores electrical energy in the form of electric field.

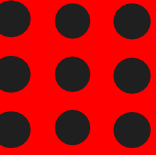**Circuit:** A circuit is a path that starts and stops at the same place





# DEFINITION



- The potential difference (voltage) across an ideal conductor is proportional to the current through it. The constant of proportionality is called the "resistance",  $R$ .

- $I = V/R$
- $V = IR$
- $R = V/I$

$I$  = Current


$V$  = Voltage

$R$  = Resistance

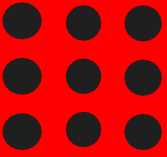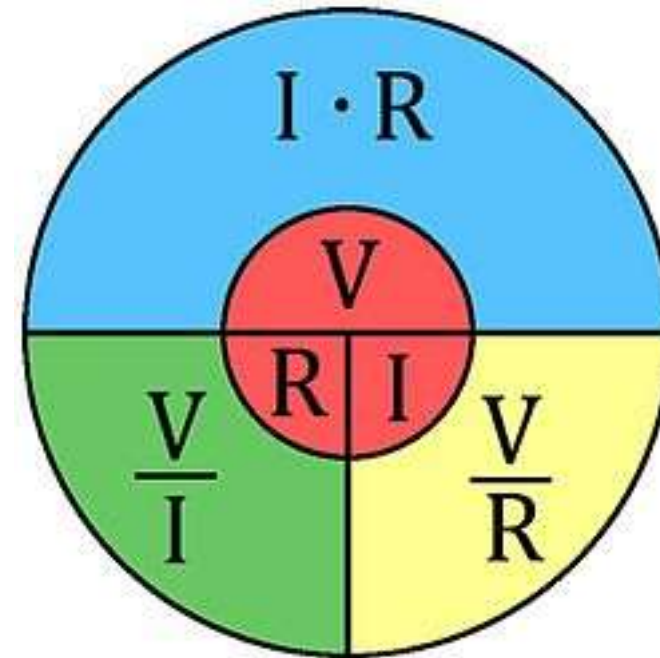





# Simple Circuits with Ohm's Law

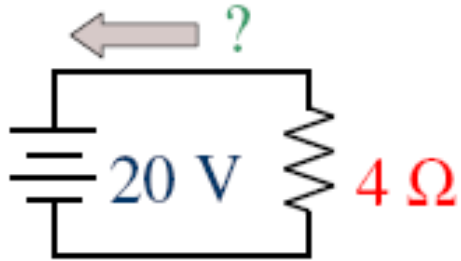


$$I = (20/4) = 5 \text{ A}$$

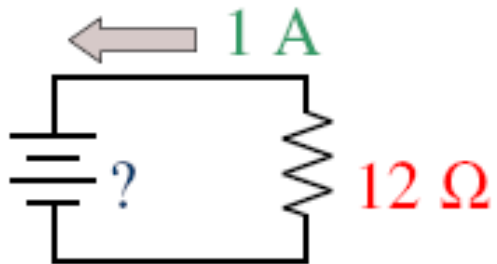

$$V = 1 \times 12 = 12 \text{ V}$$

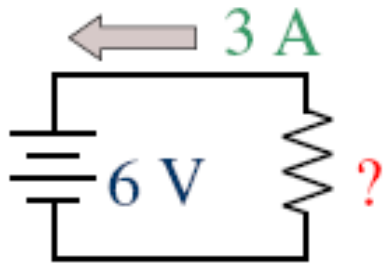


$$R = (6 / 3) = 2 \text{ ohms}$$

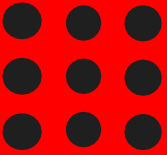






# Can you solve?

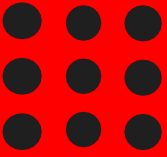1.  $V = 14 \text{ V}, I = 2 \text{ A}, R = ?$
2.  $V = 25 \text{ V}, I = 5 \text{ A}, R = ?$
3.  $V = 6 \text{ V}, I = 1.5 \text{ A}, R = ?$
4.  $V = 24 \text{ V}, I = 4 \text{ A}, R = ?$






# LINEAR PROPORTION BETWEEN V & I

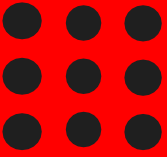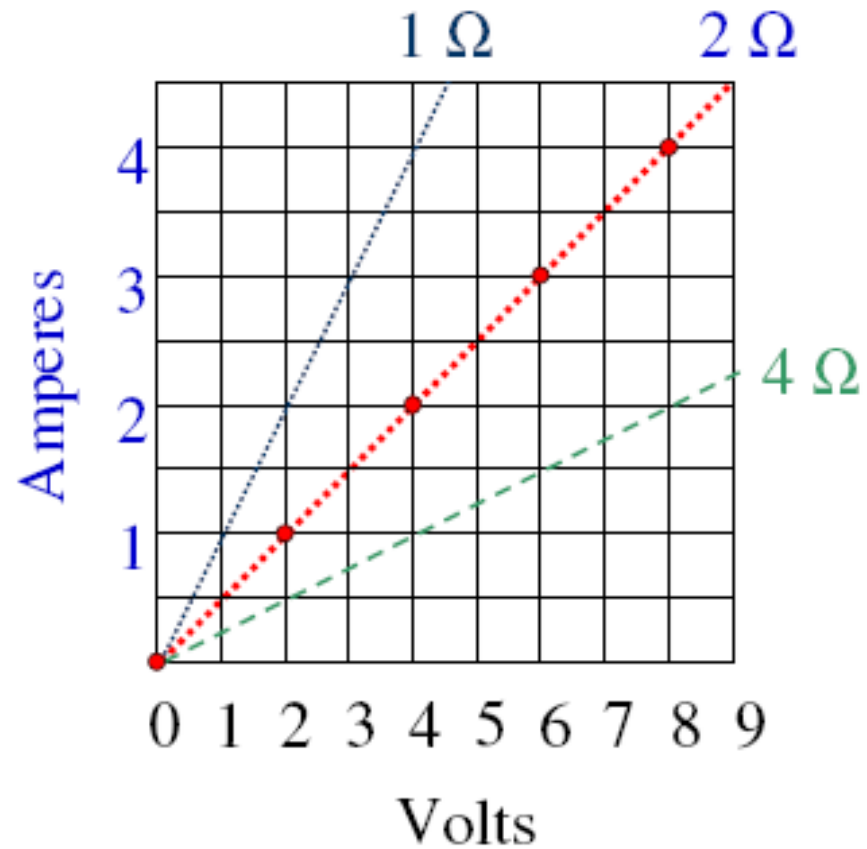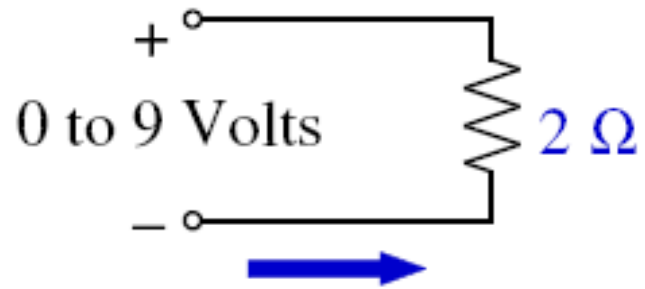


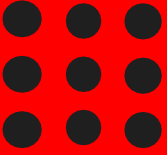
# Power Dissipation in Resistance

- The amount of power dissipated in a resistance may be calculated using any one of three formulas, depending on which factors are known
- $P = I^2 \times R$
- $P = V^2 / R$
- $P = V \times I$





# Assessment 2

1. Solve for the power,  $P$ , dissipated by the resistance,  $R$


a.  $I = 1 \text{ A}$ ,  $R = 100\Omega$ ,  $P = ?$

b.  $I = 20 \text{ mA}$ ,  $R = 1\Omega$ ,  $P = ?$

c.  $V = 5 \text{ V}$ ,  $R = 150\Omega$ ,  $P = ?$

d.  $V = 22.36 \text{ V}$ ,  $R = 1\Omega$ ,  $P = ?$

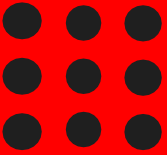2. How much power is dissipated by an  $8\Omega$  load if the current in the load is  $200 \text{ mA}$ ?








# Limitations of Ohm's Law

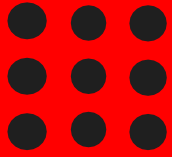- 1) This law cannot be applied to unilateral networks.
- 2) Ohm's law is also not applicable for non - linear elements.





# REFERENCES

1. Bhattacharya. S.K, “Basic Electrical and Electronics Engineering”, Pearson Education , (2017)
2. Muthu subramanian R, SalivahananS,“ Basic Electrical and Electronics Engineering”, Tata McGraw Hill Publishers, (2009)
3. V.Mittle“ Basic Electrical Engineering”, Tata McGraw Hill Publishers, (2017)
4. Nagrath. I.J, “Electronics: Analog and Digital”, Prentice Hall India Pvt. Ltd., (2013)
5. Black & Decker , “The complete guide to Electrical Wiring” , S.Chand & Company Ltd,(2012)

**THANK YOU**

