




# SNS COLLEGE OF ENGINEERING

(Autonomous)  
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



## S PARAMETERS

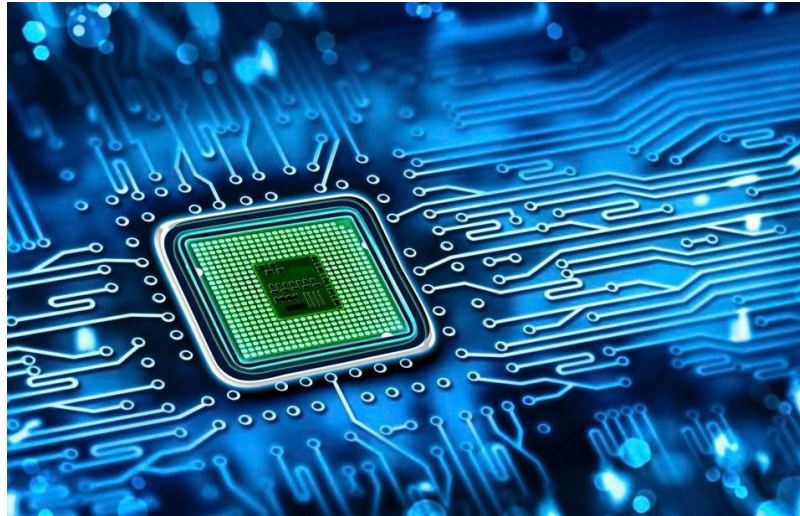

## S-Parameters:

s-parameters consists of two fundamental topics:

1. two-port networks,
2. reflections on transmission lines.

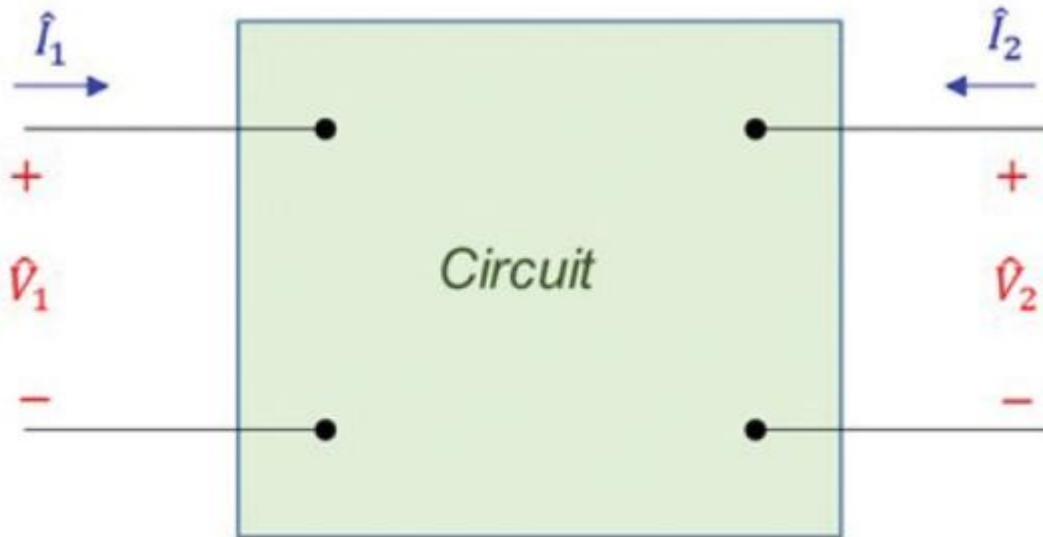


Figure 1: Two-port network





# S PARAMETERS



two-port system provides relations between the input and output reflected waves  $b_1$  and  $b_2$  and the input and output incident waves  $a_1$  and  $a_2$  when the structure is to be connected to a source resistance  $R_G$  and a load resistance  $R_L$

The notion of waves rather than voltages and currents is better suited for microwave structures. For a two-port system, the equations relating the incident and reflected waves and the S parameters are given by

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$





# S PARAMETERS



For a two-port system, the equations relating the incident and reflected waves and the  $S$  parameters are given by

$$\begin{aligned}b_1 &= S_{11}a_1 + S_{12}a_2 \\b_2 &= S_{21}a_1 + S_{22}a_2\end{aligned}$$

These equations can be summarized in the matrix form  $(b) = (S)(a)$ , where

$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$$

The parameter  $S_{11}$ , called the *input reflection coefficient*,





# S PARAMETERS




The parameter  $S_{11}$ , called the *input reflection coefficient*, can be computed by setting the output incident wave  $a_2$  to zero and taking the ratio of the input reflected wave over the input incident wave:

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

The parameter  $S_{21}$ , called the *forward transmission coefficient*, can be computed by setting the output incident wave  $a_2$  to zero and taking the ratio of the output reflected wave over the input incident wave:

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$



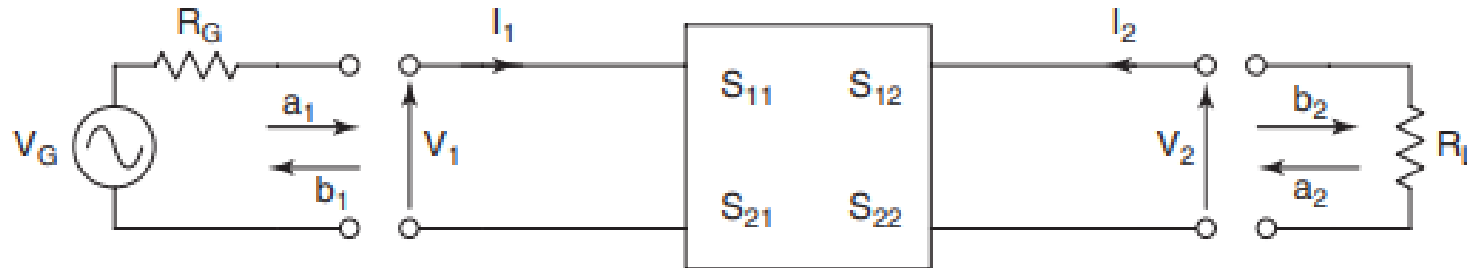

**Figure 1.1** Notation used in defining the scattering matrix of a two-port system.

The parameter  $S_{22}$ , called the *reflection coefficient at the output of the system*, can be computed by setting the input incident wave  $a_1$  to zero and taking the ratio of the output reflected wave over the output incident wave:

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$





# S PARAMETERS



The parameter  $\hat{S}_{12}$ , called the *reverse transmission coefficient*, can be computed by setting the input incident wave  $a_1$  to zero and taking the ratio of the input reflected wave over the output incident wave:

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$





Thank  
you

