



# **SNS COLLEGE OF ENGINEERING**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**COURSE NAME : 19EE401 SYNCHRONOUS AND INDUCTION  
MACHINES**

**II YEAR /IV SEMESTER**

**Unit 3: INDUCTION MOTOR**


**Topic 5 : Equivalent Circuit of Three Phase Induction Motor**


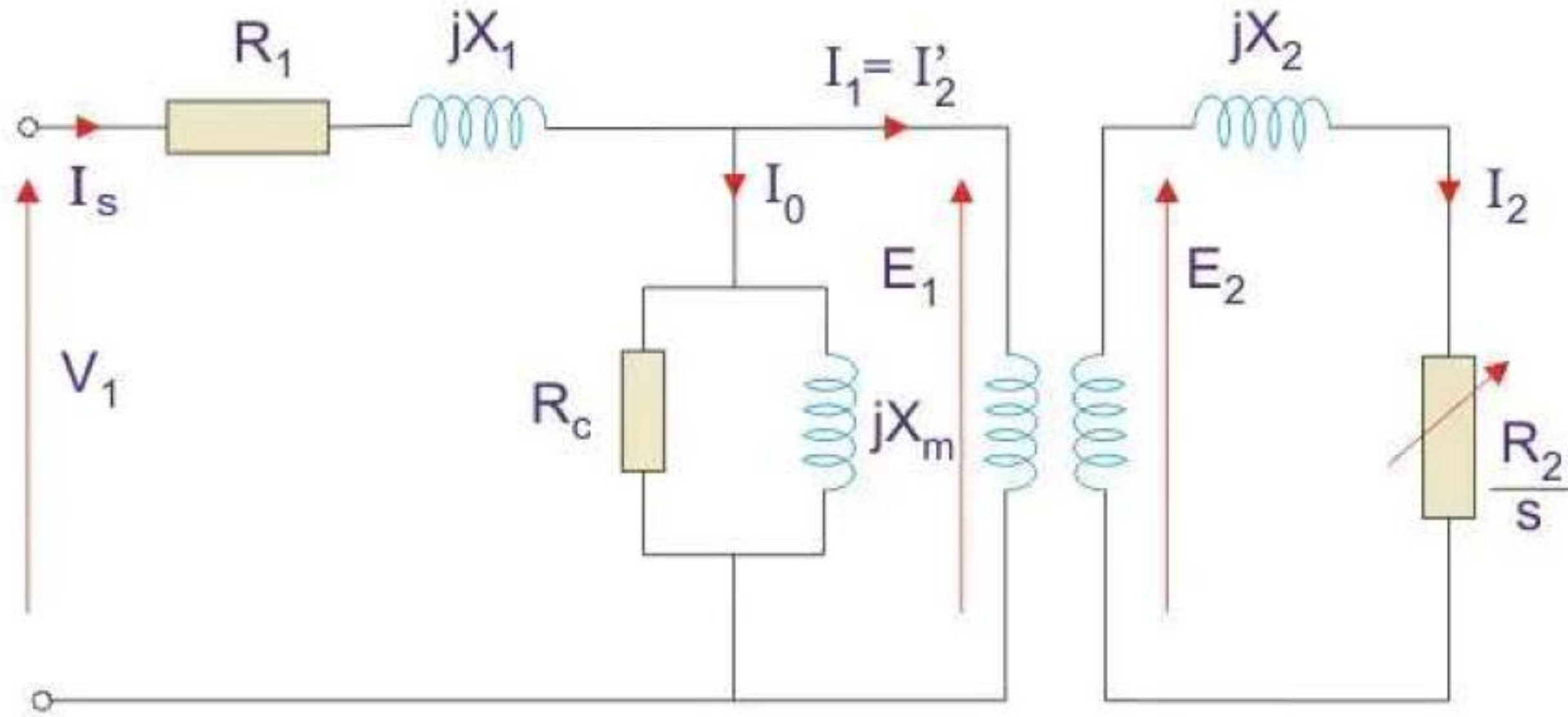
# Equivalent Circuit of Three Phase Induction Motor



An induction motor is a well-known device which works on the principle of transformer. So it is also called the rotating transformer. That is, when an EMF is supplied to its stator, then as a result of electromagnetic induction, a voltage is induced in its rotor. So an induction motor is said to be a transformer with rotating secondary. Here, primary of transformer resembles stator winding of an induction motor and secondary resembles rotor.



Here,  $R_1$  is the winding resistance of the stator.


$X_1$  is the inductance of the stator winding.

$R_c$  is the core loss component.

$X_M$  is the magnetizing reactance of the winding.

$R_2/s$  is the power of the rotor, which includes output mechanical power and copper loss of rotor.

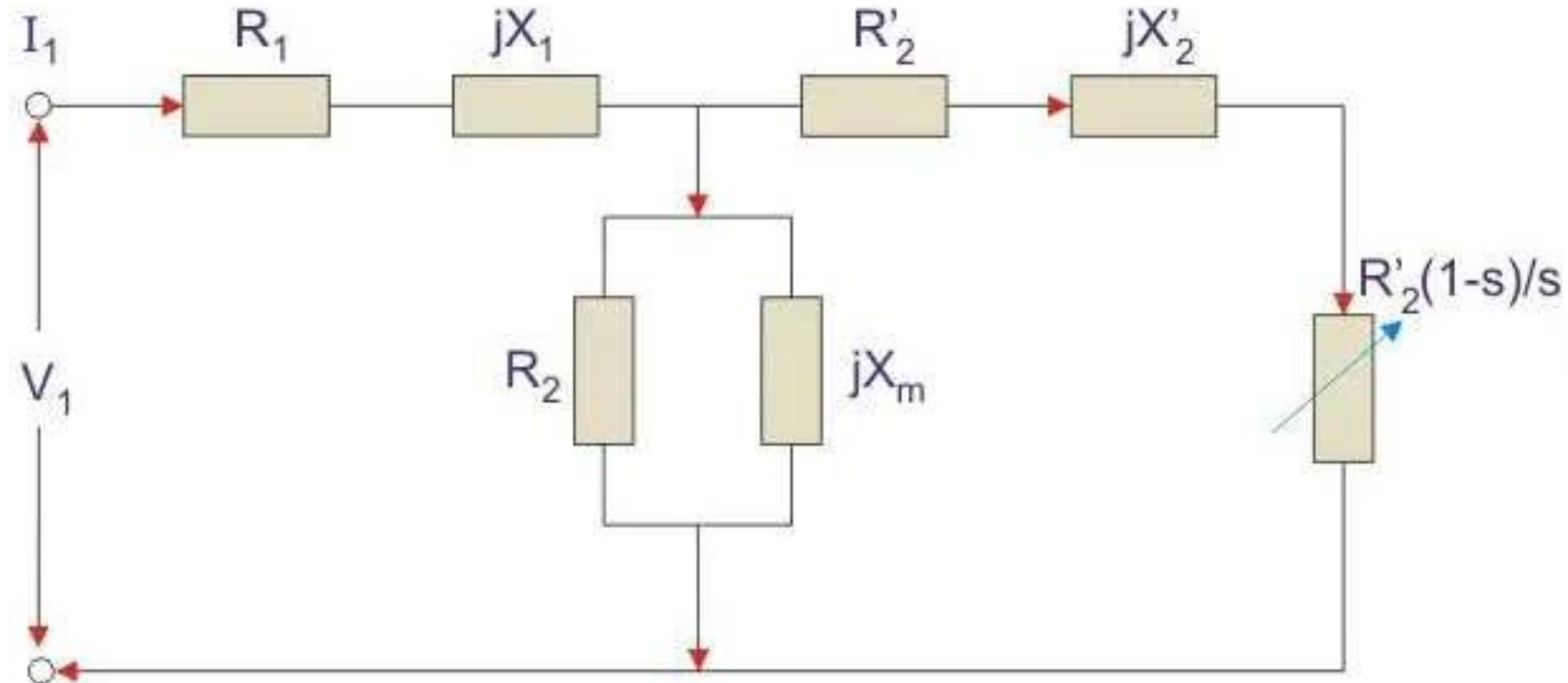
# Equivalent Circuit of Three Phase Induction Motor



$R_2'$  is the rotor winding resistance with referred to stator winding.  
 $X_2'$  is the rotor winding inductance with referred to stator winding.  
 $R_2(1 - s) / s$  is the resistance which shows the power which is converted to mechanical power output or useful power. The power dissipated in that resistor is the useful power output or shaft power.



# Three Phase Induction Motor on Load

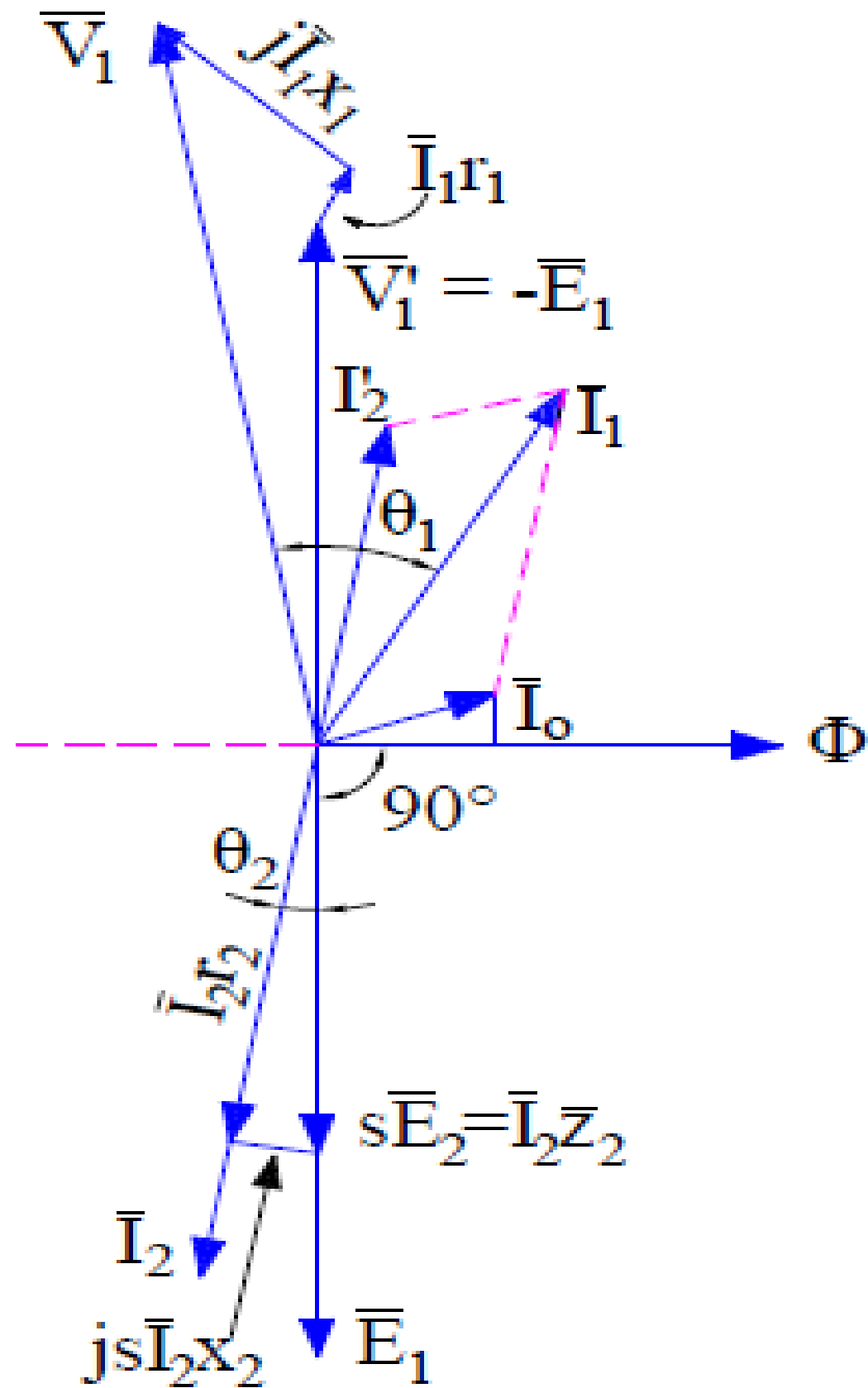

$$V_1 = V_1' + I_1(r_1 + jX_1)$$

$$E_2 = I_2 (r_2 + jX_2)$$





# Power Relation of Equivalent Circuit of Three Phase Induction Motor



➤ Input power to stator  $P_1 = 3 V_1 I_1 \cos(\theta)$

Where,  $V_1$  is the stator voltage applied,  $I_1$  is the current drawn by the stator winding.  $\cos(\theta)$  is the stator power factor.

➤ Rotor input = Power input - Stator copper and iron losses.

➤ Rotor Copper loss = Slip  $\times$  power input to the rotor.

➤ Developed Power =  $(1 - s) \times$  Rotor input power.



# References



1. Kothari, D.P., Nagrath, I.J., “Electric Machines”, McGraw Hill Publishing Company Ltd, 5<sup>th</sup> Edition, 2017.
2. Murugesh Kumar, K., “Induction and Synchronous machines”, Vikas Publishing House Private Ltd, 2016.

**Thank You**