## CONTROL OF DC DRIVES

=) conventional speed control of DC Drives:

A single motor can be used for different speeds for different works. smooth speed control is possible in DC shunt motor.

The speed of Dc motor is

NA EB CON NA V-IARA

N= K[V-IaRa]

=> Conventional Methods for Dc Motor speed control:

The conventional Methods are

(i) Armorture control Method:

By changing the resistance in the armature by using the ostat control is called Armature control method.

(ii) Field cor Flux control method:

By changing the field flux (d) is called

the field cors flux control method.

(iii) Voitage control method

By Varying the applied Voltage is called Voltage control method,

> speed control of DC shunt motors:

The methods are (i) Armature control method

(ii) Field control method

(iii) voitage control Method

(i) Armature control Method: \* A variable respstance R' is connected in series with armature circuit. There the input voltage 'V' is constant, \* The speed of the motor can be controlled by varying the resistor. The speed equation is Nd V-Ia(Ra+R) \* By increasing the controller resistance the Potential drop across the armature is decreased (because Ia decreases). \* Therefore the motor speed also decreases. 4 This method of speed control is applicable only for speed less than No load speed (base speeds : It not the speed is dangered speed R2>R1 Torque > Fig: Speed. T

## Advantages:


\* simple method of speed control.

## Disadvantages:

# Here, the input power is not charged (V+I). i.e input is constant. The output power is 'Eb.Ia'. It becomes less, .: for lower speeds more and more power is wasted in this controller resistance. Hence this method of speed control is highly inefficient.

\* charge in speed with the charge in load becomes large.

## (ii) Field (or) Flux control Method:

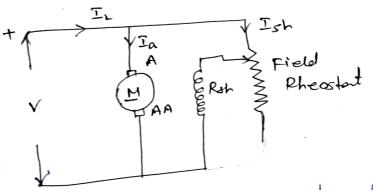

+ The speed is inversely proportional to flux ie

7 By Vanying the flux, the motor speed can be

The flux of a De motor can be changed by changing the field current (Ish). It's obtained he changing the field current (Esh). It's obtained he by a variable resistance connected in series with shunt field winding. Ish = (Riht)

\* By varying the field circuit resistance, the shunt field current can only be decreased. i.e the flux will be decreased.

,

e

