

### 4.13.1 Single-phase Half-wave converter drive

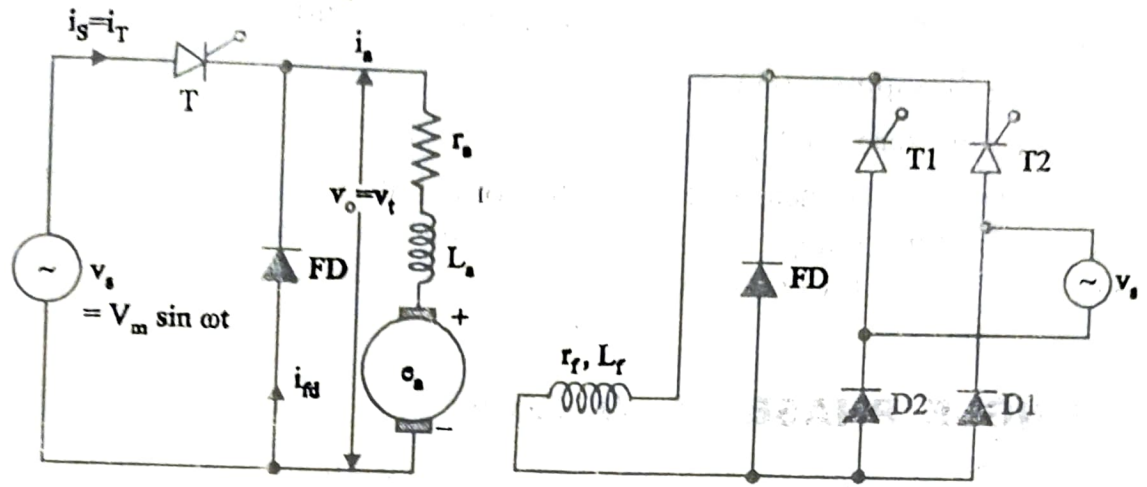


Fig. 4.18

Fig. 4.18 shows a separately excited DC motor, fed through a single phase half-wave converter. To reduce the ripples in the field circuit current, field circuit of motor is fed through a single-phase semiconverter drive. The load is highly inductive, hence the output current is considered to be continuous current. These type of drives can be used upto  $\frac{1}{2}$  kW DC motors

During the positive half cycle of the input supply,  $T$  will be forward biased and it conducts from  $\omega t = \alpha_1$  to  $\pi$ . At  $\omega t = \pi$ , the thyristor  $T$  will be reverse biased, hence output voltage will be zero driving  $\omega t = \pi$  to  $2\pi$ . The inductor  $L_a$  in the motor, will reverse its polarity due to which free wheeling diode (FD) will be forward biased and hence conducts.

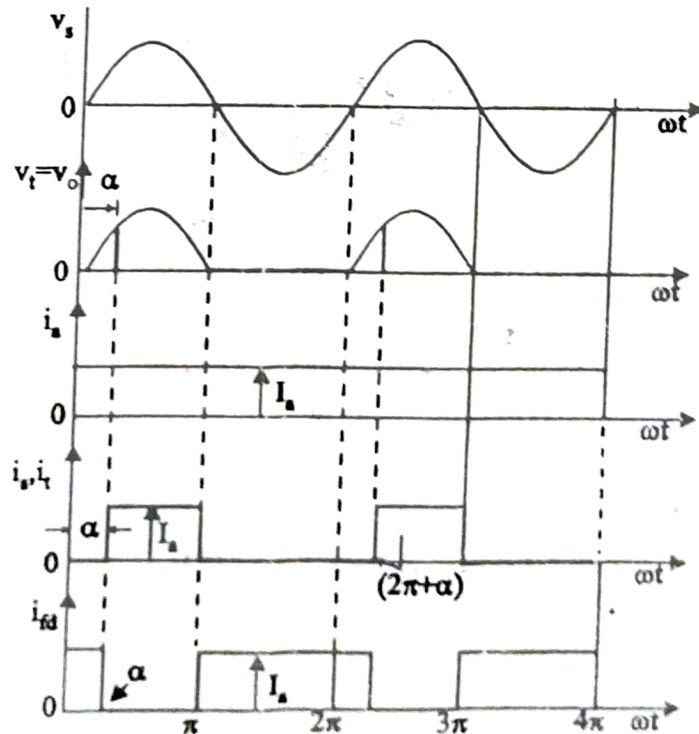


Fig. 4.19

So, the current  $I_a$  will be same and remains constant. Meanwhile during the next half cycle,  $\omega t = 2\pi + \alpha_1$  Thyristor  $T$  is again triggered and the cycle continues.

For single-phase half-wave converter, average output voltage,

$$V_0 = \frac{V_m}{2\pi} (1 + \cos \alpha_1) \text{ for } 0 < \alpha_1 < \pi$$

where,

$V_m$  - maximum value of source voltage.

### 4.13.3 Single-phase full converter Drives

Fig. 4.22 shows a single-phase full converter drive, in which there are two converter. One feeding the armature circuit of the drive and other feeding the field circuit. This scheme of operation has two-quadrant operation. It is applicable for drives upto 15 kW.

During positive half cycle of input supply,  $T_1$  and  $T_2$  will be forward biased and conducts for  $\omega t = \alpha_1$  to  $\pi + \alpha_1$  and the motor will be connected to the supply. At

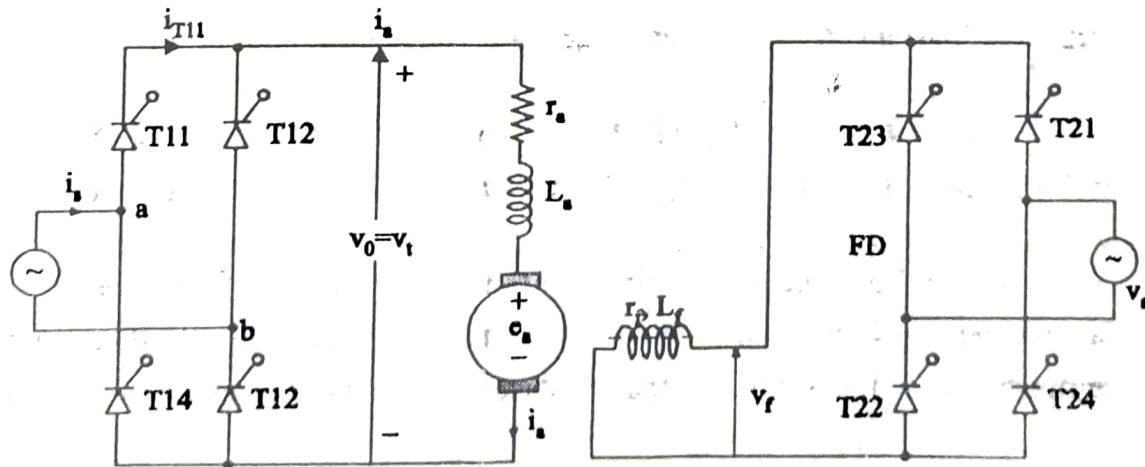


Fig. 4.22

$\omega t = \pi + \alpha_1$ ,  $T_3$  and  $T_4$  will be triggered. Hence  $T_1$  and  $T_2$  will be turned off because of reversed supply appearing across them. Now the armature current will transfer from  $T_1T_2$  to  $T_3T_4$ . Hence there is no discontinuity in armature current so free wheeling diode is not needed. During  $\omega t = \alpha_1$  to  $\pi$  energy flows from source to load. But during  $\omega t = \pi$  to  $\pi + \alpha_1$ , the energy is fed back to source from load. This is used for applying regenerative braking in the drive.

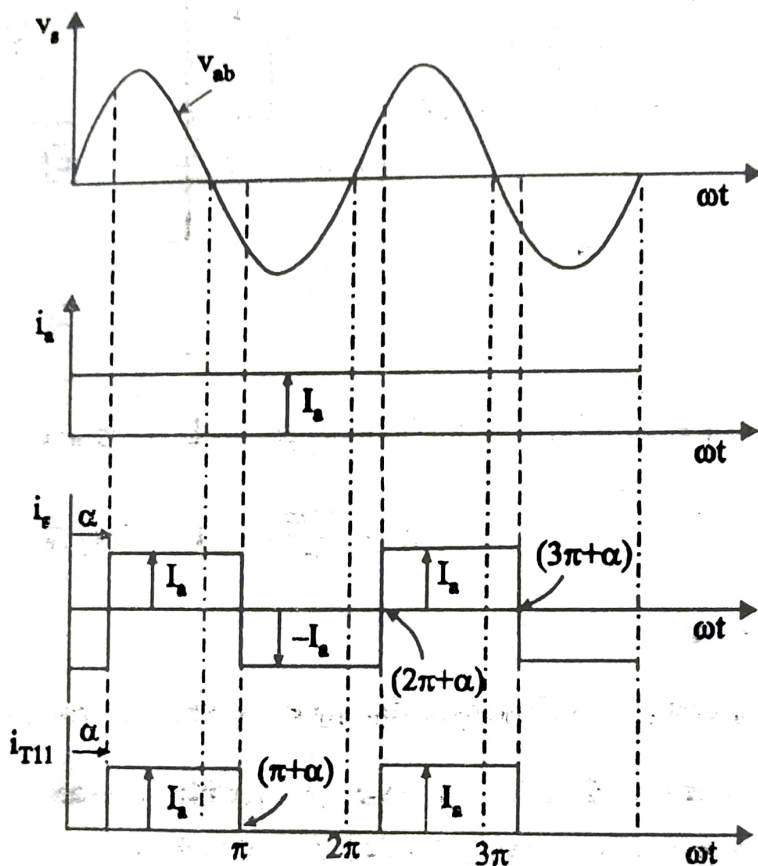


Fig. 4.23

For a single-phase full wave converter, the output voltage (applied to the armature) is given by,

$$v_0 = \frac{2v_m}{\pi} (1 + \cos \alpha) \text{ for } 0 \leq \alpha_1 \leq \pi$$