

# Medium Tr. line


Methods of solution of medium tr. line.

- i) End Condenser method
- ii) Nominal T method
- iii)  $\pi$  method
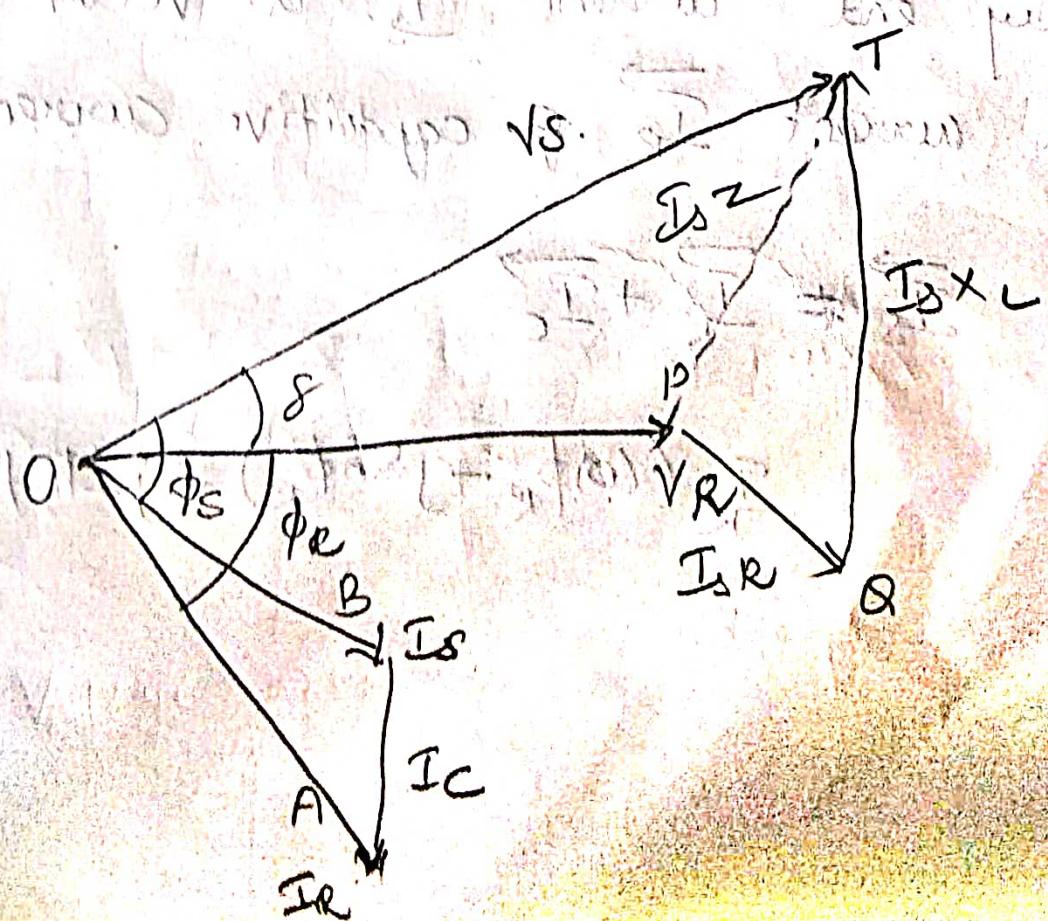
## End Condenser method.

The capacitance of line is lumped or concentrated at the receiving method.

This method of localizing capacitance at the load is end condenser method.





Let  $I_R$  be the load current / phase  
 $R$  " " = resistance / "  
 $X_L$  " " = inductive reactance / "  
 $C$  " " = capacitor / "

$V_S$  " " = sending end voltage

$V_R$  " " = receiving end voltage

$\cos \phi_R$  " " = receiving end power factor

$V_R$  is taken as ref. vector.

$$\vec{V}_R = V_R + j0$$

The current  $I_R$  lags  $V_R$  by an angle  $\phi_R$

$$\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$$

capacitive current  $\vec{I}_C = j V_R \omega C$

$$= j 2\pi f C V_R$$

Sending end current  $\vec{I}_S$  is vector sum of load current  $\vec{I}_R$  & capacitive current  $\vec{I}_C$

$$\vec{I}_S = \vec{I}_R + \vec{I}_C$$

$$= I_R (\cos \phi_R - j \sin \phi_R) + j 2\pi f C V_R$$




$$\text{Voltage drop/phase} = \vec{I}_S Z = \vec{I}_S (R + jX_L)$$

$$\text{Sending end voltage} = \vec{V}_S = \vec{V}_R + \vec{I}_S Z$$

$$= \vec{V}_R + \vec{I}_S (R + jX_L)$$

$$\% \text{ Voltage reg.} = \frac{V_S - V_R}{V_R} \times 100$$
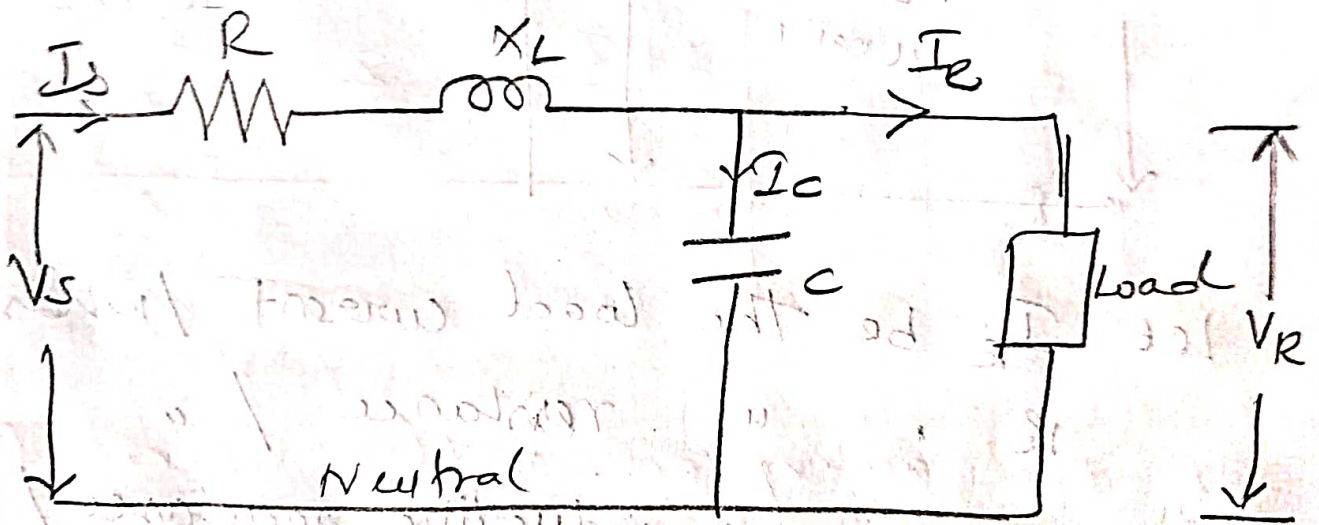
$$\% \text{ Tr. l.} = \frac{V_R I_R \cos \phi_R}{V_R I_R \cos \phi_R + I_S^2 R} \times 100$$



### Limitations

There is a considerable amount of error in calculations, because the distributed capacitance has been assumed to be lumped.