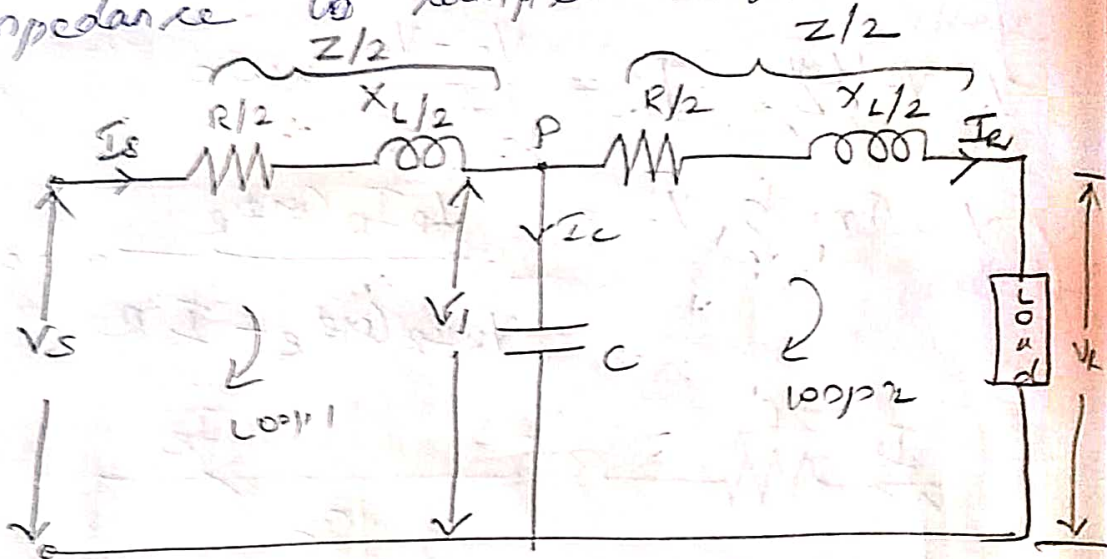


Nominal T method.

The nominal T method, the line capacitance to be concentrated at the mid point of line and half the line impedance is lumped on its either side.



Let I_R be the load current / phase

R " " resistance / μ

X_L " " inductive reactance / μ

C " " capacitance / μ

V_S " " phase voltage at sending end.

V_R " " receiving end.

V_1 be the voltage across capacitor.


Total series impedance $Z = R + jX_L$

Shunt admittance $Y = G + j\omega C$

Shunt
conductance

$$G = R$$

$$Y = j\omega C$$

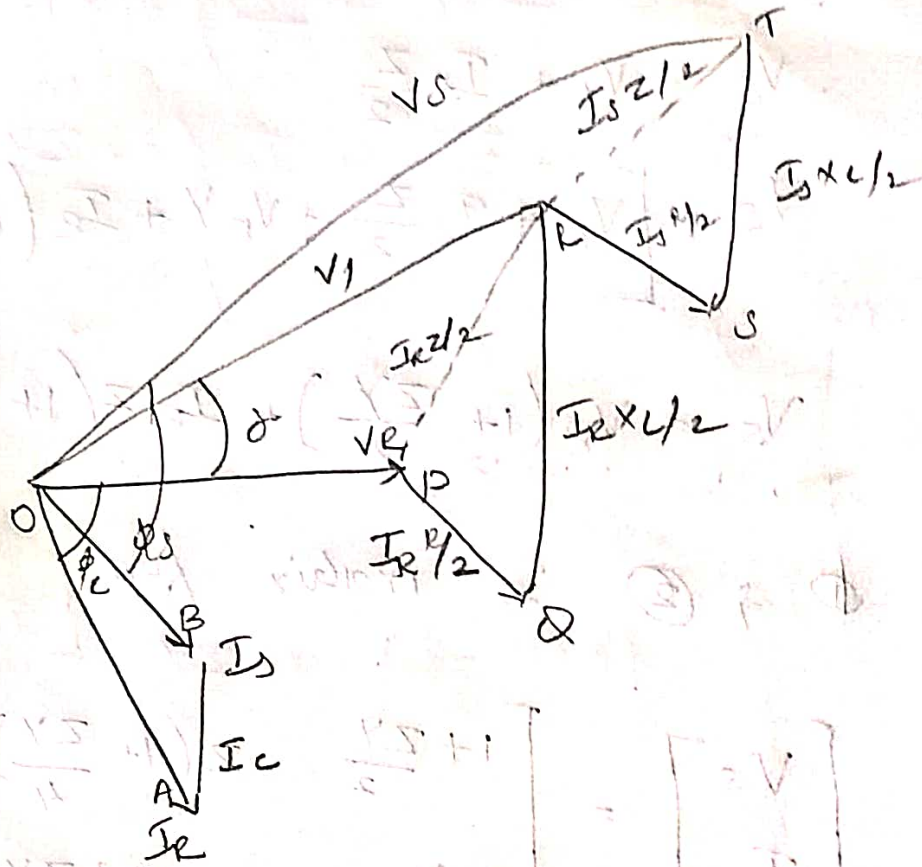

Apply KVL at loop 2

$$V_1 = V_R + I_R \frac{Z}{2}$$

Capacitive current $I_C = V_1 \cdot j\omega C$

$$I_C = Y V_1 = \left(V_R + I_R \frac{Z}{2} \right) Y$$

Apply KCL at node P.

$$I_S = I_C + I_R$$

$$I_S = I_R + V_R Y + I_R \frac{Z}{2} Y$$

$$I_S = V_R Y + I_R \left(1 + \frac{ZY}{2} \right) \quad \text{--- (1)}$$

Apply KVL at loop 1.

$$V_S = V_L + I_S \frac{Z}{2}$$

$$V_S = \left[V_R + I_R \frac{Z}{2} + V_R Y + I_R \left(1 + \frac{ZY}{2} \right) \right] \frac{Z}{2}$$

$$V_S = V_R \left(1 + \frac{ZY}{2} \right) + I_R Z \left(1 + \frac{ZY}{4} \right) \quad \text{--- (2)}$$

eq. (1) & (2) in matrix form

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \left(1 + \frac{ZY}{4} \right) \\ Y & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

Let the receiving end voltage at not load be V_R .

$$\therefore I_R = 0$$

$$I_S = I_C$$

$$V_R' = V_1$$

$$\therefore P_{in} = \frac{P_R(3\phi)}{P_R(3\phi) + 3 \left[I_R^2 \frac{R}{2} + I_S^2 \frac{R}{4} \right]}$$