


**19EE502 / POWER ELECTRONICS AND DRIVES**

**V SEM EEE**

## **Unit 2: DC CONVERTERS**


*TOPIC – Single Phase Controlled Converters (2)*

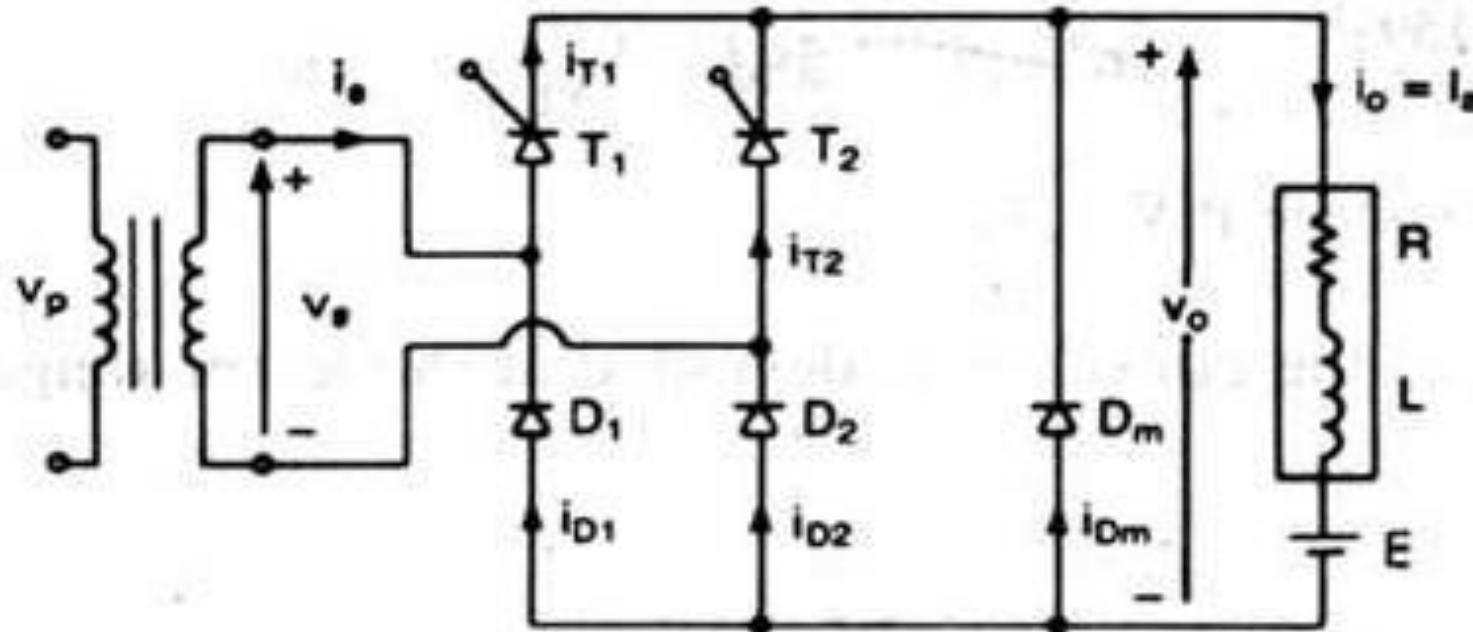
#### 4. SINGLE PHASE SEMI CONVERTER (2 Pulse)




(a) Circuit

## 4. SINGLE PHASE SEMI CONVERTER

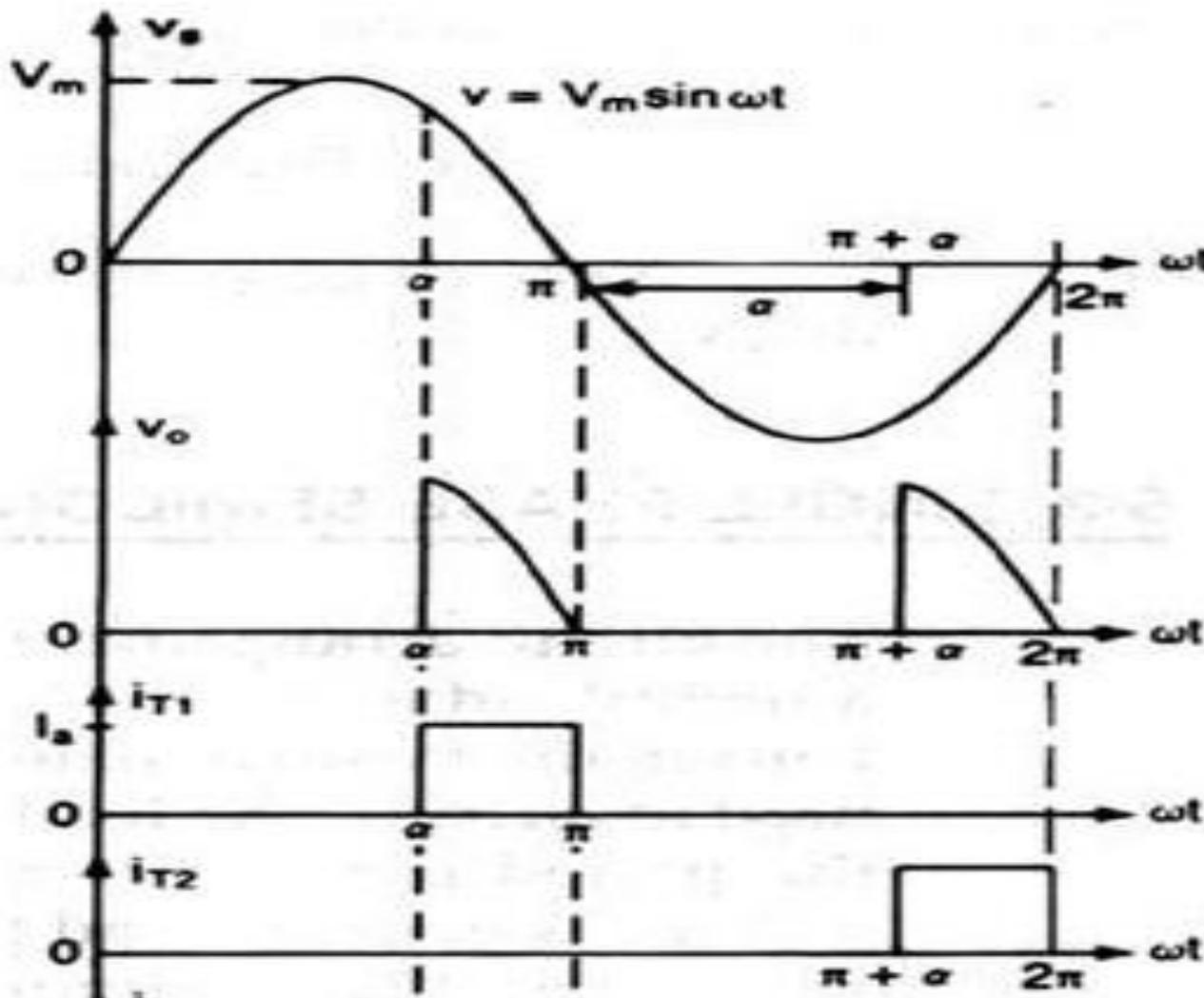


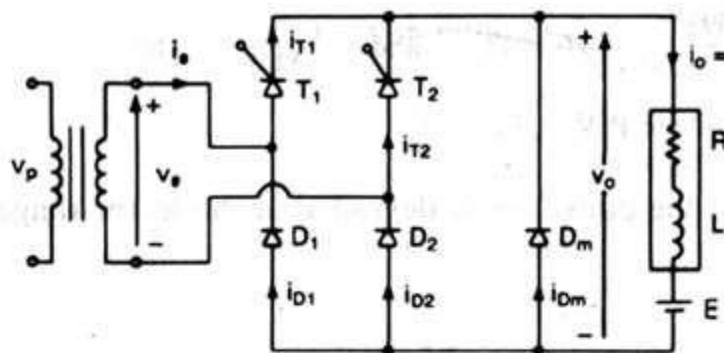

(a) Circuit

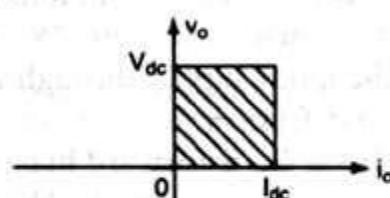

(b) Quadrant

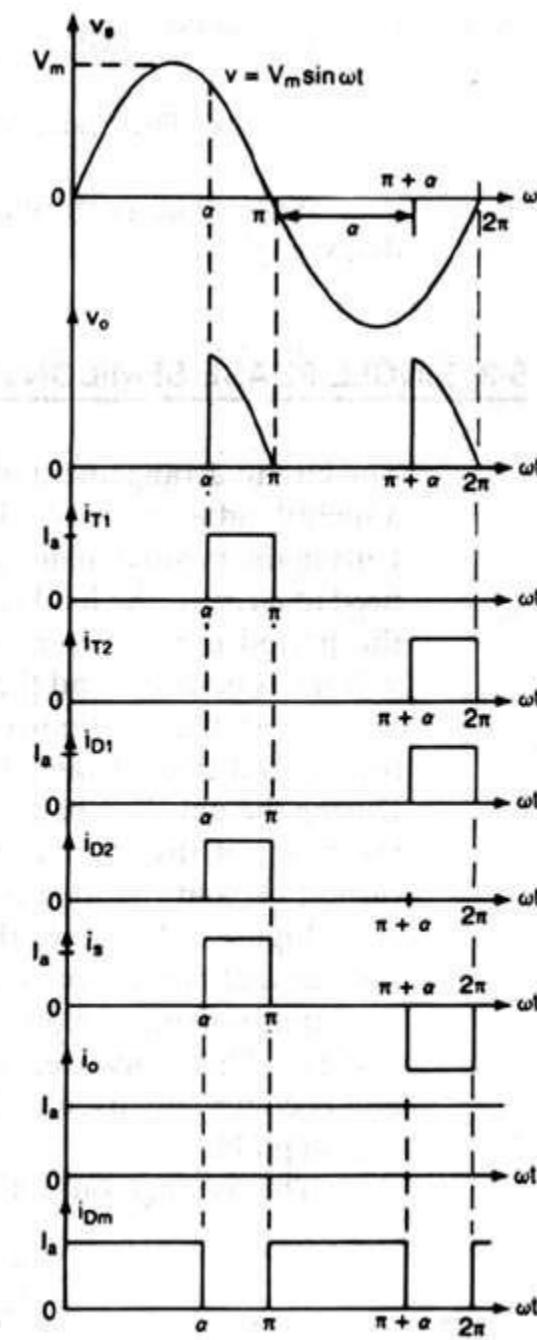

(c) Waveforms

# Single-Phase Semiconverter

$$V_{dc} = \frac{2}{2\pi} \int_{\alpha}^{\pi} V_m \sin(td(\omega t + \frac{V_m}{\pi}(1+\alpha))) \cos(td(\omega t + \frac{V_m}{\pi}(1+\alpha))) dt$$

$$V_{rms} = \sqrt{\frac{2}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2(td(\omega t + \frac{V_m}{\pi}(1+\alpha))) dt}$$

# Single-Phase Semiconverter (*RL-load*)

Mode 1  
 $0 \leq \omega t \leq \alpha$

$$L \frac{di_{L1}}{dt} + Ri_{L1} + E = 0$$

$$I_{L1} = i_{L1}(\omega t = \alpha) = I_0 e^{-\frac{R\alpha}{L}} - \frac{E}{R} \left[ \frac{1 - e^{-\frac{R\alpha}{L}}}{1 - e^{-\frac{R\omega}{L}}} \right]$$

Mode 2

$\alpha \leq \omega t \leq \pi$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

$$\theta = \tan^{-1} \frac{\omega L}{R}$$

$$L \frac{d^2i_L}{dt^2} + Ri_L + E = \sqrt{2} V_s \sin \omega t$$

$$I_{L2} = \sqrt{\frac{2}{Z}} \left[ I_{L1} + \frac{E}{R} + \frac{E - \sqrt{\frac{2V_s}{R}}}{Z} \sin(\alpha - \theta) \right] e^{\frac{R}{L} \frac{\alpha}{\omega}}$$

$$\sin(\omega t - \theta)$$

# Single-Phase Semiconverter (*RL*-load)

RMS Current

for

Thyristor

RMS Current

for

Thyristor

$$I_R = \sqrt{\frac{1}{2} \int_{\alpha}^{\pi} i_L^2 d(\omega t)}$$

$$I_A = \frac{\pi}{2} \int_{\alpha}^{\pi} i_L d(\omega t)$$

RMS Output  
Current

$$I_{rms} = \sqrt{\frac{1}{2} \int_0^{\alpha} i_{L1}^2 d(\omega t) + \frac{1}{2} \int_{\alpha}^{\pi} i_L^2 d(\omega t)}$$

t

AVG Output  
Current

$$I_{dc} = \frac{1}{2} \int_0^{\alpha} i_1 d(\omega t) + \frac{1}{2} \int_{\alpha}^{\pi} i_2 d(\omega t)$$

t

The single-phase semiconverter has an RL load of  $L = 6.5\text{mH}$ ,  $R = 2.5 \text{ Ohm}$ , and  $E = 10 \text{ V}$ . The input voltage is  $V_s = 120 \text{ V(rms)}$  at  $60 \text{ Hz}$ .

Determine the load current  $I_{L0}$  at  $\omega t = 0$ , and the load

current  $I_{L1}$  at  $\omega t = \alpha = 60^\circ$ ,

(b) the average thyristor current  $I_A$

(c) the rms thyristor current  $I_R$

(d) the rms output current  $I_{rms}$  and

(e) the average output current  $I_{dc}$