



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB204 – LINEAR AND DIGITAL CIRCUITS


II YEAR/ III SEMESTER

UNIT 1 – FUNDAMENTALS OF OPAMP

TOPIC 4 – Adder and Subtractor



Guess?????

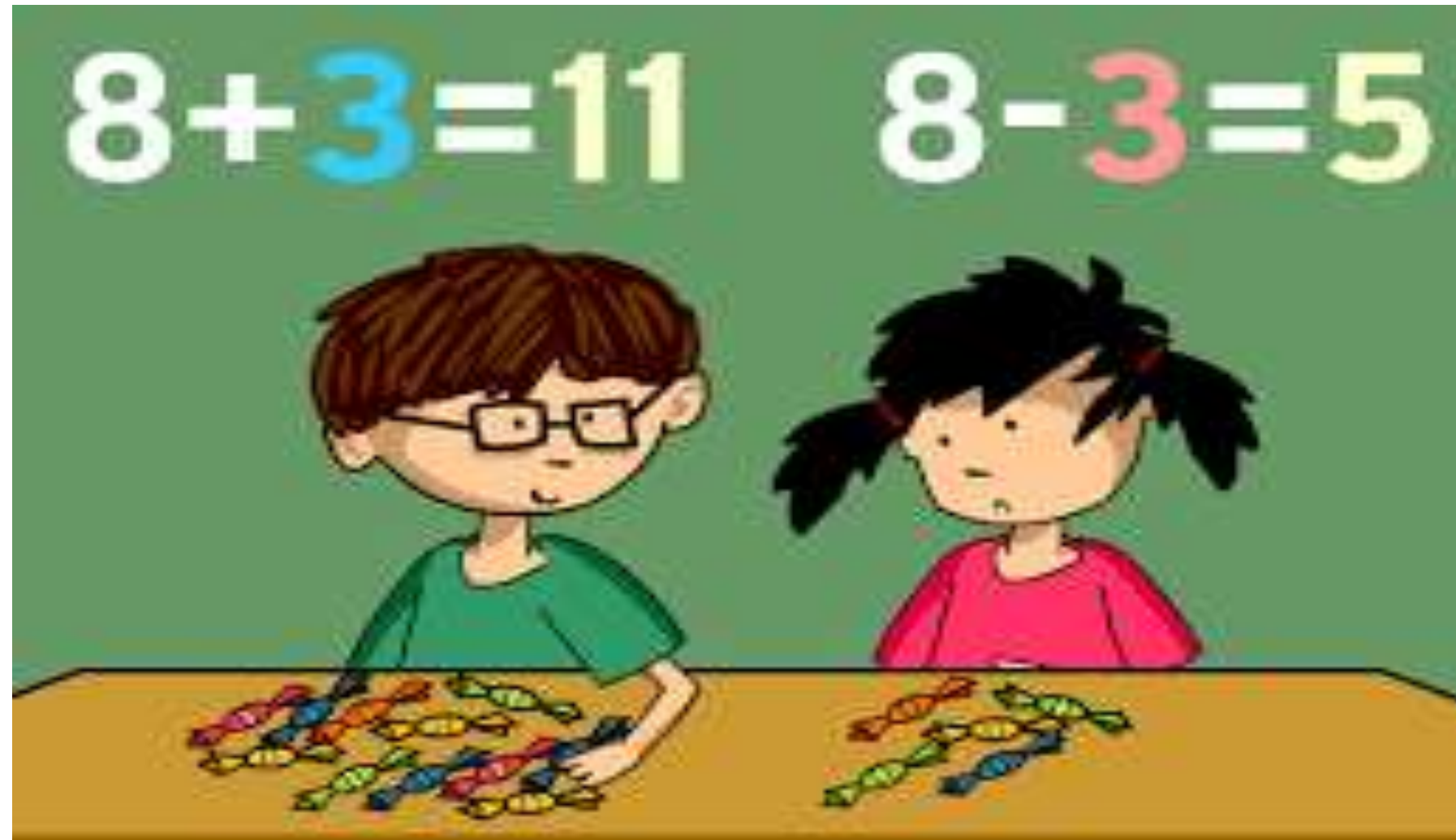




Why?



- In digital circuits, an adder–subtractor is a circuit that is capable of adding or subtracting numbers
- A circuit that does adding or subtracting depends on a control signal
- It is also possible to construct a circuit that performs both addition and subtraction at the same time
- The Subtract or also called a differential amplifier, uses both the inverting and non-inverting inputs to produce an output signal which is the difference between the two input voltages V_1 and V_2



Adder using Op Amp

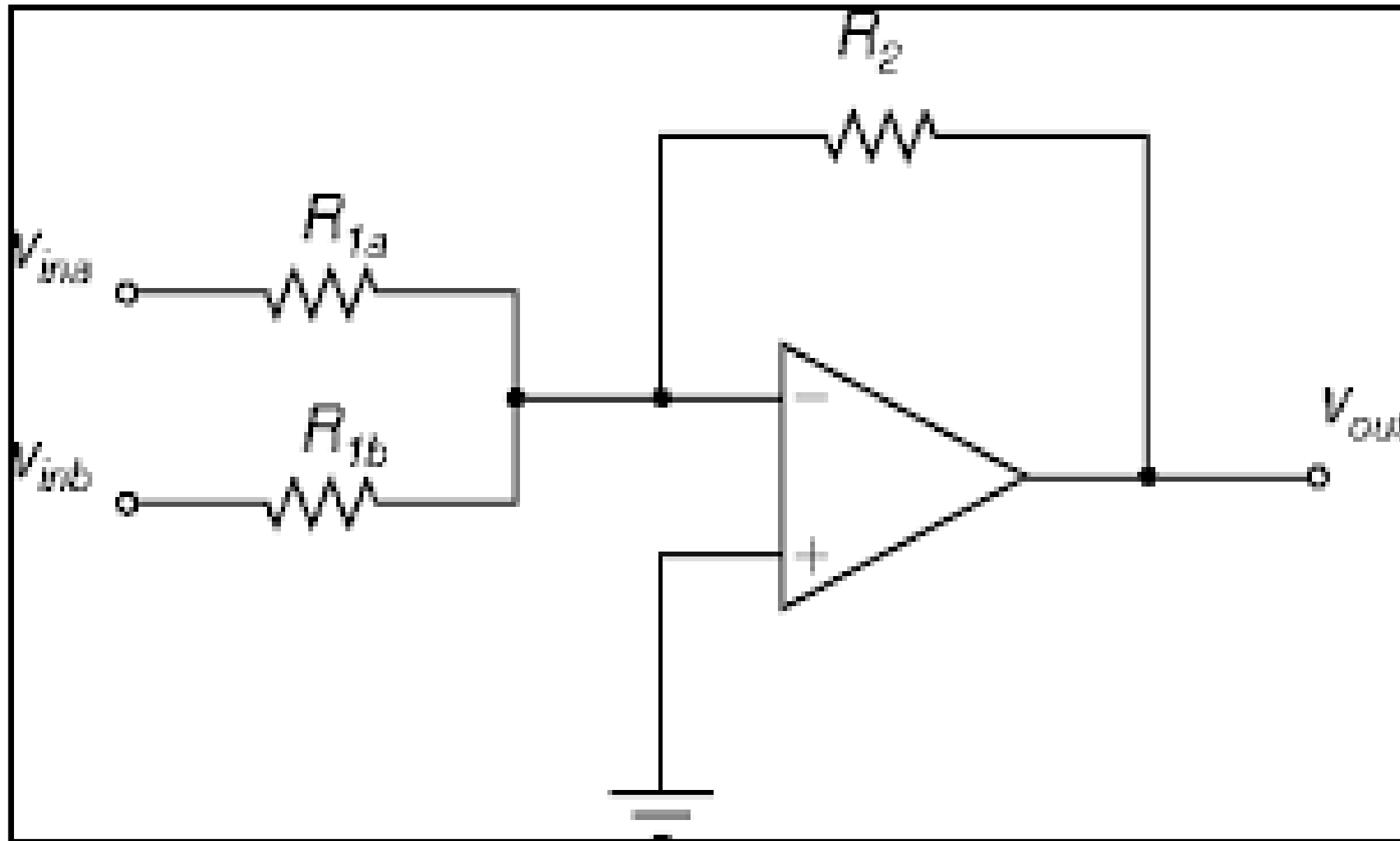




Adder using Op Amp



- ❑ Op-amp is used to design a circuit whose output is the sum of several input signals
- ❑ If the input resistors are equal in value then the summed output voltage is as given and gained +1
- ❑ If the input resistors are unequal in value then the output voltage is weighted sum and becomes
- ❑ $V_{out} = - (V_1(R_2/R_{1a}) + V_2(R_2/R_{2a}) + \text{etc})$



Subtractor using Op Amp

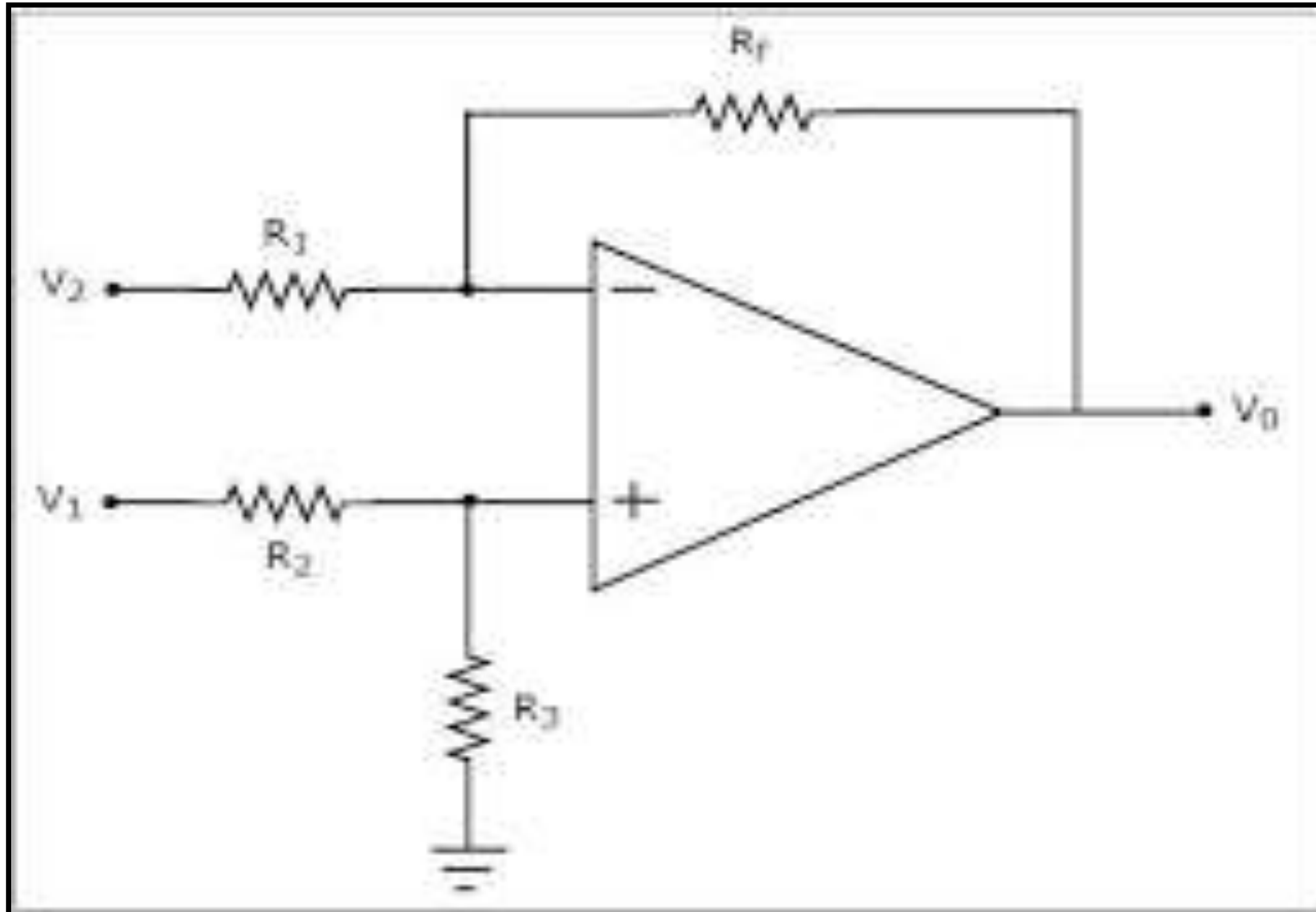



Subtractor using Op Amp



- ❑ Subtractor is used to produce an output signal which is difference between the two input voltages V_1 , V_2 allowing one signal to be subtracted from another
- ❑ If the input resistors are equal in value then the output voltage is gained as $+1$
- ❑ If the input resistance are unequal then the circuit become a differential amplifier
- ❑ Output will be, $V_0 = V_1 - V_2$



Activity



In class activity

Students should make the correct shape from the given tangram kit.




Audio Mixer



- ❑ A **mixer** is an electronic device which is often **used for** changing the quality and the levels of **audio** signals
- ❑ It is also known as a **mixing** console, an **audio mixer**, or a soundboard
- ❑ Using a **mixer** is the most convenient way to route or combine various **audio** signals and even change the timbre and dynamics of the sound



Digital to Analog conversion

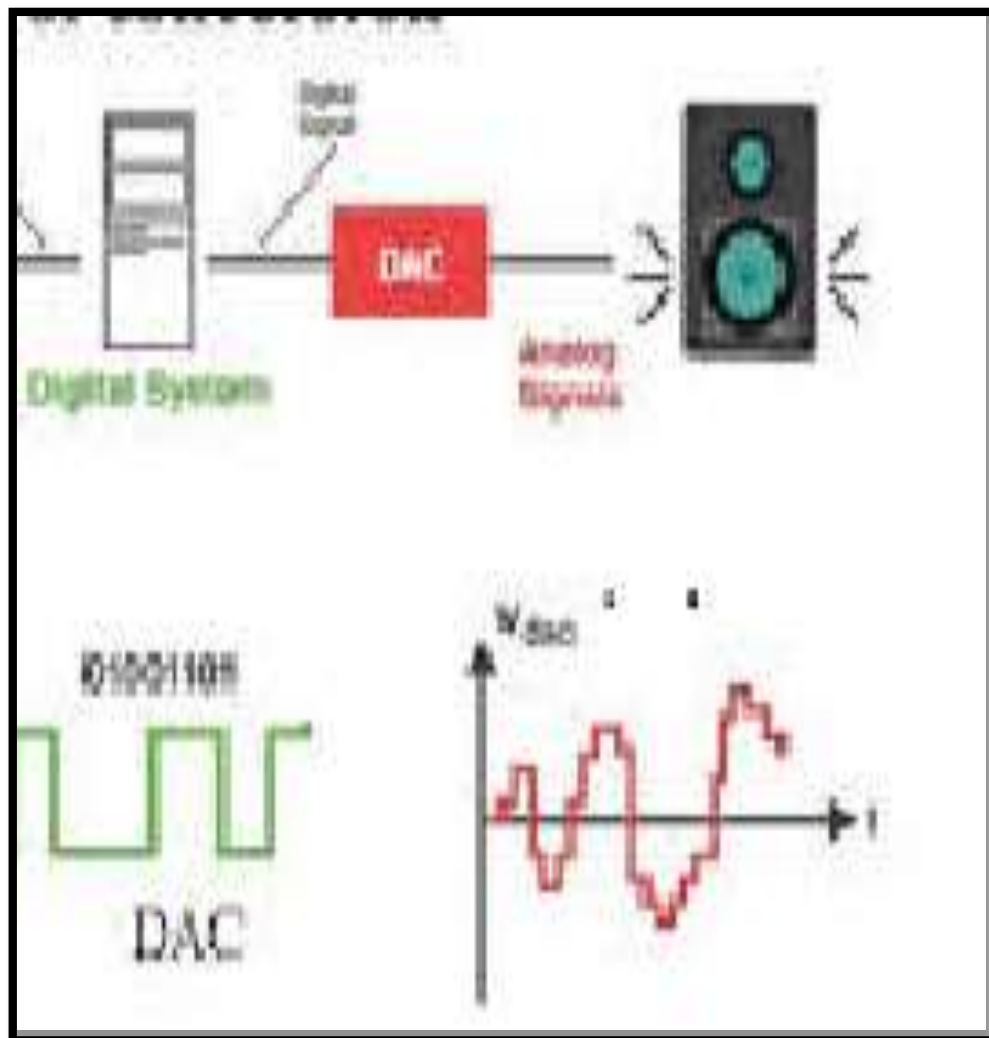

- ❑ In the real world, most data are available in the form of analog in nature.
- ❑ While manipulating the data, these two converting interfaces are essential to digital electronic equipment
- ❑ DAC will process the digital sound signal back into the analog signal that is used by audio output equipment such as a speaker



Applications






Adder and Subtractor Amplifier



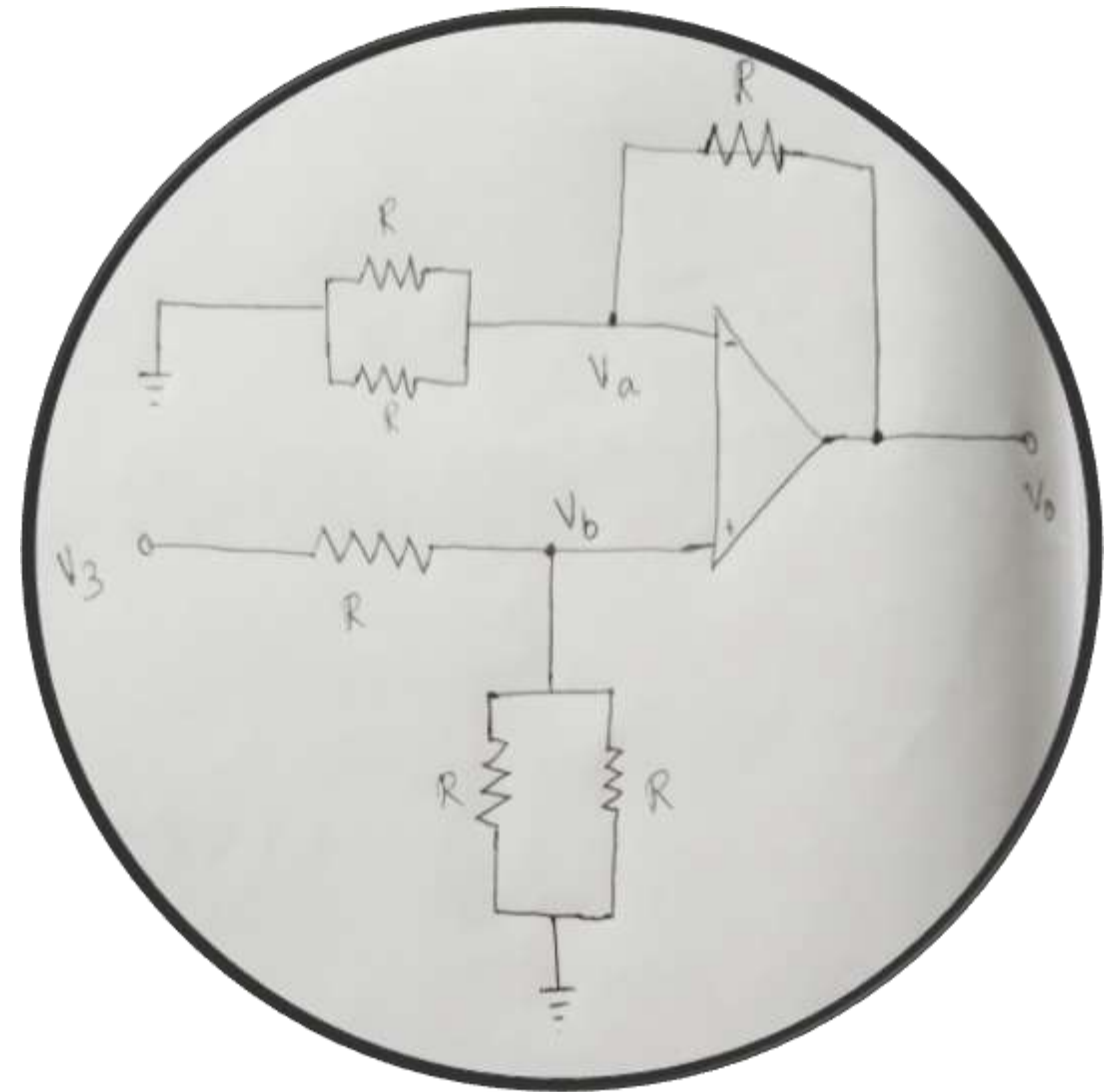- It is possible to perform addition and subtraction simultaneously with a single op-amp using the circuit
- The output voltage V_o can be obtained by using superposition theorem
- To find output voltage V_{o1} due to V_1 alone, make all other input voltages V_2, V_3 and $V_4 = 0$





Assessment



1. Determine the expression of output voltage for inverting summing amplifier consisting of four internal resistors? (Assume the value of internal resistors to be equal)

a) $V_o = -(R_f/R) \times (V_a + V_b + V_c + V_d)$

b) $V_o = (R_f/R) \times (V_a + V_b + V_c + V_d)$

c) $V_o = (R/R_f) \times (V_a + V_b + V_c + V_d)$

d) None of the mentioned

2. The summing amplifier is an application of:

a) Noninverting op-amp

b) Inverting op-amp

c) Integrator

d) Differentiator



THANK YOU