

SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



*Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai*

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

19EET301 / POWER ELECTRONICS AND DRIVES

V SEM EEE

Unit 2: DC CONVERTERS

Dr. R. Senthil Kumar

Associate Professor

Dept of EEE

TOPIC – Single Phase Controlled Converters (1)



Phase-Control Converters

Single-Phase

Three-Phase

Half & Semi conv

Half & Semi conv

Full converter

Full converter

Dual converter

Dual converter

Semiconverter

..is a one-quadrant converter and it has one polarity

Full converter

..is a two-quadrant converter and the polarity of its output can be either positive or negative.

However

the output current of full converter has one polarity only

Dual converter

..can operate in four quadrants ; both the output voltage and current can be either positive or




CLASSIFICATION OF RECTIFIERS




- BASED ON INPUT SUPPLY
 - SINGLE PHASE
 - THREE PHASE
- BASED ON QUADRANT OPERATION
 - 1 QUADRANT
 - 2 QUADRANT
 - 4 QUADRANT
- BASED ON NO. OF PULSES
 - ONE PULSE
 - TWO PULSES
 - THREE PULSES
 - SIX PULSES




PHASE CONTROLLED RECTIFIERS

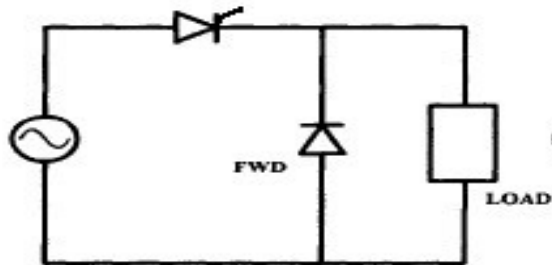


(a) 1-PHASE HALF-WAVE

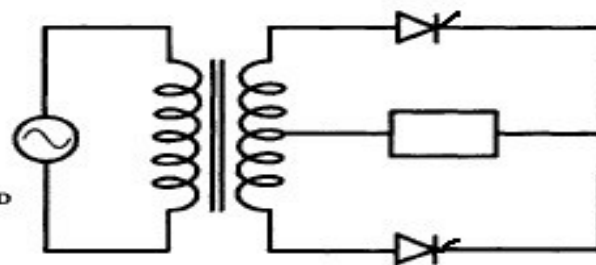


(b) 1-PHASE FULL-WAVE

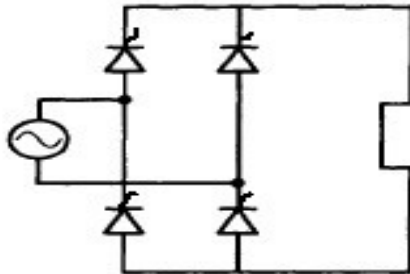


(c) 1-PHASE BRIDGE

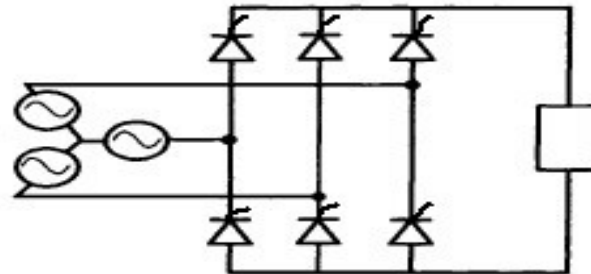

(d) 3-PHASE BRIDGE

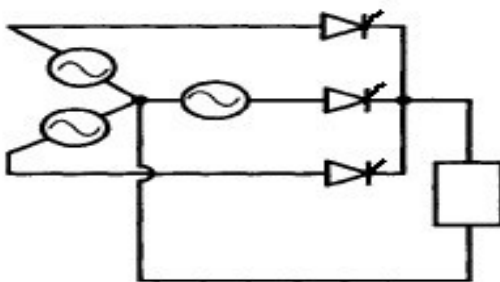

(e) 3-PHASE HALF-WAVE

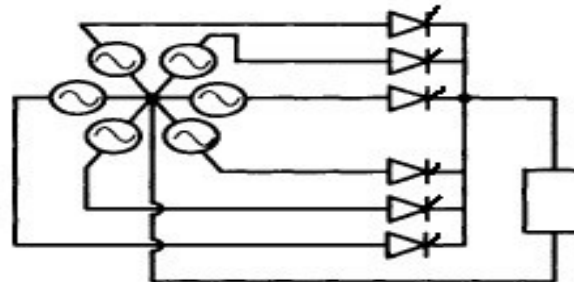

(f) 6-PHASE FULL WAVE



APPLICATIONS OF RECTIFIERS

- DC MOTOR SPEED CONTROL
- DC SUPPLY FOR INVERTERS
- ELECTROCHEMICAL PROCESSES
- DC TRACTION
- HVDC TRANSMISSION




TOPICS




1. Single Phase Half Wave Converter – R Load
2. Single Phase Half Wave Converter – RL Load
3. Single Phase Half Wave Converter – RL Load with FD
4. Single Phase Semi Converter
5. Single Phase Full Converter




1. SINGLE PHASE HWC WITH R LOAD

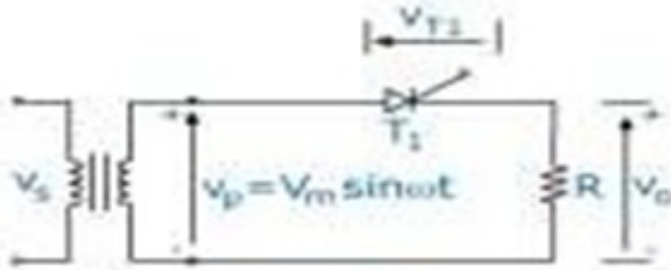

(a) Circuit

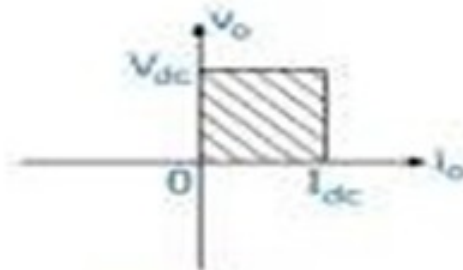

(b) Quadrant

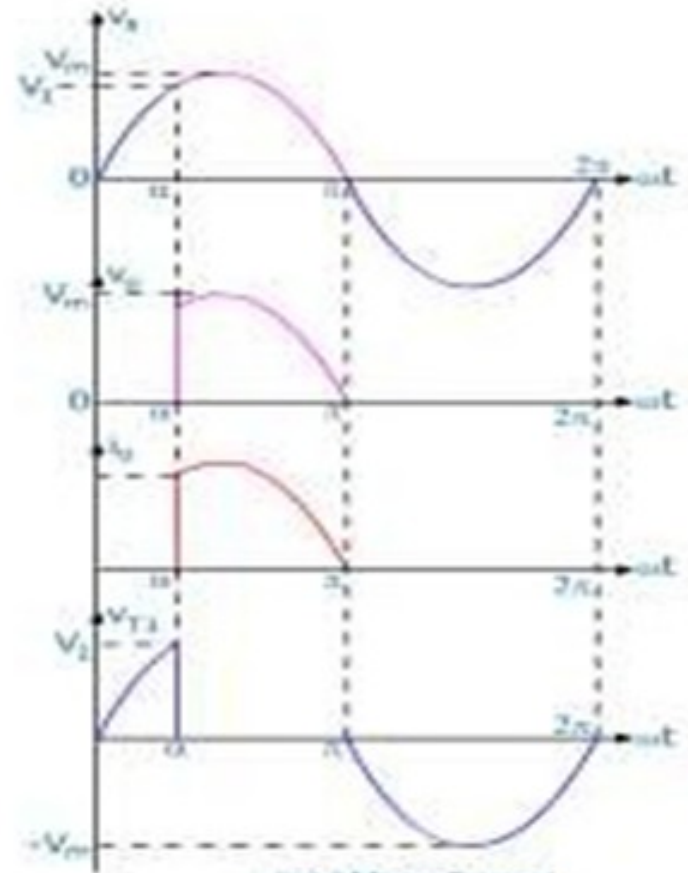

(c) Waveforms



FIRING ANGLE α

- Angle between the zero crossing of the input voltage and the instant thyristor is fired.



AVERAGE OUTPUT VOLTAGE- R LOAD



The average output voltage V_{dc} is given by

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$


$$V_{dc} = \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$V_{dc} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

The output voltage V_{dc} can be varied from V_m/π to zero as the firing angle α varies from zero to π .




2. SINGLE PHASE HWC WITH RL LOAD

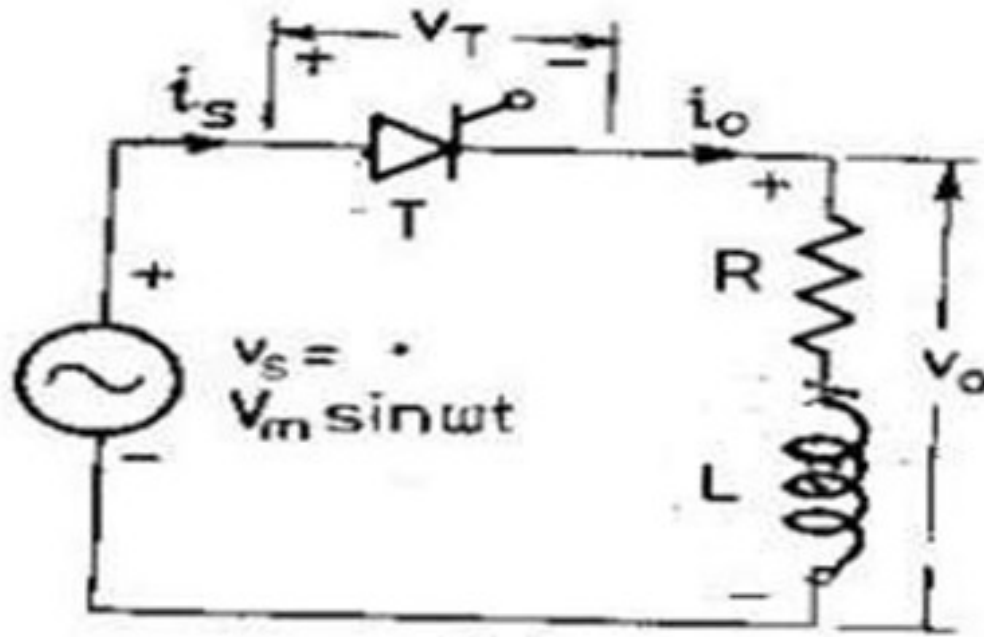




2. SINGLE PHASE HWC WITH RL LOAD

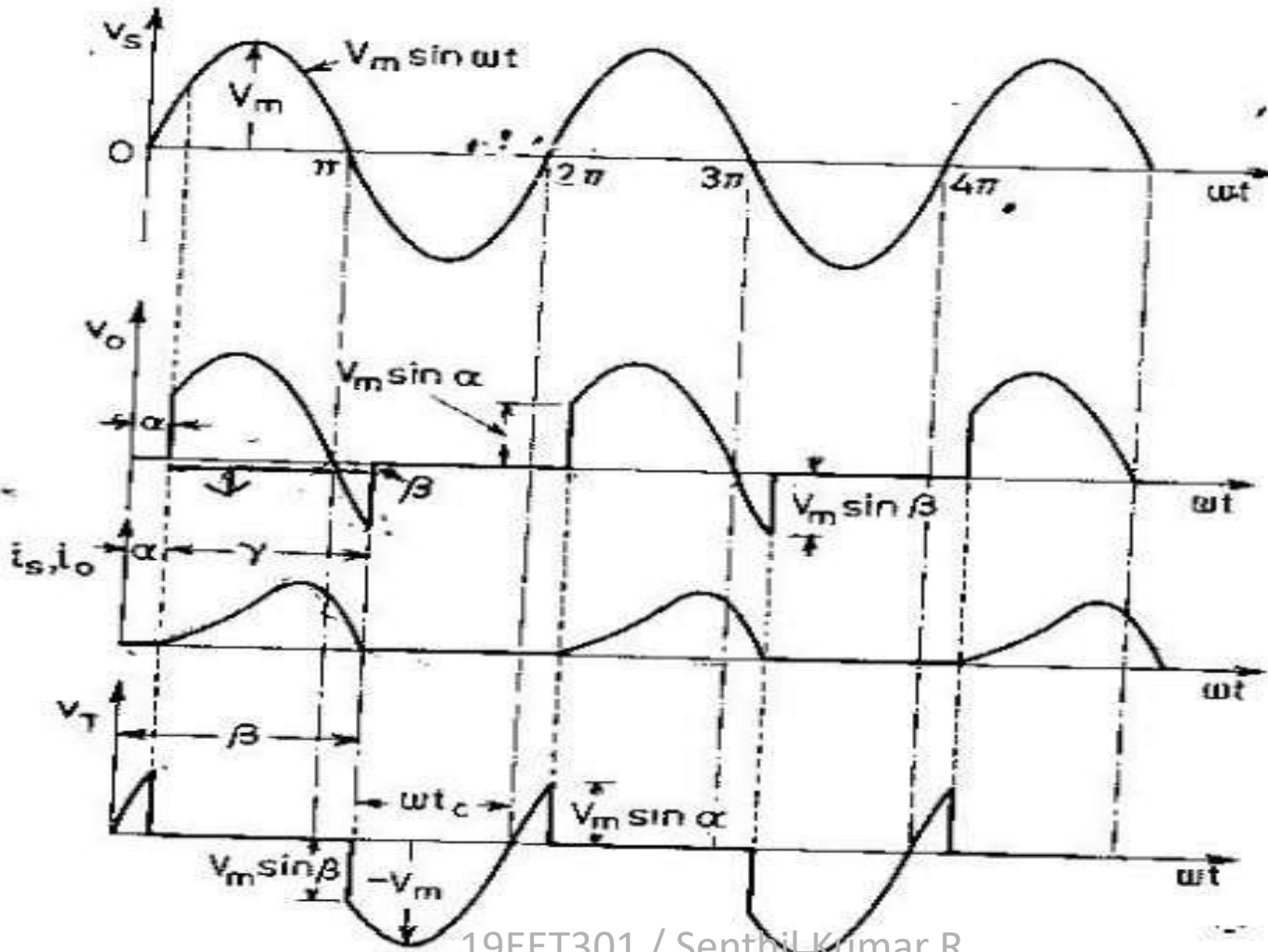




3. SINGLE PHASE HWC WITH RL LOAD AND FD

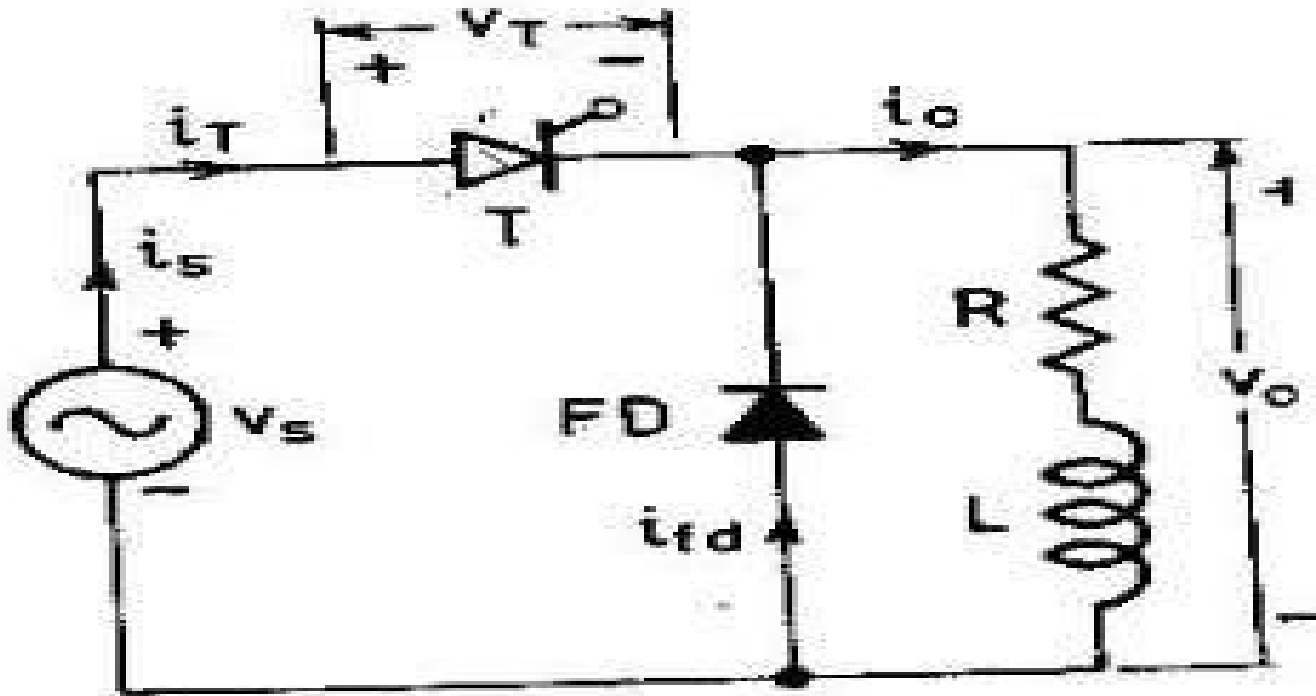



3.SINGLE PHASE HWC WITH RL LOAD AND FD

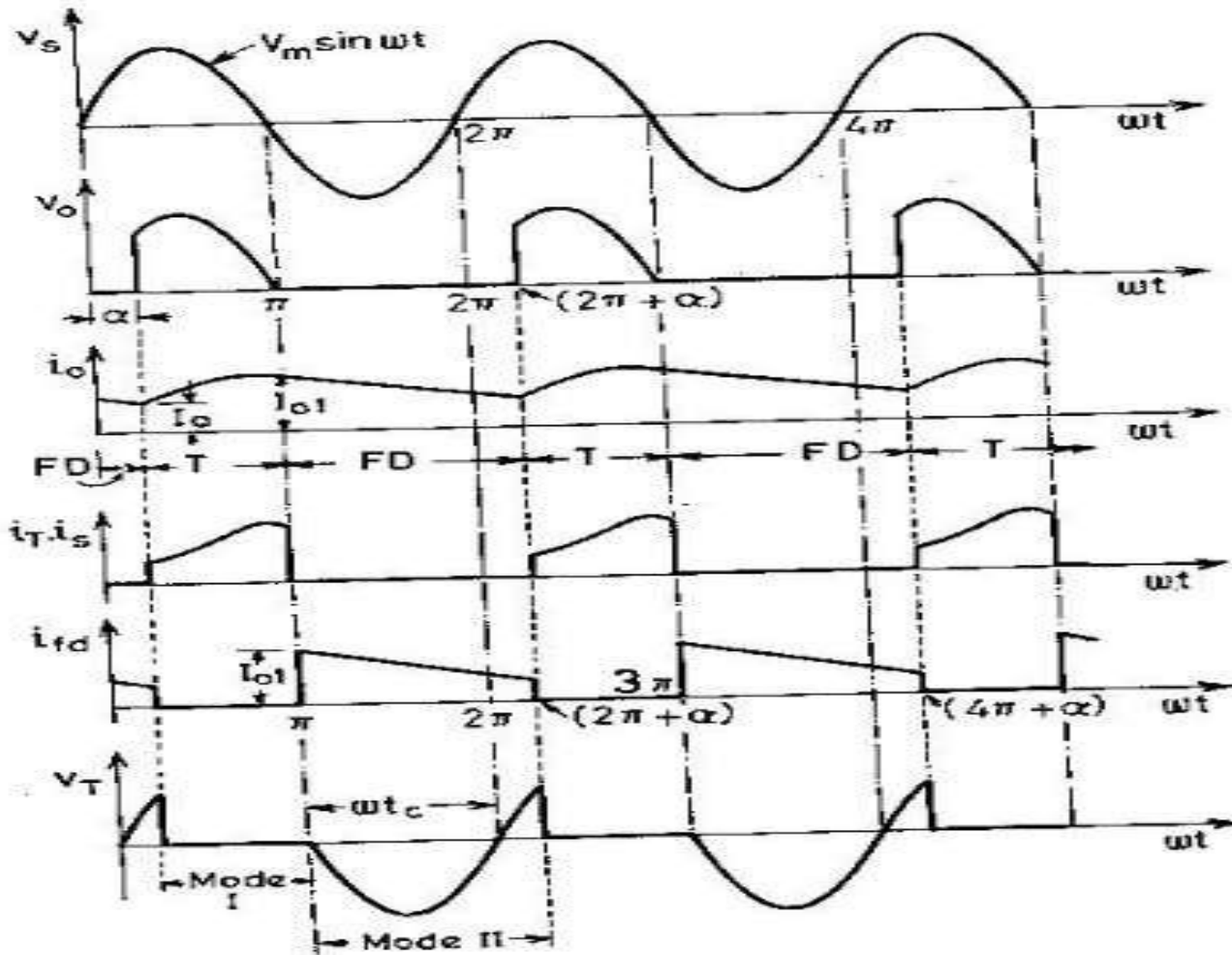



ADVANTAGES OF USING FREEWHEELING DIODE



- Input power factor is improved
- Load current waveform is improved and load performance is better.

Main functions of fwd

- It prevents the reversal of load voltage except for a small voltage drop
- It transfers the load current away from the main rectifier thereby allowing all the thyristors to regain their blocking states

Average Output Voltage

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) dt = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

Maximum Output Voltage

$$V_{dm} = \frac{V_m}{\pi}$$

Normalizing Output Voltage

$$V_n = \frac{V_{dc}}{V_{dm}} = 0.5(1 + \cos \alpha)$$

RMS Output Voltage

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2(\omega t) dt} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$



EVALUATION

