

## UNIT - II

### BJT AMPLIFIERS

#### Method of drawing Small-signal Equivalent circuit

- \* A transistor can be treated as a two port Network.
- \* The terminal behaviour of any 2 port network can be specified by the terminal voltage  $V_1$  &  $V_2$  at port 1 & port 2 respectively & currents  $i_1$  &  $i_2$  entering port 1 & 2 respectively as shown in Fig:



- \* From 4 variables  $V_1, V_2$  &  $i_1, i_2$  2 can be selected as independent variables & remaining 2 can be expressed in terms of the independent variables.

\* The transistor can be analyzed using various 2 port parameters which of the following are more important.

1. Z - parameter (or) Impedance parameter
2. Y - parameter (or) Admittance parameter
3. H - parameter (or) Hybrid parameter.

H-parameter (or) Hybrid parameters: \* 2 Mark

\* If the input current  $i_1$  & the output voltage  $V_2$  are taken as independent variables, the input voltage  $V_1$  & output current  $i_2$  can be expressed as

$$V_1 = h_{11} i_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \quad \text{--- (2)}$$

\* The 4 h-parameters  $h_{11}, h_{12}, h_{21}, h_{22}$  are defined as

$$h_{11} = \left[ \frac{V_1}{i_1} \right] \text{ with } V_2 = 0 \text{ in eqn (1)} \rightarrow \text{input impedance with output port short circuited.}$$

$h_{22} = \left[ \frac{i_2}{v_2} \right]$  with  $i_1 = 0$  in eqn ②  $\Rightarrow$  output admittance with input port short circuited.

$h_{12} = \left[ \frac{v_1}{v_2} \right]$  with  $i_1 = 0$  in eqn ①  $\Rightarrow$  Reverse voltage transfer gain with input port open circuited.

$h_{21} = \left[ \frac{i_2}{i_1} \right]$  with  $v_2 = 0$  in eqn ②  $\Rightarrow$  Forward current gain with output port short circuited.

\* The dimensions of h-parameters are

$$h_{11} = \Omega \quad h_{22} = \text{mhos} \quad h_{21} \text{ \& } h_{12} = \text{dimensionless}$$

\* Alternate subscript notation recommended by IEEE is commonly used

$i = 11 = \text{input}; \quad o = 22 = \text{output} \quad \text{--- ③}$

$f = 21 = \text{forward Transfer}; \quad r = \text{reverse Transfer} \quad \text{--- ④}$

\* According to eqn ③ & ④ for common emitter amplifier


$$h_{11} = h_{ie}; \quad h_{22} = h_{oe} \quad \text{--- ⑤}$$

$$h_{12} = h_{re}; \quad h_{21} = h_{fe} \quad \text{--- ⑥}$$

$$\text{①} \Rightarrow v_1 = h_i i_1 + h_r v_2 \quad \text{--- ⑦}$$

$$\text{②} \Rightarrow i_2 = h_f i_1 + h_o v_2 \quad \text{--- ⑧}$$

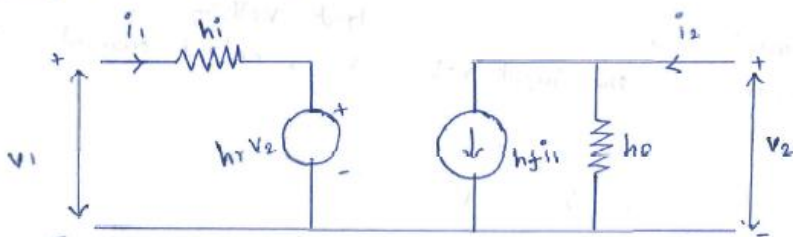\* For this equation we want to draw equivalent circuit & it verify using KVL to input, KCL to output node.



H-parameter for all the 3 configurations


Parameters	CE	CB	CC
Input resistance ( $h_{11}$ )	$h_{ie}$	$h_{ib}$	$h_{ic}$
Reverse Voltage gain	$h_{re}$	$h_{rb}$	$h_{rc}$
Forward Transfer current gain	$h_{fe}$	$h_{fb}$	$h_{fc}$
Output admittance	$h_{oe}$	$h_{ob}$	$h_{oc}$

W.K.T

$$V_1 = h_{11} i_1 + h_{12} V_2 \quad - (1)$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \quad - (2)$$

For CE Configuration :

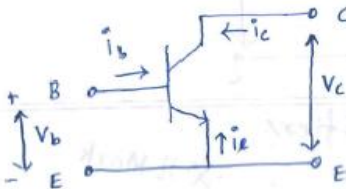


(1)  $\Rightarrow$  can be modified based on CE


$$V_b = h_{ie} i_b + h_{re} V_c \quad - (3)$$

$$i_c = h_{fe} i_b + h_{oe} V_c \quad - (4)$$

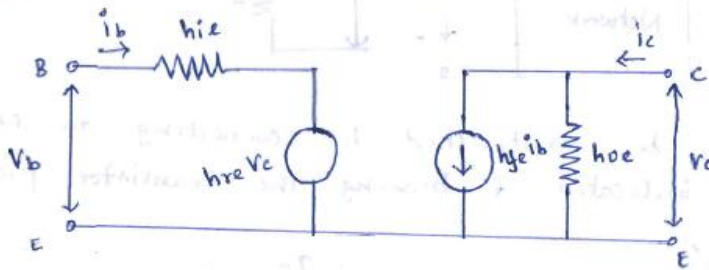For eqn (3) & (4) we have to draw the small signal equivalent circuit.




For CB configuration

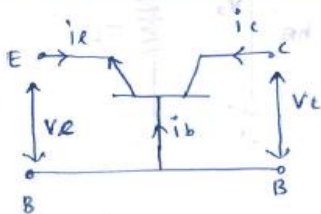


$$(1) \Rightarrow V_e = h_{ib} i_e + h_{rb} V_c \quad - (5)$$

$$(2) \Rightarrow i_c = h_{fb} i_e + h_{ob} V_c \quad - (6)$$

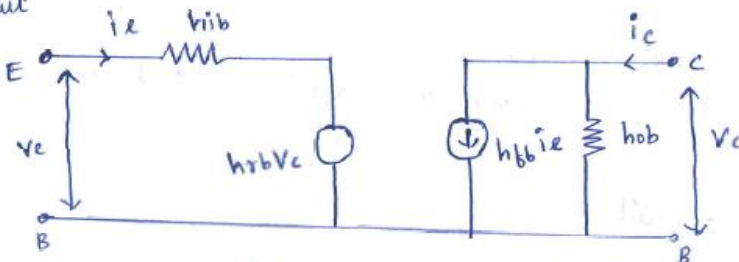For eqn (5) & (6) we have to draw the small signal equivalent circuit



For CC configuration

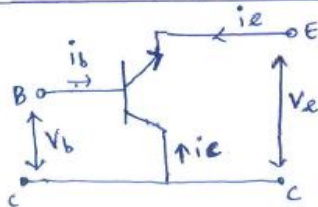


$$(1) \Rightarrow V_b = h_{ie} i_b + h_{re} V_e \quad - (7)$$

$$(2) \Rightarrow i_e = h_{fc} i_b + h_{oc} V_e \quad - (8)$$

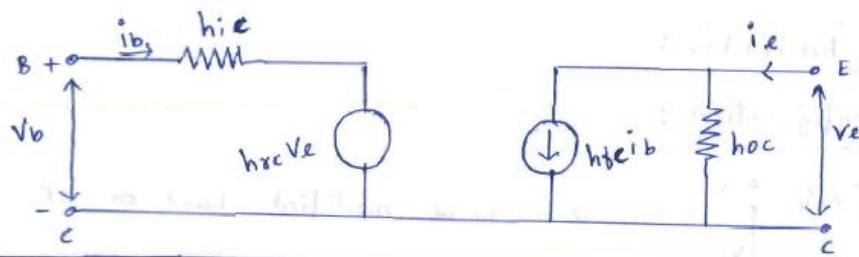
(3)

For eqn ⑦ & ⑧ We have to draw small signal equivalent circuit




### Midband Analysis of BJT single stage Amplifiers

• 16 Mark

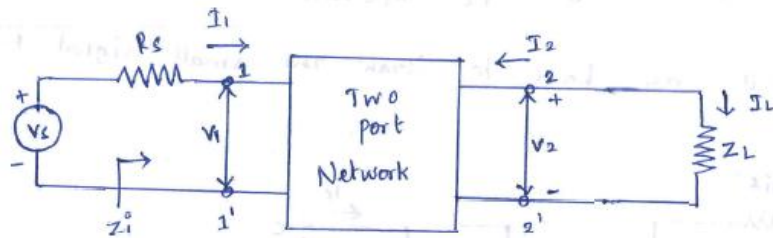

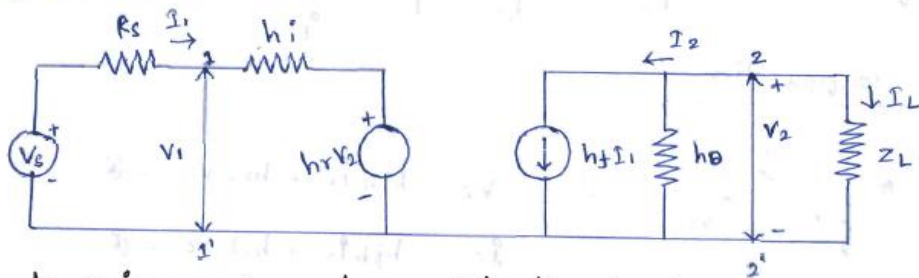A Transistor can be constructed by connecting an external load & signal source as indicated & biasing the transistor properly.



1. current gain (or) Current Amplification ( $A_I$ )

It's the ratio of output current to input current.

$$A_I = \frac{I_L}{I_1} = \frac{-I_2}{I_1}$$

Here  $I_L$  &  $I_2$  are equal in magnitude but opposite in sign  
ie  $I_L = -I_2$

From the circuit

$$I_2 = h_f I_1 + h_o V_2$$

Then

$$V_2 = I_L Z_L = -I_2 Z_L$$

Substitute  $V_2$  in  $I_2$

$$I_2 = h_f I_1 + h_o (-I_2 Z_L)$$

$$I_2 + h_o I_2 Z_L = h_f I_1$$

$$I_2 (1 + h_o Z_L) = h_f I_1$$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L}$$

$$\therefore A_I = \frac{-I_2}{I_1} = \frac{-h_f}{1 + h_o Z_L}$$

2. Input Impedance ( $Z_i$ )

$$Z_i = \frac{V_1}{I_1}$$

(20) From input circuit

$$V_1 = h_i I_1 + h_r V_2$$

Substitute  $V_2$  in  $Z_i$

$$Z_i = \frac{h_i I_1 + h_r V_2}{I_1} = h_i + h_r \frac{V_2}{I_1} \quad \text{--- (1)}$$

$$\therefore V_2 = -I_2 Z_L$$

$$= -(-A_I I_1) Z_L$$

$$V_2 = A_I I_1 Z_L \quad \text{--- (2)}$$

sub (2) in (1)

$$Z_i = h_i + h_r \frac{A_I I_1 Z_L}{I_1}$$

$$= h_i + h_r A_I Z_L$$

Sub  $A_I$  in  $Z_i$

$$Z_i = h_i + h_r \left( \frac{-h_f}{1 + h_o Z_L} \right) Z_L$$

$$= h_i - \frac{h_r h_f \cdot Z_L}{1 + h_o Z_L} = h_i - \frac{(h_r h_f) Z_L}{Z_L (\frac{1}{Z_L} + h_o)}$$

$$= h_i - \frac{h_r h_f}{\frac{1}{Z_L} + h_o}$$

$$\therefore Y_L = \frac{1}{Z_L}$$

$$\boxed{Z_i = h_i - \frac{h_r h_f}{Y_L + h_o}} \quad \text{--- (3)} \rightarrow \text{The input impedance is the function of Load impedance.}$$

### 3. Voltage gain (or) Voltage Amplification factor ( $A_v$ )

It's the ratio of output voltage to input voltage

$$A_v = \frac{V_2}{V_1}$$

$$V_2 = -I_2 Z_L = A_I I_1 Z_L$$

$$\therefore A_I = \frac{-I_2}{I_1}$$

Sub  $V_2$  in  $A_v$

$$A_v = \frac{A_I I_1 Z_L}{V_1}$$

$$\frac{I_1}{V_1} = \frac{1}{Z_i}$$

$$A_v = \frac{A_I Z_L}{Z_i}$$

### 4. Output Admittance ( $Y_o$ )

It's the ratio of output current ( $I_2$ ) to the output voltage ( $V_2$ ).

$$Y_o = \frac{I_2}{V_2} \text{ with } V_s = 0$$

$$I_2 = h_f I_1 + h_o V_2 \quad \text{--- (1)}$$

divide eqn (1) by  $V_2$

$$Y_o \leftarrow \frac{I_2}{V_2} = \frac{h_f I_1 + h_o V_2}{V_2} = \frac{h_f I_1}{V_2} + h_o \quad \text{--- (2)}$$

With  $V_s = 0$  by Apply KVL to the above circuit

$$R_s I_1 + h_i I_1 + h_r V_2 = 0$$

$$I_1 (R_s + h_i) + h_r V_2 = 0$$

$$I_1 (R_s + h_i) = -h_r V_2$$


$$\frac{I_1}{V_2} = \frac{-h_r}{(R_s + h_i)}$$

$$Y_o = h_f \left( \frac{-h_r}{(R_s + h_i)} \right) + h_o$$

$$Y_o = h_o - \frac{h_f h_r}{(R_s + h_i)}$$

Output impedance is a function of source resistance. If the source impedance is resistive then  $Y_o$  is real.

### 5. Voltage gain ( $A_{Vs}$ )

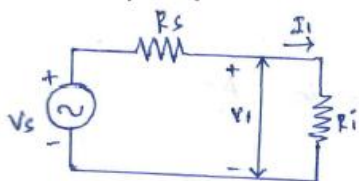

$$A_{Vs} = \frac{V_2}{V_s}$$

Multiply & divide by  $V_1$

$$A_{Vs} = \frac{V_2}{V_1} \cdot \frac{V_1}{V_s}$$

$$= A_V \cdot \frac{V_1}{V_s}$$

From the equivalent input circuit using thevenin's equivalence for the source

$$V_1 = \frac{Z_i}{Z_i + R_s} V_s$$

$$\therefore \frac{V_1}{V_s} = \frac{Z_i}{Z_i + R_s}$$

substitute this in  $A_{Vs}$

$$A_{Vs} = A_V \cdot \frac{Z_i}{Z_i + R_s}$$

$$= \frac{A_I Z_L}{Z_i} \cdot \frac{Z_i}{Z_i + R_s}$$

$$\therefore A_V = \frac{A_I Z_L}{Z_i}$$

$$A_{Vs} = \frac{A_I Z_L}{Z_i + R_s}$$


Note:

substitute  $R_s = 0$ : then  $\Rightarrow$

$$A_{Vs} = \frac{A_I Z_L}{Z_i} = A_V$$
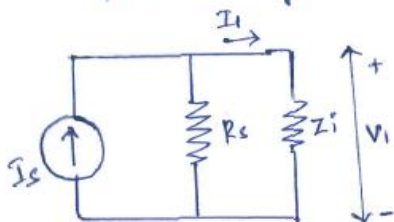
### b. Current Gain ( $A_{Is}$ )

The voltage source is replaced by current source



$$A_{Is} = \frac{-I_2}{I_s} \Rightarrow \text{Multiply & divide by } I_1$$

$$= \frac{-I_2}{I_1} \cdot \frac{I_1}{I_s}$$

$$= A_I \cdot \frac{I_1}{I_s}$$

(7)

From the above figure

$$I_1 = I_s \cdot \frac{R_s}{R_s + Z_i}$$

$$\frac{I_1}{I_s} = \frac{R_s}{R_s + Z_i} \quad \text{substitute this in } A_{I_s}$$

$$A_{I_s} = A_I \cdot \frac{R_s}{R_s + Z_i}$$

Note:

Suppose  $R_s = \infty$  Then  $\Rightarrow$   $A_{I_s} = A_I$

### 7. power gain ( $A_p$ )

It's the ratio of average power delivered to the load  $R_L$  to the input power.

$$A_p = \frac{P_2}{P_1}$$

$$P_2 = |V_2| |I_L| \cos \theta$$

$\theta$  is the phase angle between  $V_2$  &  $I_L$

Assume  $Z_L = R_L$  then the power delivered to the load is

$$P_2 = V_2 I_L = -V_2 I_2$$

The input power  $P_1$  is

$$P_1 = V_1 I_1$$

$$A_p = \frac{P_2}{P_1} = \frac{-V_2 I_2}{V_1 I_1}$$

$$\therefore A_I = \frac{-I_2}{I_1}$$

$$\therefore A_V = \frac{V_2}{V_1}$$

$$A_p = A_V A_I \quad \text{--- (1)}$$

W.K.T

$$A_V = \frac{A_I Z_L}{Z_i} \quad \text{sub in } A_p$$

$$A_p = \frac{A_I Z_L}{Z_i} A_I$$

Here  $Z_L = R_L$ ;  $Z_i = R_i$  so  $A_p = A_I \cdot \frac{R_L}{R_i} \cdot A_I$

$$A_p = A_I^2 \left( \frac{R_L}{R_i} \right)$$



## Relation between $A_{vs}$ and $A_{is}$

$$A_{vs} = \frac{A_i Z_L}{z_i + R_s} \quad A_{is} = \frac{A_i R_s}{z_i + R_s}$$

Taking the ratio of these 2 equations

$$\frac{A_{vs}}{A_{is}} = \frac{\frac{A_i Z_L}{z_i + R_s}}{\frac{A_i R_s}{z_i + R_s}} = \frac{Z_L}{R_s}$$


$$Z_L \approx R_L$$

So

$$\frac{A_{vs}}{A_{is}} = \frac{R_L}{R_s}$$

$$A_{vs} = A_{is} \left( \frac{R_L}{R_s} \right)$$

## Common Emitter Amplifier

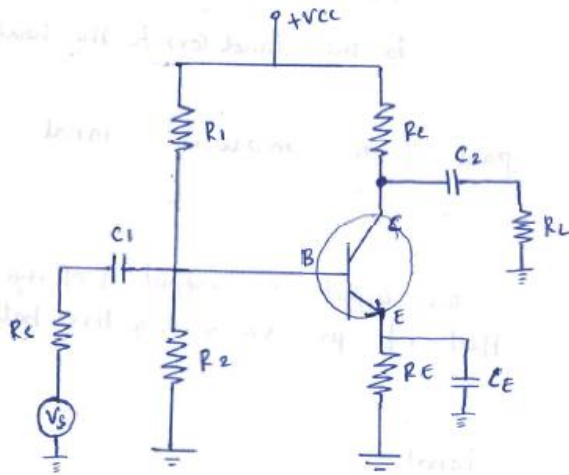

\* Amplifier is used to increase the signal level i.e. the amplifier is used to get a large signal output from a small signal input.

\* For Ex: We give sin wave as input. We get the same sin wave output. The frequency is not change but Amplitude increased.



\* To make the transistor as an amplifier, it's to be biased to operate in active region i.e. the Base-Emitter junction is forward bias and Base-collector junction is Reverse biased.

### 1. Biasing circuit

\* Resistance  $R_1$ ,  $R_2$  &  $R_E$  forms the voltage divider bias circuit for the CE amplifier.

\* It sets the proper operating point for the CE amplifier.

## 2. Input Capacitor $C_1$

- \* This capacitor couples the signal to the base of the transistor.
- \* It blocks any dc component present in the signal & passes only ac signals for amplification.
- \* Because of this biasing conditions are maintained constant.

## 3. Emitter Bypass Capacitor $C_E$

- \*  $C_E$  is connected in parallel with the  $R_E$  to provide a low resistance path to the amplified ac signal.
- \* If it's not inserted, the amplified ac signal passing through  $R_E$  will cause a voltage drop across it.
- \* This will reduce the output voltage, reducing the gain of the amplifier.

## 4. Output Coupling Capacitor $C_2$

- \*  $C_2$  couples the output of the amplifier to the load (or) to the next stage of the amplifier.
- \* It blocks dc & passes only ac part of the amplifier signal.


## 5. Phase Reversal

- \* The phase relationship between the input & output voltages can be determined by considering the effect of positive & negative half cycle separately.

Consider positive half cycle of input signal:


- \* In which terminal 'A' is positive w.r. to 'B'.
- \* Due to this 2 voltages, ac & dc will be adding each other, increased forward bias on the Base-Emitter junction.  
$$\begin{array}{ccc} \downarrow & & \downarrow \\ V_c & & V_{cc} \end{array}$$
- \* This will increase the base current  $I_B$ .
- \* The  $I_c$  is  $\beta$  times the  $I_B$  i.e.  $I_c = \beta I_B$  hence the  $I_c$  will also increase.
- \* This will increase the voltage drop across  $R_c$ .
- \* Since  $V_c = V_{cc} - I_c R_c$ , the increase in  $I_c$  results in a drop in  $V_c$ , as  $V_{cc}$  is constant.

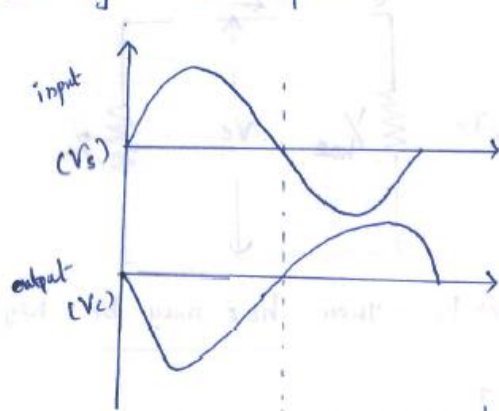\* Thus, as  $V_i$  increases in a positive direction,  $V_o$  goes in a negative direction & we get negative half cycle of output voltage for positive half cycle of the input.




Consider negative half cycle of input signal:

- \* In which terminal 'A' is negative w.r. to 'B'
- \* Due to this 2 voltages  $V_{be}$  &  $V_{dc}$  will be opposing to each other, decreased forward bias on the Base-Emitter junction.
- \* This will decrease the base current  $I_B$ .
- \* The  $I_C$  decreases & the voltage drop across  $R_C$  decreases, increase the output voltage.
- \* Thus as we get positive half cycle at the output for the negative half cycle of the input.
- \*∴ We can say that there is a phase shift of  $180^\circ$  between input & output voltages for a CE amplifier.

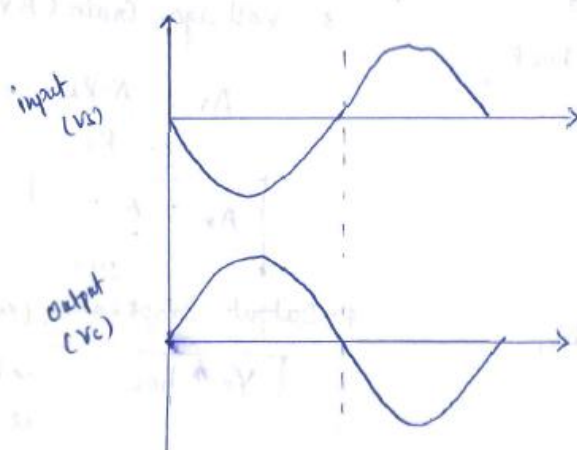

# Small signal Analysis of common Emitter / Analysis of CE circuit using Simplified Hybrid Model (single stage BJT Amplifiers)

\* 16 Mark

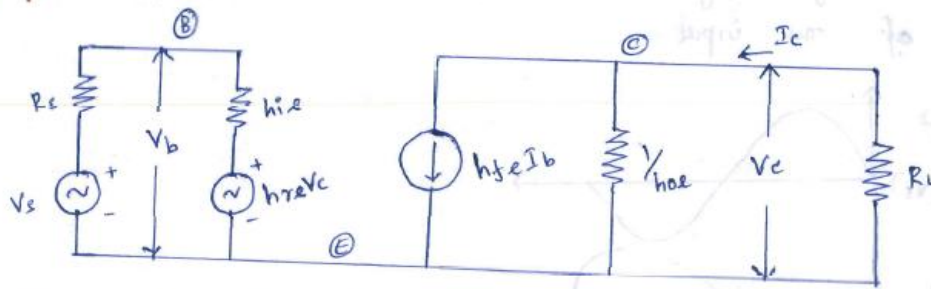

Here,  $\frac{1}{hoe} \parallel R_L$  & if  $\frac{1}{hoe} \gg R_L$ , then  $hoe$  may be neglected.


If  $hoe$  neglected  $I_c = hfe I_b$

Magnitude of voltage generator in the emitter  $hre |V_c| = hre I_c R_L$

$$= hfe I_b hre R_L$$

Since  $hre hfe \approx 0.01$  this voltage neglected in comparison with  $hie I_b$  drop across  $hie$  provided that  $R_L$  is too large.

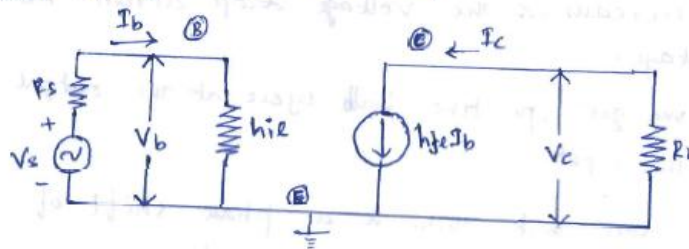$R_L$  small means  $hre, hoe$  neglected so,



1. Current Gain ( $A_I$ )

$$A_I = \frac{-I_c}{I_b} = \frac{-hfe}{1 + hoe R_L}$$

neglecting  $hoe$

$$A_I = -hfe$$

2. Input Impedance ( $R_i$ )

$$R_i = hie + hre A_I R_L$$

neglecting  $hre$

$$R_i = hie$$

3. Voltage Gain ( $A_V$ )

\* 2 Mark

$$A_V = \frac{A_I R_L}{R_i}$$

$$A_V = \frac{A_I R_L}{hie}$$

4. Output Impedance ( $Y_o$ )

$$Y_o = hoe - \frac{hfe hre}{hie + R_s}$$


by neglecting  $hoe$  &  $hre$

$$Y_o = 0$$

$$R_o = \frac{1}{Y_o} = \frac{1}{0} = \infty$$

$$R_o = \infty$$


# 1. CE Amplifier with Fixed Bias

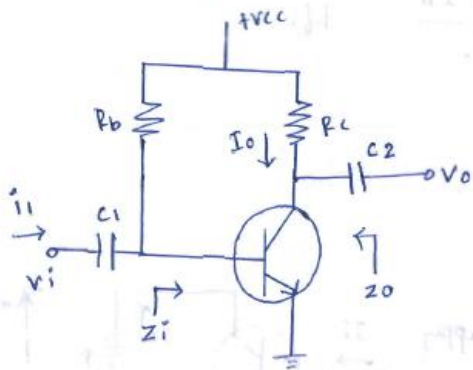

\* Remove the dc effect of power supply by grounding them.

\* Replace the capacitors ( $C_1$  &  $C_2$ ) by short circuits.

Small signal Model:

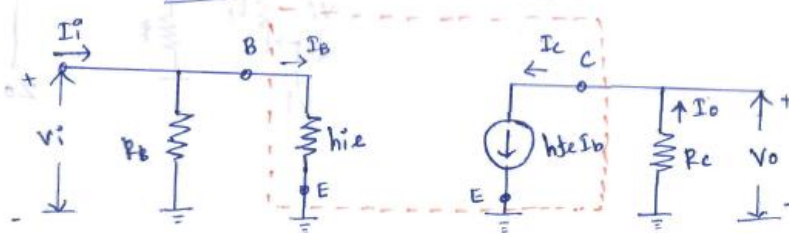

1. Input Impedance ( $Z_i$ )

$$Z_i = R_B \parallel h_{ie} \quad ; \quad R_B \gg h_{ie}$$

$$Z_i \approx h_{ie}$$

2. Output Impedance ( $Z_o$ )

It's the impedance determined with  $V_i = 0$  with  $V_i = 0, I_b = 0$ .  $h_{fe} I_b = 0$  indicating an open circuit equivalent for the current source.

$$Z_o = R_C \approx R_C$$

3. Voltage gain ( $A_v$ )

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -I_o R_C \quad \& \quad I_o = h_{fe} I_b \quad \text{substitute this in } V_o \text{ we get}$$

$$V_o = -h_{fe} I_b R_C$$

Assume that  $R_B \gg h_{ie}$

$$I_i \approx I_b \quad \& \quad V_i = I_b h_{ie}$$

$$\therefore A_v = \frac{-h_{fe} I_b R_C}{I_b h_{ie}} \Rightarrow A_v = \frac{-h_{fe} R_C}{h_{ie}}$$


\* As  $h_{fe}$  &  $h_{ie}$  are positive,  $A_v$  is negative. The negative sign indicates a 180° phase shift between input & output signals.

#### 4. Current gain ( $A_I$ )


$$A_I = \frac{I_L}{I_i} = \frac{-I_o}{I_i} = \frac{-h_{fe} I_b}{I_b} = -h_{fe}$$

$$A_I = -h_{fe}$$
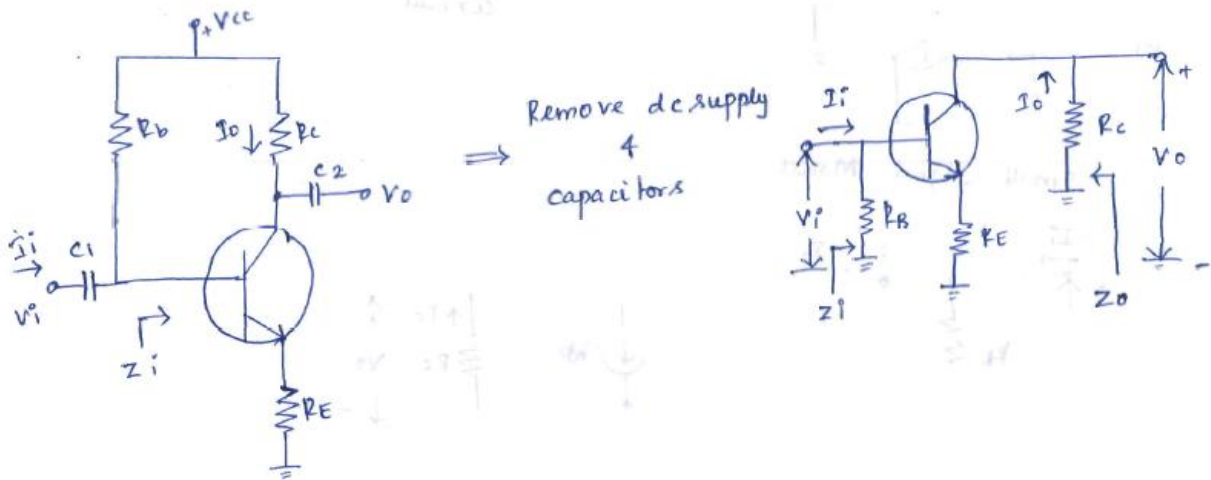
#### CE Amplifier with Unbypassed Emitter Resistor



#### Small signal Model

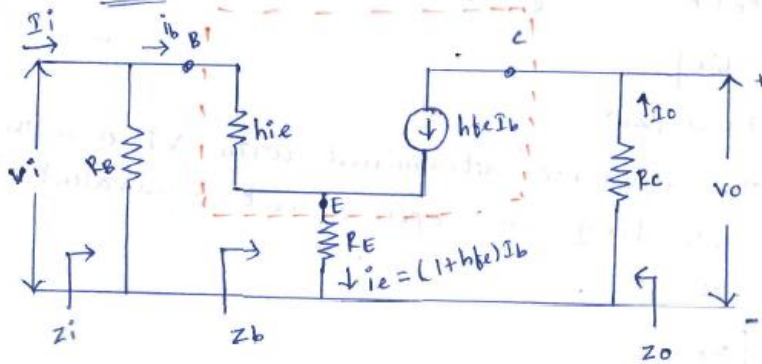

#### 1. Input Impedance ( $Z_i$ )

$$I_e = I_b + h_{fe} I_b = I_b (1 + h_{fe})$$

$$V_i = I_b * h_{ie} + (1 + h_{fe}) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \frac{I_b * h_{ie} + (1 + h_{fe}) I_b R_E}{I_b} = h_{ie} + (1 + h_{fe}) R_E$$

$$\because h_{fe} \gg 1$$

$$Z_b = h_{ie} + h_{fe} R_E$$

$$\because h_{fe} R_E \gg h_{ie}$$

$$Z_i = R_B \parallel Z_b$$

## 2. Output Impedance ( $Z_o$ )

$V_i = 0$ ,  $I_b = 0$ ,  $h_{fe} I_b = 0$  indicating open circuit for current source.

$$Z_o = R_c$$

## 3. Voltage gain ( $A_v$ )

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -I_o R_c = (-h_{fe} I_b) R_c$$

$$= -h_{fe} \left( \frac{V_i}{Z_b} \right) R_c$$

$$A_v = -h_{fe} \left( \frac{V_i}{Z_b} \right) R_c \times \frac{1}{V_i}$$

$$A_v = \frac{-h_{fe} R_c}{Z_b}$$

$$\therefore I_b = \frac{V_i}{Z_b}$$

$$\therefore Z_b \approx h_{fe} R_E$$

$$A_v = \frac{-h_{fe} R_c}{h_{fe} R_E}$$

$$A_v = \frac{-R_c}{R_E}$$

## 4. Current Gain ( $A_I$ )

$$A_I = -I_o / I_i$$

$$I_o = h_{fe} I_b$$


$$I_b = I_i \times \frac{R_B}{R_B + Z_b}$$

$$I_o = h_{fe} I_i \times \frac{R_B}{R_B + Z_b}$$

$$A_I = \frac{-I_o}{I_i} = \frac{-h_{fe} I_i \times \frac{R_B}{R_B + Z_b}}{(R_B + Z_b) I_i}$$

$$A_I = \frac{-h_{fe} R_B}{R_B + Z_b}$$

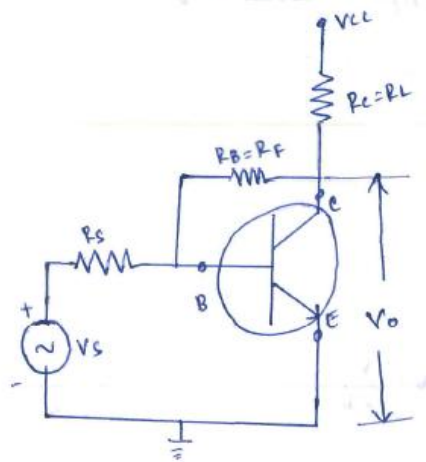
## 2. CE Amplifier with Collector to Base Bias



- \* The resistance  $R_F$  in this configuration is connected between input & output.
- \* For analysis of this circuit it's necessary to split this resistance for input & output.
- \* This can be achieved by Millers Theorem.
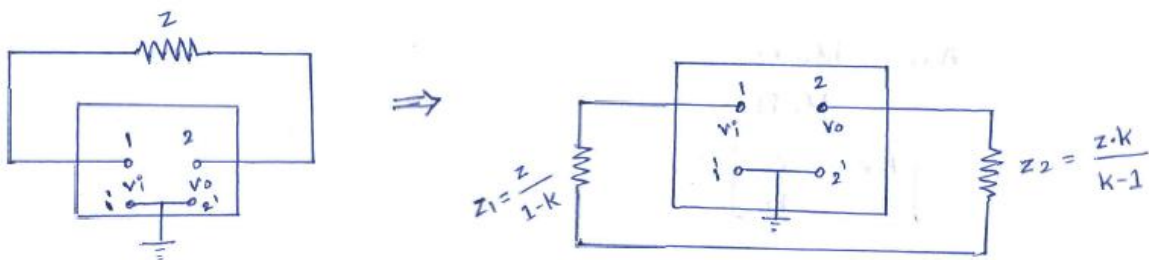
### Millers Theorem \* 2 Marks

- \* It's used for converting one circuit configuration to another circuit configuration.



- \* If  $Z$  is the impedance connected between 2 nodes, node 1 & node 2 it can be replaced by 2 separate impedances  $Z_1$  &  $Z_2$ ; where  $Z_1$  is connected b/w node 2 & ground.

- \* The  $v_i$  &  $v_o$  are the voltages at the nodes 1 & 2.

- \* The value of  $Z_1$  &  $Z_2$  can be derived from the ratio of  $v_o$  &  $v_i$ .

- \* The  $v_o/v_i$  is denoted as  $k$ .

- \* It's not necessary to know the values of  $v_i$  &  $v_o$  to calculate the value of  $Z_1$  &  $Z_2$ .


- \* The values of impedance  $Z_1$  &  $Z_2$  are given as

$$Z_1 = \frac{Z}{1-k} \quad \& \quad Z_2 = \frac{Z \cdot k}{k-1}$$



# Proof of Millers Theorem

\* A (or) 6 Mark

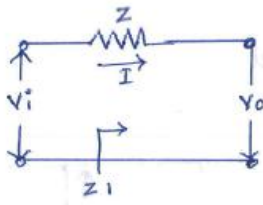

\* Millers Theorem states that, the effect of resistance  $Z$  on the input circuit is a ratio of input voltage  $V_i$  to the current  $I$  which flows from input to the output.


$$\therefore Z_1 = \frac{V_i}{I}$$

Where

$$I = \frac{V_i - V_o}{Z} = \frac{V_i \left[ 1 - \frac{V_o}{V_i} \right]}{Z} = \frac{V_i [1 - A_v]}{Z} \quad \because A_v = \frac{V_o}{V_i} = k$$

$$Z_1 = \frac{V_i}{\frac{V_i [1 - A_v]}{Z}} = \frac{Z}{1 - A_v}$$

$$\boxed{Z_1 = \frac{Z}{1 - k}}$$

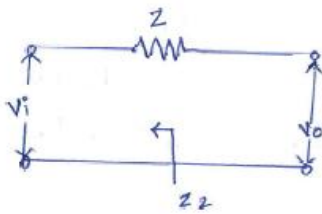

\* Millers Theorem states that, the effect of resistance  $Z$  on the output circuit is the ratio of output voltage  $V_o$  to the current  $I$  which flows from the output to the input.

$$\therefore Z_2 = \frac{V_o}{I}$$

$$\text{Where } I = \frac{V_o - V_i}{Z} = \frac{V_o \left[ 1 - \frac{V_i}{V_o} \right]}{Z} = \frac{V_o \left[ 1 - \frac{1}{A_v} \right]}{Z}$$

$$= \frac{V_o \left[ \frac{A_v - 1}{A_v} \right]}{Z}$$



$$\therefore Z_2 = \frac{V_o}{\frac{V_o \left[ \frac{A_v - 1}{A_v} \right]}{Z}} = \frac{Z}{\frac{A_v - 1}{A_v}}$$

$$\therefore Z_2 = \frac{Z \cdot A_v}{A_v - 1}$$

$$\because A_v = \frac{V_o}{V_i} = k$$

$$\therefore \boxed{Z_2 = \frac{Z \cdot k}{k - 1}}$$
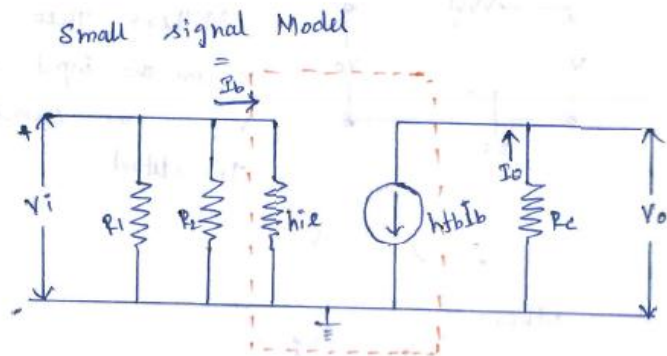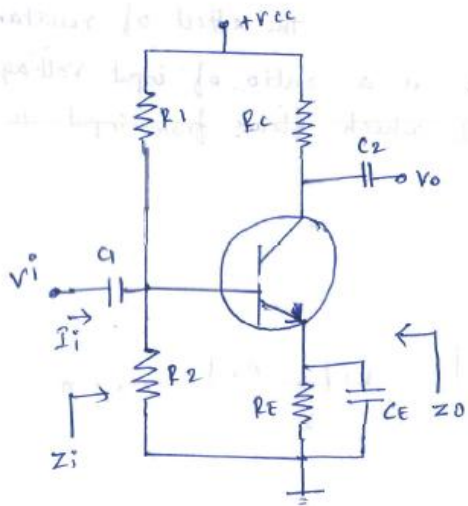
### 3. CE Amplifier with Voltage Divider Bias



#### 1. Input Impedance ( $Z_i$ )

$$Z_i = R_B \parallel h_{ie}$$

$$\because R_B \gg h_{ie}$$

$$\boxed{Z_i \approx h_{ie}}$$

#### 2. Output Impedance ( $Z_o$ )

$$V_i = 0; I_b = 0; h_{fe} I_b = 0$$

$$\boxed{Z_o = R_C}$$

#### 3. Voltage gain ( $A_v$ )

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -I_o R_C$$

$$I_o = h_{fe} I_b$$

$$V_o = -h_{fe} I_b R_C$$

$$R_B \gg h_{ie}$$

$$I_i \approx I_b$$

$$V_i = I_b h_{ie}$$

$$A_v = \frac{-h_{fe} I_b R_C}{I_b h_{ie}}$$

$$\boxed{A_v = -\frac{h_{fe} R_C}{h_{ie}}}$$

#### 4) Current gain ( $A_I$ )

$$A_I = -I_o / I_i$$

$$I_o = -h_{fe} I_b$$

$$I_b = I_i \times \frac{R_B}{R_B + h_{ie}}$$

$$I_o = -h_{fe} I_i \times \frac{R_B}{R_B + h_{ie}}$$

$$A_I = I_o / I_i$$

$$= \frac{h_{fe} I_i R_B}{(R_B + h_{ie}) * I_i}$$

$$\boxed{A_I = \frac{h_{fe} R_B}{(R_B + h_{ie})}}$$