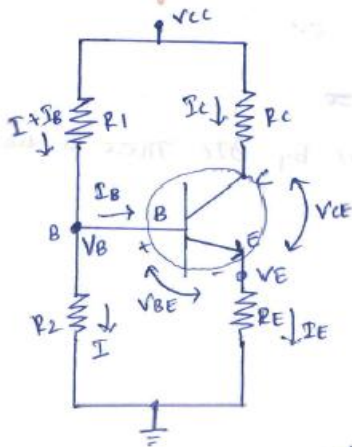


### 3. Voltage Divider Bias / Self Bias / potential divider Bias



- \* The biasing is provided by  $R_1, R_2$  &  $R_E$ .
- \* The resistors  $R_1$  &  $R_2$  act as a potential divider giving a fixed voltage to point B i.e. base.
- \* If  $I_C$  increases due to change in temperature or  $\beta$ , the  $I_E$  also increases & the voltage drop across  $R_E$  increases, decreasing the  $V_{BE}$ .
- \* Due to reduction in  $V_{BE}$ ,  $I_B$  &  $I_C$  also reduced.
- \*  $\therefore$  We can say that negative feedbacks exist in the emitter bias circuit.

- \* The voltage across  $R_2$  is the base voltage  $V_B$ .
- \* Apply voltage divider theorem to find  $V_B$  we get

$$V_B = \frac{R_2(I)}{R_1(I+I_B)+R_2(I)} \times V_{CC}$$

$\therefore I \gg I_B$  so we can omit  $I+I_B$

so

$$V_B = \frac{R_2}{R_1+R_2} V_{CC}$$

- \* The voltage across  $R_E$  is  $V_E$

$$V_E = I_E R_E = V_B - V_{BE}$$


$$\therefore I_E = \frac{V_B - V_{BE}}{R_E}$$

- \* Apply KVL to the collector-emitter circuit we get

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\therefore V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

#### Modified circuit

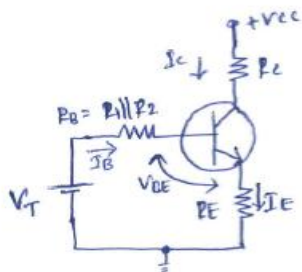

Thevenin's equivalent circuit

- \* Here,  $R_1$  &  $R_2$  are replaced by  $R_B$  &  $V_T$ , where  $R_B$  is the parallel combination of  $R_1$  &  $R_2$  &  $V_T$  is the Thevenin's voltage.

- \*  $R_B$  is calculated as  $R_B = \frac{R_1 R_2}{R_1 + R_2}$

\* Apply KVL to the Base-Emitter junction

$$\begin{aligned} V_T &= I_B R_B + V_{BE} + I_E R_E \\ &= I_B R_B + V_{BE} + (I_C + I_B) R_E \quad \because I_E = I_C + I_B \\ &= I_B R_B + V_{BE} + I_C R_E + I_B R_E \\ V_T &= I_B (R_B + R_E) + V_{BE} + I_C R_E \\ V_{BE} &= V_T - I_B (R_B + R_E) - I_C R_E \end{aligned}$$

Stability Factors

\* Here the Thevenin's voltage  $V_T$  is given by

$$V_T = \frac{R_2 V_{cc}}{R_1 + R_2} \quad \& \ R_1 \& \ R_2 \text{ replaced by } R_B$$

\* Apply KVL to the base-emitter junction

$$V_T = I_B R_B + V_{BE} + (I_B + I_C) R_E \quad \text{--- (1)}$$

\* differentiate eqn (1) w.r. to  $I_C$  &  $V_{BE}$  to be independent of  $I_C$   
we get-

$$0 = \frac{\partial I_B}{\partial I_C} R_B + 0 + \frac{\partial I_B}{\partial I_C} R_E + \frac{\partial I_C}{\partial I_C} R_E$$

$$0 = \frac{\partial I_B}{\partial I_C} (R_B + R_E) + R_E$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_B + R_E} \quad \text{--- (2)}$$

\* W.K.T

$$S = \frac{1 + \beta}{1 - \beta \left( \frac{\partial I_B}{\partial I_C} \right)} = \frac{1 + \beta}{1 - \beta \left( \frac{-R_E}{R_B + R_E} \right)} = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_B + R_E} \right)}$$

\* Take LCM

$$S = \frac{(1 + \beta)(R_B + R_E)}{R_B + R_E + \beta R_E} = \frac{(1 + \beta)(R_B + R_E)}{R_B + (1 + \beta)R_E}$$

\* Dividing each term by  $R_E$  we get-

$$S = \frac{(1 + \beta) \left( \frac{R_B}{R_E} + \frac{R_E}{R_E} \right)}{\frac{R_B}{R_E} + (1 + \beta) \frac{R_E}{R_E}} = \frac{(1 + \beta) \left( 1 + \frac{R_B}{R_E} \right)}{(1 + \beta) + \frac{R_B}{R_E}}$$

\* The ratio  $R_B/R_E$  controls value of stability factor  $S$ .

\* If  $R_B/R_E \ll 1$  then  $S = \frac{1+\beta}{1+\beta} = 1$

$S'$

$$S' = \frac{\partial I_C}{\partial V_{BE}} \mid I_{C0} + \beta \text{ constant}$$

\* W.K.T

$$I_C = (1+\beta)I_{C0} + \beta I_B \quad \text{--- (1)}$$

$$V_T = I_B R_B + V_{BE} + (I_B + I_C) R_E \quad \text{--- (2)}$$

$$V_{BE} = V_T - (R_E + R_B) I_B - R_E I_C \quad \text{--- (3)}$$

\* By rewriting the eqn (1) in terms of  $I_B$

$$I_B = \frac{I_C - (1+\beta)I_{C0}}{\beta} \quad \text{--- (4)}$$

\* substitute  $I_B$  in eqn (3) we get

$$\begin{aligned} \text{(3)} \quad V_{BE} &= V_T - (R_E + R_B) I_B - R_E I_C \\ &= V_T - (R_E + R_B) \left[ \frac{I_C - (1+\beta)I_{C0}}{\beta} \right] - R_E I_C \\ &= V_T - \frac{(R_E + R_B) I_C}{\beta} + \frac{(R_E + R_B)(1+\beta)I_{C0}}{\beta} - R_E I_C \end{aligned}$$

\* Take the common terms outside

$$V_{BE} = V_T - \left[ \frac{(1+\beta)R_E + R_B}{\beta} \right] I_C + \frac{(R_E + R_B)(1+\beta)I_{C0}}{\beta} \quad \text{--- (5)}$$

\* differentiate eqn (5) w.r.t.  $V_{BE}$

$$\frac{\partial V_{BE}}{\partial V_{BE}} = 0 - \left( \frac{(1+\beta)R_E + R_B}{\beta} \right) \frac{\partial I_C}{\partial V_{BE}} + 0$$

$$\downarrow 1$$

$$\frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B + (1+\beta)R_E}$$

$$S' = \frac{-\beta}{R_B + (1+\beta)R_E}$$

$S''$ :

$$S'' = \frac{\partial I_C}{\partial \beta} \mid I_{C0} + V_{BE} \text{ as constants}$$

