

Substitute the value of V_{GS} in eqn ①

$$\begin{aligned} \textcircled{1} \Rightarrow I_D &= I_{DSS} \left(1 - \frac{(-I_D R_S)}{V_P} \right)^2 \rightarrow \text{for n-channel} \\ &= I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2 \end{aligned}$$

Apply KVL to the Drain to source junction

$$V_S + V_{DS} + I_D R_D - V_{DD} = 0$$

$$\begin{aligned} \therefore V_{DS} &= V_{DD} - V_S - I_D R_D \\ &= V_{DD} - I_D R_S - I_D R_D \end{aligned}$$

$$\therefore V_{DS} = V_{DD} - I_D (R_S + R_D)$$



Design of Biasing for MOSFET

* MOSFET - Metal Oxide Semiconductor Field Effect Transistor

* It has a Gate, Source & Drain like the JFET.

* The Drain current (I_D) in the MOSFET is controlled by the Gate-Source Voltage V_{GS} .

* There are 2 types of MOSFETs

  

* MOSFET is also referred to as a I_{GATE} because the gate is isolated from the channel.

1. DMOSFET

* It is similar to the circuit used for JFET biasing

* The primary difference b/w the two is the fact that depletion type MOSFETs also permits operating points with positive value of V_{GS} for n-channel & negative values of V_{GS} for p-channel.


* To have positive values of V_{GS} for n-channel & negative value of V_{GS} for p-channel self bias circuit is unsuitable.

- [^{V_{GS} only}
1. Fixed bias
2. Voltage divider bias]

2. MOSFET


- * It's similar to the circuit used for JFET biasing.
- * The primary difference b/w the two is the fact that Enhancement type MOSFETS also permits operating points with positive value of V_{GS} for n-channel & negative values of V_{GS} for p-channel.
- * To have positive values of V_{GS} the n-channel & negative value of V_{GS} for p-channel self bias circuit is unsuitable.
- * Here, we will discuss only feedback bias & voltage divider bias circuit.

1. Feed Back Bias

 

Dc Analysis:

 - * For dc analysis we can replace coupling capacitors by open circuit & replace the R_G by a short circuit equivalent, since $I_G = 0$.
- * The Drain & Gate terminals are shorted.
 $V_D = V_G + V_{DS} = V_{GS} \quad \because V_S = 0$



- * Apply KVL to the Drain-source junction


$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$\therefore V_{DS} = V_{DD} - I_D R_D$$

(or)

$$V_{GS} = V_{DD} - I_D R_D$$

2. Voltage Divider Bias

 

- * The biasing resistors R_1 & R_2 are designed to provide positive gate to source voltage.

- * Apply KVL to the Gate-source junction

$$V_{G1} - V_{GS} - V_S = 0$$

$$\therefore V_{GS} = V_{G1} - V_S$$

ko