



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB302–VLSI DESIGN

III YEAR/ V SEMESTER

UNIT 3 –SEQUENTIAL LOGIC CIRCUITS

TOPIC 4 –PIPELINES



OUTLINE



- Introduction
- Architectural techniques : critical path
- Synchronous timing
- Self-timed pipelined data path
- Completion signal using current sensing
- Architectural techniques :pipelining
- Activity
- Architectural techniques : fine-grain pipelining
- Unrolling the loop using pipelining
- Architectural techniques : parallel processing
- Assessment
- Summary & thank you



INTRODUCTION



Combinational logic

output depends on current inputs


Sequential logic

output depends on current and previous inputs


Requires separating previous, current, future

Called state or tokens

Ex: FSM, pipeline

 

Finite State Machine

 

Pipeline




ARCHITECTURAL TECHNIQUES : CRITICAL PATH



Critical path in any design is the longest path between

 
1. Any two internal latches/flip-flops
2. An input pad and an internal latch
3. An internal latch and an output pad
4. An input pad and an output pad

- Use FFs right after/before input/out pads to avoid the last three cases (off-chip and packaging delay)





SYNCHRONOUS TIMING

 


Pipelining:

- Comes from the idea of a water pipe: continue sending water without waiting the water in the pipe to be out
- Used to reduce the critical path of the design





SELF-TIMED PIPELINED DATA PATH

 

11/2/2022



COMPLETION SIGNAL USING CURRENT SENSING

  




ARCHITECTURAL TECHNIQUES : PIPELINING



 
Original System: (Critical path = τ_1 Max operating freq: $f_1=1/\tau_1$)



2 cycles
later

Pipelined version: (Critical path = τ_2 Max operating freq: $f_2=1/\tau_2$)

 - Smaller Critical Path \longrightarrow higher throughput ($\tau_2 < \tau_1 \longrightarrow f_2 > f_1$)
- Longer latency



3 cycles
later




ARCHITECTURAL TECHNIQUES : PIPELINE DEPTH




Pipeline depth: 0 (No Pipeline)

Critical path: 3 Adders

 
 
```
wire w1, w2;  
assign w1 = X + a;  
assign w2 = w1 + b;  
assign Y = w2 + c;
```







ARCHITECTURAL TECHNIQUES : PIPELINE DEPTH



 - Pipeline depth: 1 (One Pipeline register Added)
 - Critical path: 2 Adders


 
```
wire w1;  
reg w2;  
assign w1 = X + a;  
  
always @(posedge Clk)  
w2 <= w1 + b;
```






ARCHITECTURAL TECHNIQUES : PIPELINE DEPTH



 - Pipeline depth: 2 (One Pipeline register Added)
 - Critical path: 1 Adder



```
reg w1, w2;  
assign Y = w2 + c;  
always @(posedge Clk)  
begin  
    w1 <= X + a;  
    w2 <= w1 + b;  
end
```






ARCHITECTURAL TECHNIQUES : PIPELINING



- Clock period and throughput as a function of pipeline depth:

- Clock period : $\tau_{\text{CLK}} \propto \frac{1}{n}$
- Throughput: $T \propto n$

 Adding register layers improves timing by dividing the critical path into two paths of smaller delay





Architectural Techniques : Pipelining



General Rule:

- Pipelining latches can only be placed across **feed-forward cutsets** of the circuit.

Cut set:

- A set of paths of a circuit such that if these paths are removed, the circuit becomes disjoint (i.e., two separate pieces)

Feed-Forward Cutset:

- A cutset is called feed-forward cutset if the data move in the forward direction on all the paths of the cutset





ARCHITECTURAL TECHNIQUES : PIPELINING



  - **Example:**

- FIR Filter
- Three feed-forward cutsets are





CLASS ROOM ACTIVITY



Group Discussion & Debate


15



ARCHITECTURAL TECHNIQUES : PIPELINING




Critical Path: 1M+2A

 

```
assign w1 = a*Xn; assign  
w2 = b*Xn_1; assign w3  
= w1 + w2; assign w4 =  
c*Xn_2; assign Y = w3 +  
w4; always @(posedge  
Clk) begin  
    Xn_1 <= Xn;  
    Xn_2 <= Xn_1;  
end
```


Critical Path: 2A

 

```
assign Y = r3 + w1; assign  
w1 = r1 + r2; always  
@(posedge Clk) begin  
    Xn_1 <= Xn;  
    Xn_2 <= Xn_1; r1  
    <= a*Xn;  
    r2 <= b*Xn_1; r3  
    <= c*Xn_2;  
end
```



ARCHITECTURAL TECHNIQUES : PIPELINING

 


Cloc k	Input	1	2	3	4	5	Output
0	X(0)	aX(0)	-	aX(0)	-	aX(0)	Y(0)
1	X(1)	aX(1)	bX(0)	aX(1)+bX(0)	-	aX(1)+bX(0)	Y(1)
2	X(2)	aX(2)	bX(1)	aX(2)+bX(1)	cX(0)	aX(2)+bX(1)+cX(0)	Y(2)
3	X(3)	aX(3)	bX(2)	aX(3)+bX(2)	cX(1)	aX(3)+bX(2)+cX(1)	Y(3)



ARCHITECTURAL TECHNIQUES : PIPELINING



Even more pipelining

 



Clock	Input	1	2	3	4	5	Output
0	X(0)	-	-	-	-	-	-
1	X(1)	aX(0)	-	-	-	-	-
2	X(2)	aX(1)	bX(0)	aX(0)	-	aX(0)	Y(0)
3	X(3)	aX(2)	bX(1)	aX(1)+bX(0)	-	aX(1)+bX(0)	Y(1)
4	X(3)	aX(2)	bX(1)	aX(2)+bX(1)	cX(0)	aX(2)+bX(1)+cX(0)	Y(2)



ARCHITECTURAL TECHNIQUES : FINE-GRAIN PIPELINING



  - Pipelining at the operation level
 - Break the multiplier into two parts






UNROLLING THE LOOP USING PIPELINING



 - Calculation of X^3
 - Throughput = $8/3$, or 2.7
- Timing = One multiplier in the critical path
- Iterative implementation:
- No new computations can begin until the previous computation has completed



```
module power3( output reg
[7:0] X3, output finished,
input [7:0] X, input clk,
start); reg [7:0] ncount;
reg [7:0] Xpower, Xin;
assign finished = (ncount == 0);
always@(posedge clk)
if (start) begin XPower <= X;
Xin<=X; ncount <= 2;
X3 <= XPower; end
else if(!finished) begin ncount
<= ncount - 1; XPower <=
XPower * Xin;
End
endmodule
```





ARCHITECTURAL TECHNIQUES : PARALLEL PROCESSING




In parallel processing the same hardware is duplicated to

 - Increases the throughput without changing the critical path
- Increases the silicon area




Pipelining

 

Clock Freq: $2f$

Throughput: $2M$ samples

Parallel Processing

 

Clock Freq: f

Throughput: $2M$ samples



ADVANTAGEOUS



- Reduction in the critical path
- Higher throughput (number of computed results in a give time)
- Increases the clock speed (or sampling speed)
- Reduces the power consumption at same speed

11/2/2022

PIPELINES /19ECB302-VLSI
DESIGN/SWAMYNATHAN.S.M/ECE/SNSCT



ASSESSMENT



- Define critical path
- List out the needs of Pipeline
- Draw the FIR filter using pipeline processing
- Compare pipeline and parallel processing



SUMMARY & THANK YOU