



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

19EET301 / POWER ELECTRONICS AND DRIVES

V SEM EEE

UNIT 2 –DC CONVERTERS

2 . STEP UP – DC DC CONVERTER

Dr. R SENTHIL KUMAR

ASP/EEE, SNSCT



2. Step-Up DC Converter




DC Fixed Voltage



**DC Output Voltage
(Step up)**




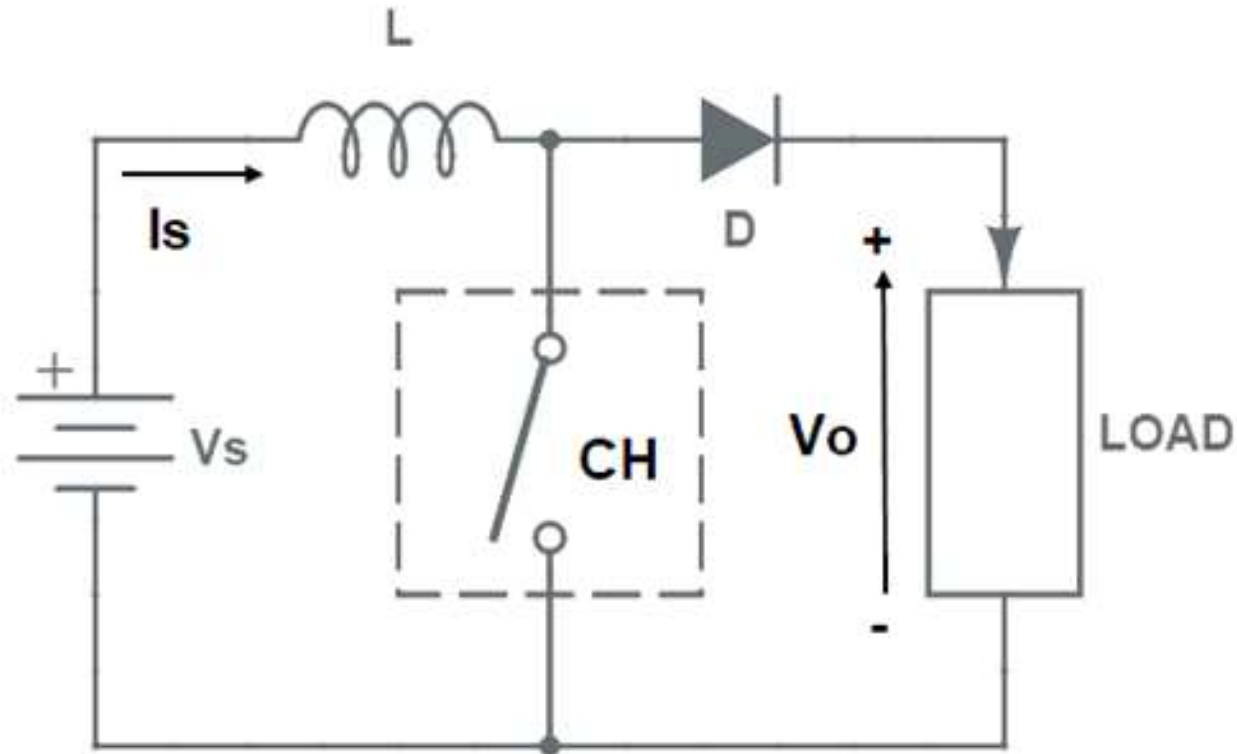Step Up Chopper or Boost converter which increases the input DC voltage to a specified DC output voltage. A typical Boost converter is shown below.





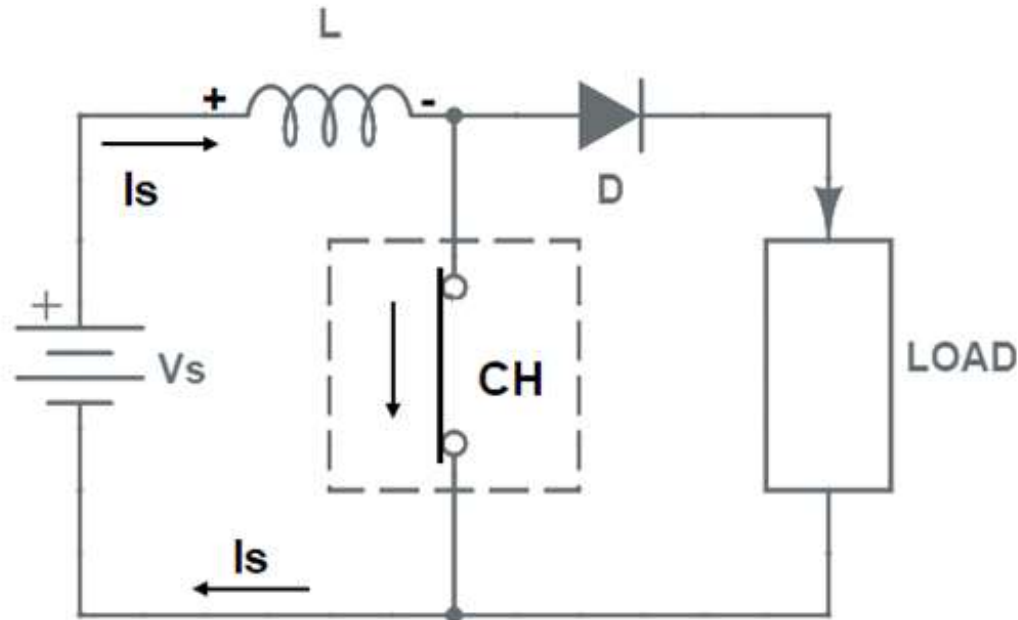Switch ON Period (mode I): When chopper (CH) is switched ON, the current will flow through the closed path formed by supply source V_s , inductor L and chopper CH.




Also, during the TON period, energy is stored in the inductor L . This energy storage in L is essential to boost the load output voltage above the source voltage. Therefore, a large value of L is essential in a step-up chopper.

During this period, no current will flow through the load. Only source current ' i_s ' will flow and the value of load current ' i_o ' will be ZERO during the ON period.



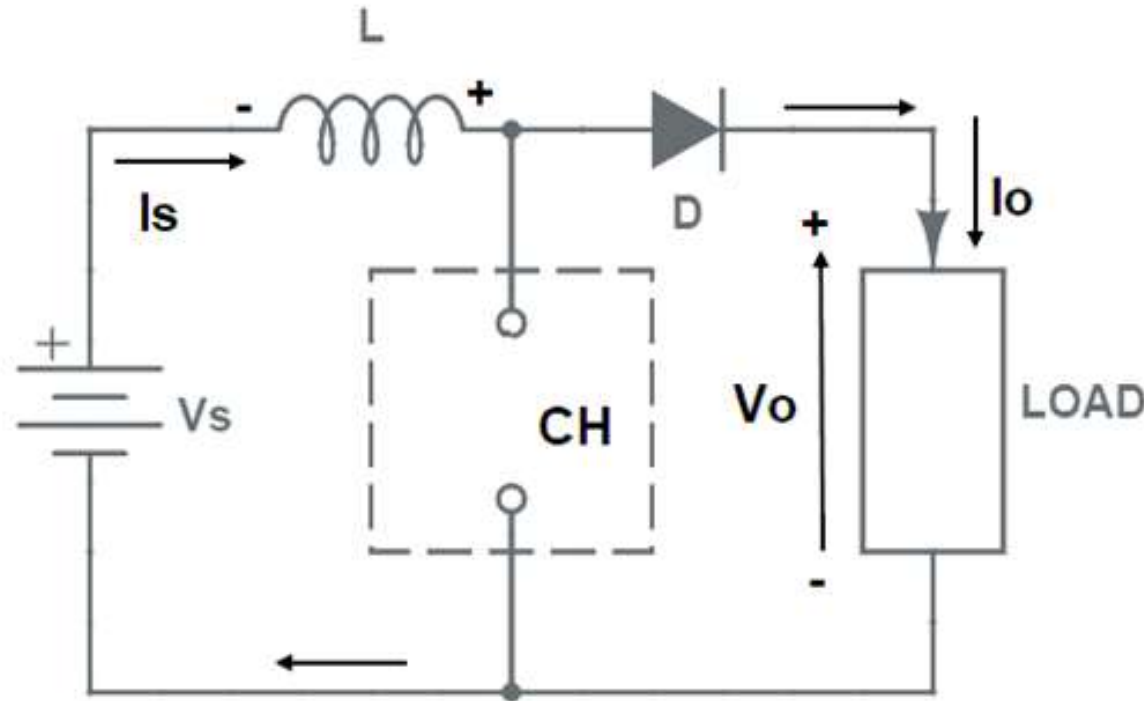
Switch OFF period (mode II): When the chopper CH is switched OFF, the current through the L can not die instantaneously rather it decays exponentially. Due to this behavior of L, it will force the current through the diode D and load for the entire time period TOFF. This is shown in figure below.



$$V_o = V_s + L(di/dt)$$



Output Waveform

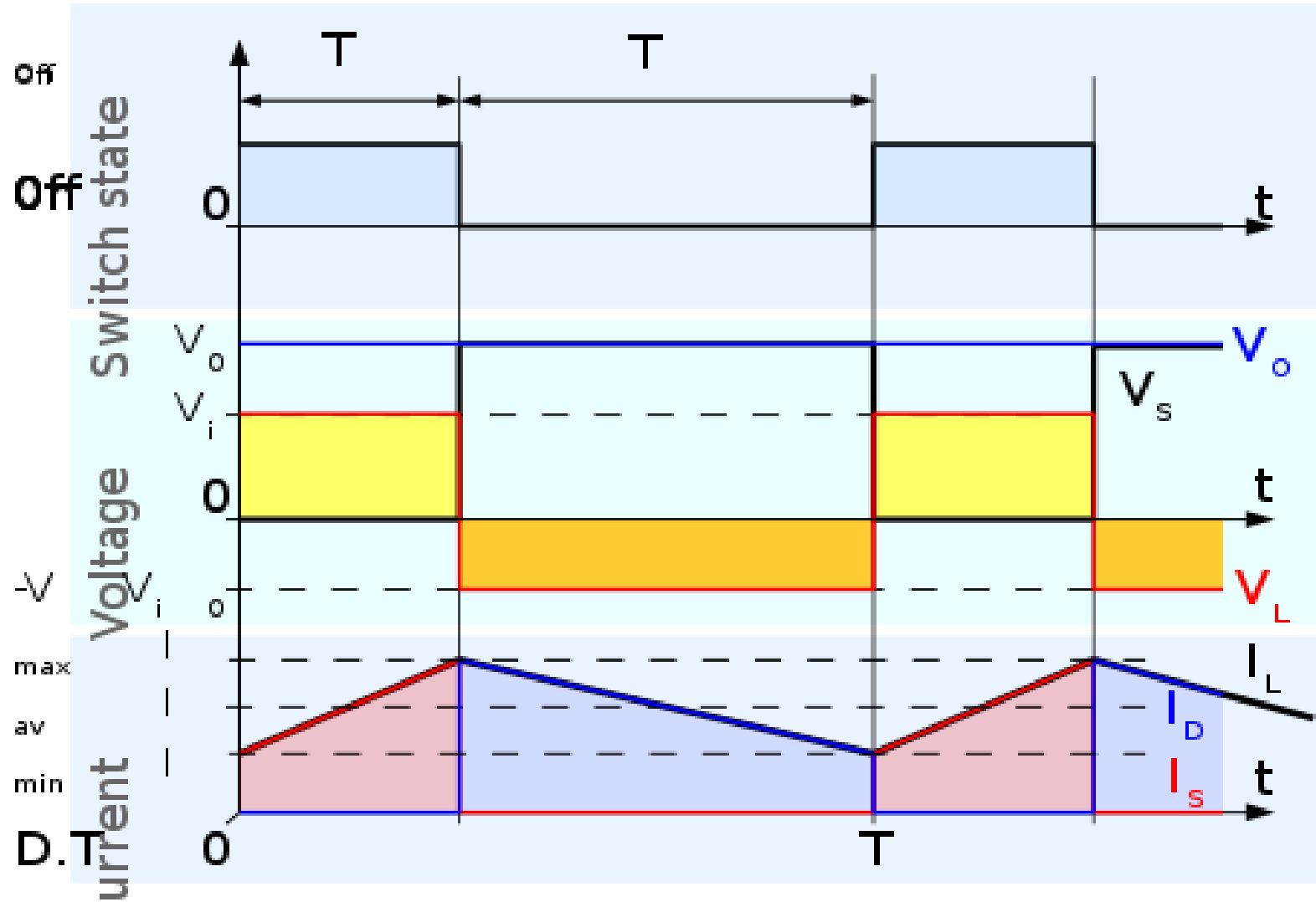



Analysis of Step Up Converter

Let us now analyse the **Boost converter** in steady state operation for Mode II using KVL.

$$\therefore V_{in} = V_L + V_o$$

$$\therefore V_L = L \frac{di_L}{dt} = V_{in} - V_o$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_{in} - V_o}{L}$$

Since the switch is open for a time

$$T_{OFF} = T - T_{ON} = T - DT = (1-D)T$$

we can say that

$$\Delta t = (1-D)T$$

$$(\Delta i_L)_{open} = \left(\frac{V_{in} - V_o}{L} \right) (1-D)T$$

It is already established that the net change of the inductor current over any one complete cycle is zero.


$$\therefore (\Delta i_L)_{closed} + (\Delta i_L)_{open} = 0$$

$$\left(\frac{V_{in} - V_o}{L} \right) (1-D)T + \left(\frac{-V_o}{L} \right) DT = 0$$

$$\frac{V_o}{V_{in}} = \frac{1}{1-D}$$




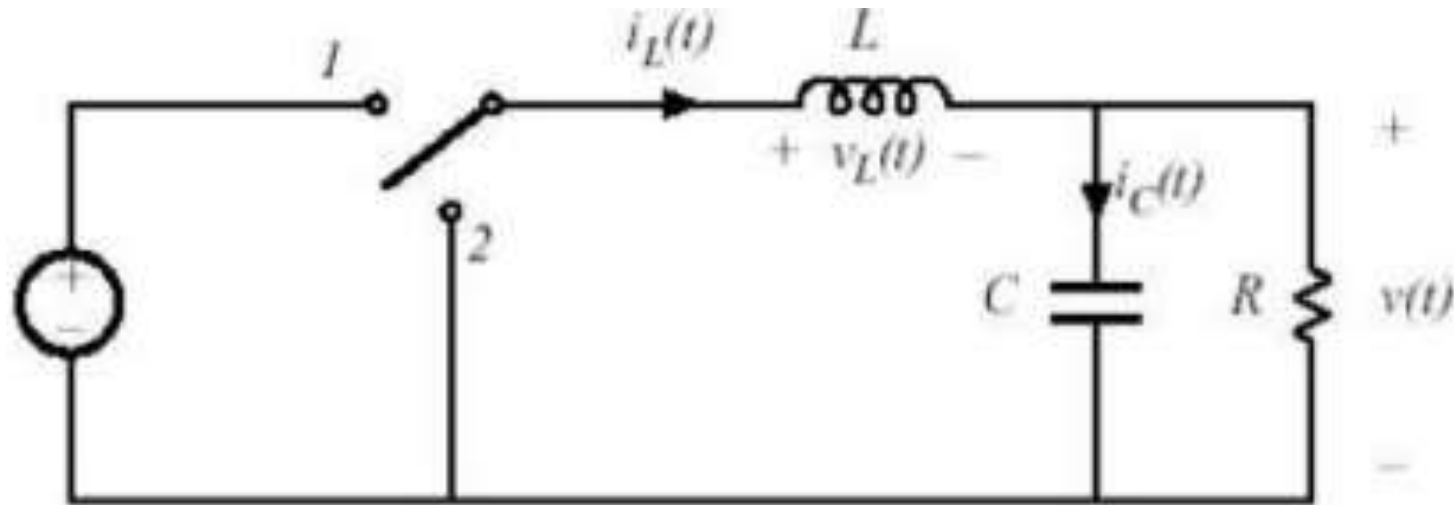Assessment - Draw the equivalent circuit for the Following.





Buck converter (Step-down converter)

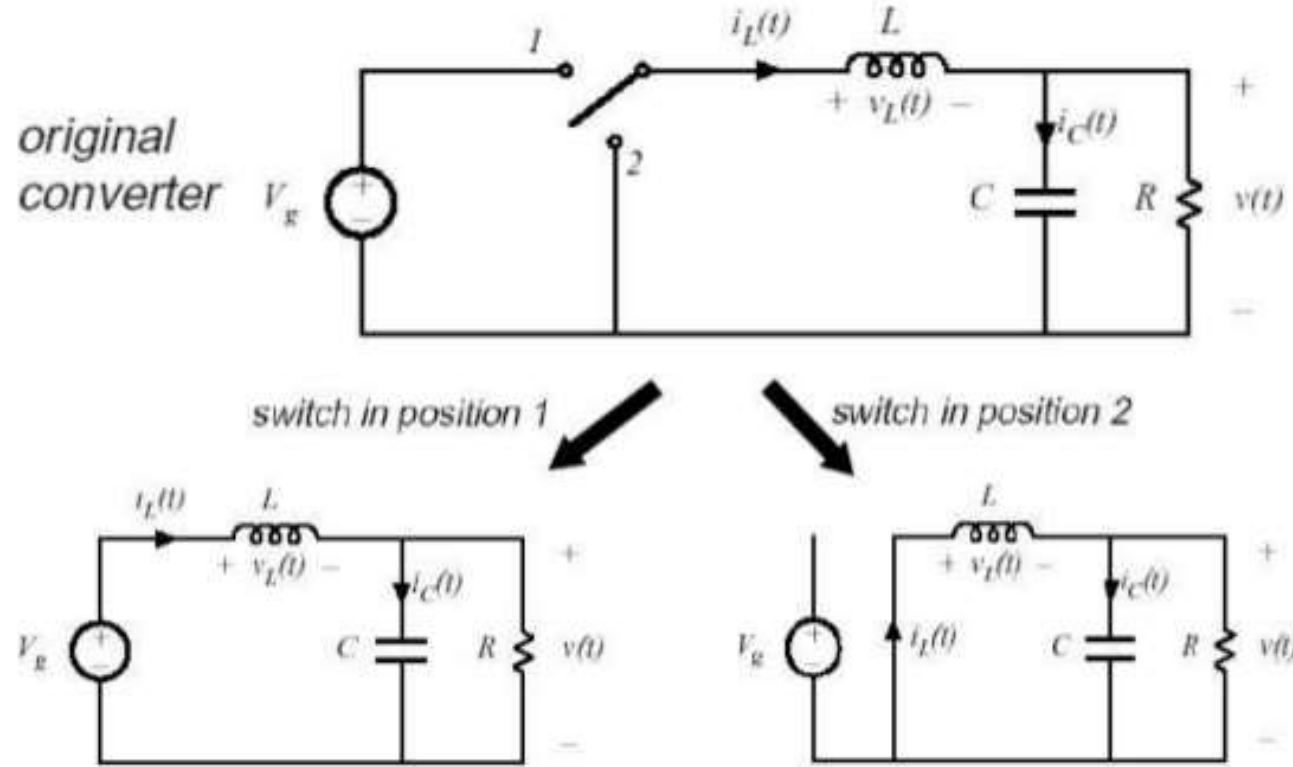

A. K. Gautam





References

1. https://www.tutorialspoint.com/power_electronics/power_electronics_introduction.htm#:~:text=Power%20Electronics%20refers%20to%20the,efficiency%20and%20reliability%20is%2010%25.
2. <http://www.egr.unlv.edu/~eebag/EE-442-642%20Introduction%20F14.pdf>
3. <https://www.youtube.com/watch?v=djbJm-xWo2w>
4. <https://www.youtube.com/watch?v=jx5l2Fbil8U>

