



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF COMPUTER SCIENCE ENGINEERING**

### **19ECB231 – DIGITAL ELECTRONICS**

II YEAR/ III SEMESTER

#### **UNIT 2 – COMBINATIONAL CIRCUITS**

**TOPIC – DECODER AND ENCODER**


---


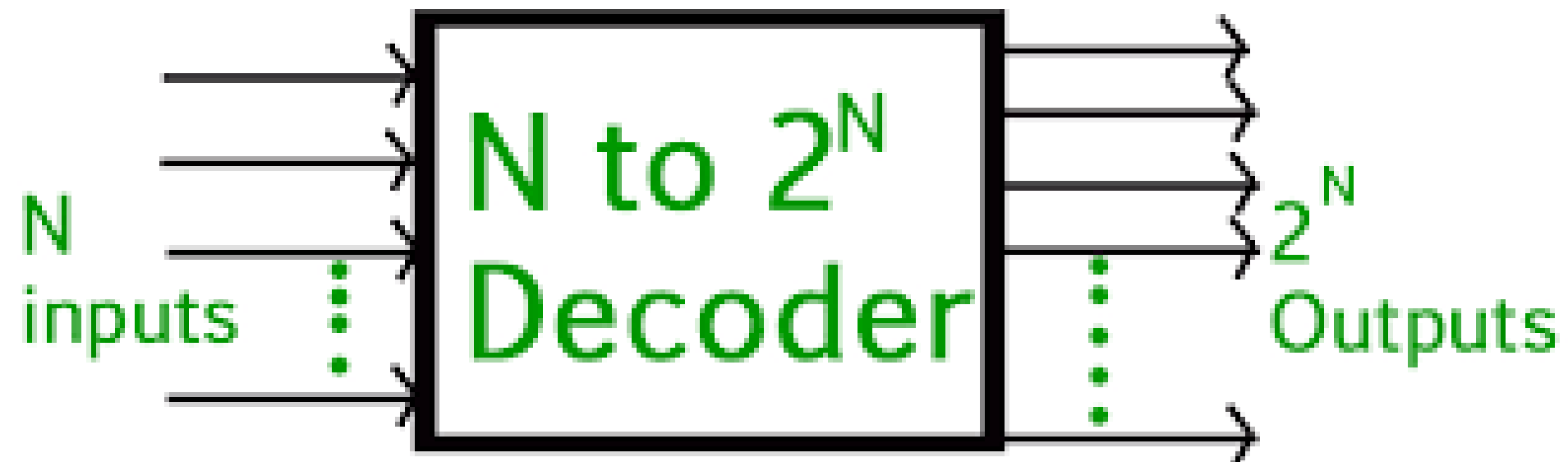
## WHAT IS A DECODER?



- **Decoder** is a combinational logic circuit that converts binary information from the  $n$  coded inputs to a maximum of  $2^n$  unique outputs.





# DECODER




A decoder has

- $n$  inputs
  - $2^n$  outputs
- A decoder selects one of  $2^n$  outputs by decoding the binary value on the  $n$  inputs.
  - The decoder generates all of the minterms of the  $n$  input variables.
- Exactly one output will be active for each combination of the inputs.

What does "active" mean?



# DECODER

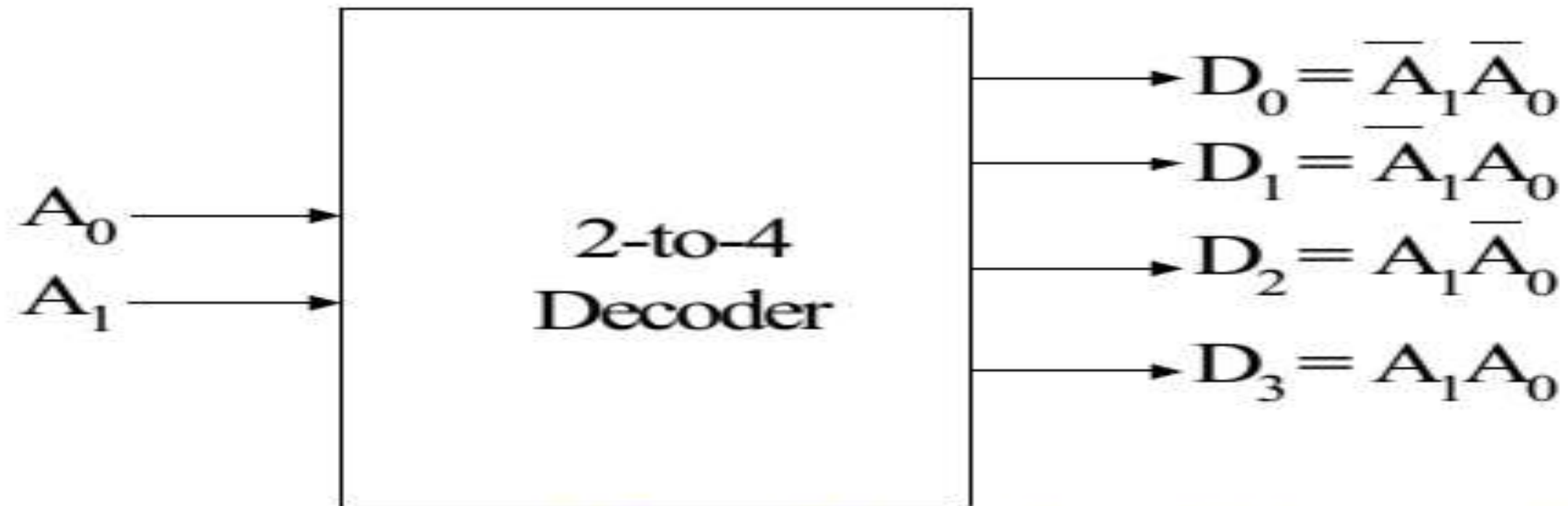

A 2-to-4 decoder without enable

Decimal #	Input		Output			
	$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1


Truth table for 2-to-4 decoder



# DECODER



Logic Diagram

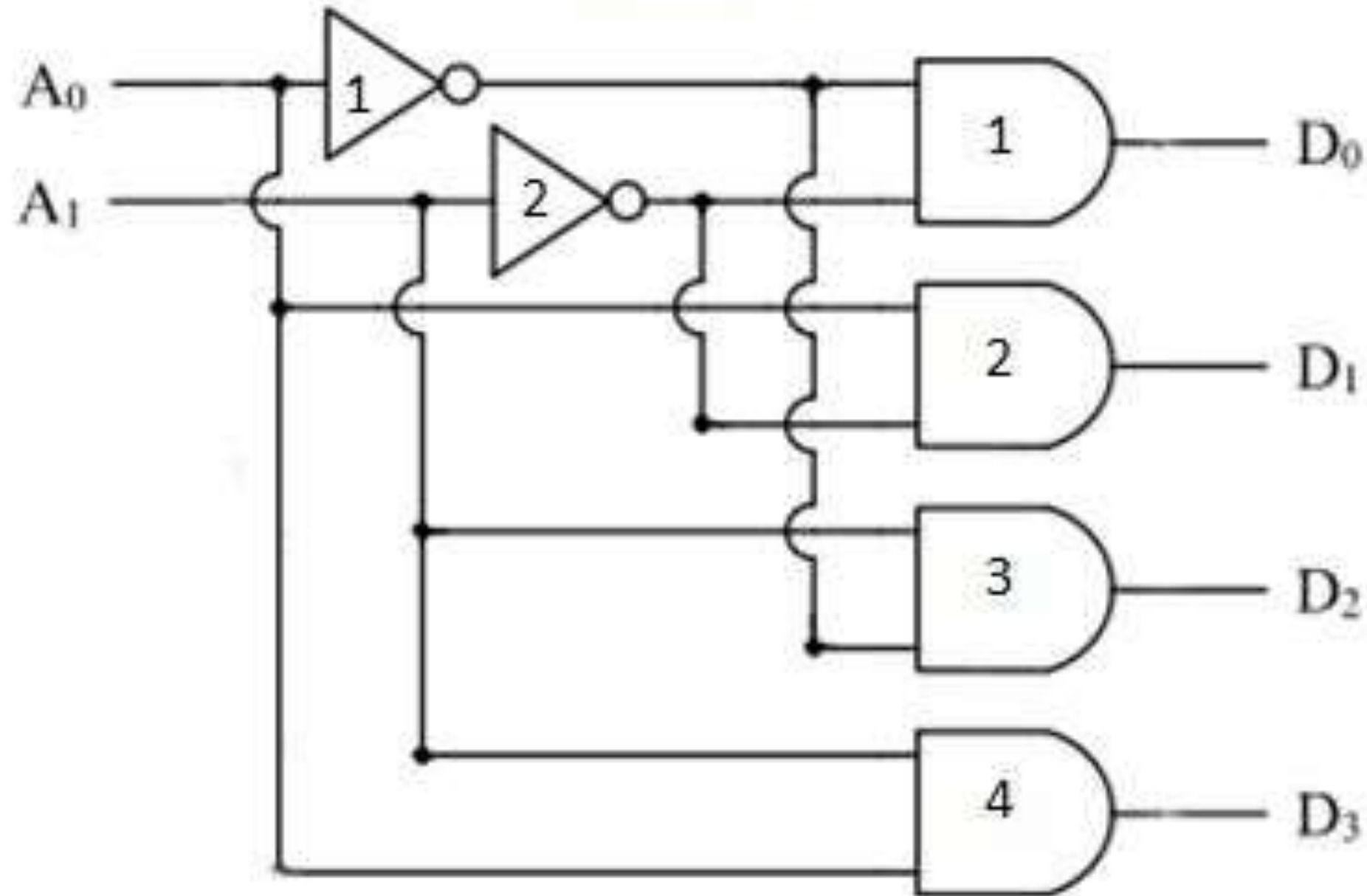

Truth Table

A <sub>1</sub>	A <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Equations

$$D_0 = \overline{A_1} \cdot \overline{A_0}$$


$$D_1 = \overline{A_1} \cdot A_0$$

$$D_2 = A_1 \cdot \overline{A_0}$$

$$D_3 = A_1 \cdot A_0$$




# DECODERS

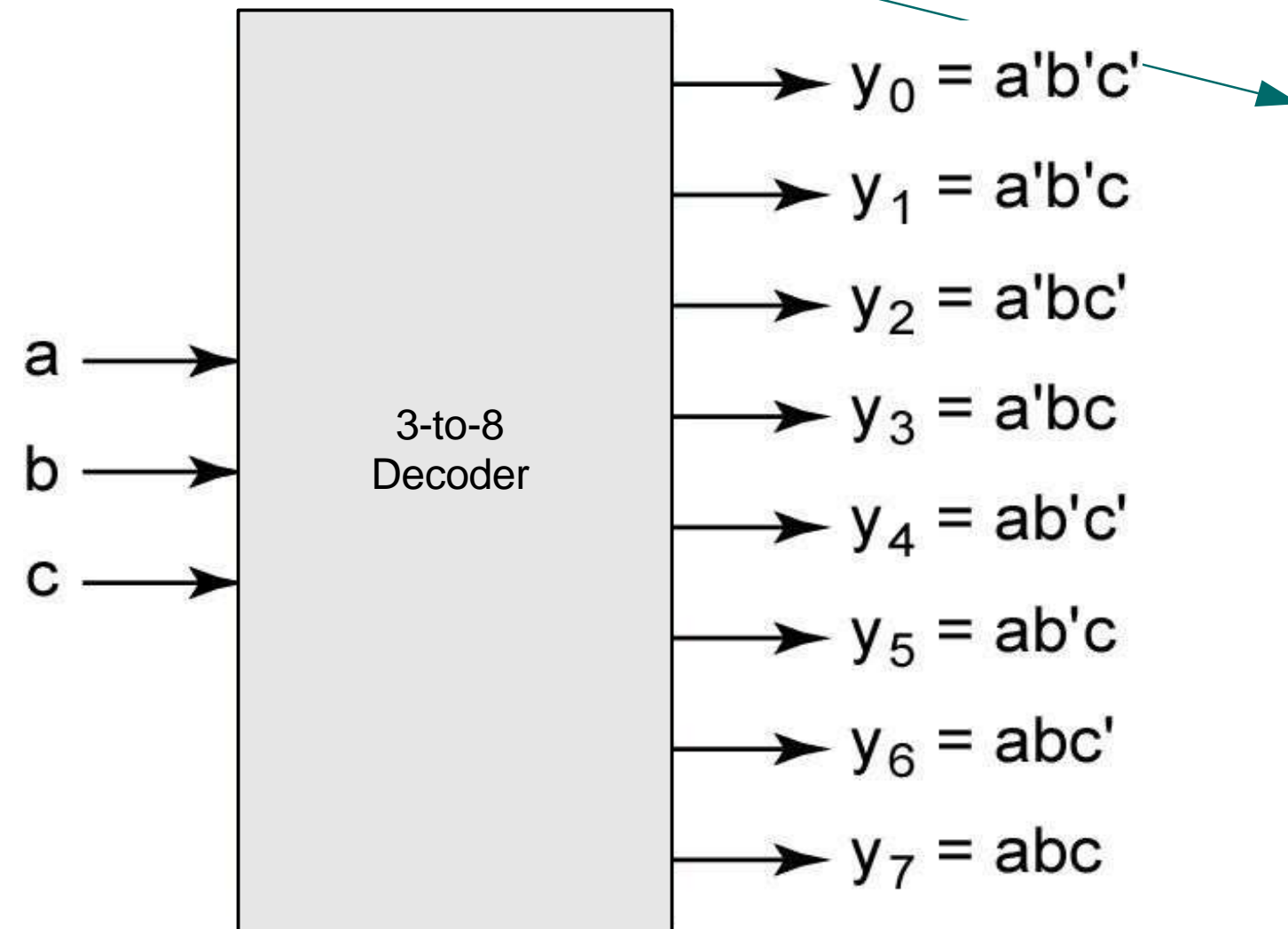

$a$	$b$	$c$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



# Decoder with Enable

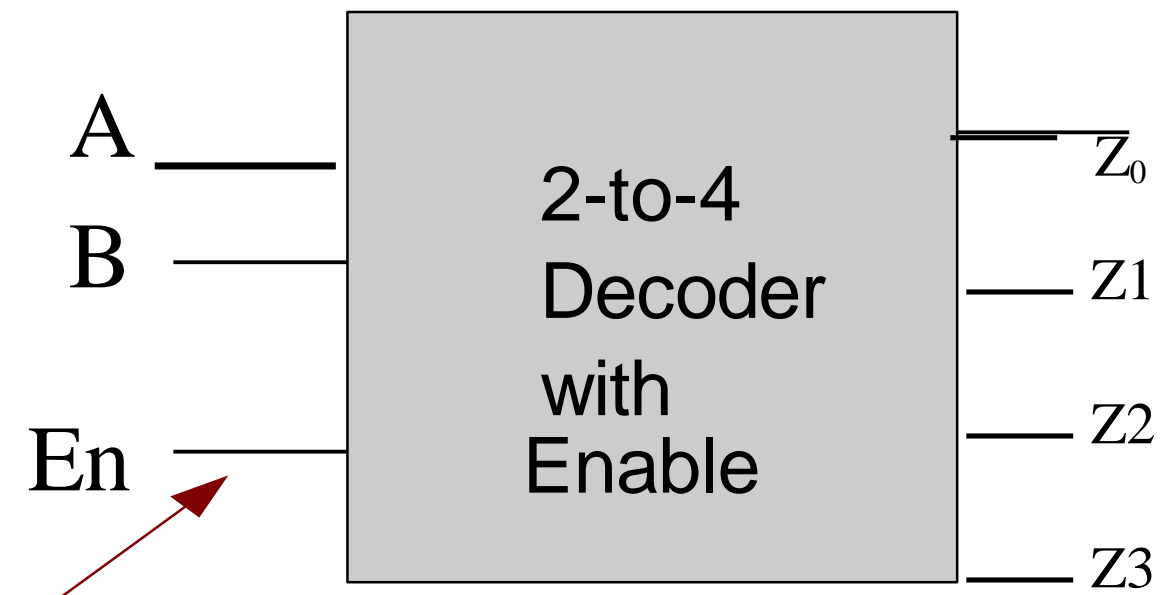

active-high enable


enabled

disabled

En	A	B	Z <sub>0</sub>	Z <sub>1</sub>	Z <sub>2</sub>	Z <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0



# Decoder with Enable

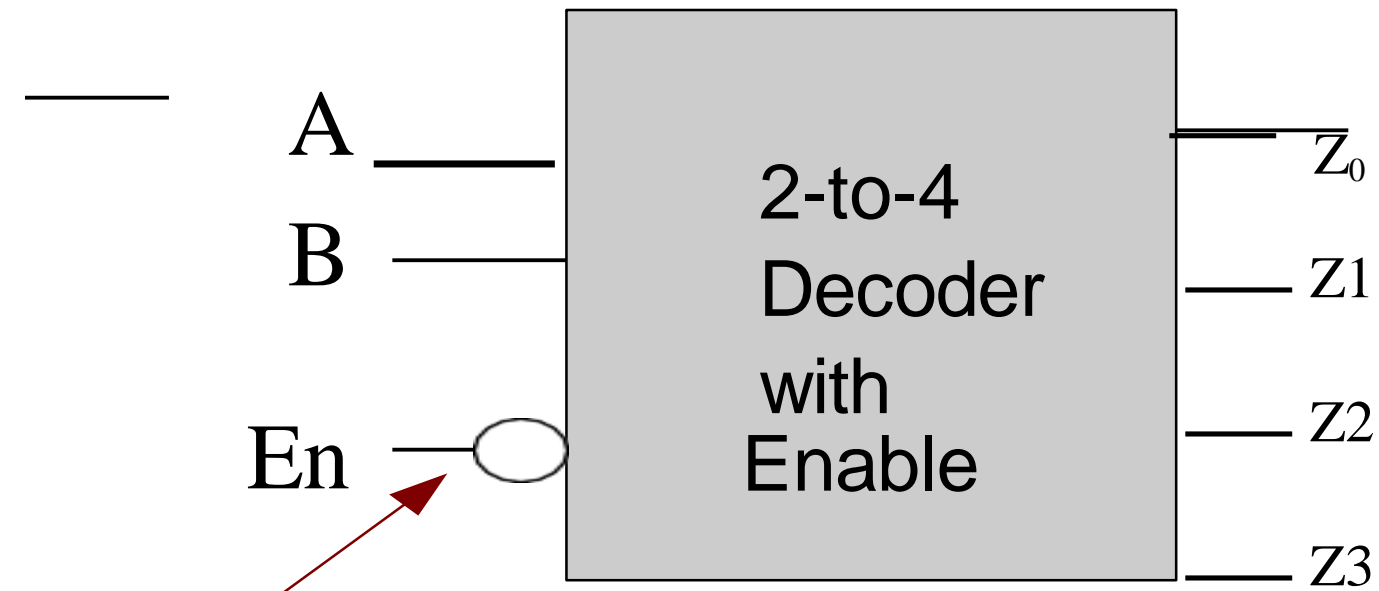

active-Low enable

enabled

disabled

En	A	B	Z <sub>0</sub>	Z <sub>1</sub>	Z <sub>2</sub>	Z <sub>3</sub>
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	x	x	0	0	0	0





## WHY ENCODERS?




An encoder has

- $2^n$  inputs
- $n$  outputs

Outputs the binary value of the selected (or active) input.


Performs the inverse operation of a decoder. Issues

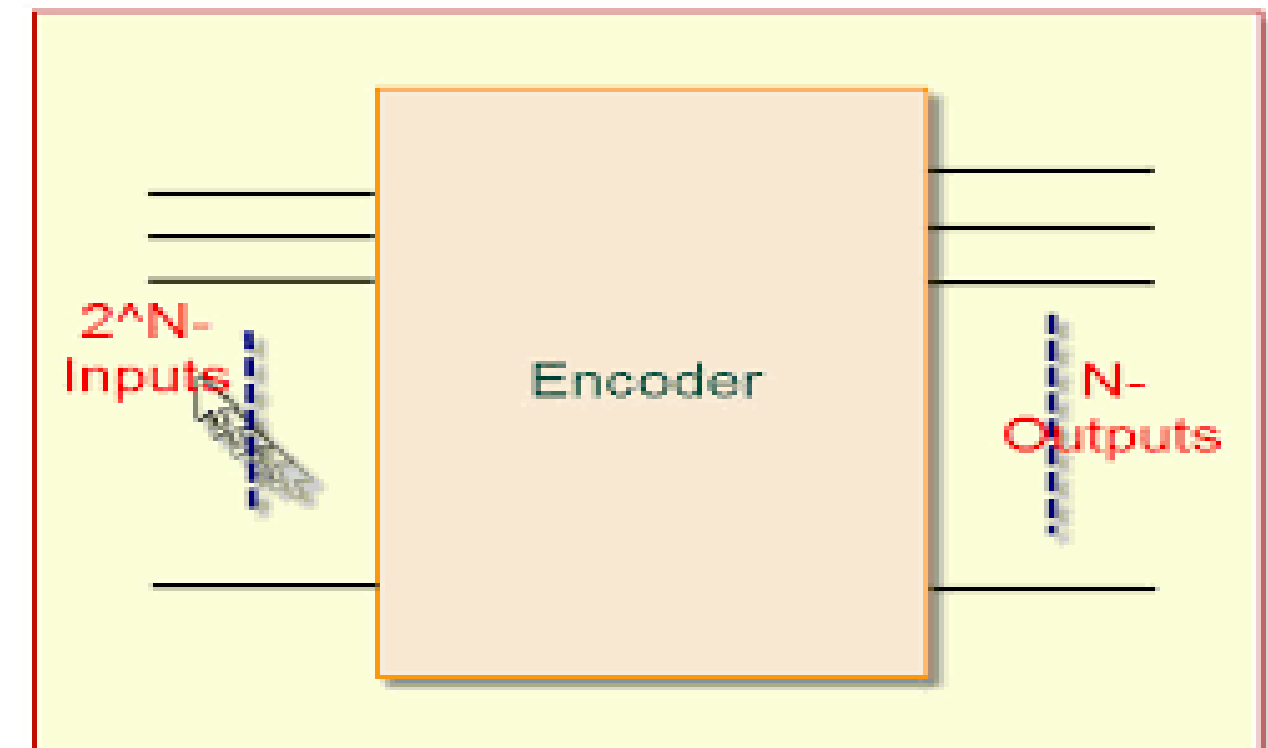- What if more than one input is active?
- What if no inputs are active?





# Encoders

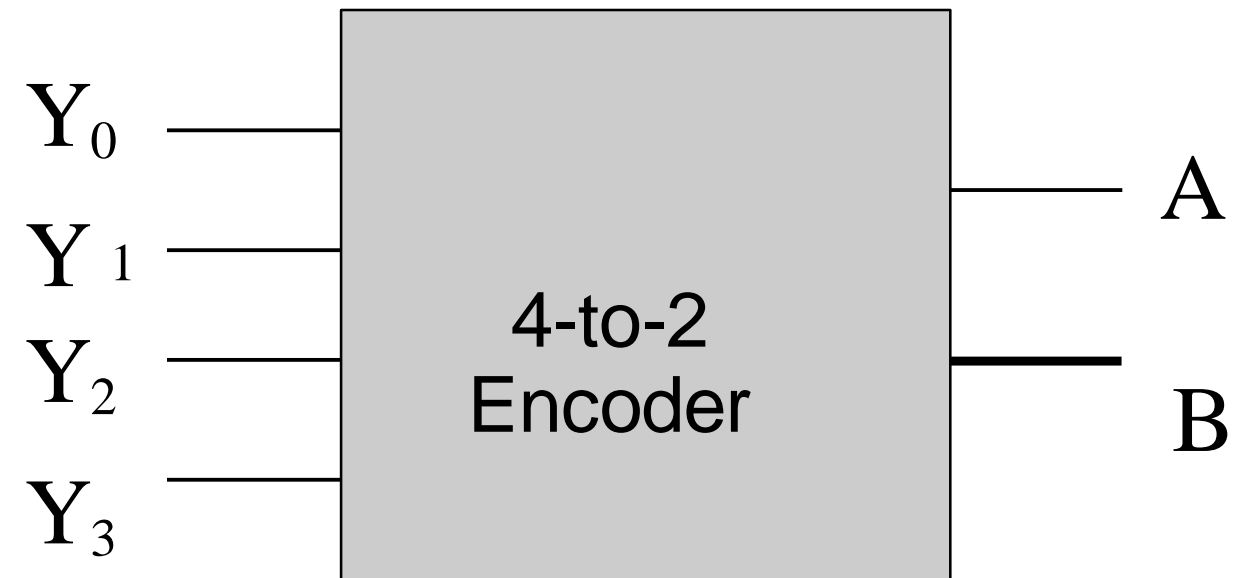

Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	A	B
1	0	0 <sub>10</sub>	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1




# Encoders



## 4 TO 2 LINE ENCODER

Logic diagram

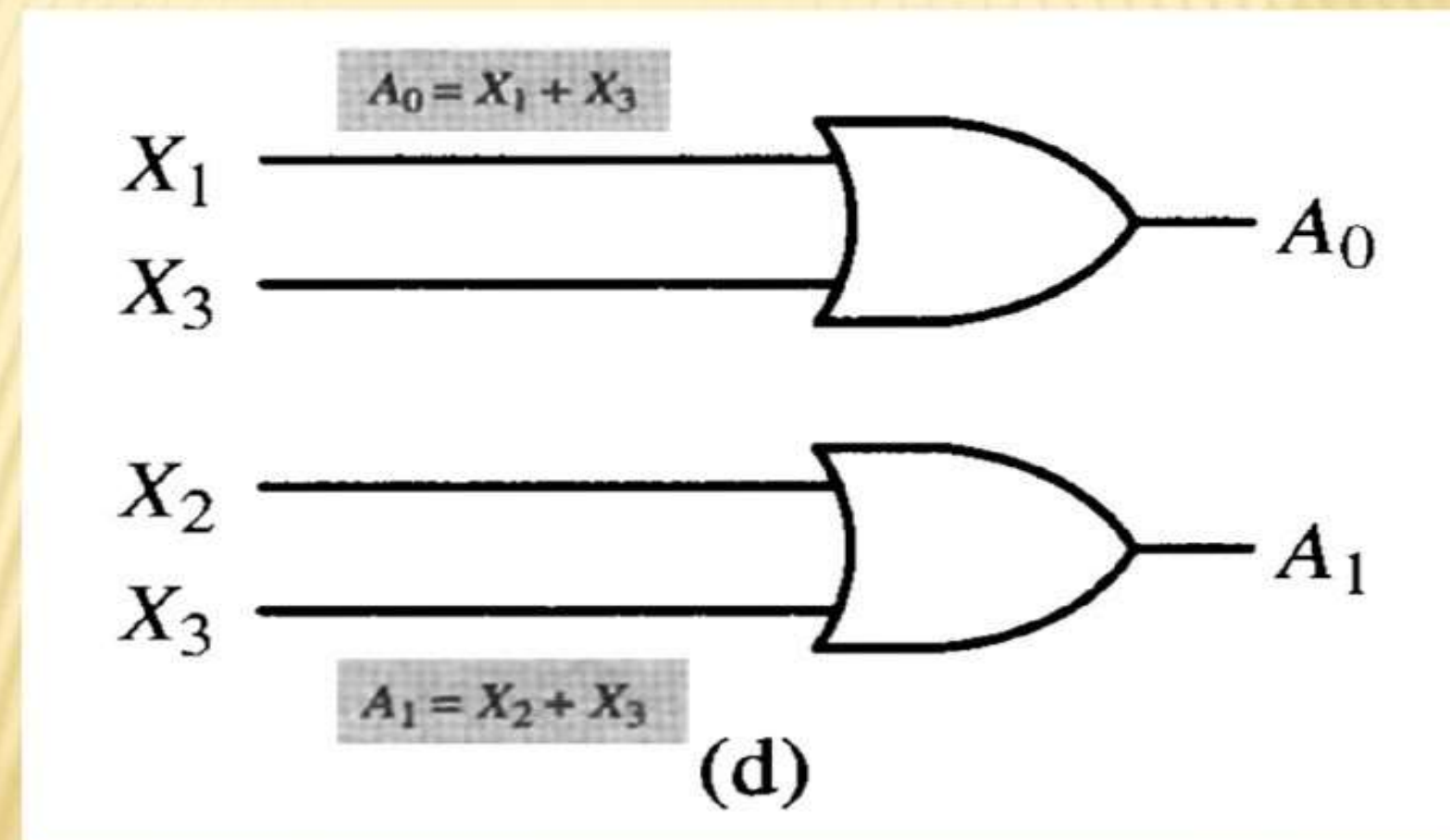



# Priority Encoders




- If more than one input is active, the higher-order input has priority over the lower-order input.
  - The higher value is encoded on the output
- A valid indicator,  $d$ , is included to indicate whether or not the output is valid.
  - Output is invalid when no inputs are active
    - $d = 0$
  - Output is valid when at least one input is active
    - $d = 1$

12



# Priority Encoders

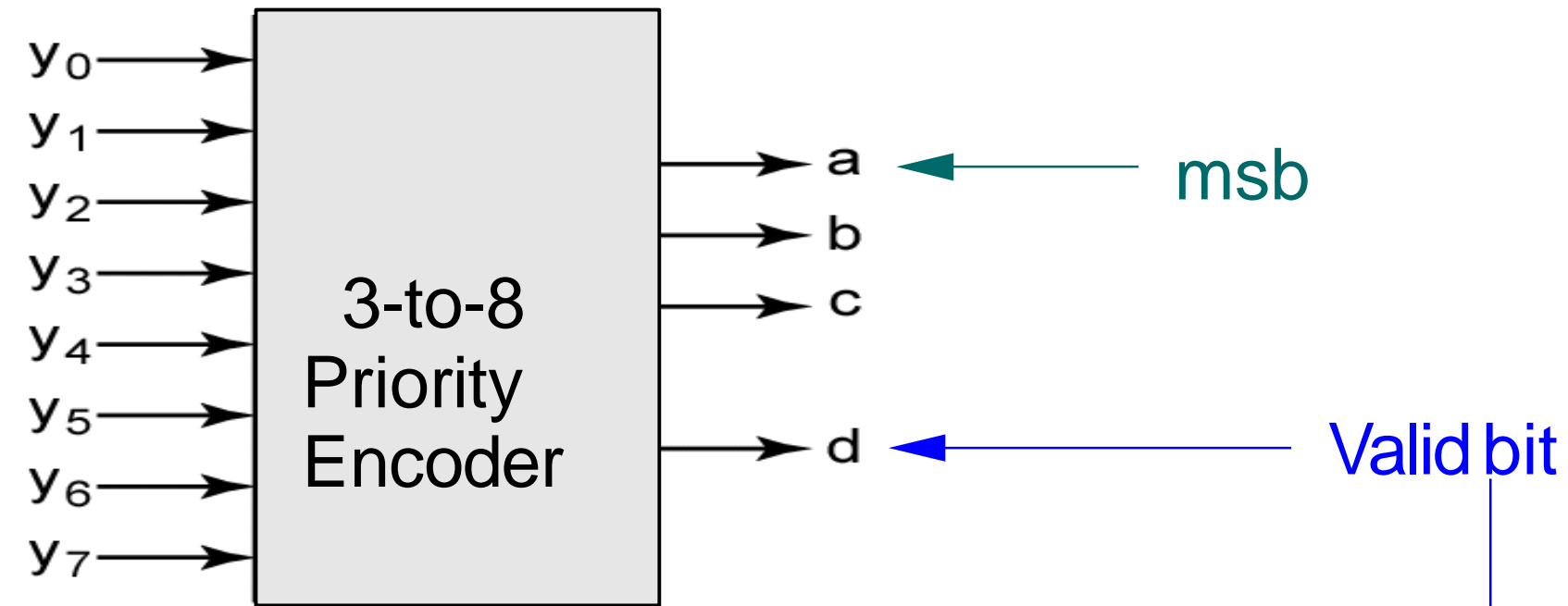

$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1



## Using an $n$ -output Decoder



- Use an  $n$ -output decoder to realize a logic circuit for a function with  $n$  minterms.
- Each minterm of the function can be mapped to an output of the decoder.
- For each row in the truth table, for the function, where the output is 1, sum (or “OR”) the corresponding outputs of the decoder.
- That is, for each minterm in the minterm expansion of the function, OR the corresponding outputs of the decoder.
- Leave remaining outputs of the decoder unconnected.



# Using an $n$ -output Decoder



## Example

- Using a 3-to-8 decoder, design a logic circuit to realize the following Boolean function
- $F(A,B,C) = \sum m(2, 3, 5, 6, 7)$



# Using an $n$ -output Decoder



## Example

- Using a 2-to-2 decoder, design a logic circuit to realize the following Boolean function

16

$$F(A,B,C) = \sum m(0, 1, 4, 6, 7)$$





# ASSESSMENT



1. What is a Encoder?
2. Device which converts an input device state into a binary representation of ones or zeros is termed as
  1. **Encoder**
  2. Decoder
  3. Multiplexer
  4. Data selector
3. A decoder converts n inputs to \_\_\_\_\_ outputs.( $2^n$ )
4. ----- are building blocks of encoders.(Ans - OR gate)
5. Draw the block diagram of 2x4 decoder.

17



**THANK YOU**