

Reg.No:

--	--	--	--	--	--	--	--




**SNS College of Technology, Coimbatore-35.**  
(Autonomous)

**B.E/B.Tech Internal Assessment -I**  
**Academic Year 2022-2023(ODD)**

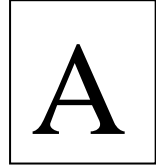**Third Semester**

**Electronics and Communication Engineering**  
**19ECB204 – Linear and Digital Circuits**



**Time: 1<sup>1/2</sup> Hours**

**Maximum Marks: 50**

**Answer All Questions**

**PART - A (5 x 2 = 10 Marks)**

				<b>CO</b>	<b>Blooms</b>
1.		Define an Integrated circuit.		CO1	Rem
2.		Outline the characteristics of an ideal op-amp.		CO1	Und
3.		Why integrators are preferred over differentiators in analog computers?		CO1	App
4.		Distinguish between Schmitt trigger and comparator.		CO2	Ana
5.		List out the applications of 555 timer.		CO2	Ana
<b>PART – B (2 x 13 = 26 Marks)</b>					
				<b>CO</b>	<b>Blooms</b>
6.	(a)	Analyze the DC and AC Characteristics of an Operational Amplifier.	13	CO1	Ana
		(or)			
	(b)	Outline the operation of an adder and subtractor using Op-Amp.	13	CO1	Und
7.	(a)	Explain the functional block of IC555 Timer circuit and its characteristics with necessary diagrams	13	CO2	Und
		(or)			
	(b)	Examine the Voltage regulators and its types with suitable expressions and diagrams.	13	CO2	Ana

PART – C (1 x 14 = 14 Marks)						
					CO	Blooms
8.	(a)	How the RC integrator and differentiator work? The input of a passive RC integrator circuit is wired to a resistance, and the output voltage is drawn from across a resistance. How the signal was produced by the integrator and differentiator?	14	CO1	Und	
		(or)				
	(b)	Design an Instrumentation Amplifier for the Heart Rate Measurement with Low Power Consumption	14	CO2	App	
		*****				

**Abbreviations:**

**CO** – Course Outcomes; **Rem-** Remembering; **Und** – Understanding; **App** – Applying; **Ana** – Analyzing

Reg.No:

--	--	--	--	--	--	--



**SNS College of Technology, Coimbatore-35.**  
(Autonomous)

**B.E/B.Tech Internal Assessment -I**  
**Academic Year 2022-2023(ODD)**

**Third Semester**

**Electronics and Communication Engineering**  
**19ECB204 – Linear and Digital Circuits**

<b>B</b>
----------

**Time: 1<sup>1/2</sup> Hours**

**Maximum Marks: 50**

**Answer All Questions**

**PART - A (5 x 2 = 10 Marks)**

			CO	Blooms	
1.	Define an Operational Amplifier		CO1	Rem	
2.	Compare ideal and practical characteristics of an op-amp.		CO1	Und	
3.	Why integrators are preferred over differentiators in analog computers?		CO1	App	
4.	What is a zero crossing detector?		CO2	Ana	
5.	List out the major blocks of 555 timer functional diagram		CO2	Rem	
<b>PART – B (2 x 13 = 26 Marks)</b>					
			CO	Blooms	
6.	(a)	Analyze the ideal Characteristics of an Operational Amplifier.	13	CO1	Ana
		(or)			
	(b)	Outline the operation of V to I and I to V convertors using Op-Amp.	13	CO1	Und
7.	(a)	Explain the working of Comparator and zero crossing detector in detail.	13	CO2	Und
		(or)			
	(b)	Discuss the applications of IC555 Timer with appropriate circuits and waveforms.	13	CO2	App

PART – C (1 x 14 = 14 Marks)					
				CO	Blooms
8.	(a)	Design a half wave and centre tapped full wave rectifier, then analyse the voltage signal it produces.	14	CO1	Ana
		(or)			
	(b)	Design an Inverting, Non-inverting adder with neat circuit diagram and derive its mathematical expressions.	14	CO2	App
		*****			

**Abbreviations:**

**CO** – Course Outcomes; **Rem-** Remembering; **Und** – Understanding; **App** – Applying;  
**Ana** – Analyzing