


# PARALLEL BINARY ADDER (RIPPLE CARRY ADDER)

## Definition

A binary adder is a digital circuit that produces the arithmetic sum of two binary numbers.

→ It can be constructed with full adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder in the chain.

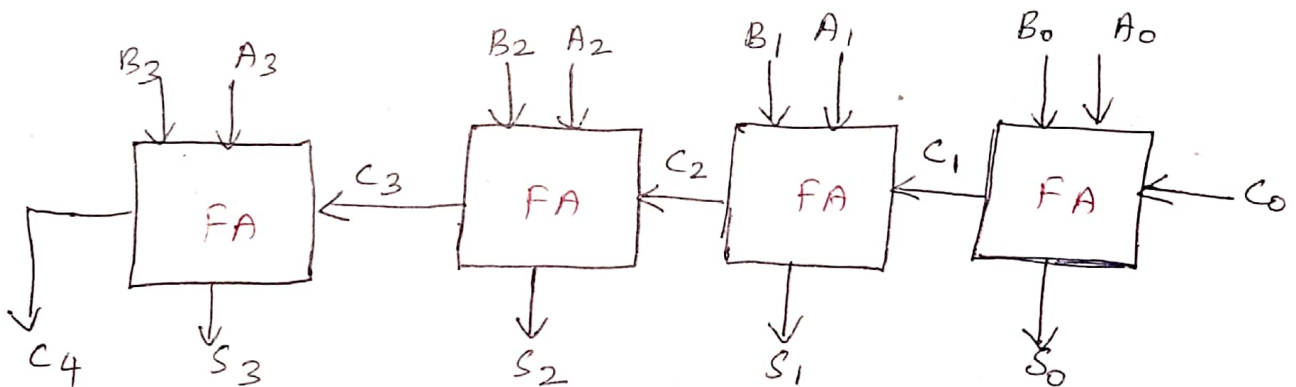→ Addition of  $n$  bit numbers requires a chain of  $n$  full adders.



EX: 4 bit adder block diagram.

Subscript  $i$ :

Input carry	$C_i$	0	1	1	0
Augend	$A_i$	1	0	1	1
Addend	$B_i$	0	0	1	1
Sum	$S_i$	1	1	1	0
output carry	$C_{i+1}$	0	0	1	1

← ripple carry of LSB → 0

# PARALLEL BINARY SUBTRACTOR

→ Subtraction of unsigned binary numbers can be done by means of complements.

→  $A - B$  is done by taking 2's complement of  $B$  and adding it to  $A$ .

$$A - B \Rightarrow A + (\text{2's complement of } B)$$


2's complement  $\Rightarrow$  1's complement + 1 to the LSB

EX: 2's complement 1100

1's complement of 1100  $\rightarrow$  0011

2's complement  $\rightarrow$   $\begin{array}{r} 0011 \\ + 1 \\ \hline 0100 \end{array}$

1's complement can be implemented with inverters, and a '1' can be added to the sum through the input carry.

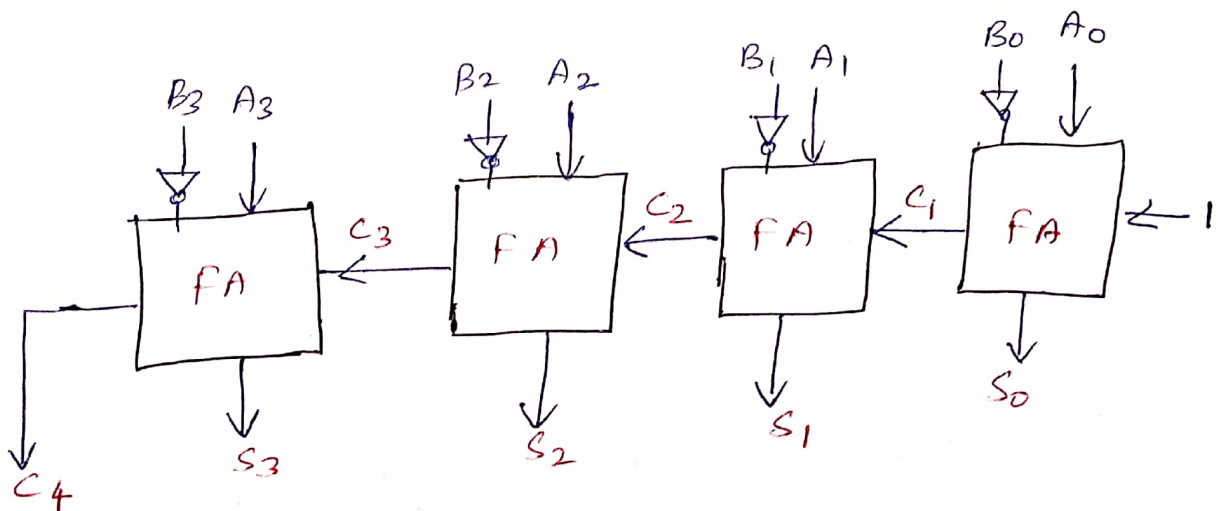

(Fig 7) 4 bit binary subtractor.



---

The FA receives the value of B & the input carry is 0 & the circuit performs addition.  
→ ~~When  $M=0$~~

When  $M=1$ ,  $B \oplus 1 = B'$  &  $C_0 = 1$

The B inputs are complemented & a '1' is added through the input carry, the circuit performs the operation subtraction.

i.e.  $A + (2's \text{ complement of } B)$