



# **SNS COLLEGE OF TECHNOLOGY**

## **An Autonomous Institution**

### **Coimbatore-35**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB301-ANALOG AND DIGITAL COMMUNICATION**

III YEAR/ V SEMESTER


### **UNIT 2 – RADIO TRANSMITTER & RECEIVER**

TOPIC – FM RECEIVER

---



# FM RECEIVER

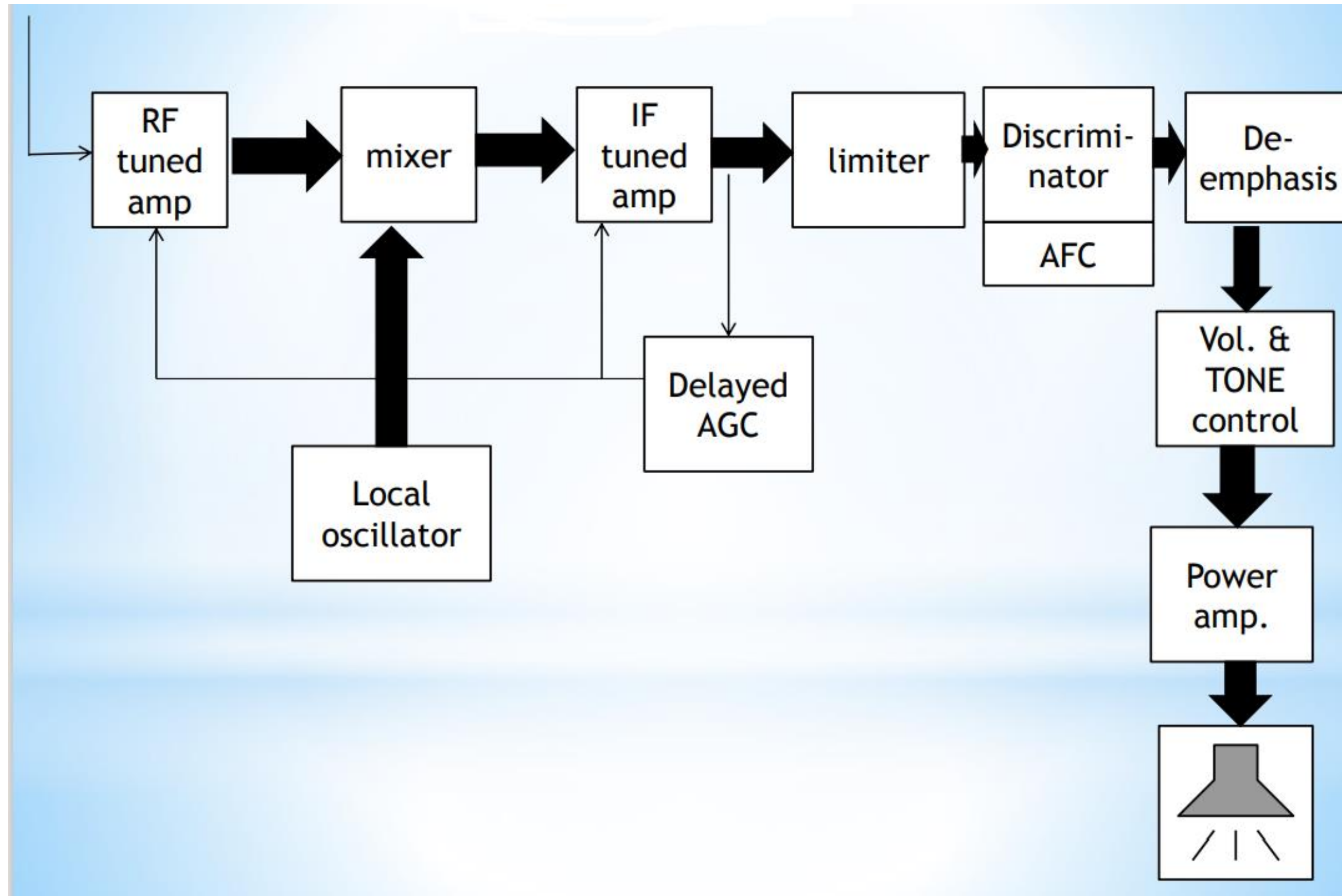



# FM RECEIVER



## RF tuned amplifier-

These amplifiers are used for impedance matching to minimise noise level

## Mixers-

These oscillator circuits are take any form to mix up the frequency modulated signal for performing the operation in such circuit central frequency are change but deviation are constant

## Intermediate frequency amplifier-

The IF amplifier provides most of the gain and bandwidth requirement of the receiver.





# FM RECEIVER



## Limiters-

Limiters are those circuit which allows the certain frequency range to pass out and block the other signals

## Discriminator-

The discriminator change FM into AM. A simple diode detection then recover the intelligence contained in the envelop of the AM waveform.

## De-emphasis-

The artificial boosting given to the higher modulating frequencies in the process of pre-emphasis is nullified or compensated at the receiver by the process of De-emphasis



# FM RECEIVER



## Vol & tone controller-

In this circuit it control the efficiency of audio signal. The signal whose efficiency is more then audible range are neglected in this circuit.

## Power amplifier-

The power amplifier gives the required power level to the signal which passes through the loudspeaker.





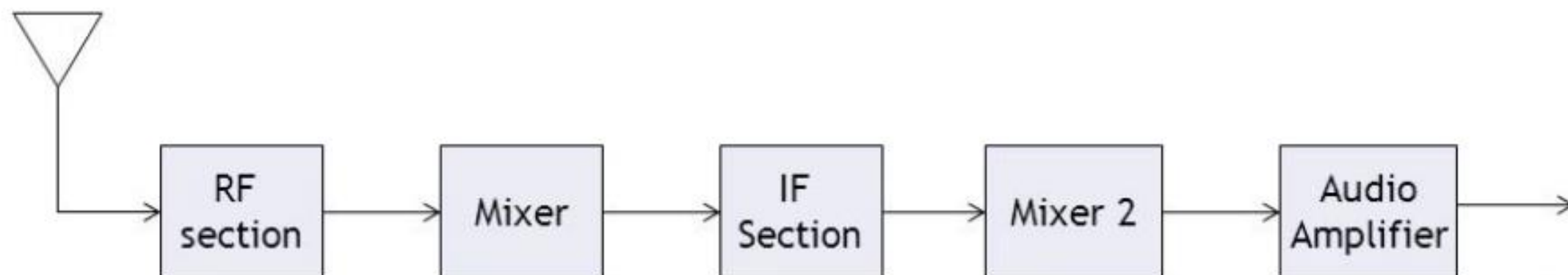
## SSB RECEIVER



- The receiver is of the normal **superhet** design. The first stages are the same as we met for DSBFC.
- The incoming signal is amplified by the RF Amplifier and passed to the mixer.
- The other input to the mixer is the local oscillator that is running at 455kHz above the frequency to which the receiver is tuned.
- The mixer generates sum and difference signals and the lower of the two is the resulting IF signal occupying a range of frequencies around 455kHz.
- The audio information must now be separated from these IF frequencies.





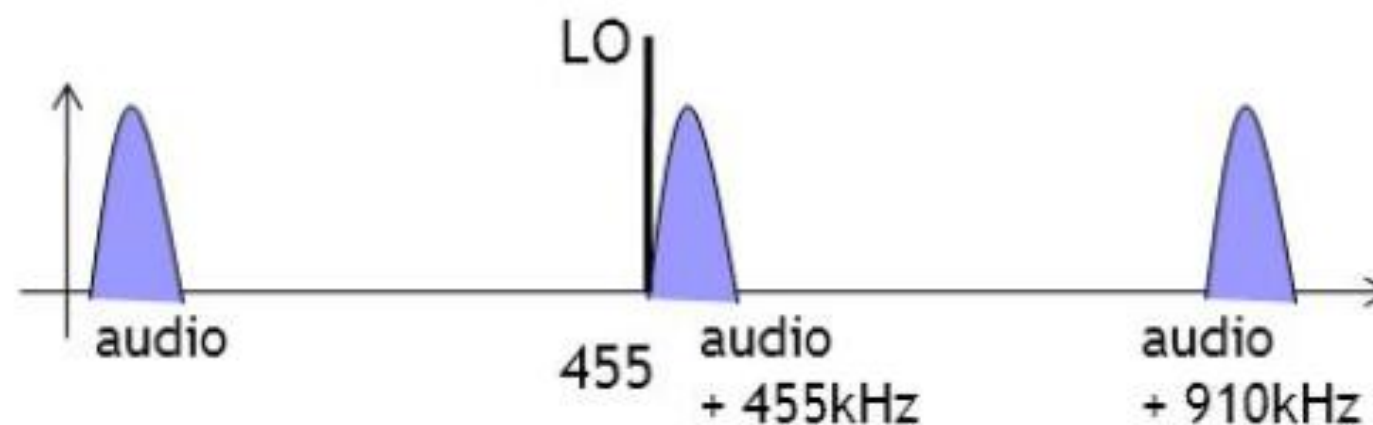
## SSB RECEIVER



- One way of extracting the audio signals is to use a mixer to shift the frequencies.
- If a mixer combined an input of (audio + 455kHz) with another input of 455kHz, the resultant outputs would be the usual 'sum' and 'difference' frequencies.
  - The 'sum' would be  $(\text{audio} + 455\text{kHz}) + (455\text{kHz}) = (\text{audio} + 910\text{kHz})$  which is far too high a frequency to be of much interest to us.
  - The 'difference' frequency is just what we wanted  $(\text{audio} + 455\text{kHz}) - (455\text{kHz}) = (\text{audio})$ .





**THANK YOU**