



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC
with 'A+' Grade

Approved by AICTE, New Delhi & Affiliated to Anna
University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECT201 – ELECTRICAL ENGINEERING & INSTRUMENTATION


II YEAR/ III SEMESTER

UNIT 2 – TRANSFORMER

**TOPIC 5 – TRANSFORMER ON LOAD NO LOAD-EQUIVALENT CIRCUIT -
REGULATION OF TRANSFORMER**



IDEAL TRANSFORMER ON NO LOAD

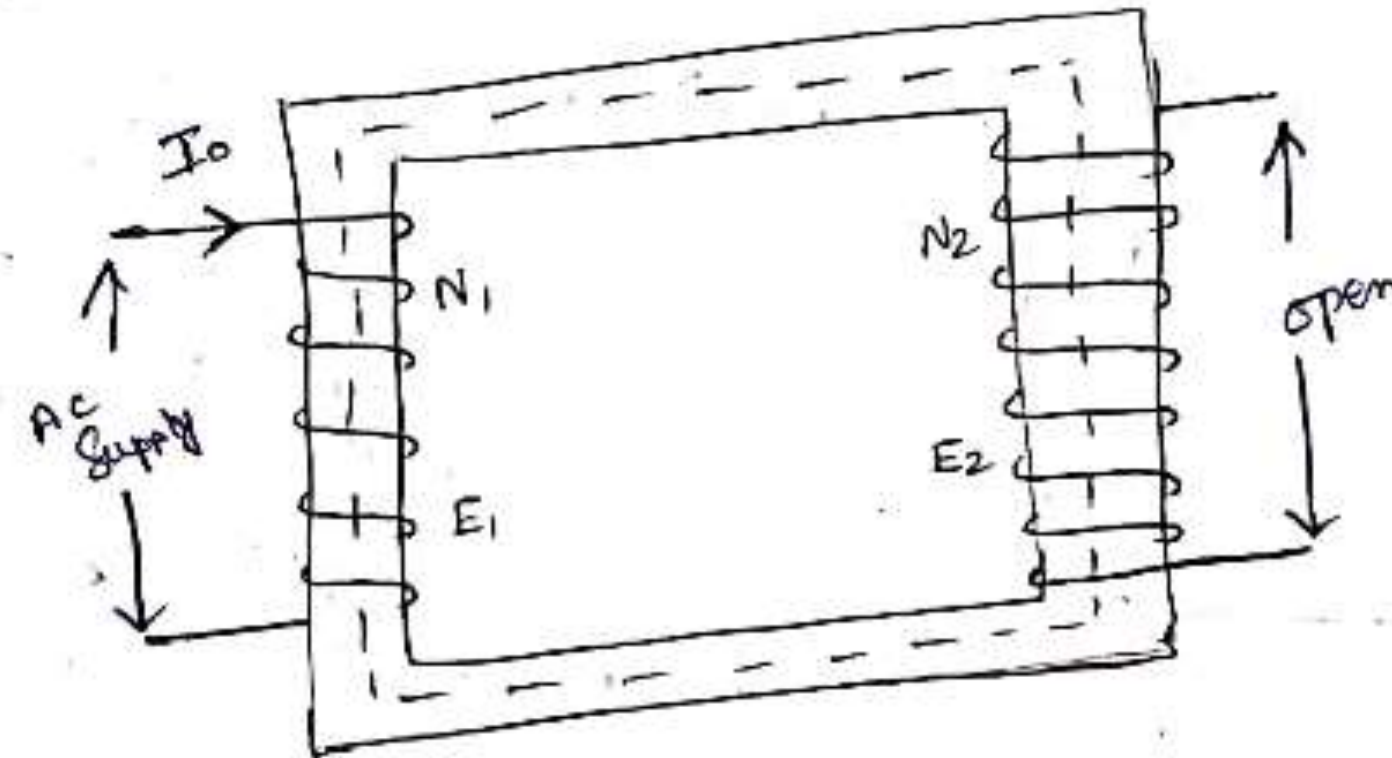

No load current
2 to 10% of
rated current

I_0 - No load current

Losses:

- * Core loss
 - * Copper loss
- In secondary - 0
 Φ will be lesser
in primary winding

I_0 is divided as

- I_w - Working Component Current or Active Current.
- I_M - Magnetizing Current or reactive Current.
- V_1 - Supply voltage
- E_1, E_2 = Rms value of primary & Secondary voltage.



IDEAL TRANSFORMER ON NO LOAD

PHASOR DIAGRAM:-

From the phasor diagram


$$\cos \phi_0 = \frac{I_w}{I_0}$$
$$I_w = I_0 \cos \phi_0 \rightarrow (1)$$
$$\sin \phi_0 = \frac{I_m}{I_0}$$
$$I_m = I_0 \sin \phi_0 \rightarrow (2)$$

Square and add eqn (1) & (2)

$$I_w^2 + I_m^2 = I_0^2 \cos^2 \phi_0 + I_0^2 \sin^2 \phi_0$$
$$= I_0^2 (\cos^2 \phi_0 + \sin^2 \phi_0)$$
$$= I_0^2$$
$$\therefore I_0 = \sqrt{I_w^2 + I_m^2}$$




IDEAL TRANSFORMER ON LOAD

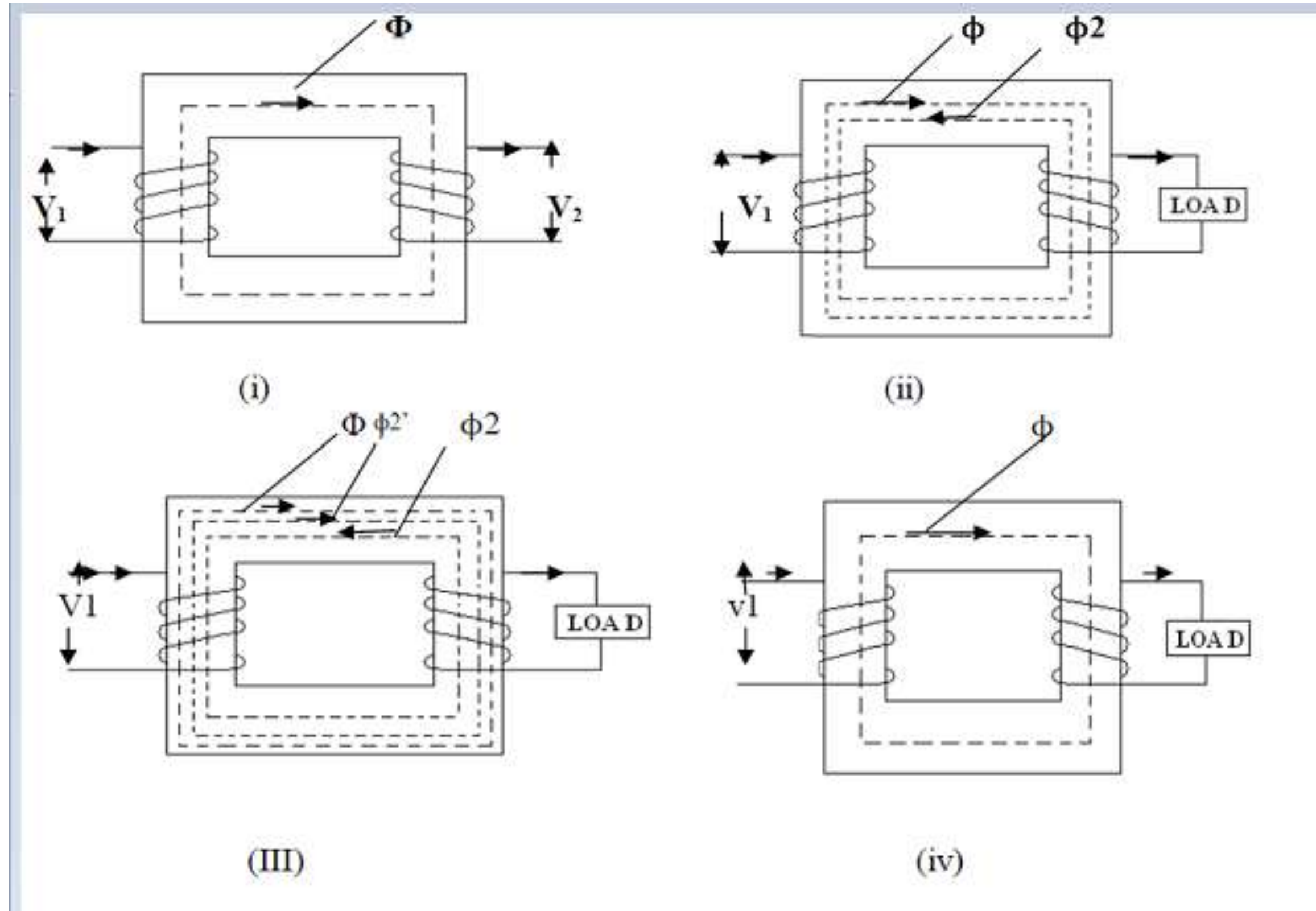



EQUIVALENT CIRCUIT OF TRANSFORMER

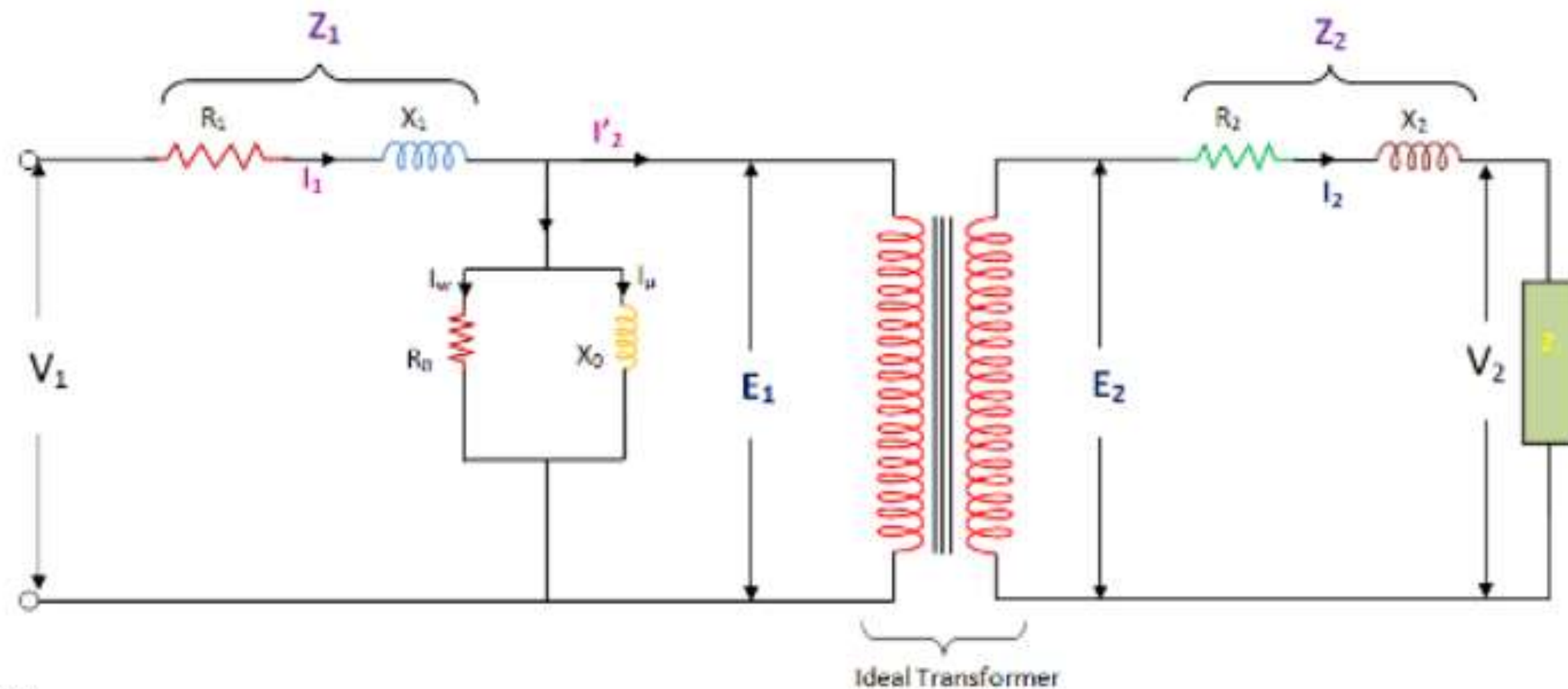

Where,

R_1 = Primary Winding Resistance.

R_2 = Secondary winding Resistance.


I_0 = No-load current.

I_μ = Magnetizing Component,


I_w = Working Component,



EQUIVALENT CIRCUIT OF TRANSFORMER

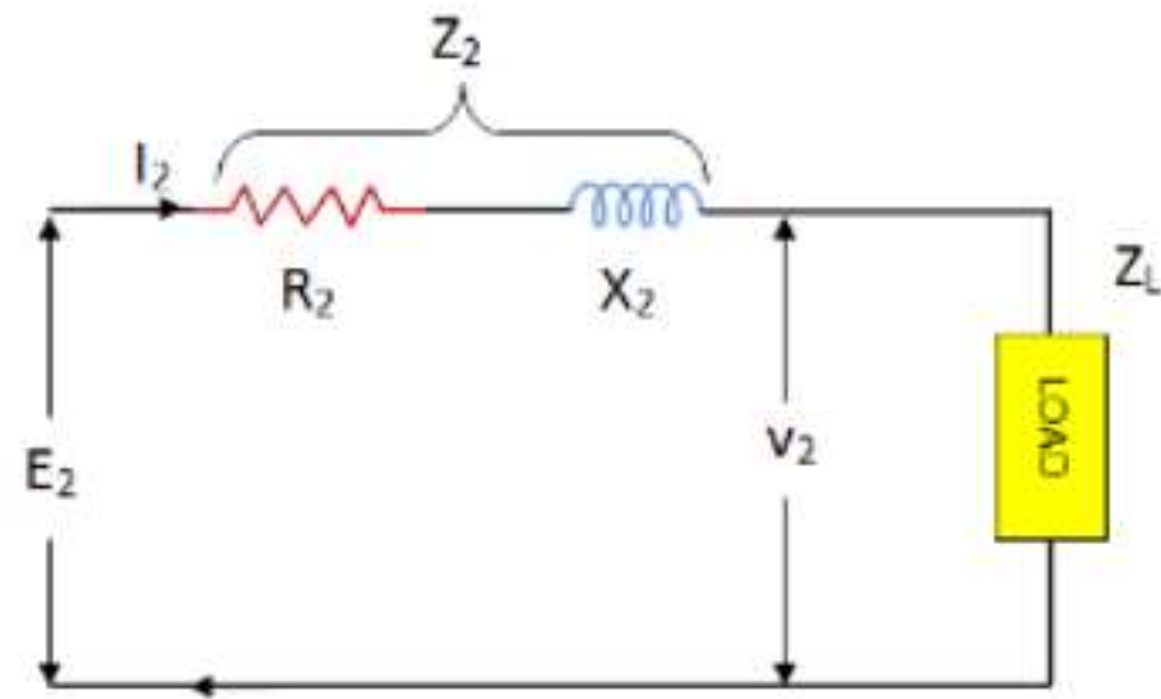

SECONDARY CIRCUIT

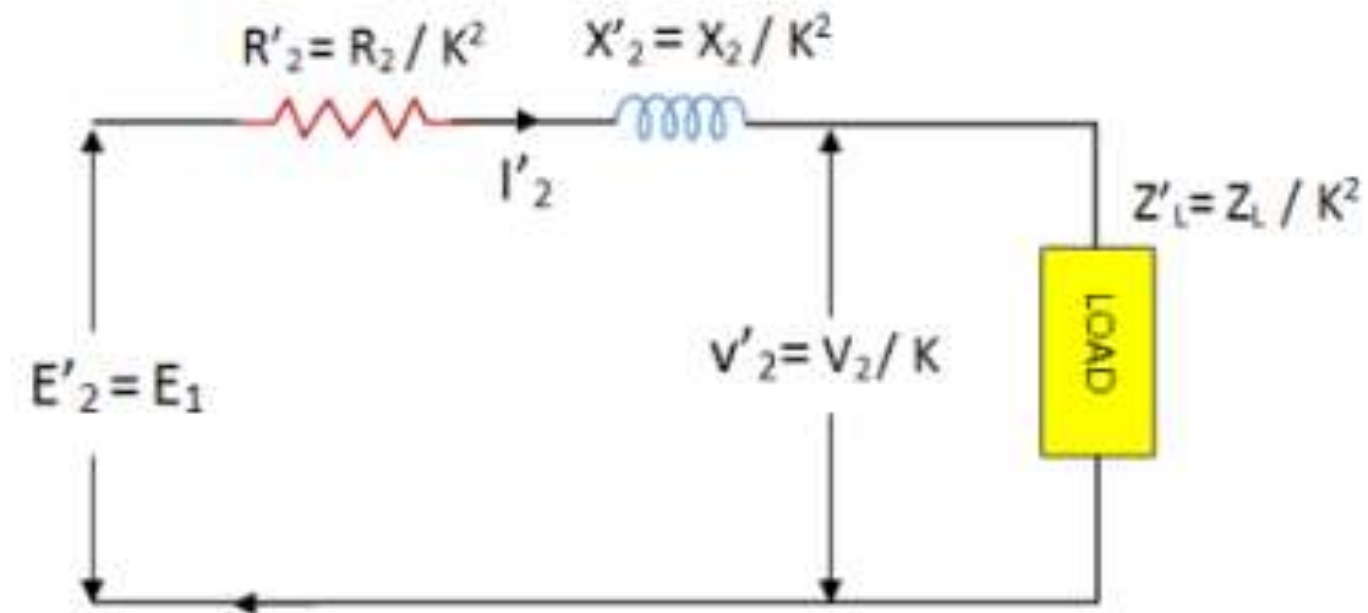

SECONDARY CIRCUIT EQUIVALENT PRIMARY VALUE


- Transferring resistance or reactance from primary to secondary, multiply it by K^2
- Transferring resistance or reactance from secondary to primary, divide it by K^2
- Transferring voltage or current from one winding to other, only K is used By EMF Eqn

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

$$E_1 = 4.44 f N_1 \Phi_m$$
$$E_2 = 4.44 f N_2 \Phi_m$$




EQUIVALENT CIRCUIT OF TRANSFORMER

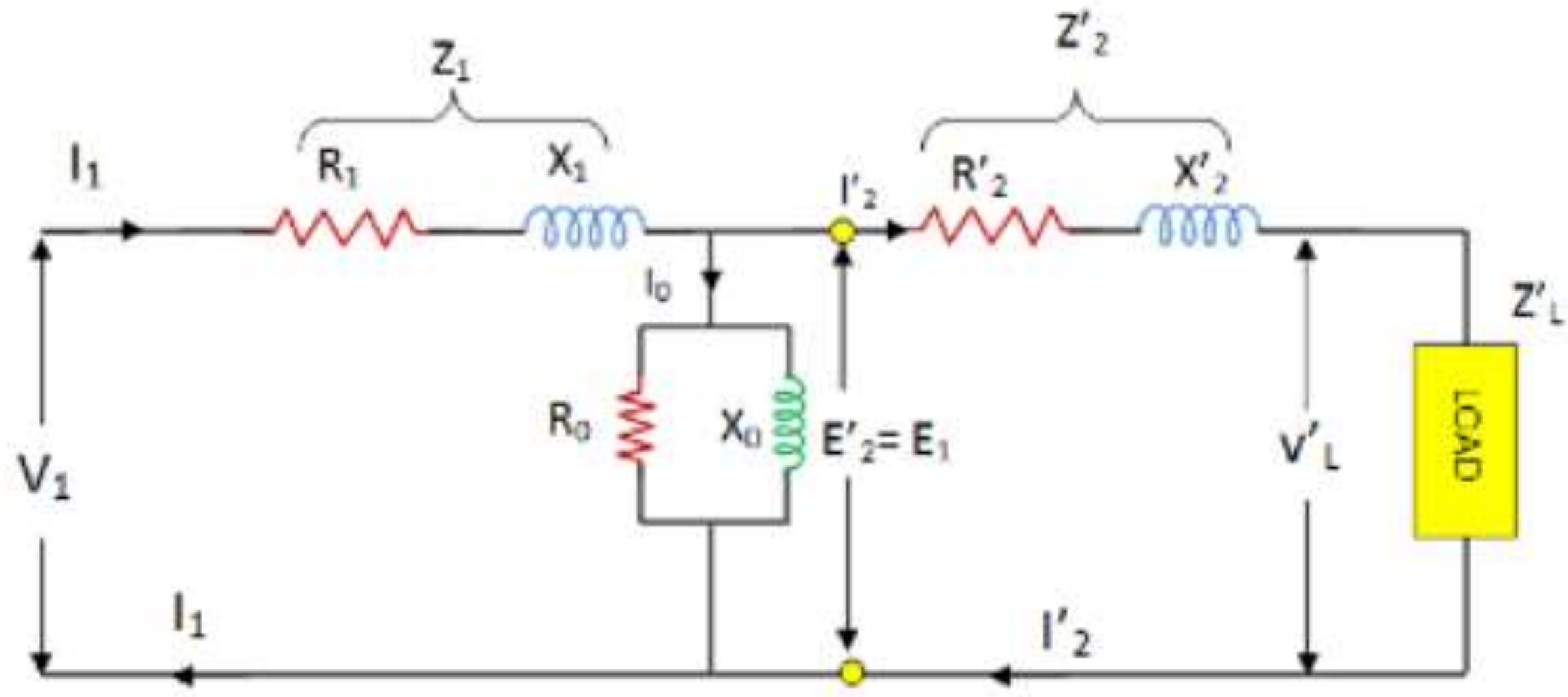




EQUIVALENT CIRCUIT OF TRANSFORMER

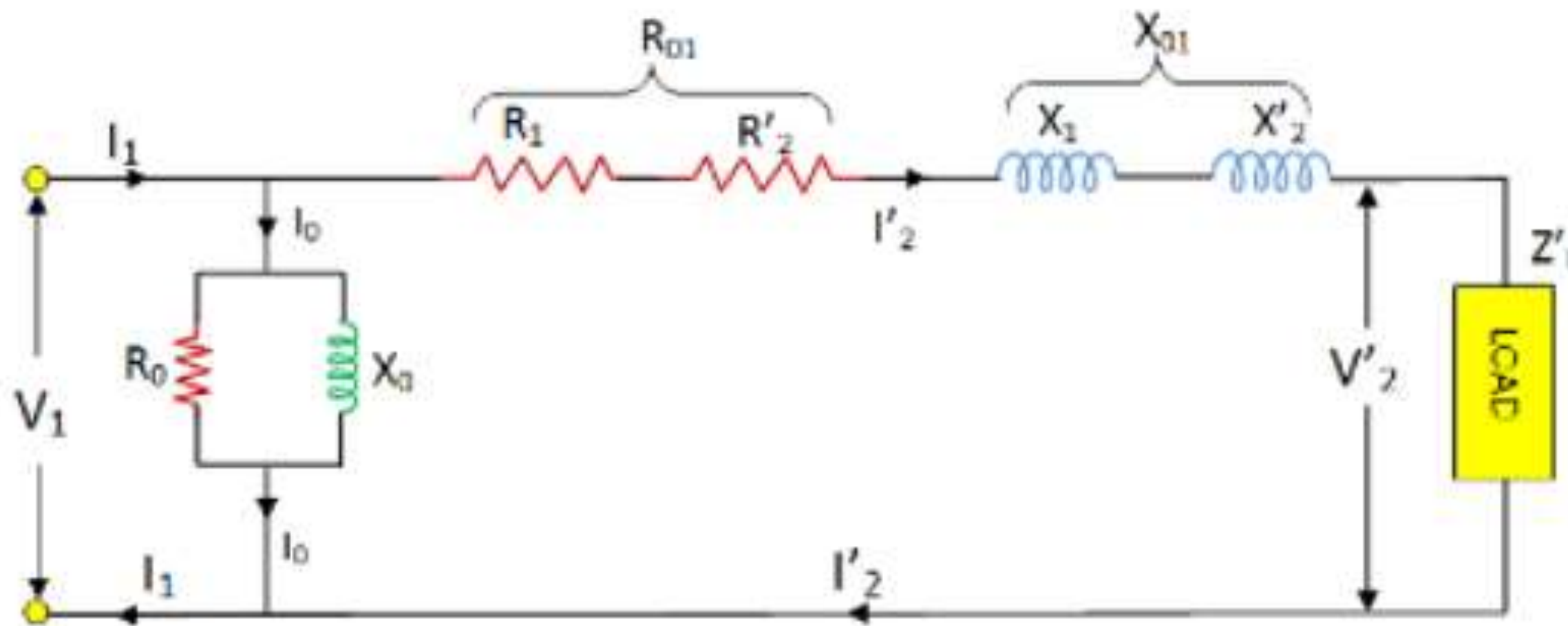



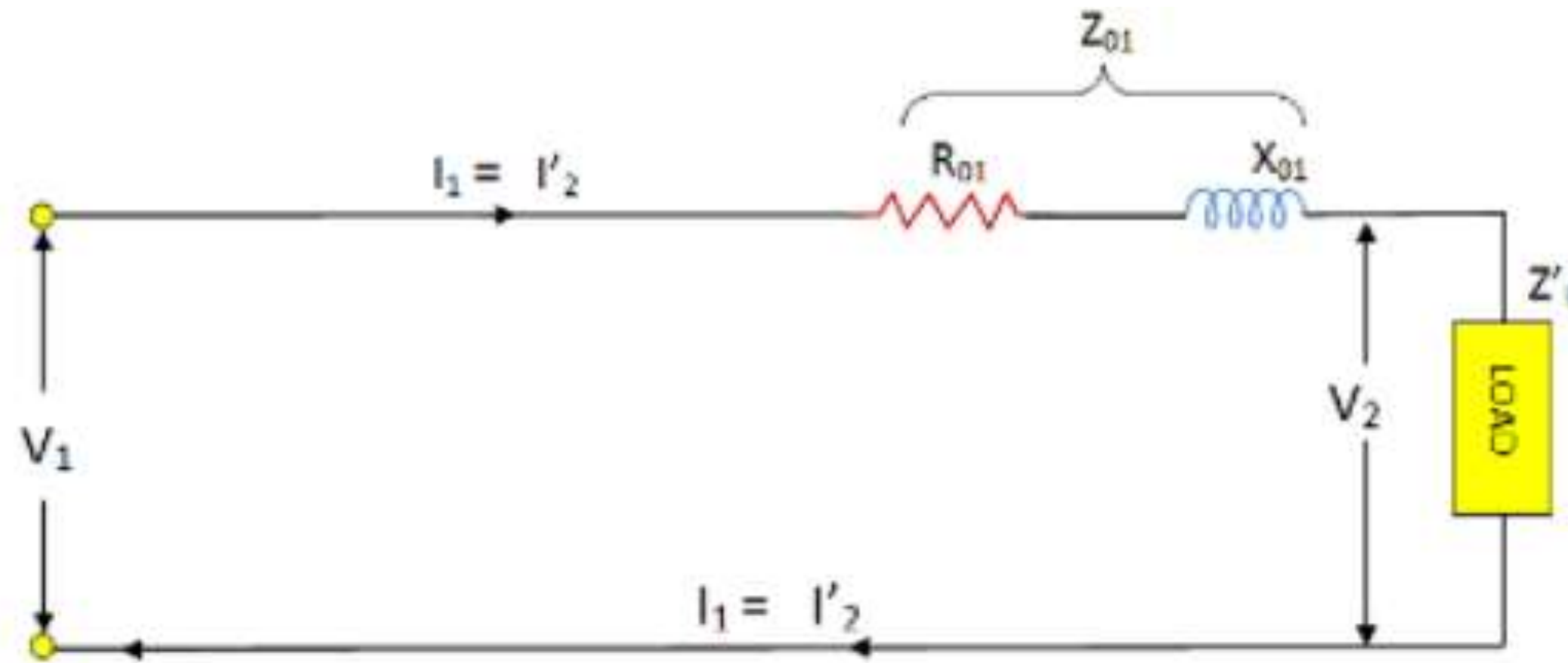SIMPLIFIED EQUIVALENT CIRCUIT OF TRANSFORMER





VOLTAGE REGULATION OF TRANSFORMER

The voltage regulation of a transformer is the arithmetic difference between the no – load secondary voltage (E_2) and the secondary voltage on load expressed as percentage of no – load voltage.

$$\% R = \frac{E_2 - V_2}{V_2} \times 100$$

The ratio $(E_2 - V_2)/V_2$ is called per unit regulation.

E_2 = no load secondary voltage = KV_1

V_2 = secondary voltage on load

The secondary voltage also depends on the power factor of the load

$V_2 < E_2$ - lagging power factor - '+ve Regulation

$E_2 < V_2$ - leading power factor - '-ve Regulation



EXPRESSION FOR VOLTAGE REGULATION

$$\% R = \frac{E_2 - V_2}{V_2} \times 100 = \frac{\text{Total voltage drop}}{V_2} \times 100$$

By using the expression of voltage drop from approximate voltage drop

$$\text{Total voltage drop} = I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi.$$

Substitute in above we get

$$\% R = \frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \times 100$$

Note:

‘+’ve – sign for lagging power factor

‘-’ve - sign for leading power factor



EFFICIENCY OF TRANSFORMER

Efficiency of a Transformer

Like any other electrical machine, the efficiency of a transformer is defined as the ratio of output power (in watts or kW) to input power (watts or kW) i.e.,

$$\text{Power output} = \text{power input} - \text{Total losses}$$

$$\begin{aligned} \text{Power input} &= \text{power output} + \text{Total losses} \\ &= \text{power output} + P_i + P_{cu} \end{aligned}$$

$$\text{Efficiency} = \frac{\text{power output}}{\text{power input}}$$

$$\text{Efficiency} = \frac{\text{power output}}{\text{power input} + P_i + P_{cu}}$$

Power output = $V_2 I_2 \cos \phi$, $\cos \phi$ = load power factor

Transformer supplies full load of current I_2 and with terminal voltage V_2

P_{cu} = copper losses on full load = $I_2^2 R_{2e}$

➤ **IN ELECTRICAL MACHINE EFFICIENCY:99% IS COMMON AT SAFER OPERATING CONDITIONS**



EFFICIENCY OF TRANSFORMER

$$\text{EFFICIENCY} = \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_i + I_2^2 R_{02}}$$

$V_2 I_2 = \text{VA rating of a transformer}$

$$\text{EFFICIENCY} = \frac{(\text{VA rating}) \times \cos \phi}{(\text{VA rating}) \times \cos \phi + P_i + I_2^2 R_{02}}$$

This is full load efficiency and $I_2 = \text{full load current}$.

We can now find the full-load efficiency of the transformer at any p.f. without actually loading the transformer.


➤ **TRANSFORMER FAILURE RATE IN INDIA IS 20% .WERE IT SHOULD BE ONLY 4%**



*Thank
You*




OPEN CIRCUIT TEST ON TRANSFORMER

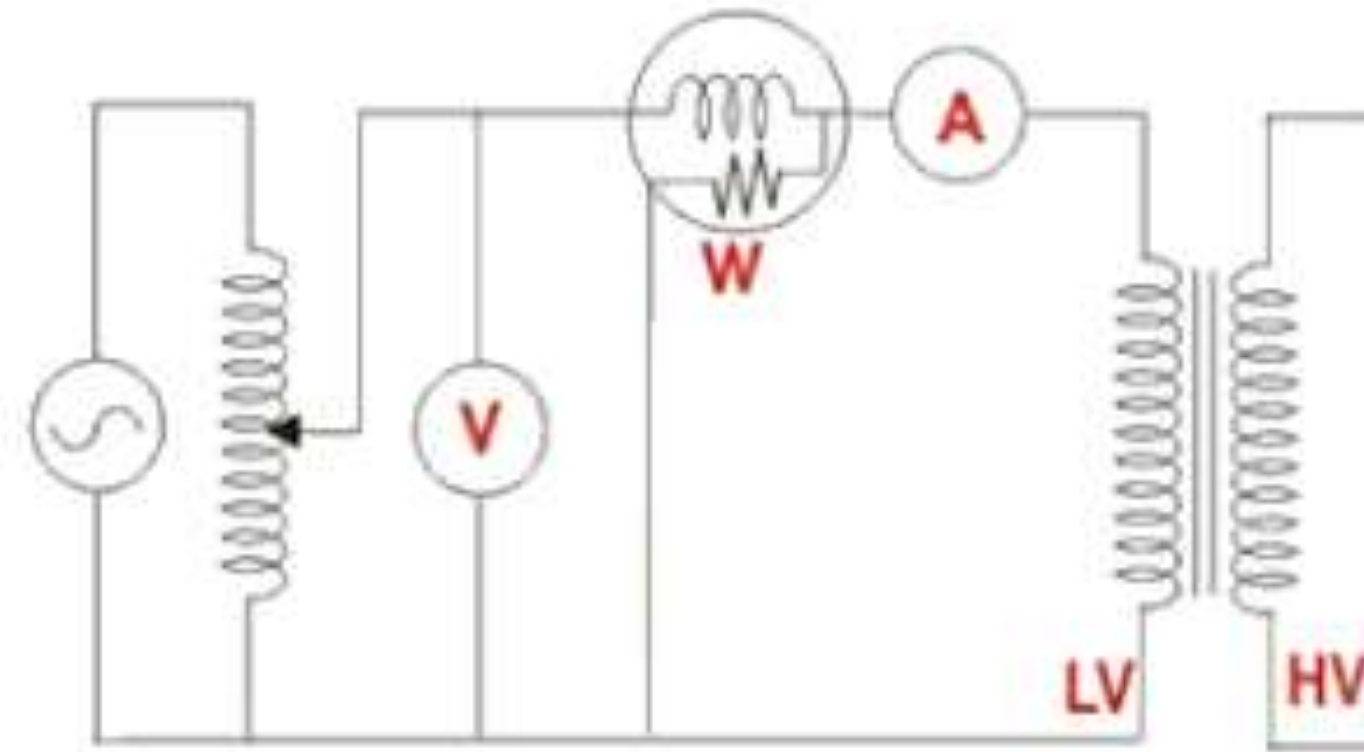

Open Circuit Test on Transformer



SHORT CIRCUIT TEST ON TRANSFORMER

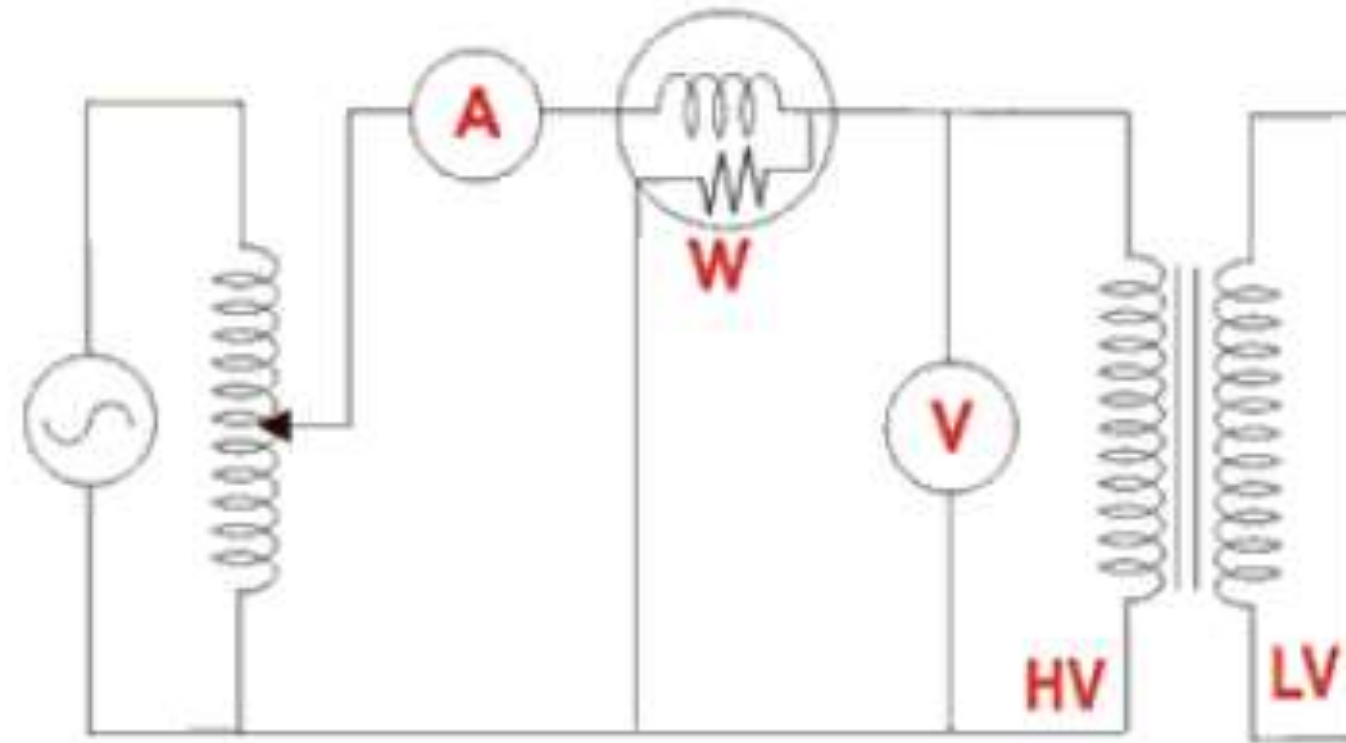

Short Circuit Test on Transformer



WHY TRANSFORMER IS RATED IN KVA?

Example: 1KVA Transformer 115/230V

- Numerator will be always primary
- Denominator will be always secondary

$$V_1 I_1 = V_2 I_2 = VA$$

$$115(I_1) = 1000 = 8.69A$$

$$230(I_2) = 1000 = 4.347A$$