



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

19ECB202 – LINEAR AND DIGITAL CIRCUITS

II YEAR/ III SEMESTER

Flip Flops/19ECB204/ LINEAR AND DIGITAL
CIRCUITS/Mr.N.Arunkumar/AP/ECE/SNSCT

1

UNIT 5 – SEQUENTIAL CIRCUITS and PLC


TOPIC 1 – FLIP FLOP FUNDAMENTALS and SR Flipflop



Sequential Circuits



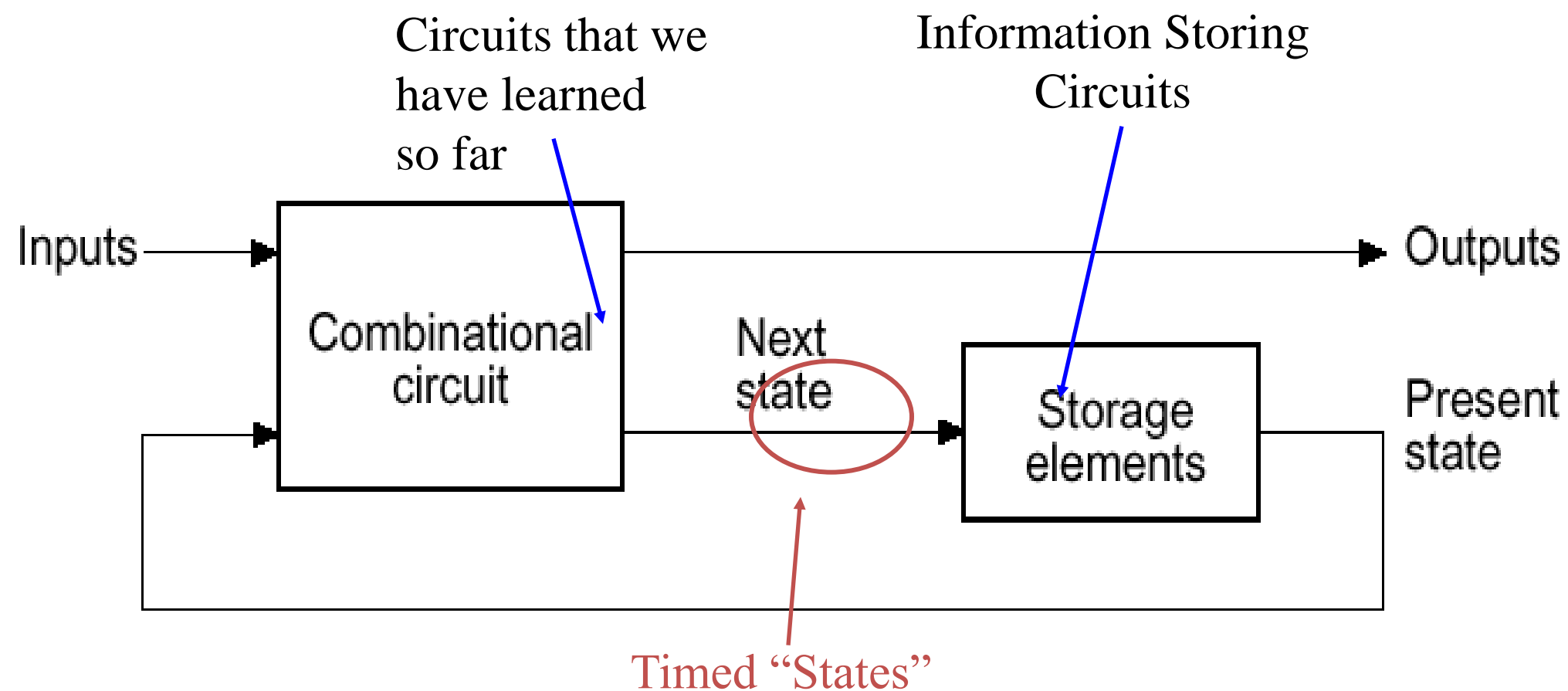- Sequential Logic:
 - Output depends not only on current input but also on past input values, e.g., design a counter
 - Need some type of memory to remember the past input values






Sequential Circuits



- Sequential Logic circuits remember past inputs and past circuit state.
- Outputs from the system are “fed back” as new inputs
 - With gate delay and wire delay
- The storage elements are circuits that are capable of storing binary information: memory.

There are two types of sequential circuits:

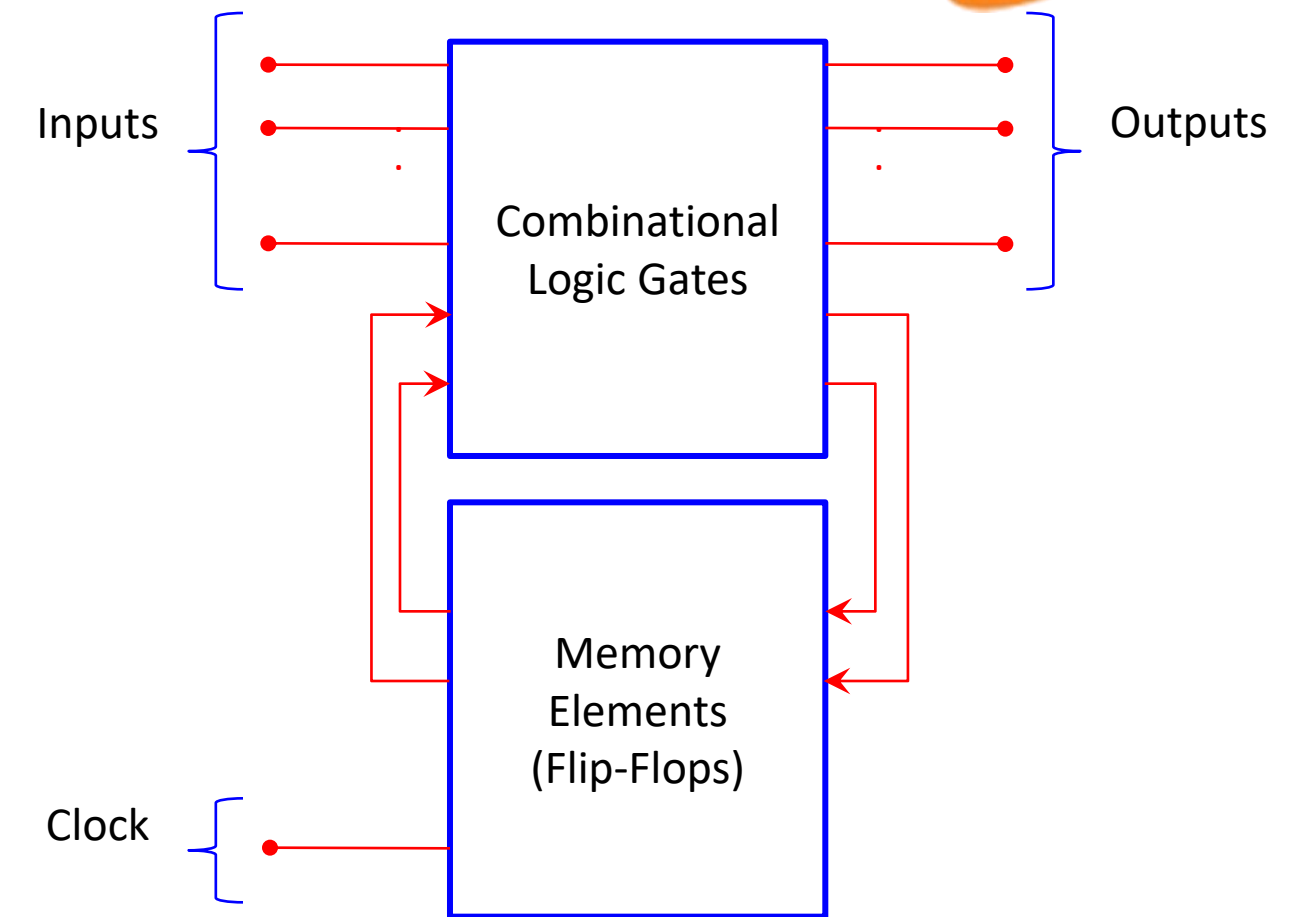- **Synchronous sequential circuit:** circuit output changes only at some discrete instants of time. This type of circuits achieves synchronization by using a timing signal called the clock.
- **Asynchronous sequential circuit:** circuit output can change at any time (clockless).





Flip Flops



- In electronics a flip-flop or latch is a circuit that has two stable states and can be used to store state information –a bistable multivibrator.
- The circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs.
- Flip-flops and latches are fundamental building blocks of digital electronics systems used in computers, communications, and many other types of systems.
- Flip-flops and latches are used as data storage elements.
- A flip-flop is a device which stores a single bit(binary digit) of data; one of its two states represents a "one" and the other represents a “zero”.



Flip Flops




- Flip flop is a sequential circuit
- It samples its inputs and changes its outputs only at particular instants of time and not continuously.
- Flip flop is said to be edge sensitive or edge triggered rather than being level triggered like latches

TYPES


- SR Flip-Flop
- D Flip-Flop
- JK Flip-Flop
- T Flip-Flop



SR Flip Flop

 

Symbol

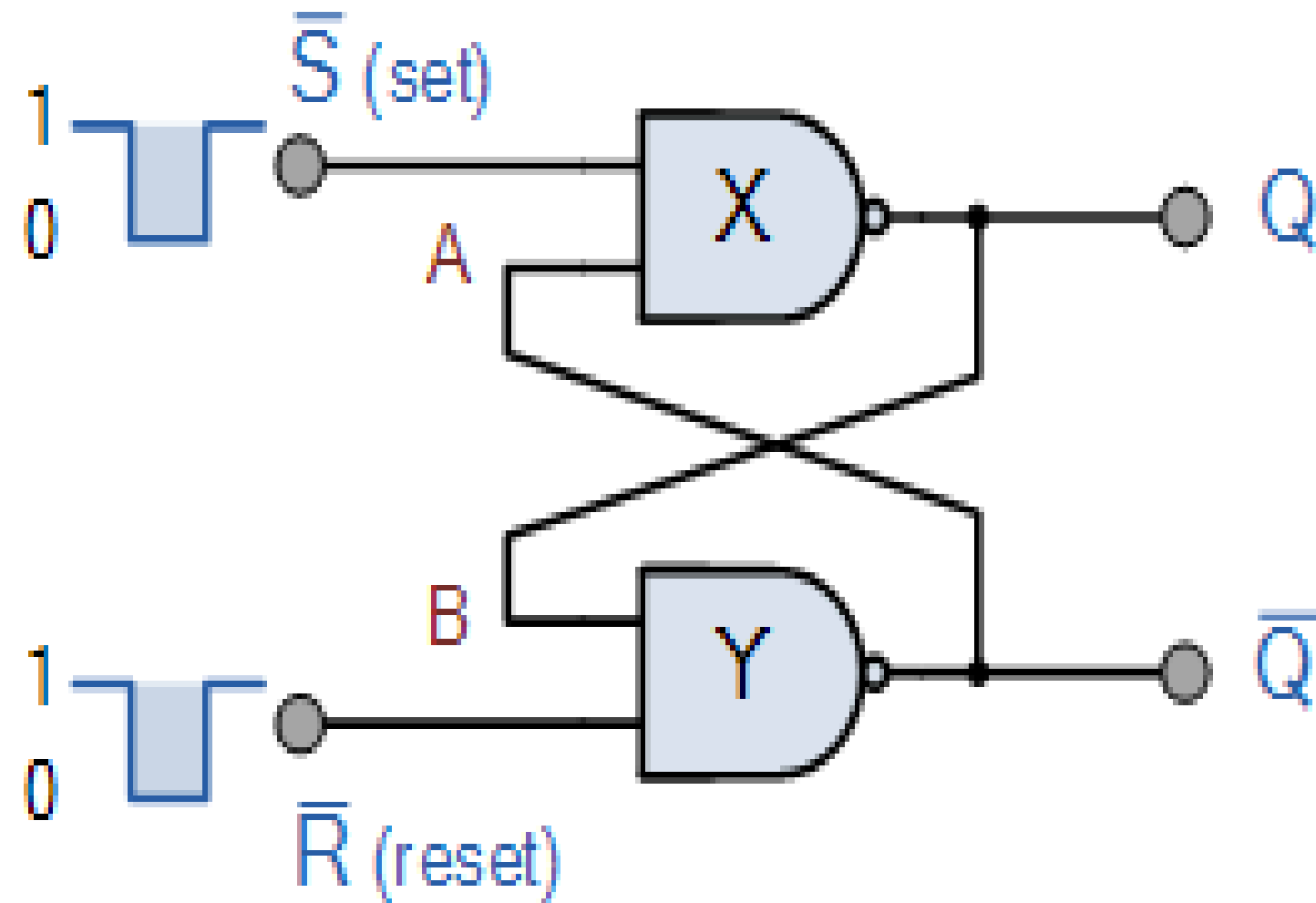

Circuit



SR Flip Flop



The Set State

- If the input R is at logic level “0” ($R = 0$) & S is at logic level “1” ($S = 1$)
Its output \overline{Q} must be at a logic level “1”.
- Output \overline{Q} is also fed back to input “A”
 - Both inputs to NAND gate X are at logic level “1”
 - Its output Q must be at logic level “0”.

- If the reset input R changes state, and goes HIGH to logic “1” with S remaining HIGH also at logic level “1”
 - NAND gate Y inputs are now $R = “1”$ and $B = “0”$.
 - Since one of its inputs is still at logic level “0” the output at \overline{Q} still remains HIGH at logic level “1” and there is no change of state.
 - Therefore, the flip-flop circuit is said to be “Latched” or “Set” with $\overline{Q} = “1”$ and $Q = “0”$.



SR Flip Flop



Reset State

- \overline{Q} is at logic level “0”, its inverse output at Q is at logic level “1”
Given by $R = “1”$ and $S = “0”$.
- As gate X has one of its inputs at logic “0” its output Q must equal logic level “1”
Output Q is fed back to input “B”, so both inputs to NAND gate Y are at logic “1”, therefore, $\overline{Q} = “0”$.
- If the set input, S now changes state to logic “1” with input R remaining at logic “1”
 - output \overline{Q} still remains LOW at logic level “0” and there is no change of state.
- Therefore, the flip-flop circuits “Reset” state has also been latched



SR Flip Flop Truth Table

S-R flip flop behavior

Present state

The state of Q output at the time the input signals are applied.

Next state

The state of Q output after the flipflop has reacted to the input signals.

State	S	R	Q	\overline{Q}	Description
Set	1	0	0	1	Set $\overline{Q} \gg 1$
	1	1	0	1	no change
Reset	0	1	1	0	Reset $\overline{Q} \gg 0$
	1	1	1	0	no change
Invalid	0	0	1	1	Invalid Condition




SR Flip Flop Truth Table

- When both inputs $S = "1"$ and $R = "1"$ the outputs Q and \bar{Q} can be at either logic level "1" or "0", depending upon the state of the inputs S or R BEFORE this input condition existed.
- Therefore the condition of $S = R = "1"$ does not change the state of the outputs Q and \bar{Q} .
- The input state of $S = "0"$ and $R = "0"$ is an undesirable or invalid condition
- The condition of $S = R = "0"$ causes both outputs Q and \bar{Q} to be HIGH together at logic level "1"
- The result is that the flip-flop loses control of Q and \bar{Q}
- The flip-flop becomes unstable and switches to an unknown data state based upon the unbalance



SR Flip Flop Characteristic Equation

 

$$Q(t+1) = S + R'Q(t)$$



SR Flip Flop Switching Diagram

