



SNS COLLEGE OF TECHNOLOGY

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

COURSE NAME : 19ECB201-ANALOG ELECTRONIC CIRCUITS

II YEAR /III SEMESTER

Unit 4- OSCILLATORS & MULTIVIBRATOR CIRCUITS

**Topic 1 : Mechanism for start of oscillation and stabilization of
amplitude**







Classification of oscillators




According to the waveform generated

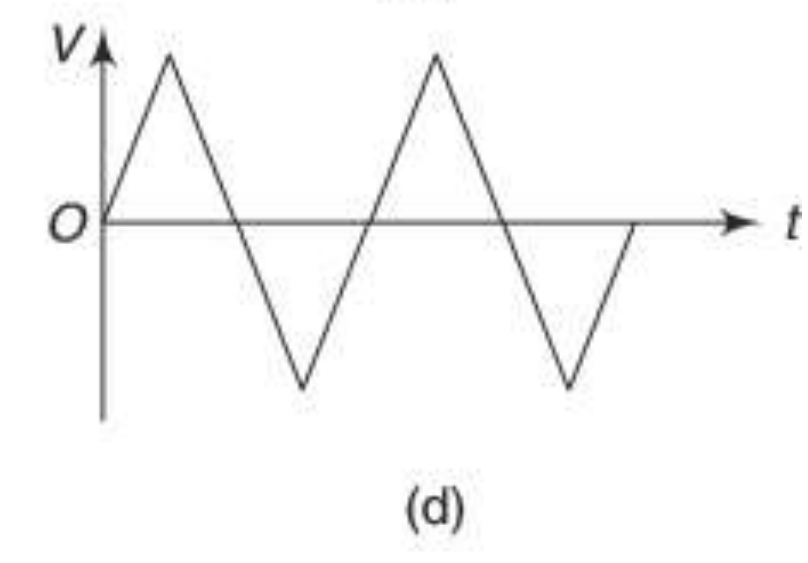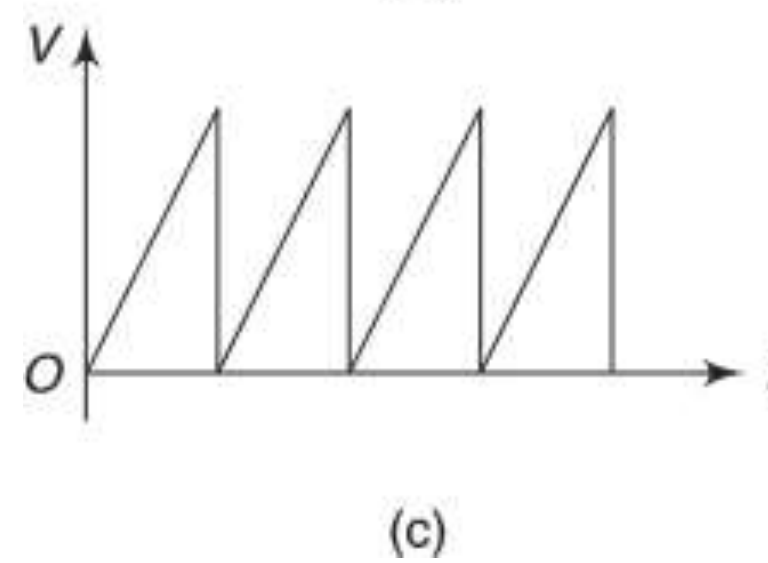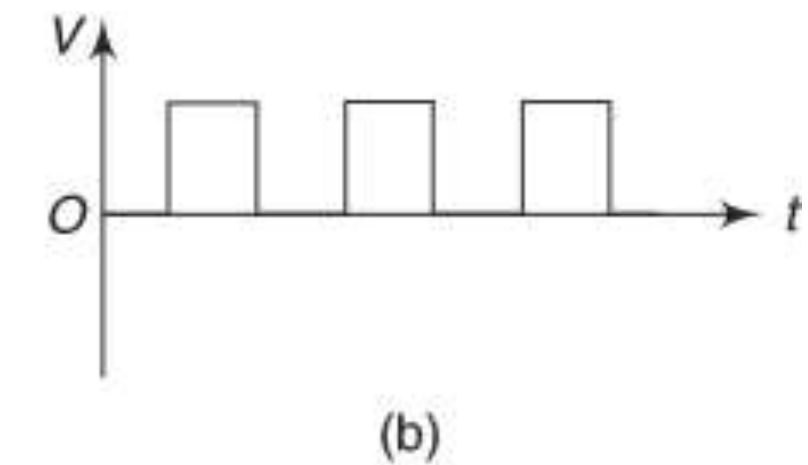
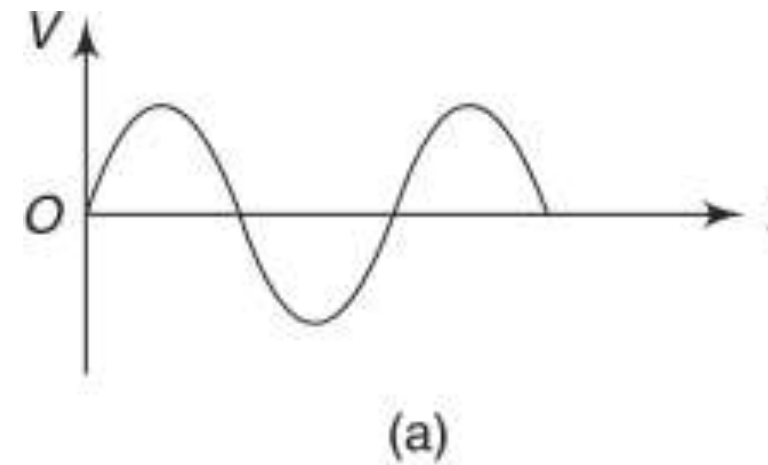
- Harmonic oscillator
- Relaxation oscillator






Classification of oscillator

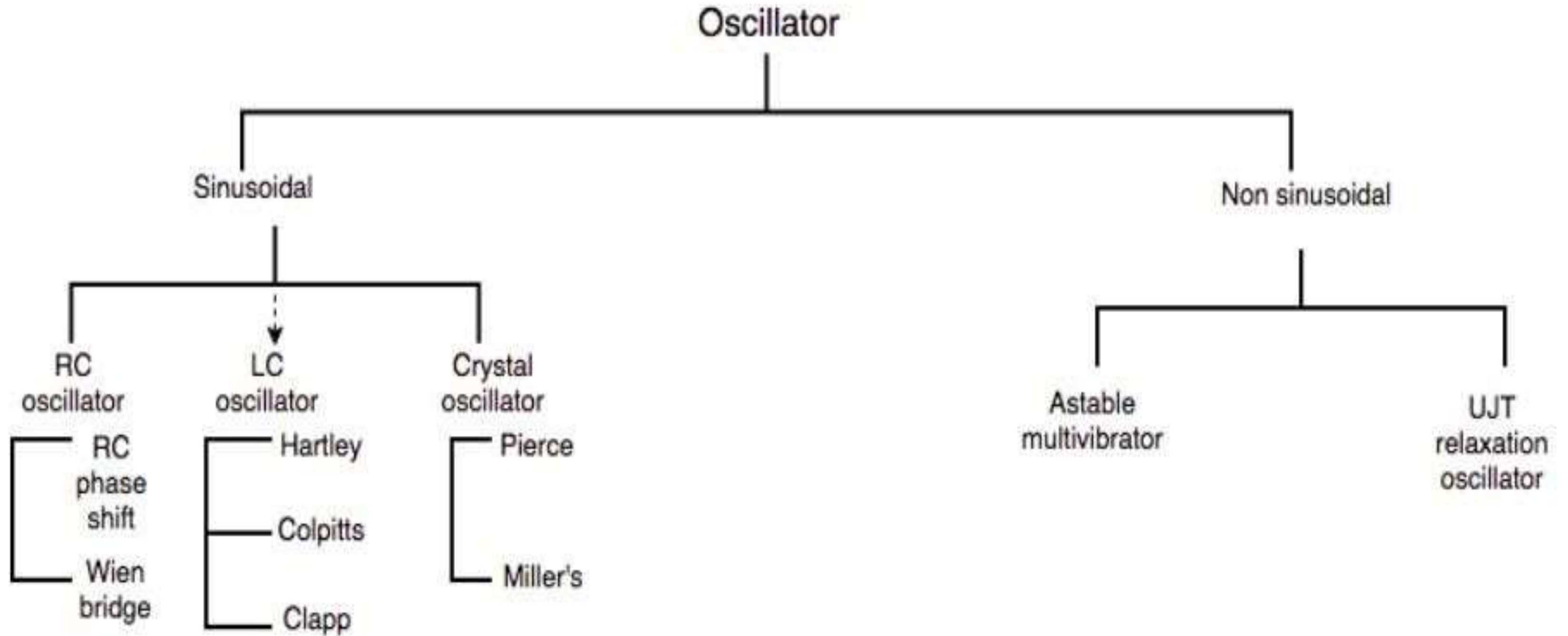


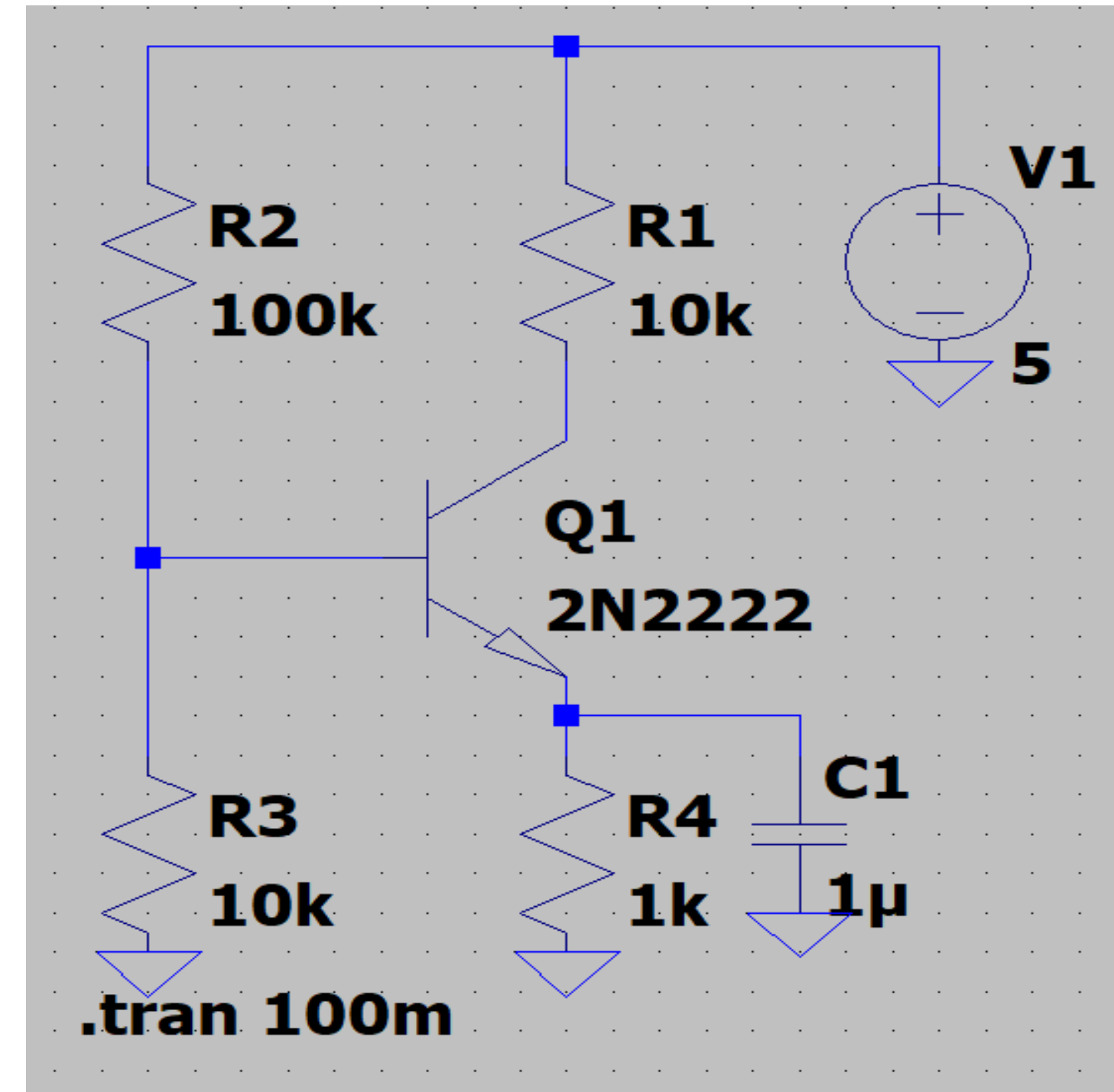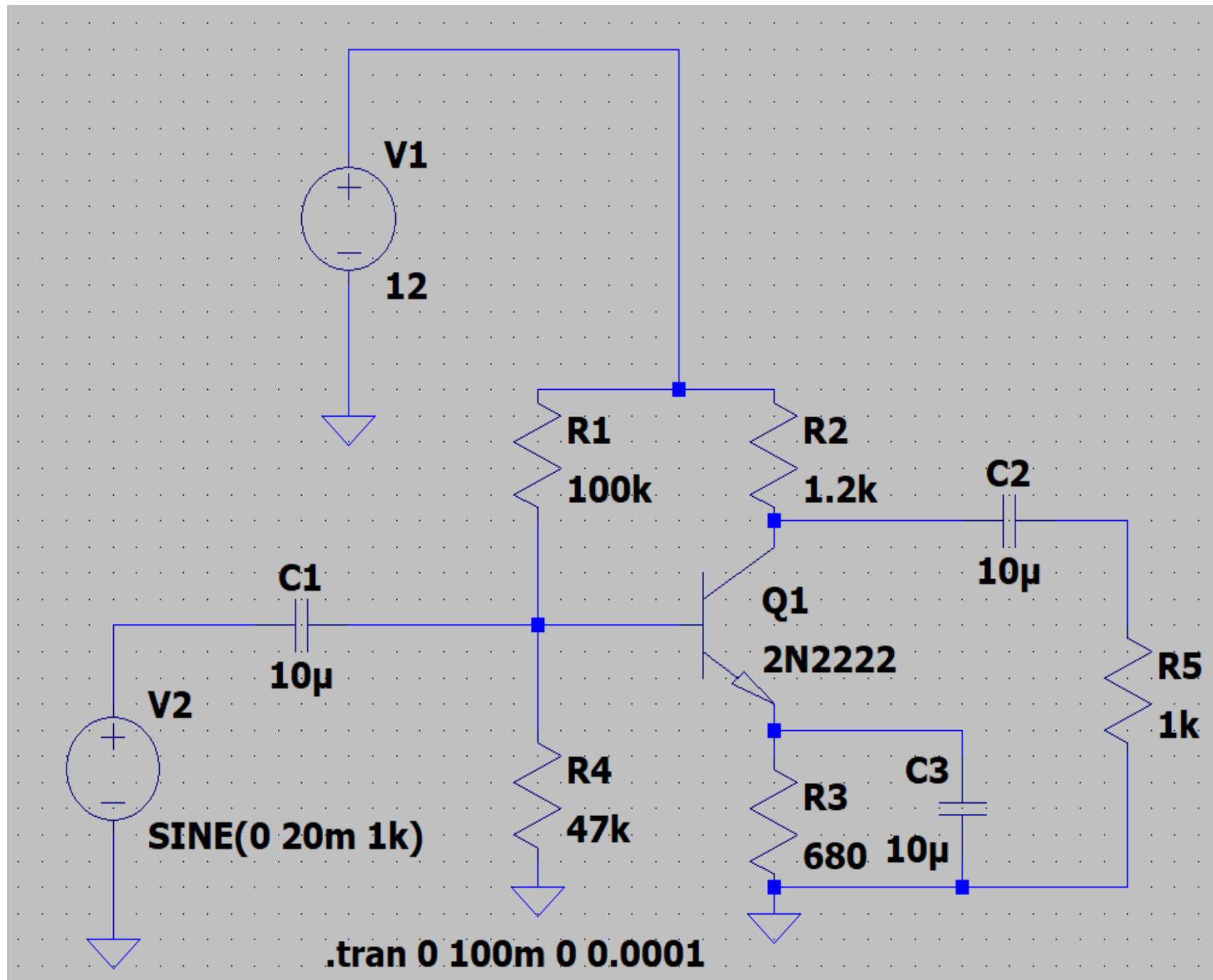

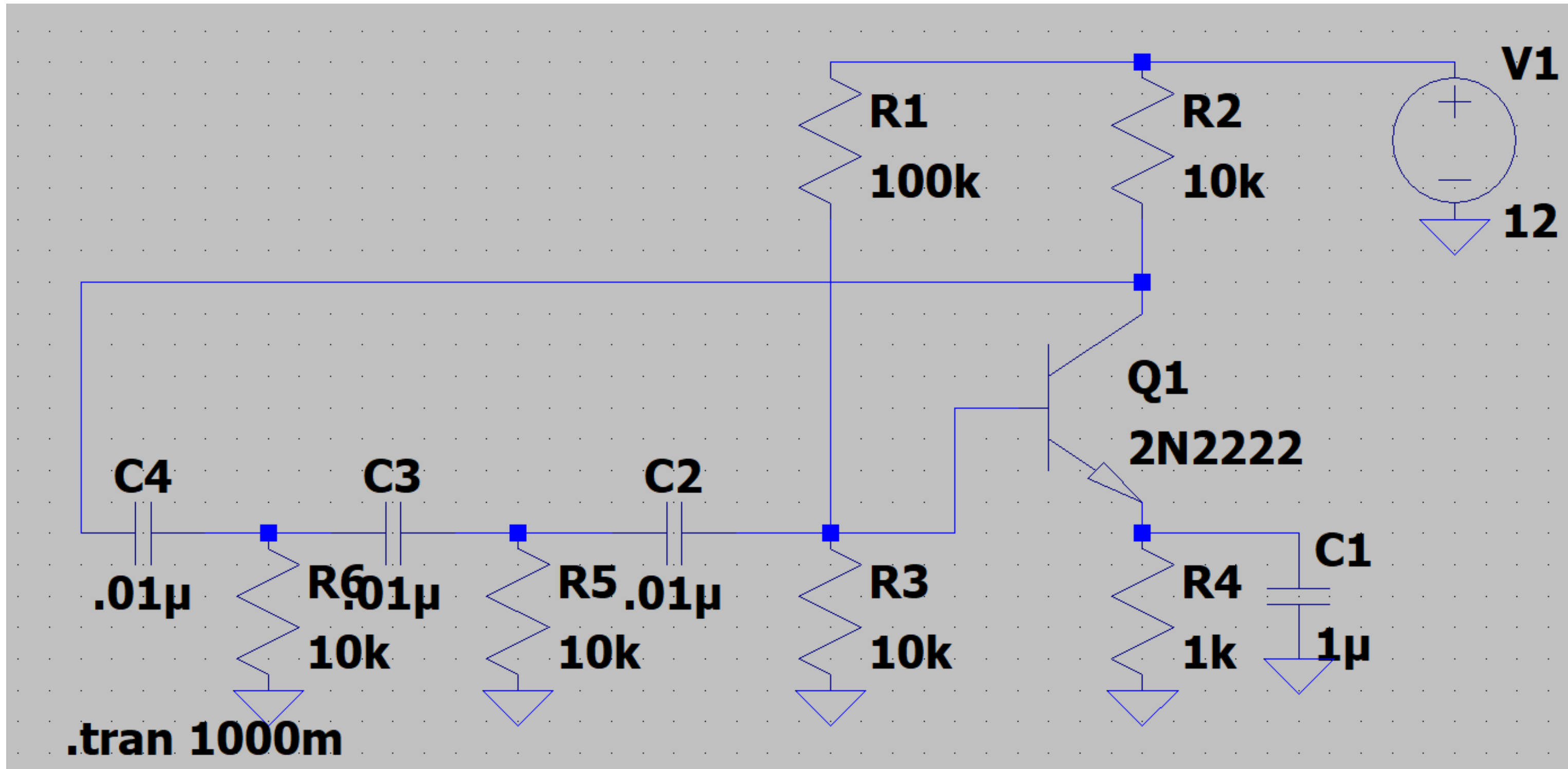



Block diagram of sinusoidal oscillator

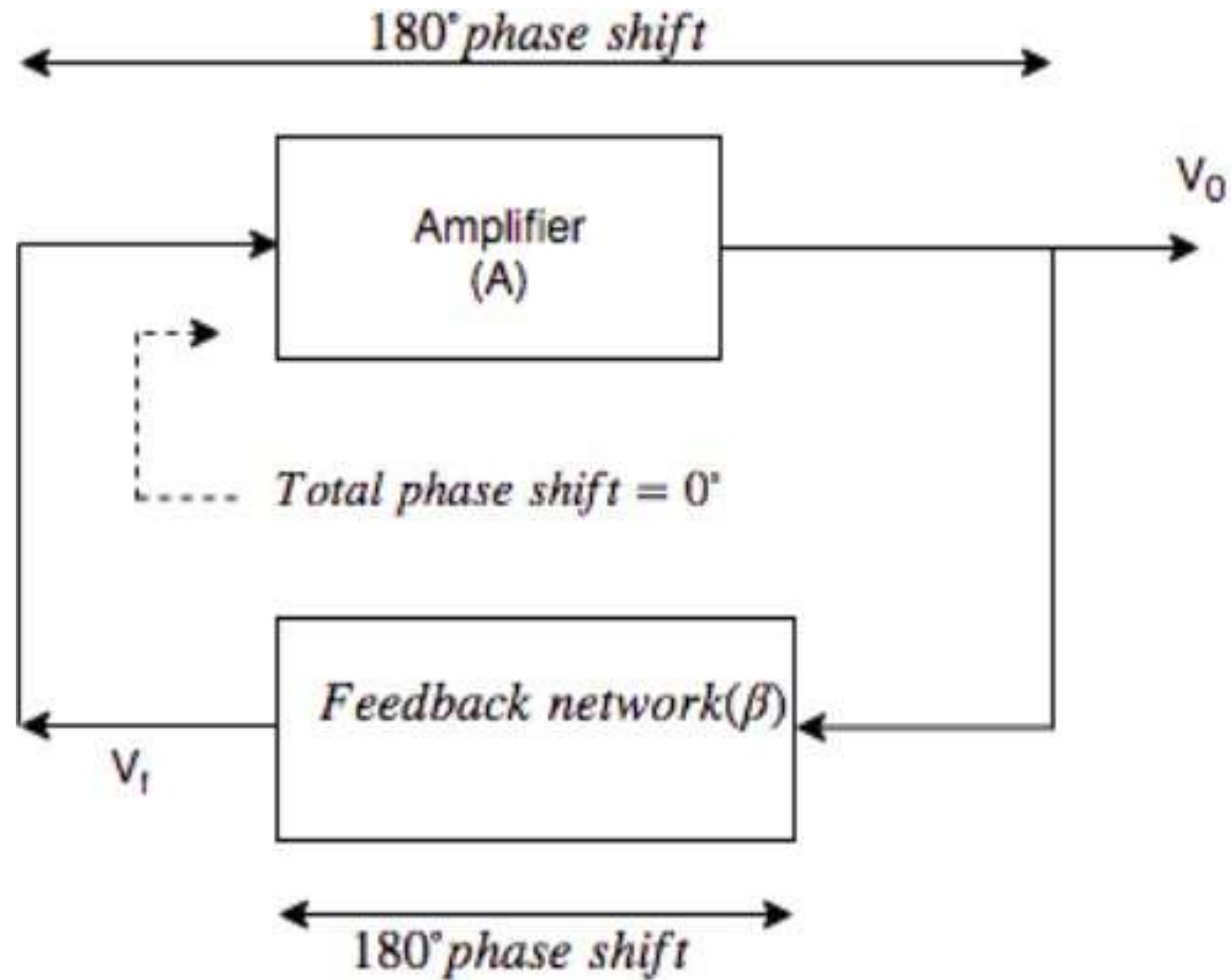



Classification of oscillators



According to frequency generated


- Audio Frequency Oscillator: Upto 20kHz
- Radio Frequency Oscillator: 20 kHz to 30 MHz
- Very High Frequency Oscillator: 30 MHz to 300 MHz
- Ultra High Frequency Oscillator: 300 MHz to 3 GHz
- Microwave Frequency Oscillator: Above 3 GHz



Mechanism for Start of Oscillations



IDEATE

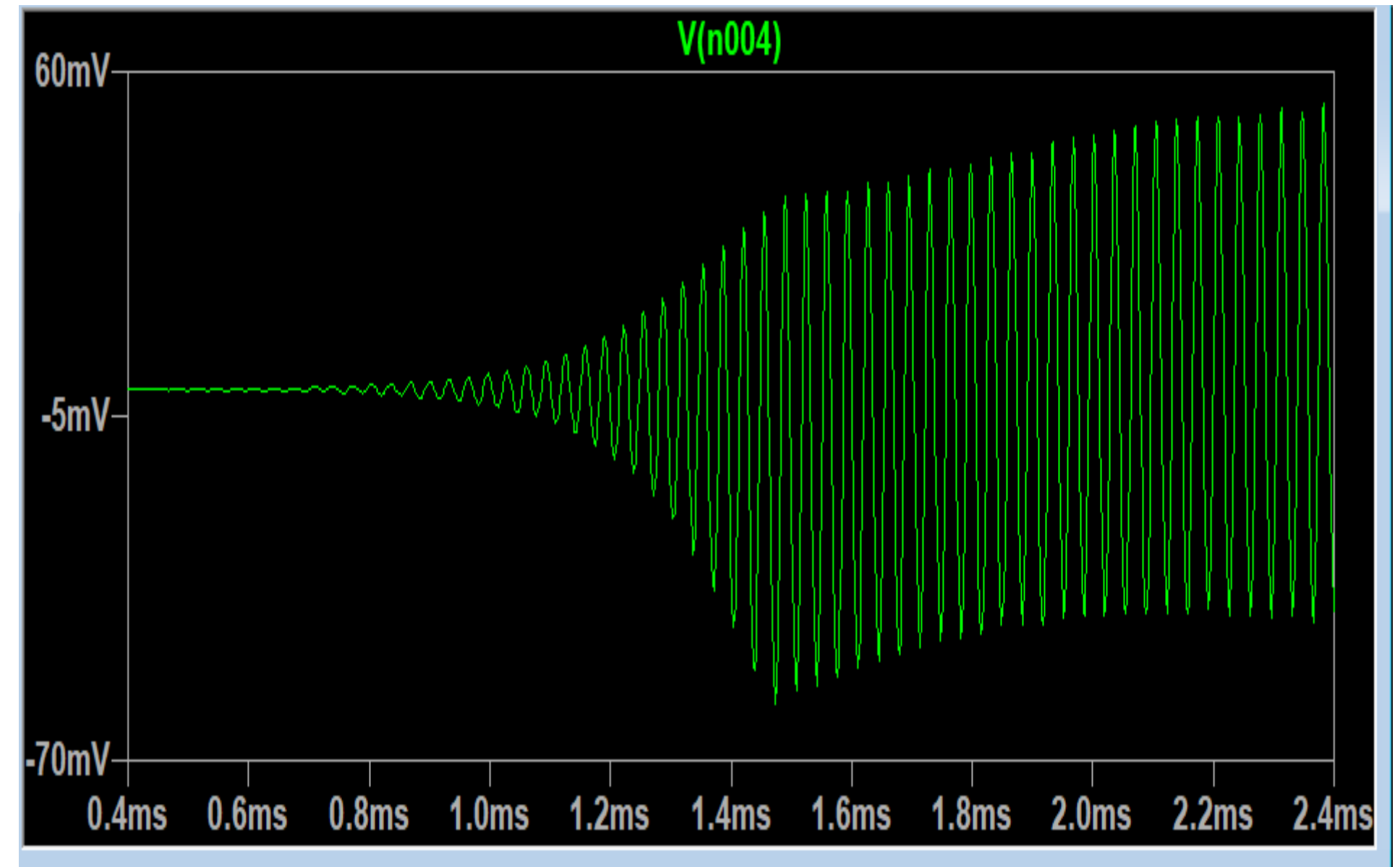




Barkhausen Criterion



The essential conditions for maintaining oscillations are:

1. $|A\beta| = 1$, i.e. the magnitude of loop gain must be unity.
2. The total phase shift around the closed loop is zero or 360 degrees.

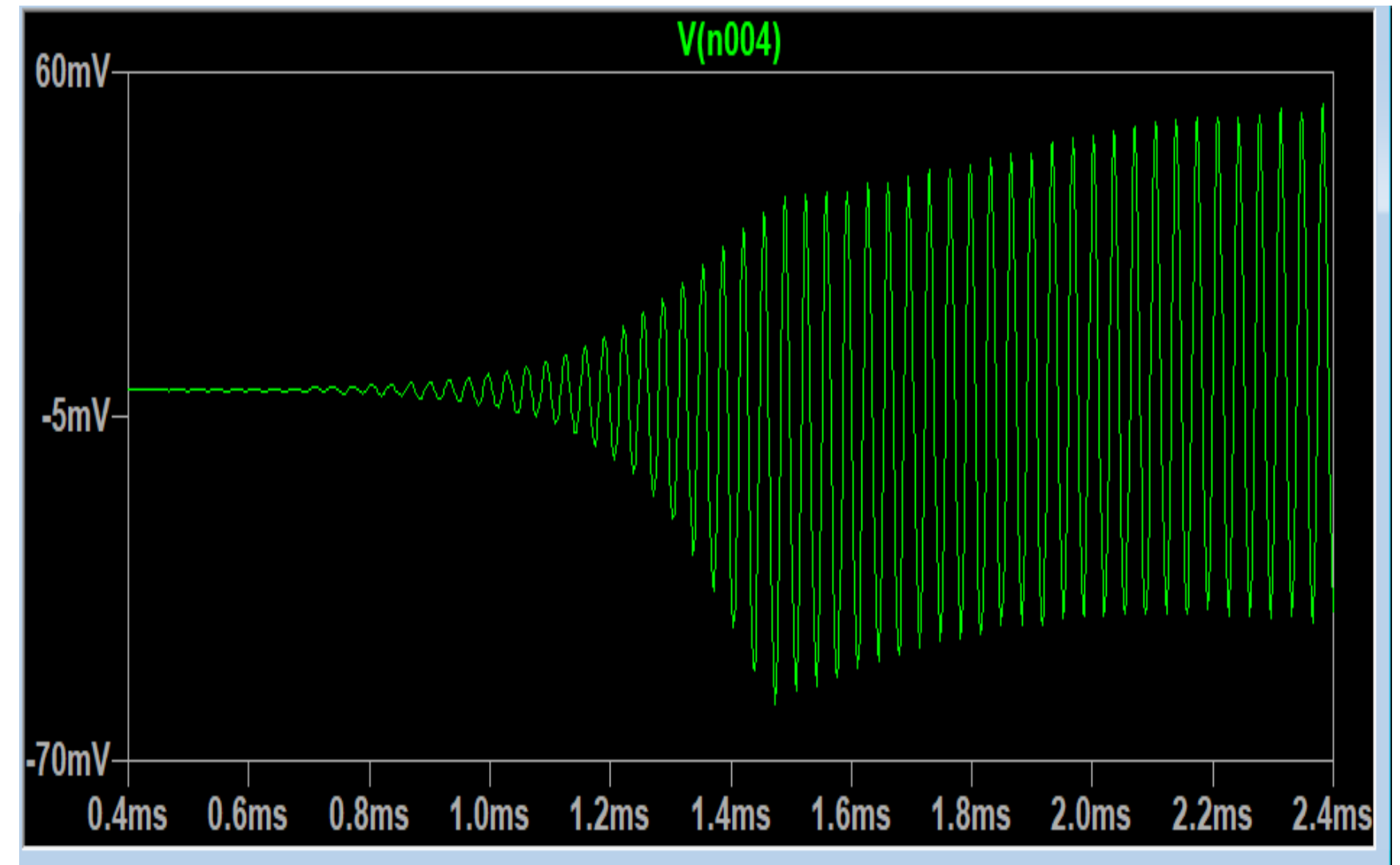



Amplitude Stability of Oscillators

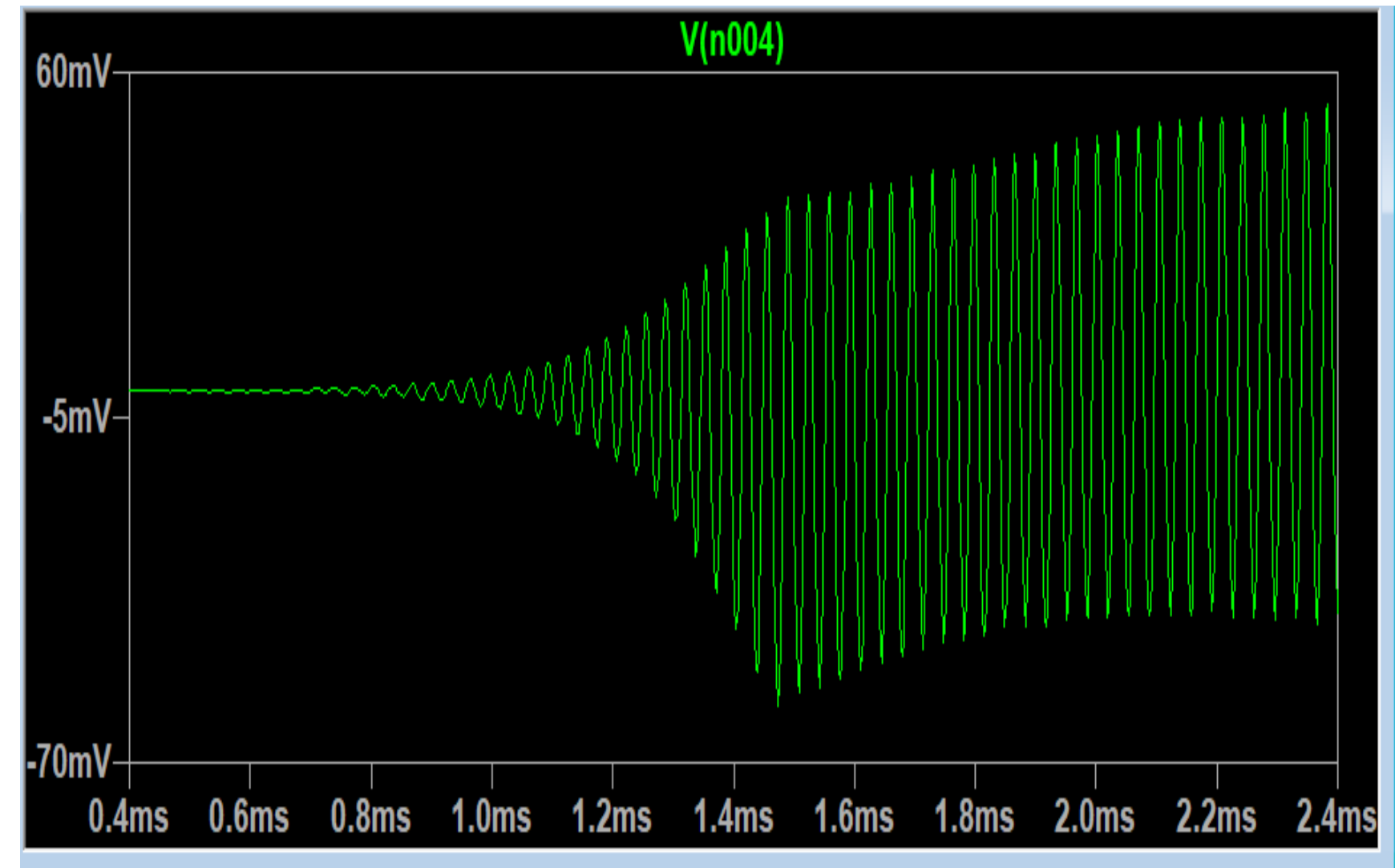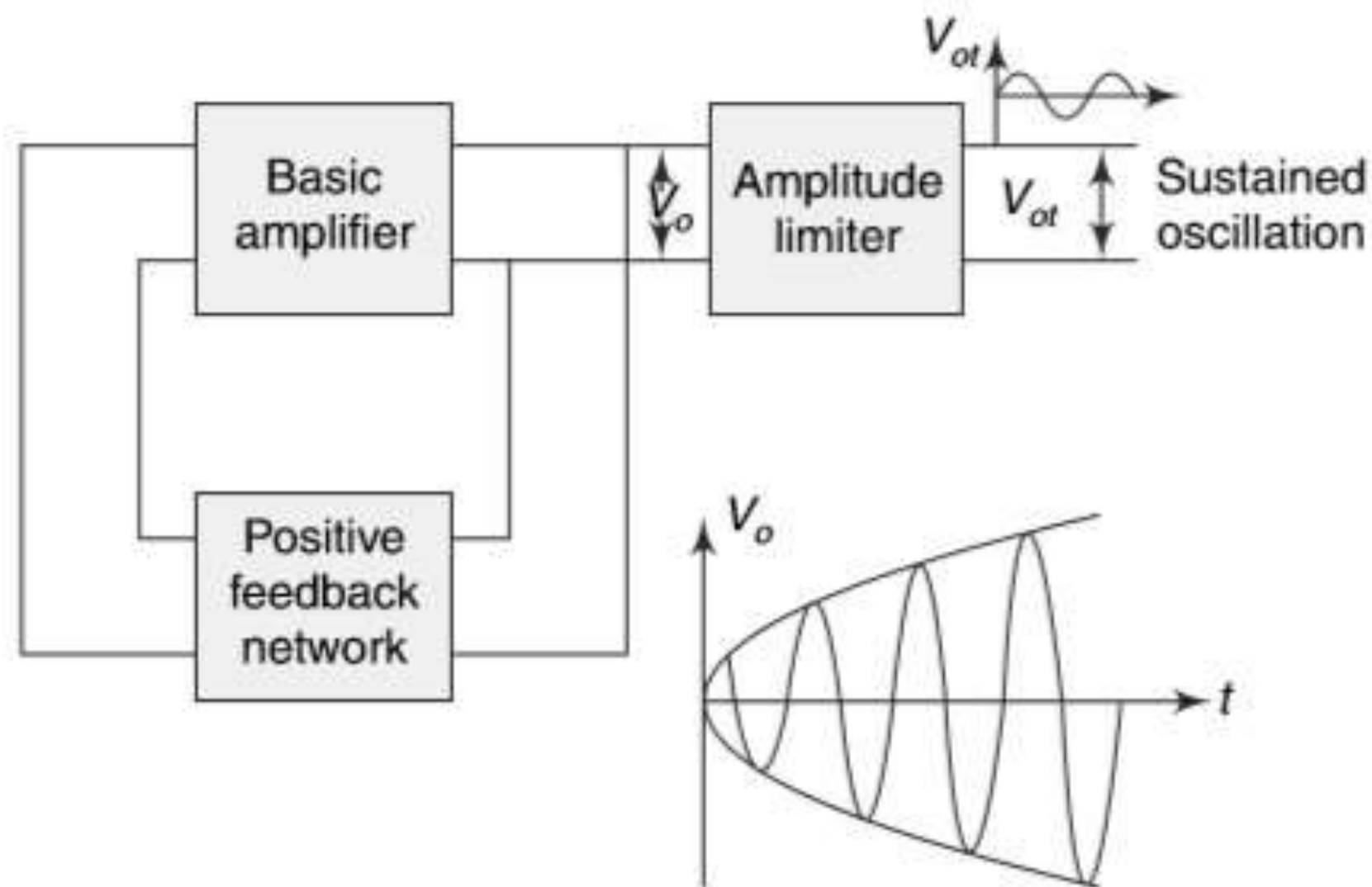




General Form of an Oscillator





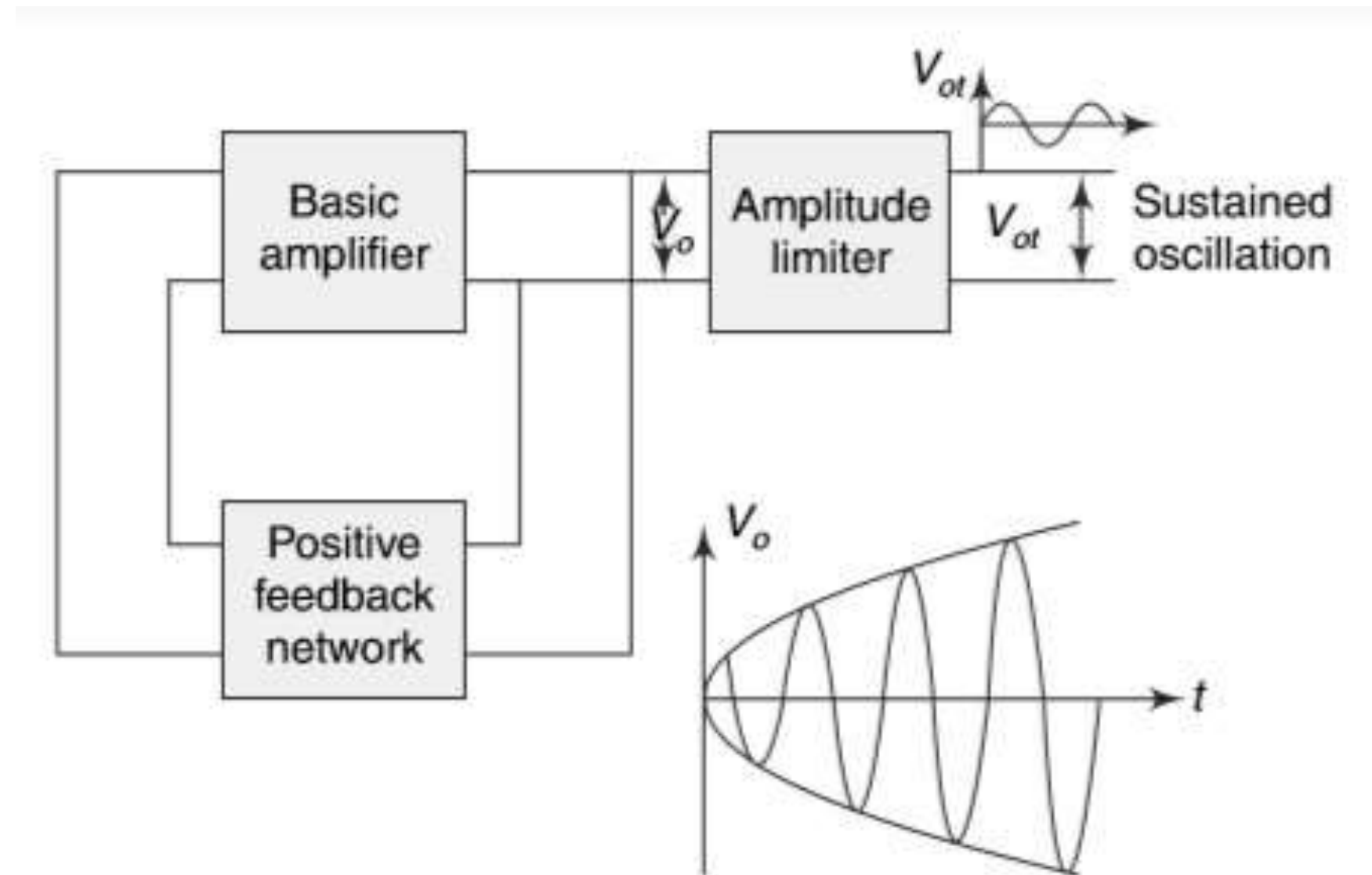- ❖ Basic Amplifier
- ❖ Amplitude Limiter
- ❖ Positive feedback network





Why Positive Feedback in Oscillators?

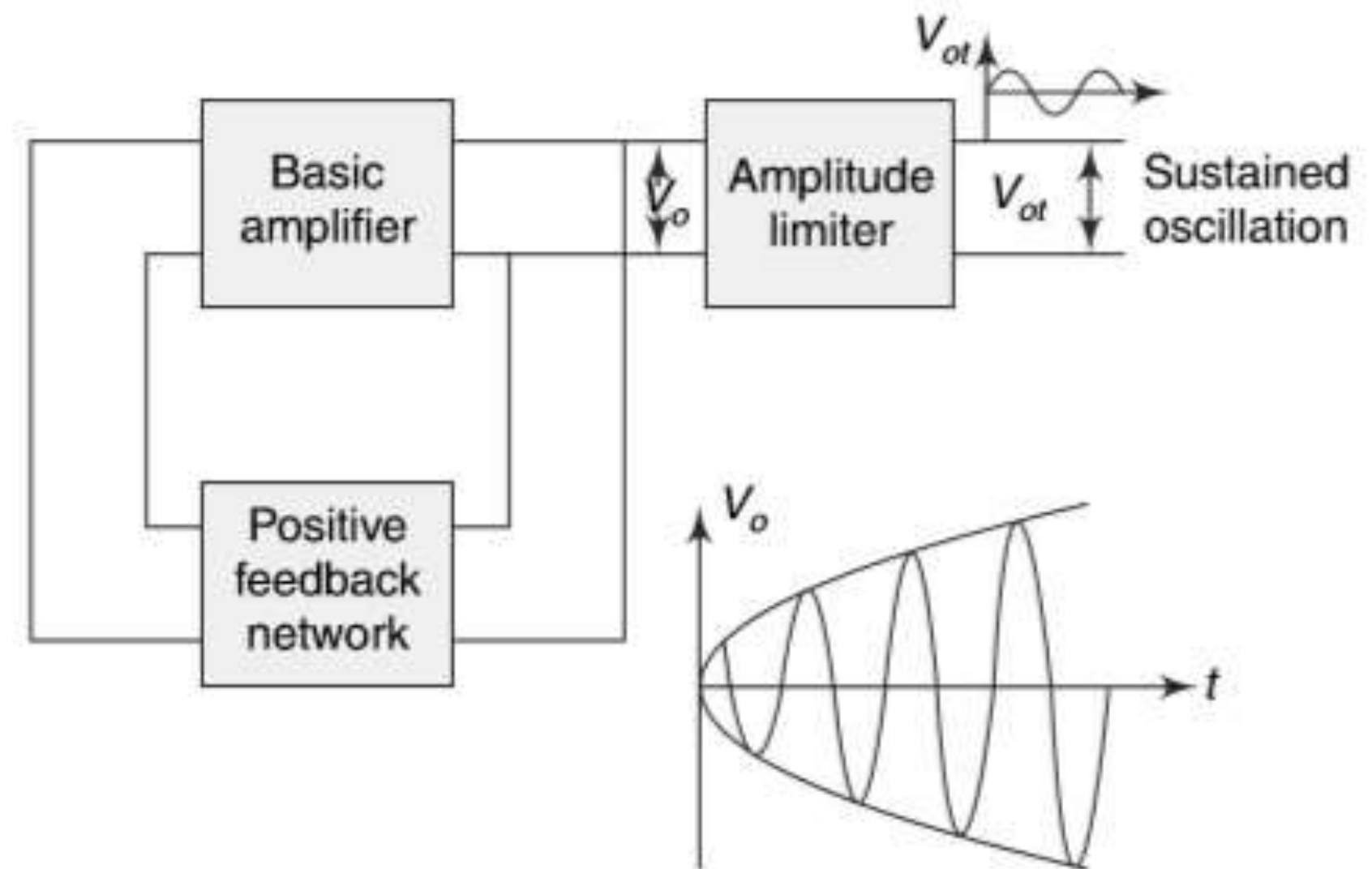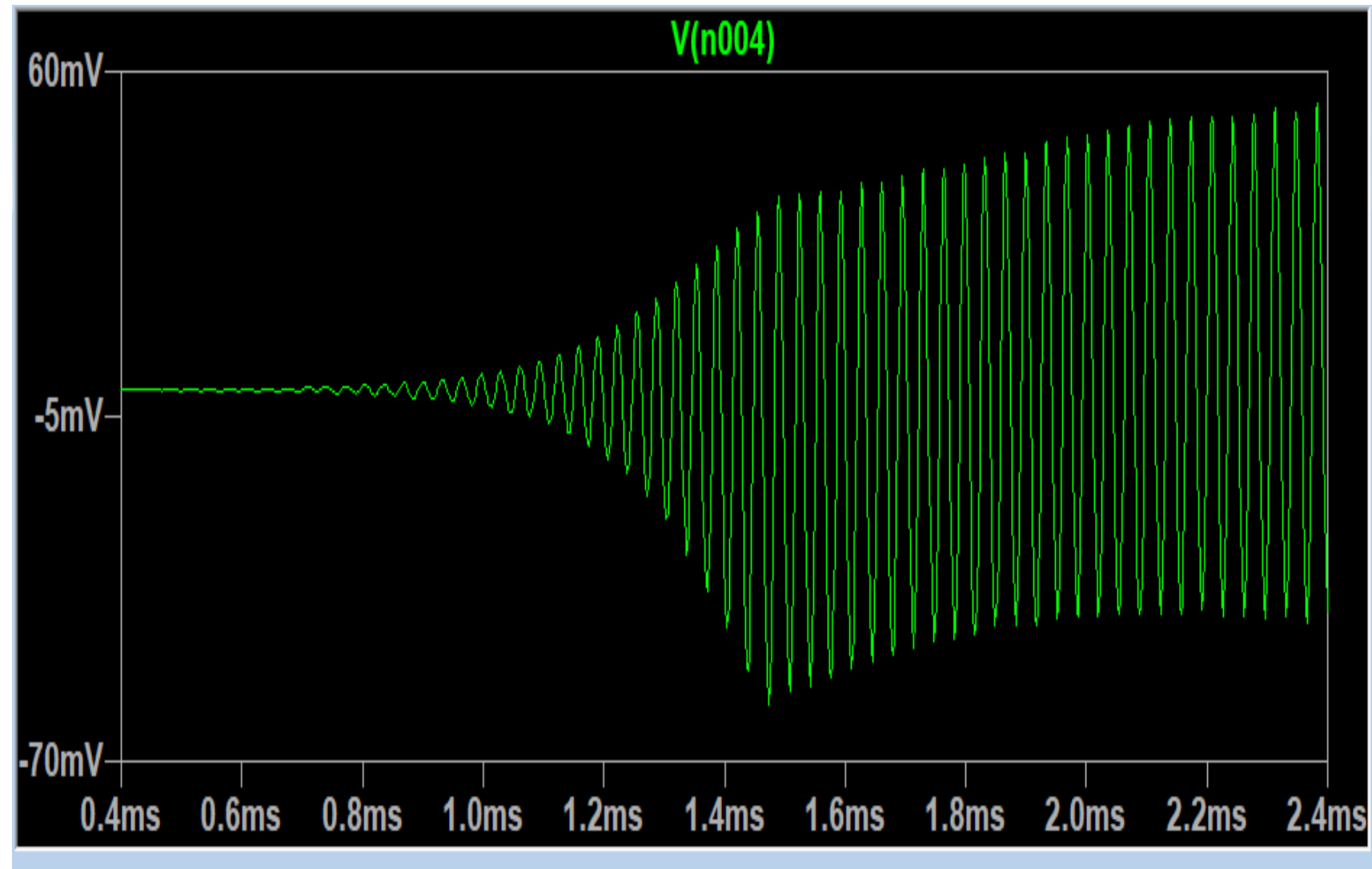




Equivalent Circuit



Load Impedance

$$\frac{1}{Z'} = \frac{1}{Z_1} + \frac{1}{h_{ie}}$$

$$Z' = \frac{Z_1 h_{ie}}{Z_1 + h_{ie}}$$

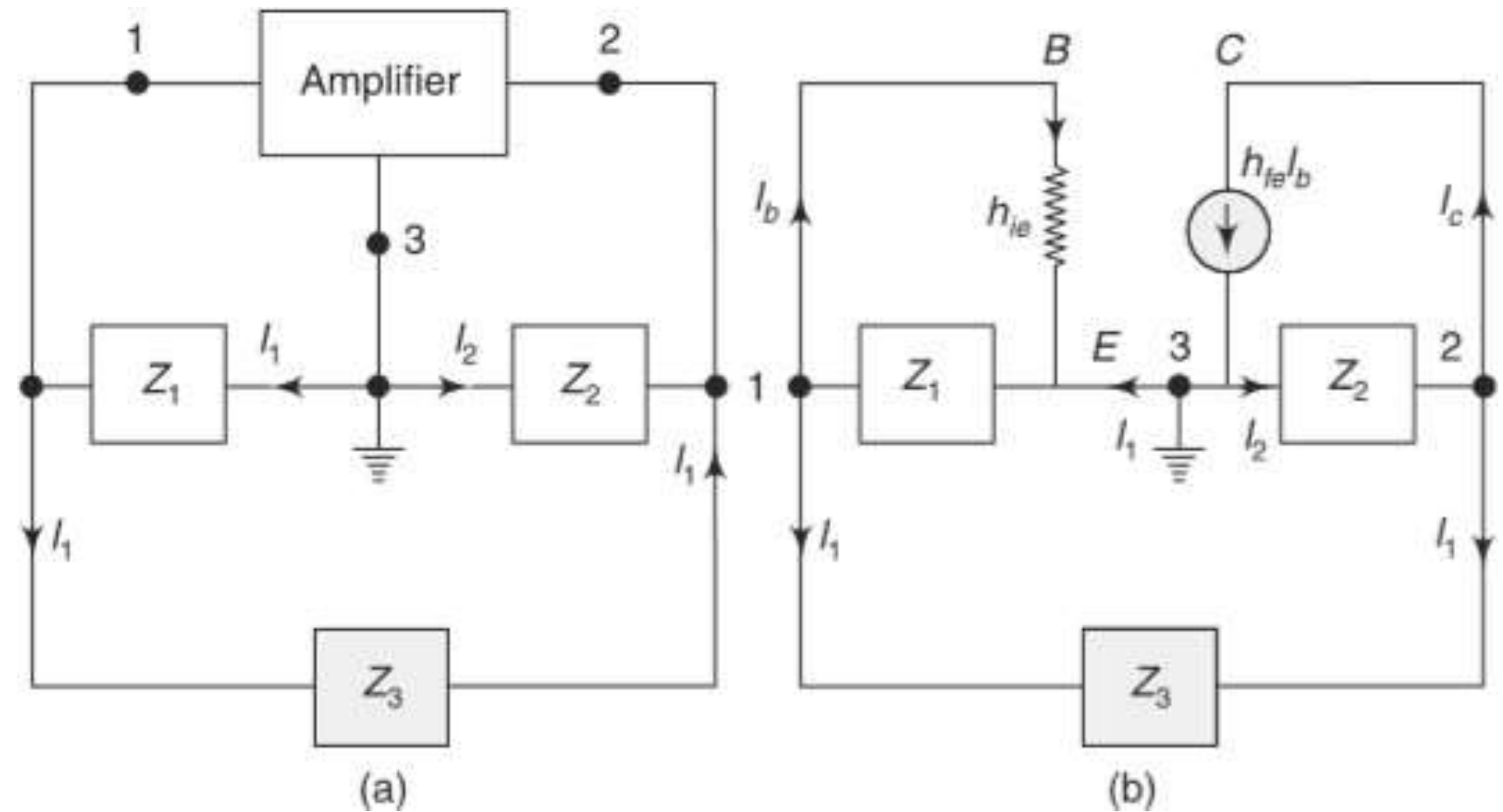




Calculation of Load Impedance



$$\frac{1}{Z_L} = \frac{1}{Z_2} + \frac{1}{Z' + Z_3}$$

Derive
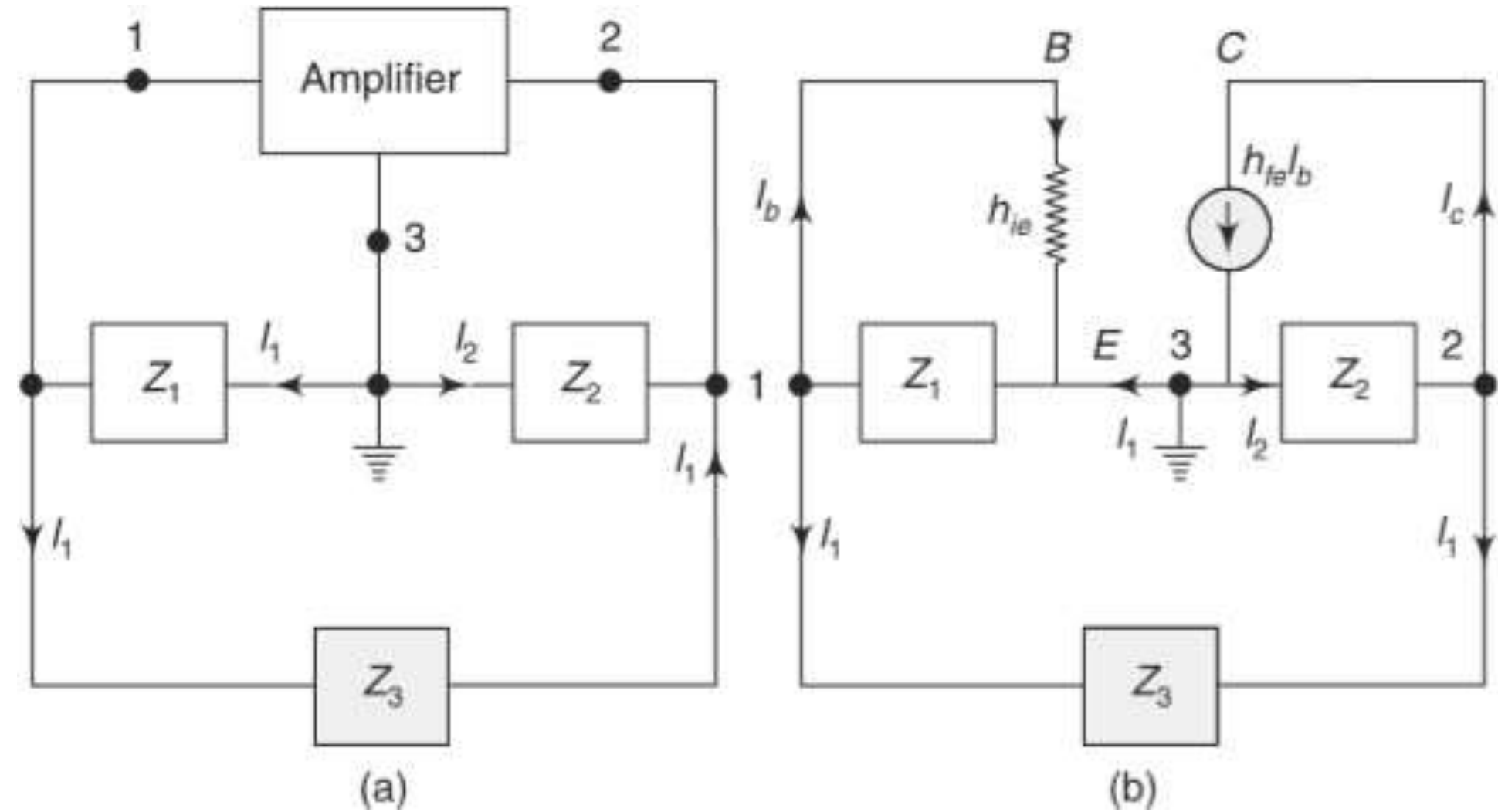
$$Z_L = \frac{Z_2[h_{ie}(Z_1 + Z_3) + Z_1 Z_3]}{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3}$$






Load Impedance


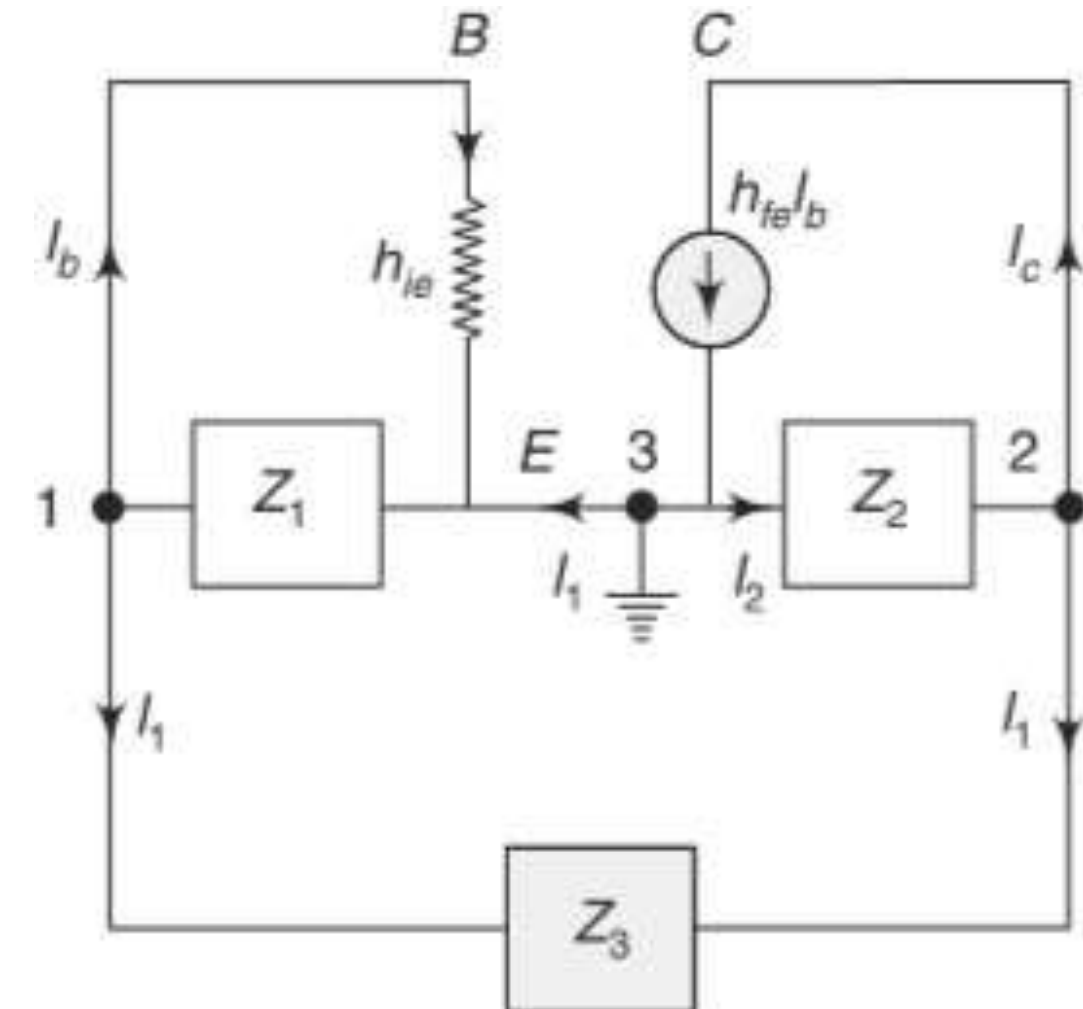
$$\begin{aligned} &= \frac{1}{Z_2} + \frac{1}{\frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3} \\ &= \frac{1}{Z_2} + \frac{Z_1 + h_{ie}}{Z_1 h_{ie} + Z_1 Z_3 + h_{ie} Z_3} \\ &= \frac{1}{Z_2} + \frac{Z_1 + h_{ie}}{h_{ie} (Z_1 + Z_3) + Z_1 Z_3} \end{aligned}$$






Load Impedance


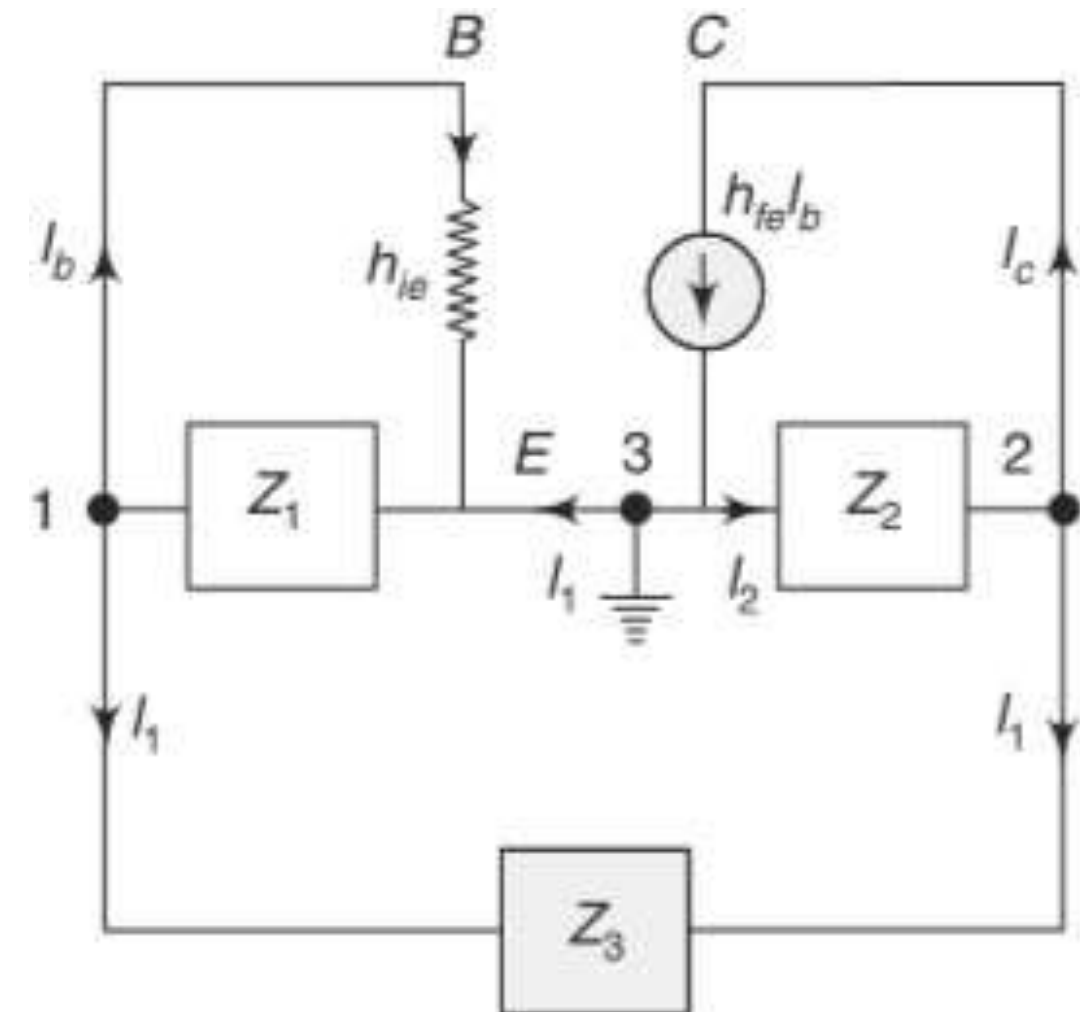
$$\begin{aligned} &= \frac{h_{ie}(Z_1 + Z_3) + Z_1 Z_3 + Z_2(Z_1 + h_{ie})}{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]} \\ &= \frac{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3}{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]} \\ Z_L &= \frac{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]}{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3} \end{aligned}$$






Voltage Gain Without Feedback



$$A_{ve} = -\frac{h_{fe} Z_L}{h_{ie}}$$
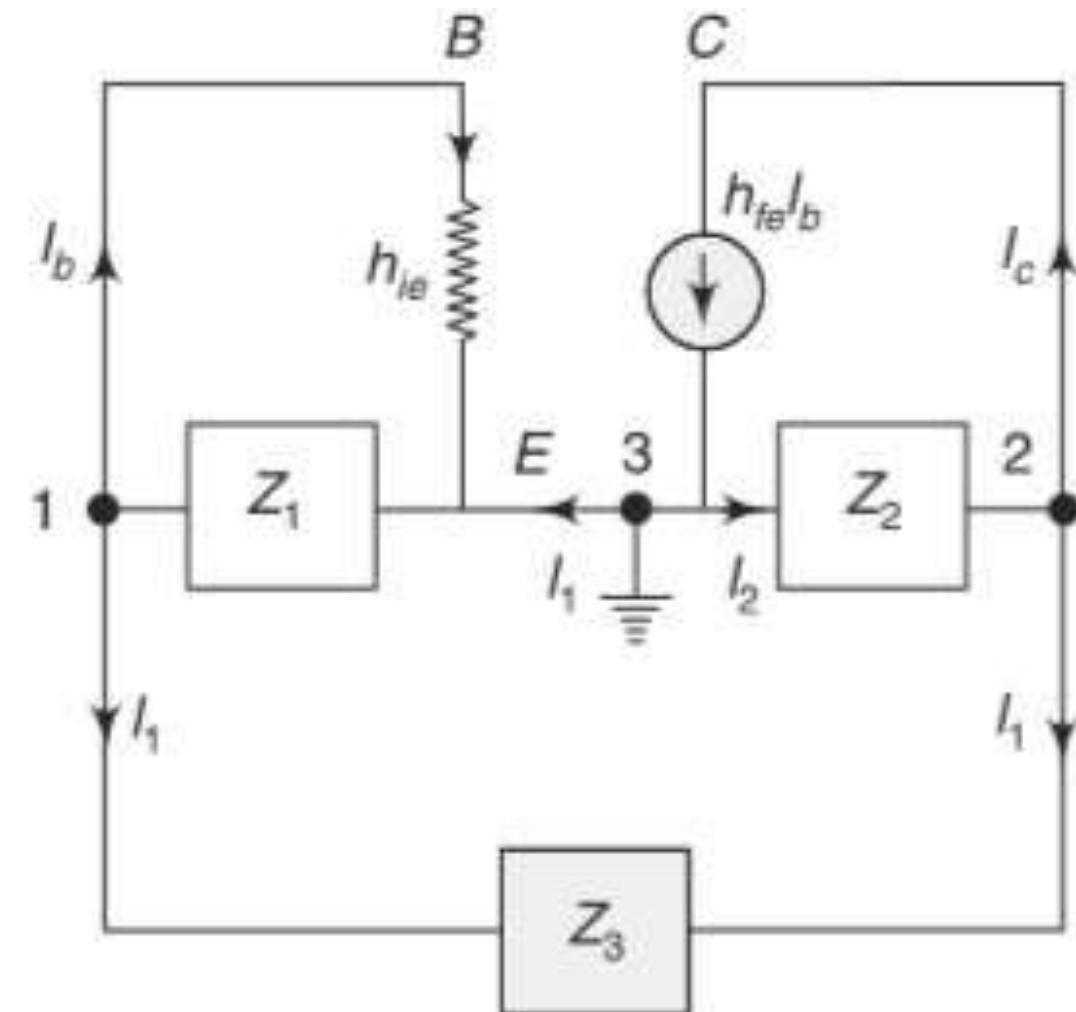
$$V_0 = -I_1 (Z' + Z_3) = -I_1 \left(\frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3 \right)$$
$$= -I_1 \left(\frac{h_{ie} (Z_1 + Z_3) + Z_1 Z_3}{Z_1 + h_{ie}} \right)$$






Feedback Factor



$$\beta = \frac{V_{fb}}{V_o} = I_1 \left(\frac{Z_1 h_{ie}}{Z_1 + h_{ie}} \right) \left[\frac{Z_1 + h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3} \right] \cdot \frac{1}{I_1}$$
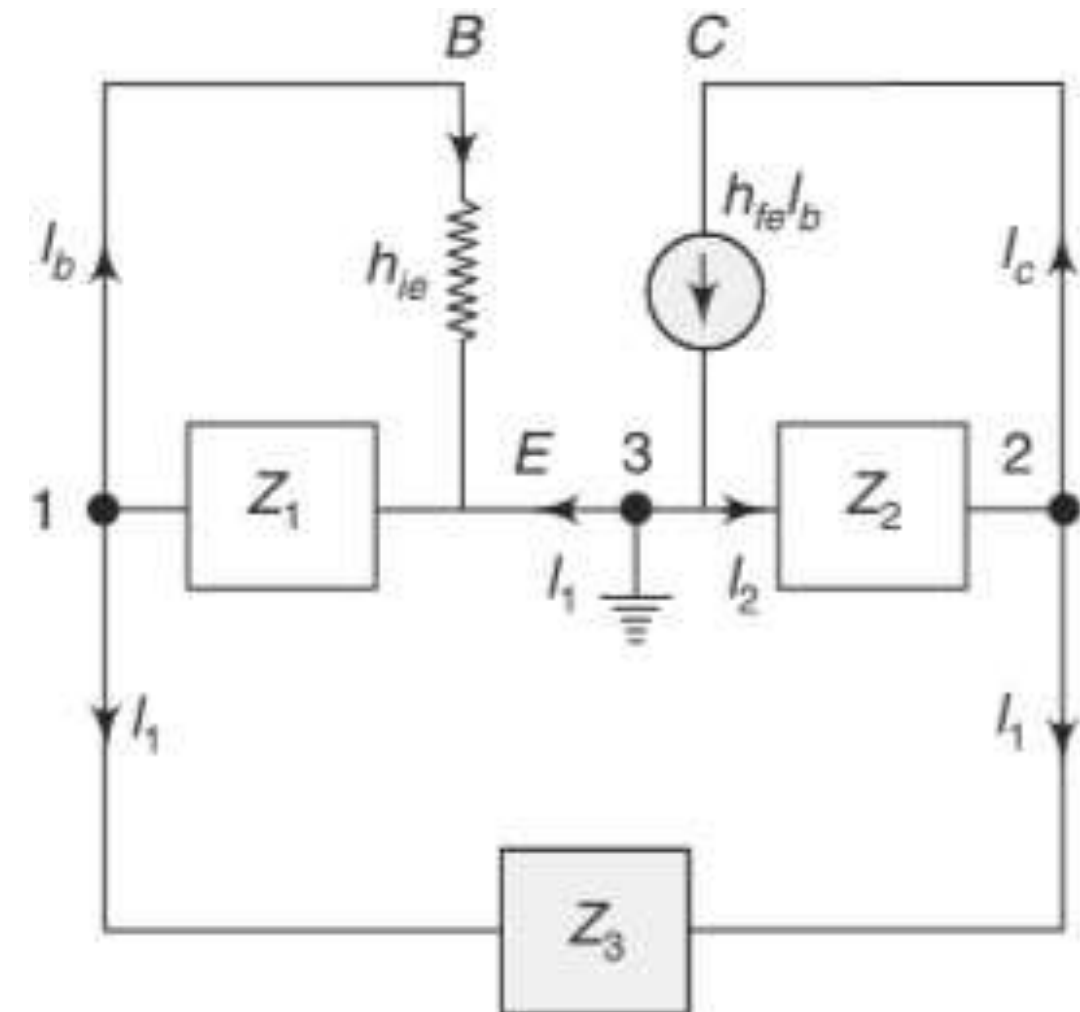
$$\beta = \frac{Z_1 h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3}$$





Assessment 1 (Answer)



Derive the Equation of oscillator

Hints

$$A_{ve} \beta = 1$$



Answer

$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0$$



References



Electronic Devices and Circuits By Salivahanan

Thank You