

### **SNS COLLEGE OF TECHNOLOGY**



Coimbatore-35
An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

### DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB204 - LINEAR AND DIGITAL CIRCUITS

II YEAR/ III SEMESTER

UNIT 4 – COMBINATIONAL and SEQUENTIAL CIRCUITS


TOPIC 1 – DEMULTIPLEXER


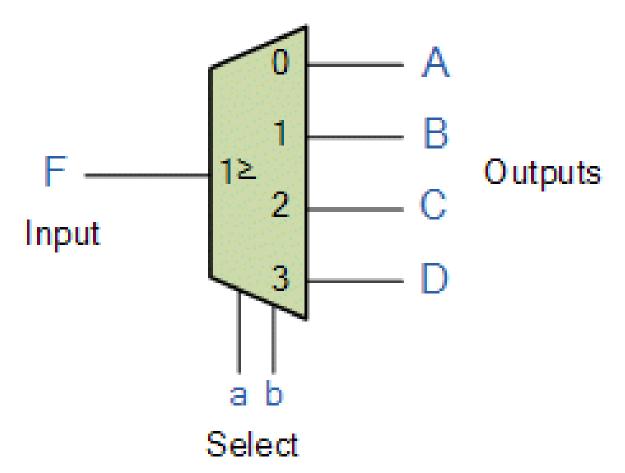
### What is De Multiplexer?




- ➤ De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of 2n outputs.
- ➤One of these data inputs will be connected to the output based on the values of selection lines..





## DeMultiplexer - Types



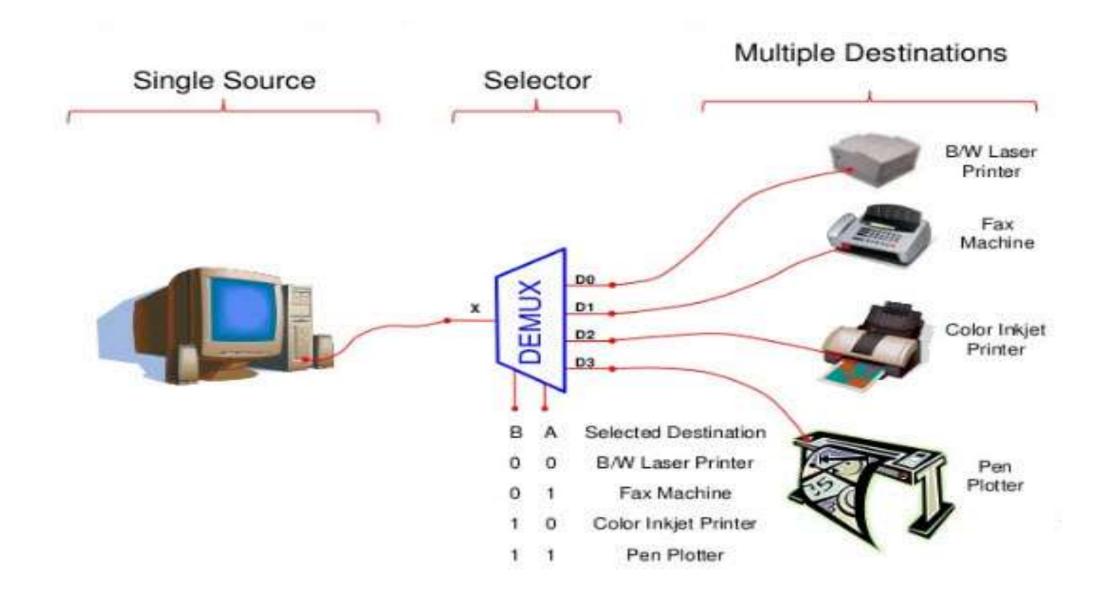


06/23/2020 3/13


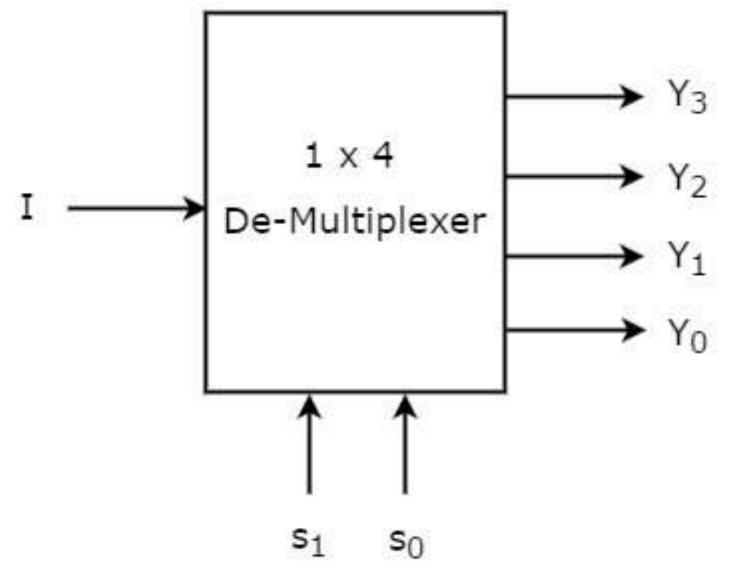
## 1x4 De-Multiplexer



> 1x4 De-Multiplexer has one input I, two selection lines, s1 & s0 and four outputs Y3, Y2, Y1 & Y0.








The single input 'I' will be connected to one of the four outputs, Y3 to Y0 based on the values of selection lines s1 & s0. The Truth table of 1x4 De-Multiplexer is shown below.

Selectio	Outputs					
S <sub>1</sub>	<b>S</b> <sub>0</sub>	<b>Y</b> <sub>3</sub>	Y <sub>2</sub>	<b>Y</b> <sub>1</sub>	<b>Y</b> <sub>0</sub>	
0	0	0	0	0	I	
0	1	0	0	I	0	
1	0	0	I	0	0	
1	1	I	0	0	0	





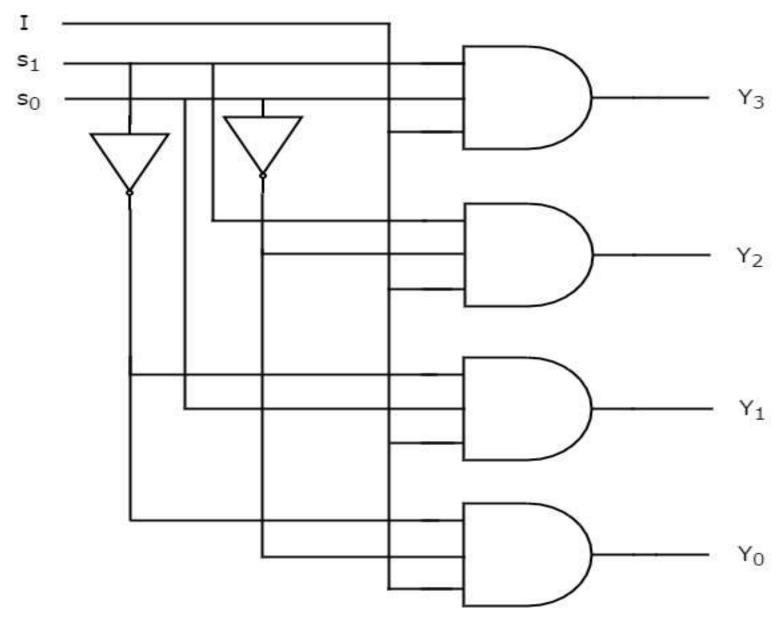We can implement these Boolean functions using Inverters & 3-input AND gates. The circuit diagram of 1x4 De-Multiplexer is shown in the following figure.





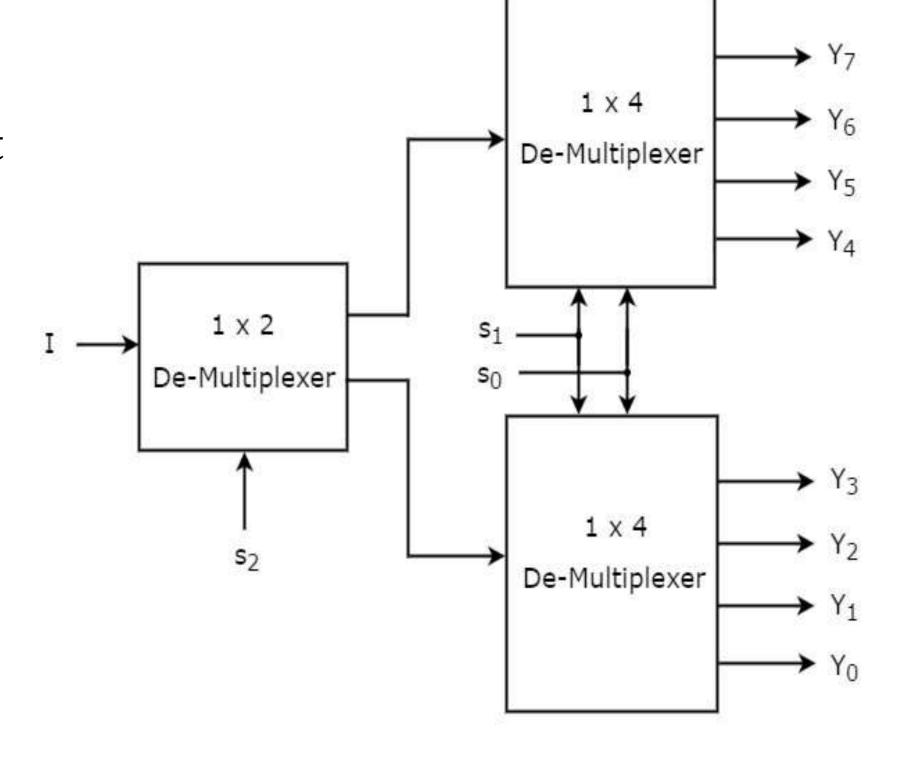
## 1x8 De-Multiplexer



1x8 De-Multiplexer has single input, three selection lines and eight outputs.







# 1x8 De-Multiplexer has one input I, three selection lines s2, s1 & s0 and outputs Y7 to Y0. The Truth table of 1x8 De-Multiplexer is shown below.

Selection Inputs			Outputs							
s <sub>2</sub>	s <sub>1</sub>	s <sub>0</sub>	<b>Y</b> <sub>7</sub>	<b>Y</b> <sub>6</sub>	<b>Y</b> <sub>5</sub>	Y <sub>4</sub>	<b>Y</b> <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	<b>Y</b> <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	I
0	0	1	0	0	0	0	0	0	I	0
0	1	0	0	0	0	0	0	I	0	0
0	1	1	0	0	0	0	I	0	0	0
1	0	0	0	0	0	I	0	0	0	0
1	0	1	0	0	I	0	0	0	0	0
1	1	0	0	I	0	0	0	0	0	0
1	1	1	I	0	0	0	0	0	0	0



### **Activity Time**







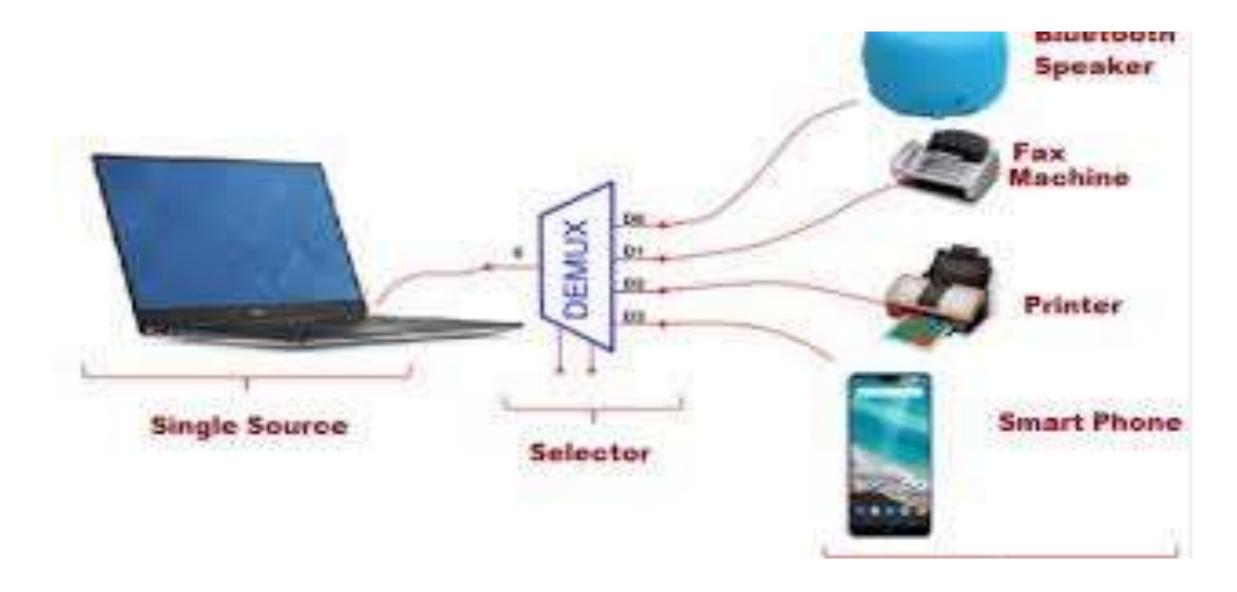
### **Applications**




Demultiplexer is used to connect a single source to multiple destinations. The main application area of demultiplexer is communication system where multiplexer are used.







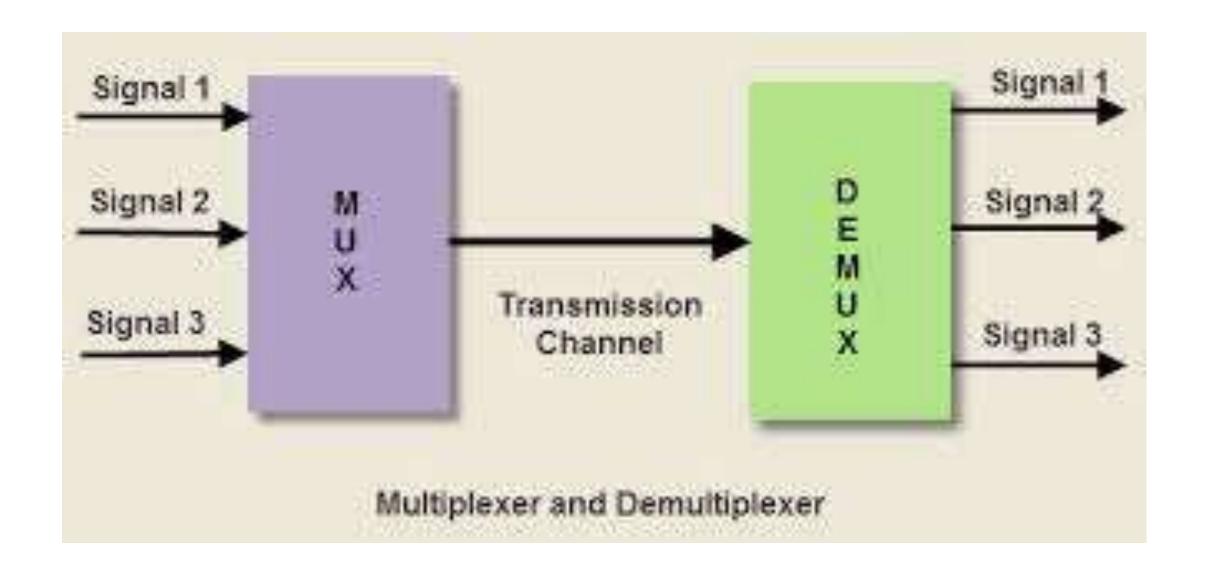

#### **ASSESSMENTS**











(Whole class)





### **THANK YOU**