



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB231 – DIGITAL ELECTRONICS**

II YEAR/ III SEMESTER

UNIT 3 – SEQUENTIAL CIRCUITS

TOPIC – Modulo n Counters



## Modulus Counter (MOD-N Counter)



The 2-bit counter is called as MOD-4 counter and 3-bit counter is called as MOD-8 counter. So in general, an n-bit counter is called as modulo-N counter. Where, MOD number =  $2^n$ .

- 2-bit up or down (MOD-4)
- 3-bit up or down (MOD-8)
- 4-bit up or down (MOD-16)



## Design Synchronous MOD-6 Counter Using JK flip flop

**Step 1 : Find number of flip-flops required to build the counter.**

Flip-flops required are :  $2^n \geq N$ .

Here  $N = 6 \quad \therefore n = 3$

i.e. Three flip-flops are required.

**Step 2 : Write an excitation table for JK flip-flop.**

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



# Design Synchronous MOD-6 Counter Using JK flip flop



Step 3 : Determine the transition table.

Present state			Next state			Flip-flop inputs					
Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>A+1</sub>	Q <sub>B+1</sub>	Q <sub>C+1</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	0	0	0	x	1	0	x	x	1
1	1	0	x	x	x	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x	x	x	x





# Design Synchronous MOD-6 Counter Using JK flip flop



Step 4 : K-map simplification for flip-flop inputs.

For  $J_A$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	0	0	1	0
1	X	X	X	X

$J_A = Q_B Q_C$

For  $K_A$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	X	X	X	X
1	0	1	X	X

$K_A = Q_C$

For  $J_B$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	0	1	X	X
1	0	0	X	X

$J_B = \bar{Q}_A Q_C$

For  $K_B$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	X	X	1	0
1	X	X	X	X

$K_B = Q_C$

For  $J_C$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	1	X	X	1
1	1	X	X	X

$J_C = 1$

For  $K_C$

$Q_A$ \ $Q_B Q_C$	00	01	11	10
0	X	1	1	X
1	X	1	X	X

$K_C = 1$



# Design Synchronous MOD-6 Counter Using JK flip flop



Step 5 : Implement the counter.

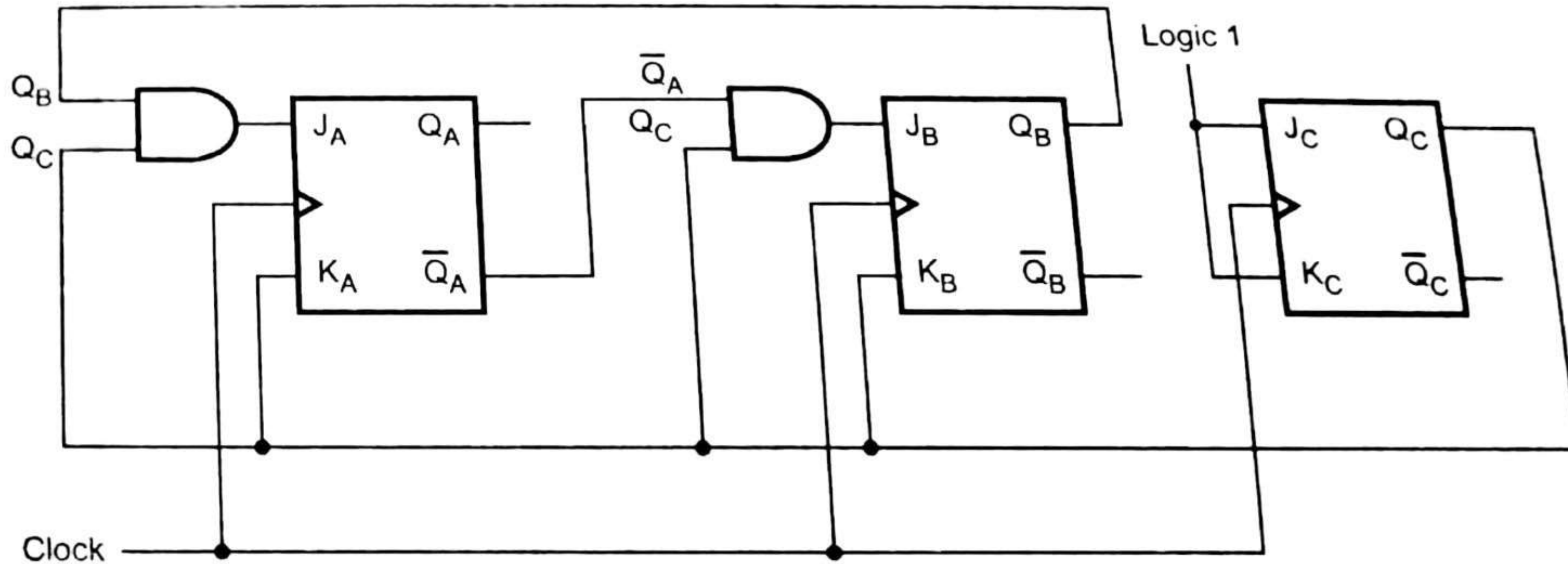


Fig. 7.79 Implementation of MOD 6 synchronous counter



## Design Synchronous MOD-6 Counter Using D flip flop



**Step 1 : Find number of flip-flops required to build the counter.**

Flip-flops required are :  $2^n \geq N$

Here  $N = 6 \therefore n = 3$

i.e. Three flip-flops are required.





## Design Synchronous MOD-6 Counter Using D flip flop



**Step 2 : Determine the transition table.**

Present state			Next state		
$Q_A$	$Q_B$	$Q_C$	$Q_{A+1}$	$Q_{B+1}$	$Q_{C+1}$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	x	x	x
1	1	1	x	x	x







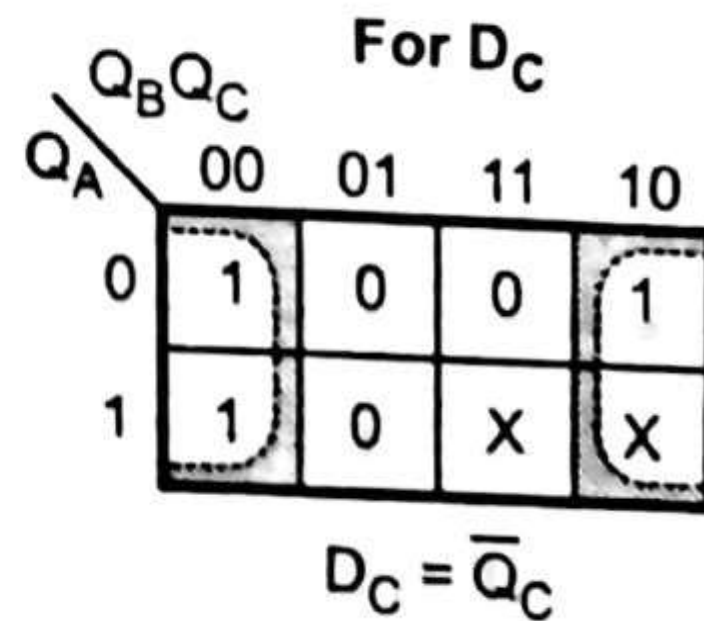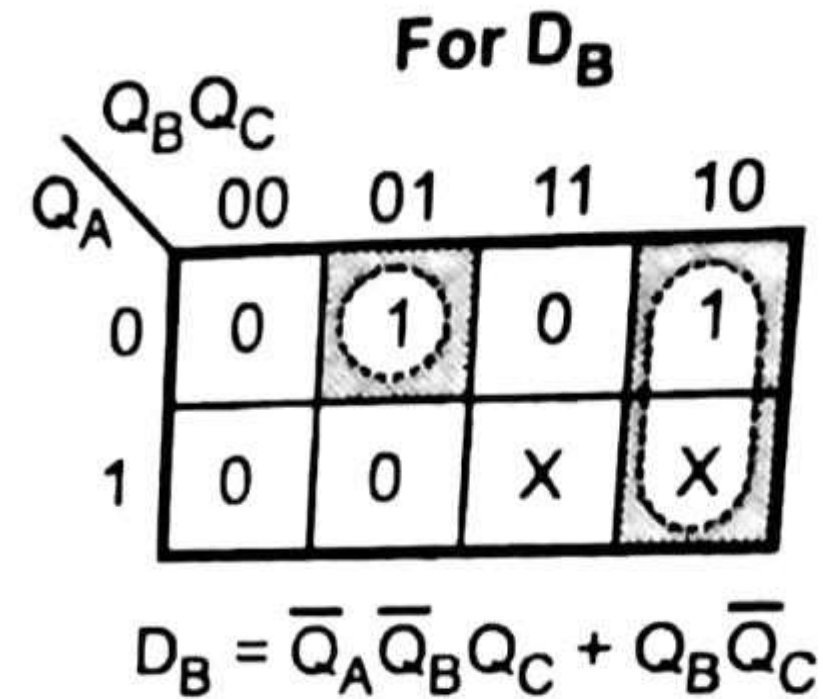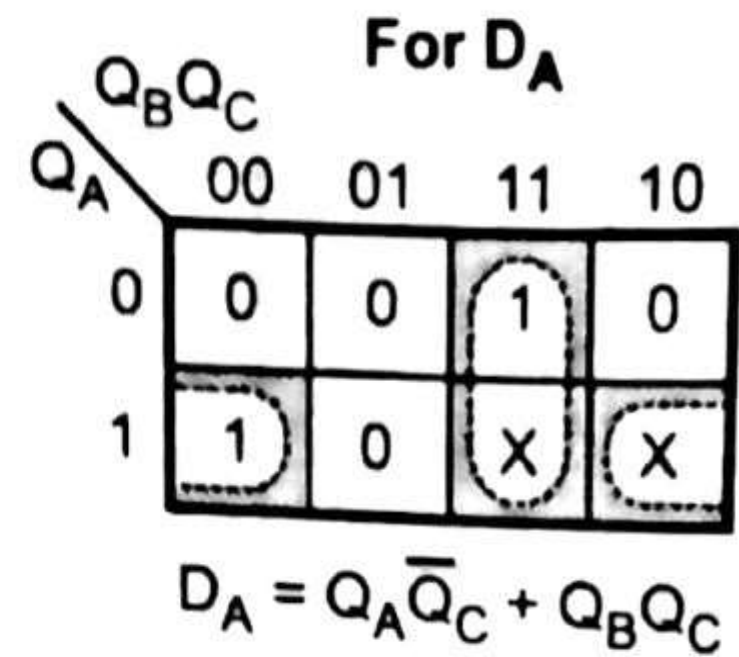
# Design Synchronous MOD-6 Counter Using D flip flop




Step 3 : K-map simplification for flip-flop inputs.




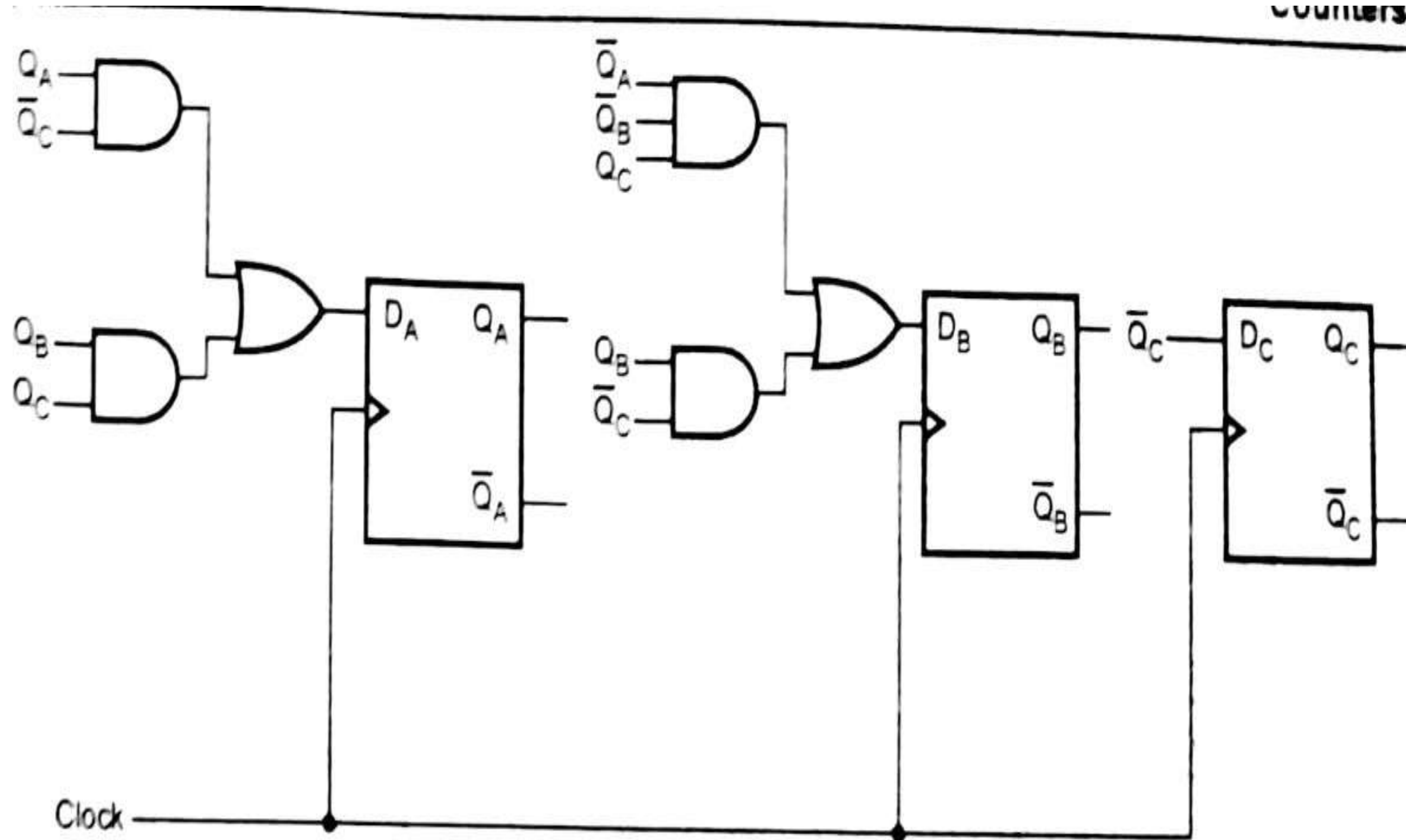
# Design Synchronous MOD-6 Counter Using D flip flop





## ASSESSMENTS



1. What is MOD N Counter?
2. Design MOD 5 counter using T flip flop.
3. Difference between synchronous and Asynchronous counter .



THANK YOU