



Op-Amp Characteristics



An ideal op amp is usually considered to have the following characteristics:

- Infinite open-loop gain $G = v_{out} / v_{in}$...
- Infinite input impedance R_{in} , and so zero input current.
- Zero input offset voltage.
- Infinite output voltage range.
- Infinite bandwidth with zero phase shift and infinite slew rate.



Inverting and Non-Inverting Operational Amplifiers



An operational amplifier is a **three-terminal device** consisting of **two high impedance input terminals**, one is called the **inverting input** denoted by a **negative sign** and the other is the **non-inverting input** denoted with a **positive sign**. The third terminal is the output of the Op-Amp.



Inverting Operational Amplifier



In the inverting operational amplifier circuit, the signal is applied at the inverting input and the non-inverting input is connected to the ground.


In this type of amplifier, the output is 180° out of phase to the input, i.e. when positive signal is applied to circuit, the output of the circuit will be negative.

By assuming the Op-Amp is ideal, then the concept of virtual short can be applied at the input terminals of the Op-Amp.

So that voltage at the inverting terminal is equal to the voltage at non-inverting terminal.



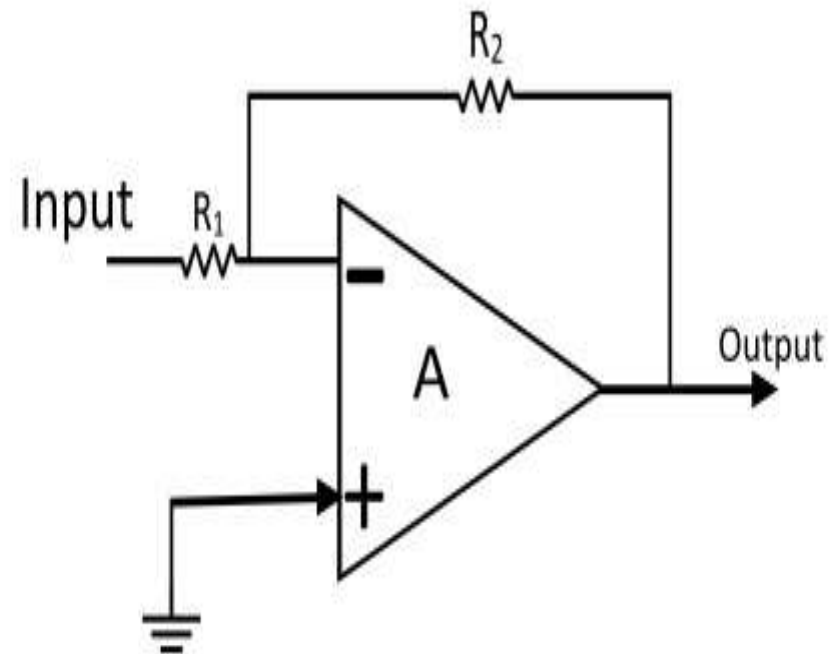Inverting Operational Amplifier- circuit diagram





Inverting Operational Amplifier Gain Formula



$$\text{VoltageGain}(A_v) = V_{\text{out}} / V_{\text{in}} = -R_2 / R_1$$



Non Inverting Operational Amplifier




When the signal is applied at the non-inverting input, the resulting circuit is known as Non-Inverting Op-Amp.

In this amplifier the output is exactly in phase with the input i.e. when a positive voltage is applied to the circuit, the output will also be positive.

By assuming the Op-Amp is ideal, then concept of virtual short can be applied i.e. the voltage at the inverting and non-inverting terminal is equal.



Non Inverting Operational Amplifier

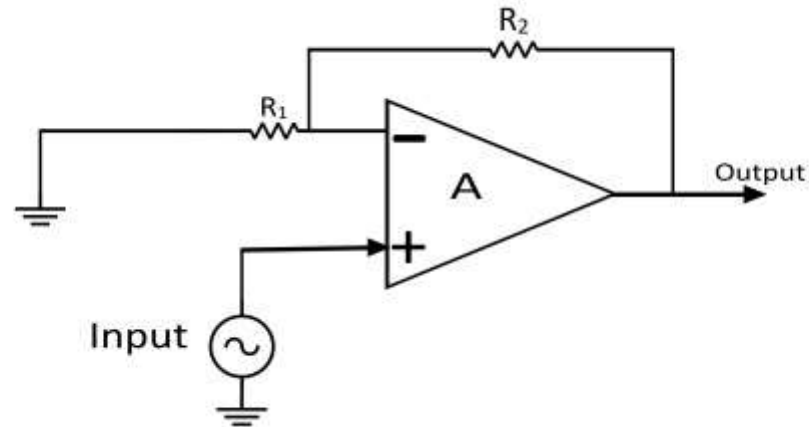

$$\text{VoltageGain}(A_v) = V_{\text{out}} / V_{\text{in}} = 1 + R_2 / R_1$$



Difference Between Inverting & Non Inverting Operational Amplifier



Inverting Op-Amp	Non-Inverting Op-Amp
The type of feedback used is voltage shunt.	The type of feedback used is voltage series.
The input and output voltages of this amplifier are 180° out of phase.	The input and output voltages are in phase.
Voltage Gain(A_v)= $V_{out}/V_{in}=-R_2/R_1$	Voltage Gain(A_v)= $V_{out}/V_{in}=1+R_2/R_1$



Advantages & Disadvantages of Op-Amp



Advantages

High input impedance: The input impedance of op-amp is extremely high, which leads to low current loading of the input signal source.

High Gain: The gain of op-amp is extremely high, which makes it suitable for applications such as amplification, filters, and oscillators.

Disadvantages

voltage Supply Limitations.

- Finite Bandwidth Limitations.
- Input Offset Voltage Limitations.
- Input Bias Current Limitations.
- Output Offset Voltage Limits.
- Slew Rate Limitation.
- Short Circuit Output Limits.
- Limited Common Mode Rejection Ratio.