



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19EET204 / DIGITAL ELECTRONICS AND INTEGRATED CIRCUITS II YEAR / IV SEMESTER

UNIT-II: DESIGN OF COMBINATIONAL AND SEQUENTIAL CIRCUITS

FLIP FLOPS – SR, D



TOPIC OUTLINE



Memory devices

RS Flip Flop

D Flip Flop

IC Devices

Recap






RS FLIP FLOP


RS Flip Flop

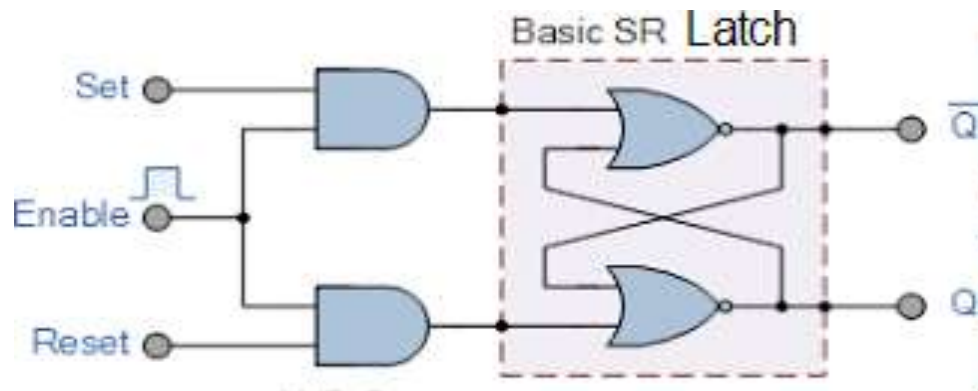- The RS flip flop is the basic memory element with **clock input** as enable point (**Clocked RS Latch**)
- Two input signals, S - set and R - signal.
- E - clock signal acting as enable.





RS Flip Flop – Circuit, Truth table

 

S	R	Q	Q'
0	0	1	0
0	1	0	1
1	0	1	0
1	1	?	?





RS Flip-Flop - Characteristics table



C	S	R	$Q(t)$	$Q(t+1)$	
0	X	X	0	0	No change
0	X	X	1	1	
1	0	0	0	0	No change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	?	Forbidden
1	1	1	1	?	



RS Latch / RS Flip Flop

  

Latch

  


Flip-flop



D FLIP FLOP


D Flip flop

 - The D stands for “Data” or “Delay” Flip flop
- It has one input signal, **D which is set when it is “1” and reset when it is “0”**
- The demerit of SR flip flop is forbidden value, ie the input - S & R is ‘1’. It is over comed here.






D Flip-Flop: Circuit, block, truth table

 

Inputs		Outputs	
CK	D	Q	\overline{Q}
0	X	No change	
1	0	0	1
1	1	1	0

 



D Flip-Flop: Ch. table

C	D	$Q(t)$	$Q(t+1)$	
0	X	0	0	No change
0	X	1	1	
1	0	0	0	Reset
1	0	1	0	
1	1	0	1	Set (Data)
1	1	1	1	



LATCH / FLIP-FLOP DEVICES

Device	# of Elements	Description
74LS73A	2	Negative-edge triggered JK flip-flop with clear
7474	2	Positive-edge triggered D flip-flop with preset and clear
74LS75	4	D Latch with enable
7476	2	Pulse-edge triggered JK flip-flop with preset and clear
74111	2	Master-slave JK flip-flop with preset, clear, and data lock out
74116	2	4-bit hazard-free D latch with clear and dual enable
74175	4	Positive-edge triggered D flip-flop with clear
74273	8	Positive-edge triggered D flip-flop with clear
74276	4	Negative-edge triggered JK flip-flop with preset and clear
74279	4	SR latch with active-low inputs



SUMMARIZE



**...A CASE STUDY &
THANK YOU**