



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19EEB102 / ELECTRIC CIRCUIT ANALYSIS

I YEAR / II SEMESTER



UNIT-I: BASIC CIRCUIT ANALYSIS

MESH AND NODAL ANALYSIS



TOPIC OUTLINE

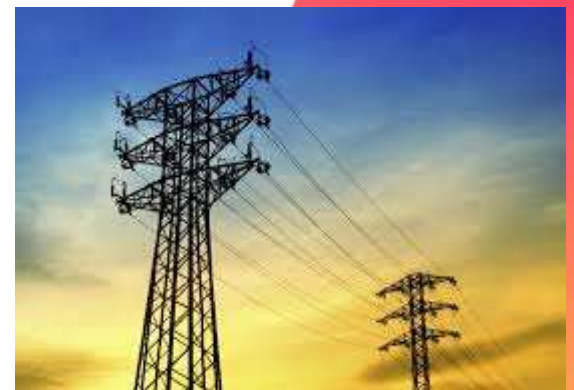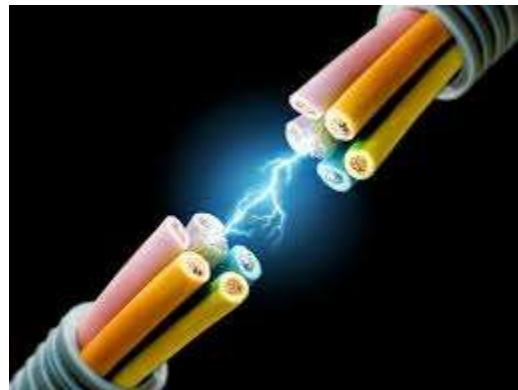- KVL/KCL recap
- Mesh Analysis
 - Problems
- Nodal Analysis
 - Problems





KVL -RECAP


Kirchoff's **V**oltage **L**aw (**KVL**):

- The algebraic sum of voltages around each **loop is zero**
- Σ voltage drops - Σ voltage rises = 0
- **Or** Σ voltage drops = Σ voltage rises



MESH ANALYSIS

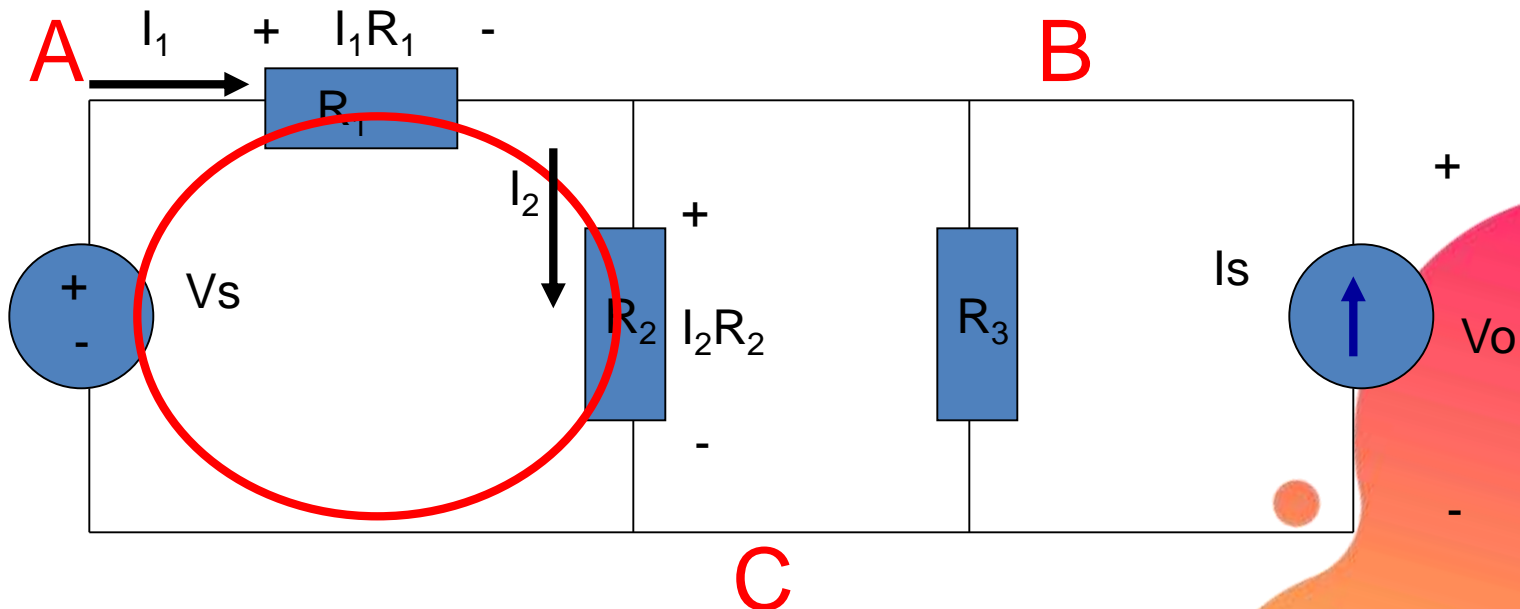- Kirchoff's Voltage Law around 1st Loop (mesh)




Assign current variables and directions

Use Ohm's law to assign voltages and polarities consistent with passive devices (current enters at the + side)



MESH ANALYSIS

- Kirchoff's Voltage Law around 1st Loop

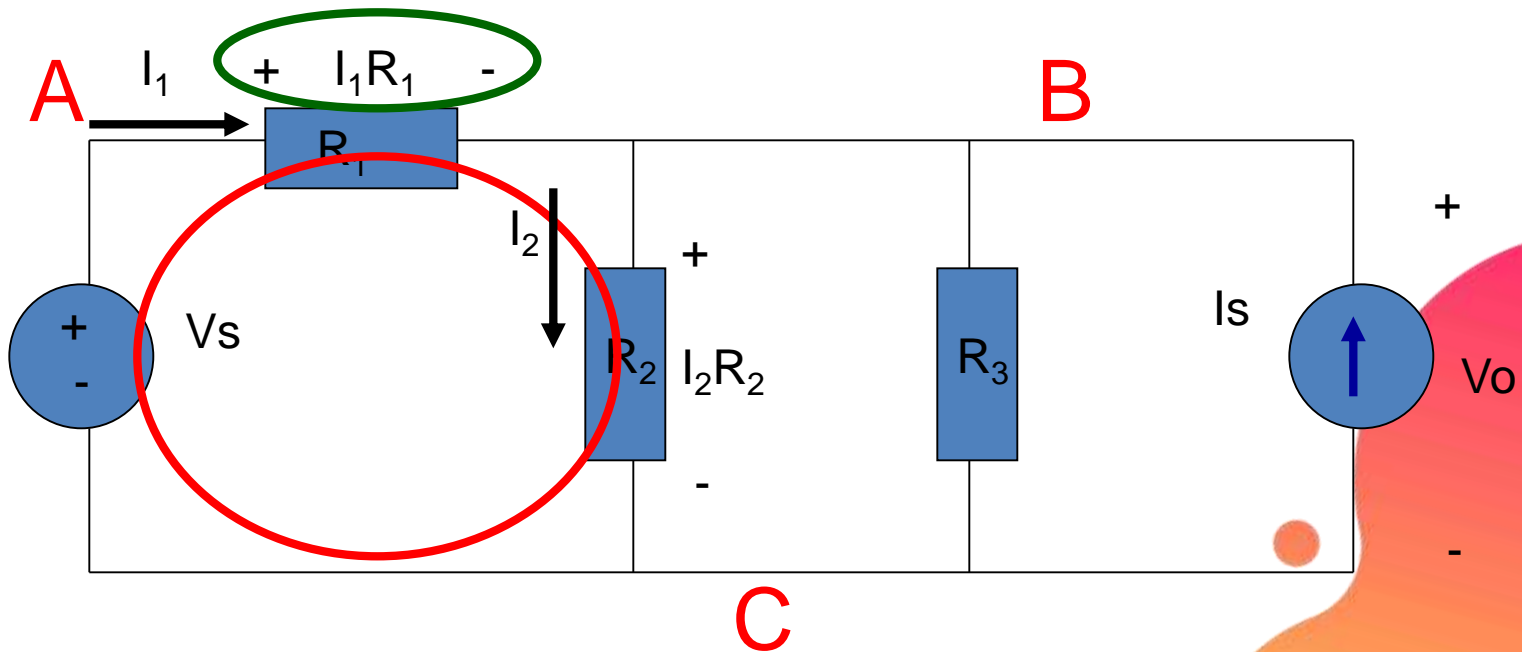


Starting at node A, add the 1st voltage drop: $+ I_1 R_1$



MESH ANALYSIS

- Kirchoff's Voltage Law around 1st Loop

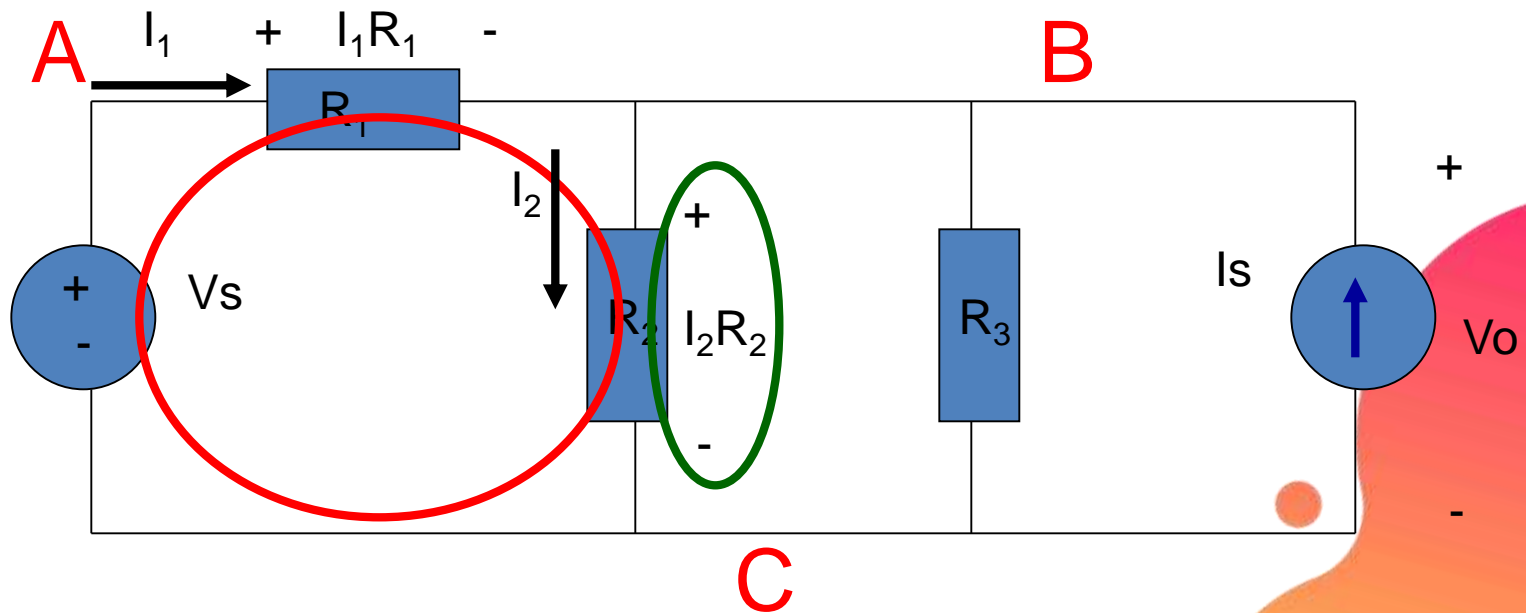


Add the voltage drop from B to C through R_2 : $+ I_1 R_1 + I_2 R_2$



MESH ANALYSIS

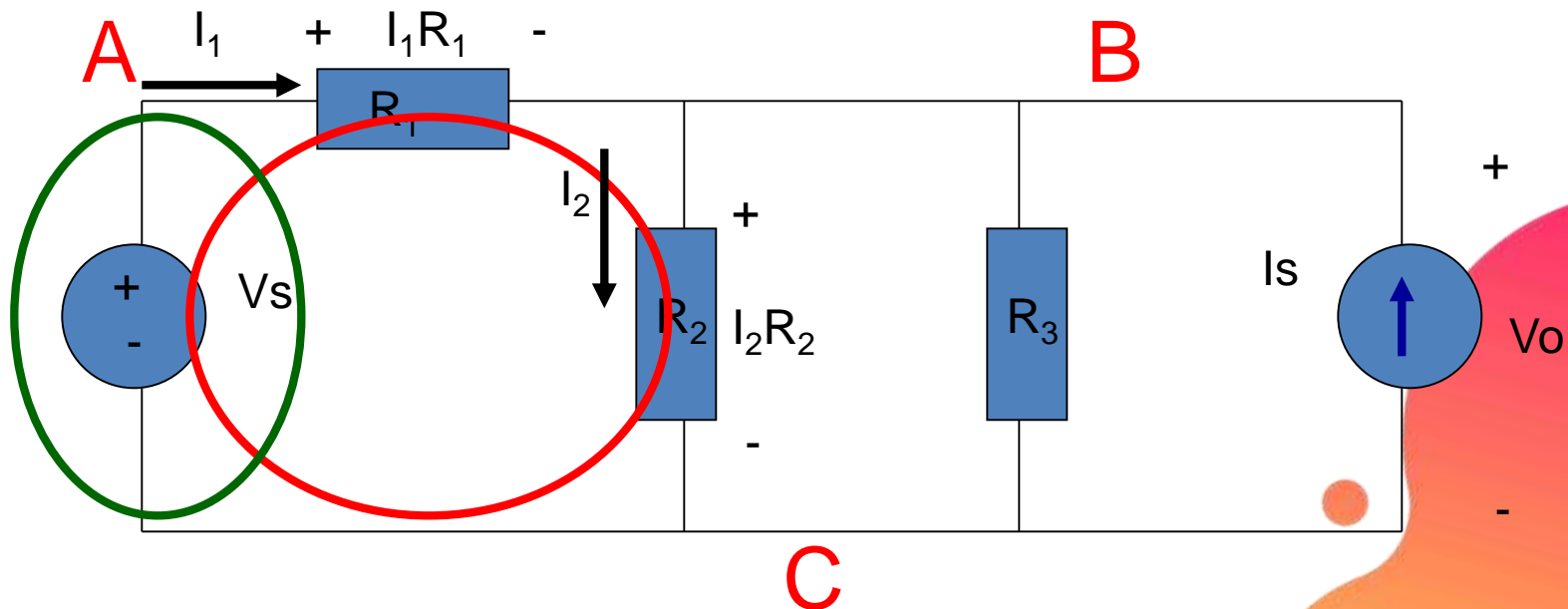- Kirchoff's Voltage Law around 1st Loop (mesh)




Subtract the voltage rise from C to A through V_s : $+I_1R_1 + I_2R_2 - V_s = 0$

Notice that the sign of each term matches the polarity encountered 1st



EXAMPLE 1

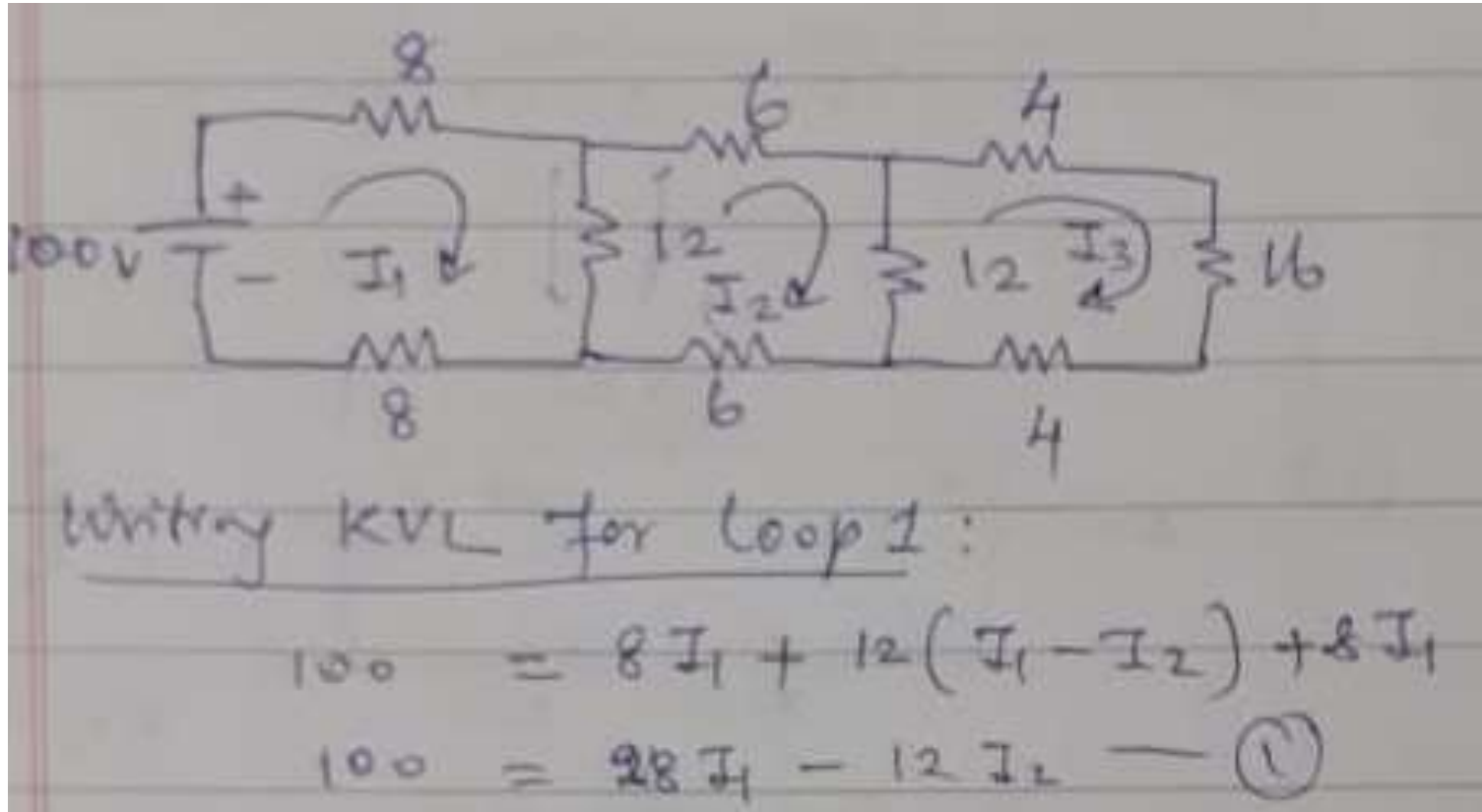



EXAMPLE 1

Writing KVL for loop 2:

$$0 = 12(I_2 - I_1) + 6I_2 + 12(I_2 - I_3) + 6I_2$$

$$0 = -12I_1 + 36I_2 - 12I_3 \quad \text{--- (2)}$$


Writing KVL for loop 3:

$$0 = -12I_2 + 36I_3 \quad \text{--- (3)}$$

$$\begin{bmatrix} 28 & -12 & 0 \\ -12 & 36 & -12 \\ 0 & -12 & 36 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix}$$



EXAMPLE 2

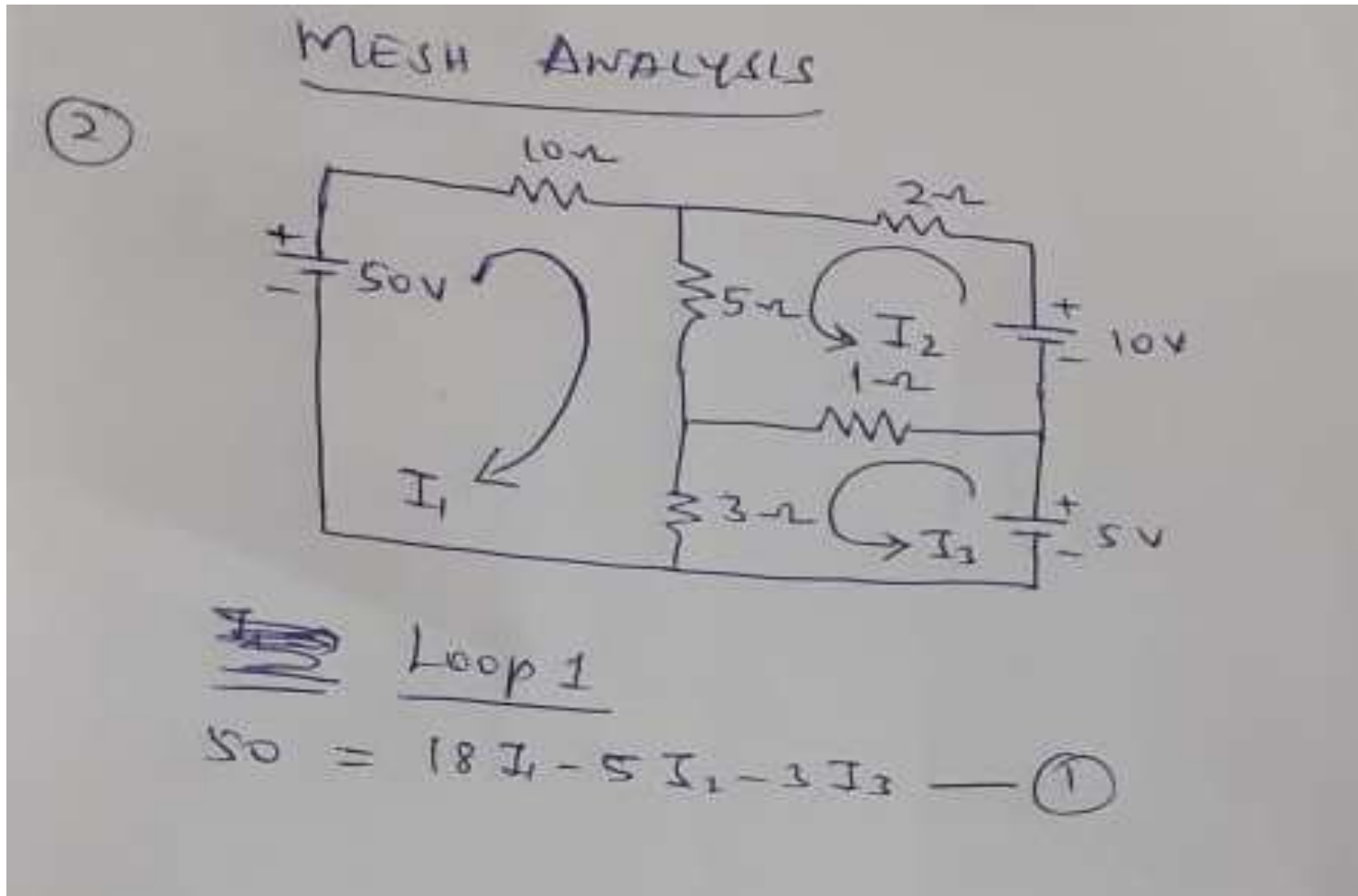



EXAMPLE 2

Loop 2:

$$10 = 2I_2 + 5(I_2 + I_1) + 1(I_1 - I_2)$$

$$10 = 5I_1 + 8I_2 - I_3 \quad \text{--- (2)}$$

Loop 3:

$$3I_1 - I_2 + 4I_3 = 5 \quad \text{--- (3)}$$

$$I_1 = 3.3 \text{ A} //$$

$$I_2 = -0.9 \text{ A} //$$

$$I_3 = 1.47 \text{ A} //$$



EXAMPLE 2

(Matrix method-solving)

$$\begin{aligned} 50 &= 18 I_1 - 5 I_2 - 2 I_3 & \text{--- (1)} \\ 10 &= 5 I_1 + 8 I_2 - I_3 & \text{--- (2)} \\ 5 &= 3 I_1 - I_2 + 4 I_3 & \text{--- (3)} \end{aligned}$$

$$\begin{bmatrix} 18 & -5 & -2 \\ 5 & 8 & -1 \\ 3 & -1 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 10 \\ 5 \end{bmatrix}$$

$$\Delta = 18(32 - (-1)) + (-5)(20 - (-3)) + ((-5) - 24) \cdot (-3)$$

$$\Delta = 0$$

$$\Delta I_1 = \begin{bmatrix} 50 & -5 & -2 \\ 10 & 8 & -1 \\ 5 & -1 & 4 \end{bmatrix} = 0$$

$$\Delta I_2 = 0 \quad \Delta I_3 = 0$$


$$I_1 = \frac{\Delta I_1}{\Delta} = 0 \quad I_2 = \frac{\Delta I_2}{\Delta} = 0 \quad I_3 = \frac{\Delta I_3}{\Delta} = 0$$



KCL - RECAP

- Kirchoff's **C**urrent **L**aw (**KCL**) :

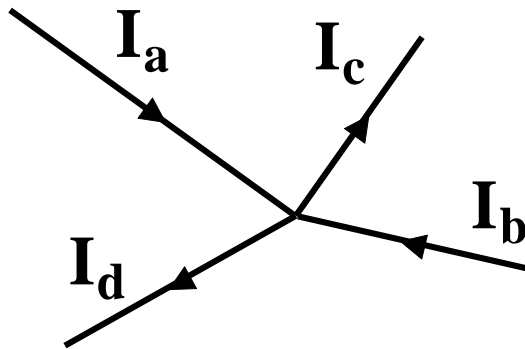The sum of the **current entering** a node (junction point) equal to the sum of the **currents leaving**.



$$I_a + I_b = I_c + I_d$$

I_a , I_b , I_c , and I_d can each be either a positive or negative number.



NODAL ANALYSIS

NODAL ANALYSIS :

5A \uparrow 10Ω 3Ω V_1 5Ω V_2 1Ω $10V$ V_3 (Ref)

2 Eqn: (node - 1 = No. of)

Using kcl

At node 1 $5 = \frac{V_1 - V_3}{10} + \frac{V_1 - V_2}{3}$



NODAL ANALYSIS

$$5 = \frac{V_1}{10} + \frac{V_1 - V_2}{3} \quad \text{--- (1)}$$

Using KCL
At node 2

$$0 = \frac{V_2 - V_1}{3} + \frac{V_2 - V_2}{5} + \frac{V_2 - 10}{1}$$
$$0 = \frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - 10}{1} \quad \text{--- (2)}$$



NODAL ANALYSIS

Handwritten equations for nodal analysis:

$$5 = \frac{V_1}{10} + \frac{V_1}{3} - \frac{V_2}{3} \quad \text{--- (1)}$$



~~5~~

$$0 = \frac{V_2}{3} - \frac{V_1}{3} + \frac{V_2}{5} + \frac{V_2}{1} - 10$$

Solving equations, the nodal voltages are:
 $V_1 = 19.85$ volts, $V_2 = 10.9$ volts



ANALYSIS-PROBLEMS

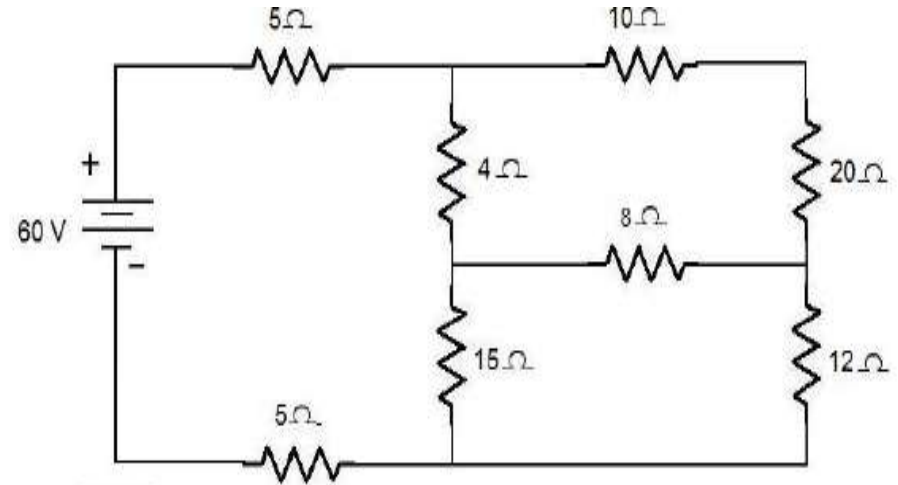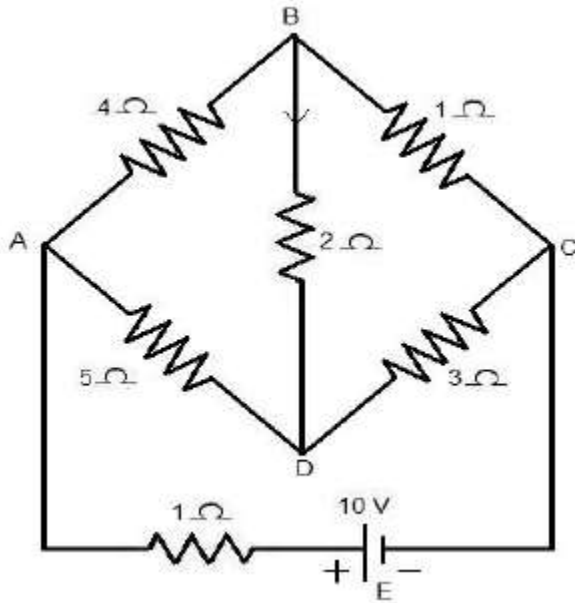


Ex 4: Find the mesh currents in the circuit shown above (left)

Ex 5: Find the nodal voltages in the circuit shown above (right)



RECAP...

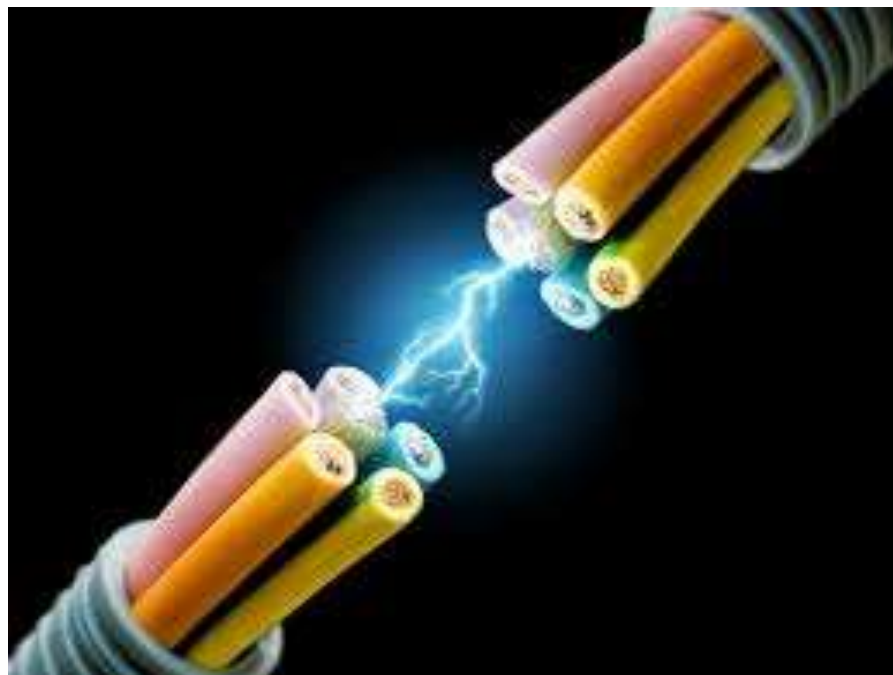

...THANK YOU