



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19EET208 / DIGITAL ELECTRONICS AND INTEGRATED CIRCUITS II YEAR / IV SEMESTER UNIT-IV: OPERATIONAL AMPLIFIER

OP-AMP BASICS AND CHARACTERISTICS



TOPIC OUTLINE

What is an Op-Amp?

History

Pin Details IC741

Characteristics of **Ideal** Op-Amps

Characteristics of **Real** Op-Amps

Basics of Op-Amp


Inv and Non Inv Op-Amp Circuits





WHAT IS AN OP-AMP?

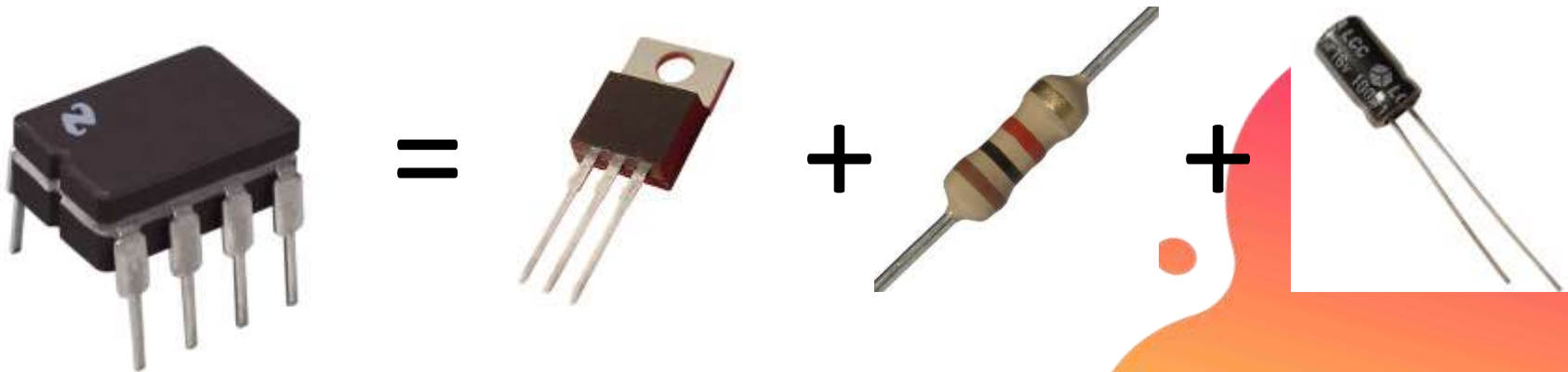
- An *Operational Amplifier* (known as an “Op-Amp”) is a device that is used to amplify a signal using an external power source
- Op-Amps are generally composed of:
 - Transistors, Resistors, Capacitors






BRIEF HISTORY

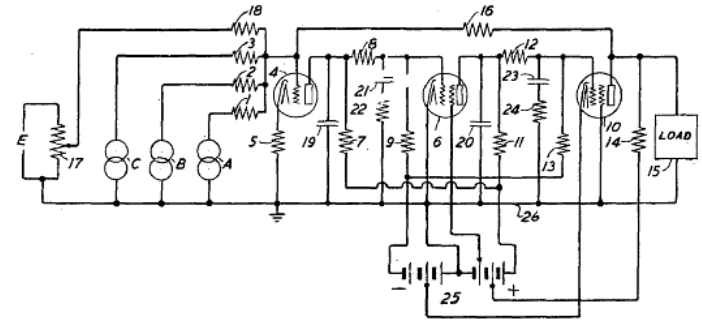- First patent for Vacuum Tube Op-Amp (1946)



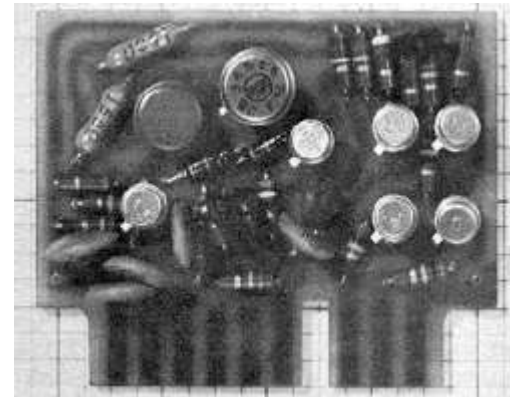- First Commercial Op-Amp available (1953)



- First discrete IC Op-Amps (1961)




- First commercially successful Monolithic Op-Amps (1965)




IC741 – PIN DETAILS

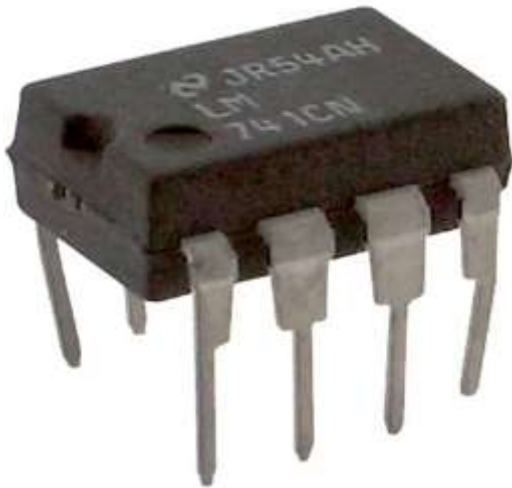- Leading to the advent of the modern IC which is still used even today (1967 – present)



Fairchild μ A741

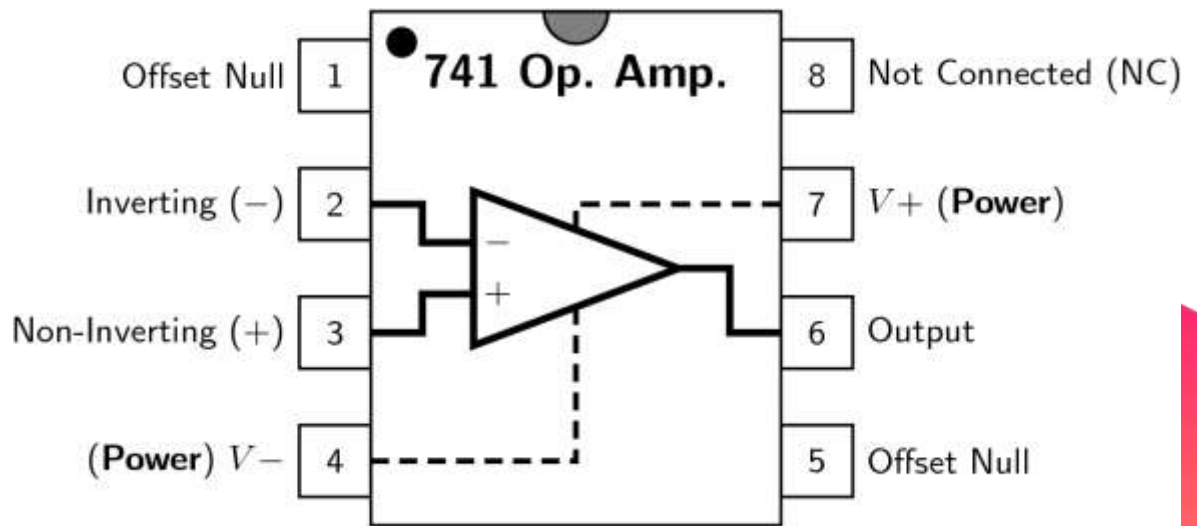

Electrical Schematic of μ A741




AN IDEAL OP-AMP

- Infinite voltage gain
- Infinite input impedance
- Zero output impedance
- Infinite bandwidth
- Zero input offset voltage (i.e., exactly zero out if zero in).




IDEAL VERSUS REAL OP-AMPS

Parameter	Ideal Op-Amp	Real Op-Amp
Voltage Gain	∞	$10^5 - 10^9$
Gain Bandwidth (Hz)	∞	1-20 MHz
Input Resistance (R_i)	∞	$10^6 - 10^{12} \Omega$
Output Resistance (R_o)	0	100 - 1000 Ω

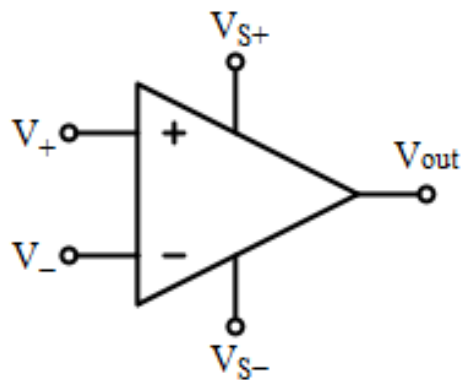

← Ideal

Real →

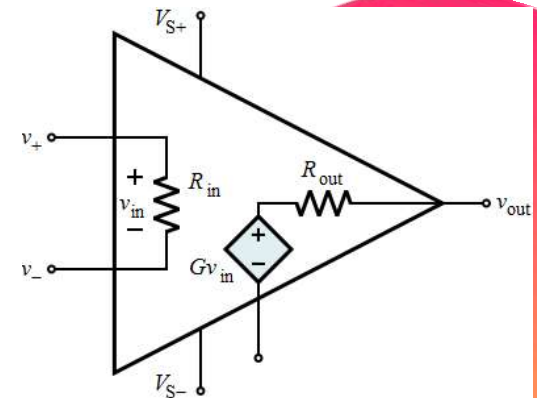



BASICS OF AN OP-AMP

- An op-amp amplifies the difference of the inputs V_+ and V_- (known as the differential input voltage)
- This is the equation for an *open loop* gain amplifier:


$$V_{out} = K(V_+ - V_-)$$

- K is typically very large – at around 10,000 or more for IC Op-Amps
- This equation is the basis for all the types of amps we will be discussing



BASICS OF AN OP-AMP

A traditional Op-Amp:

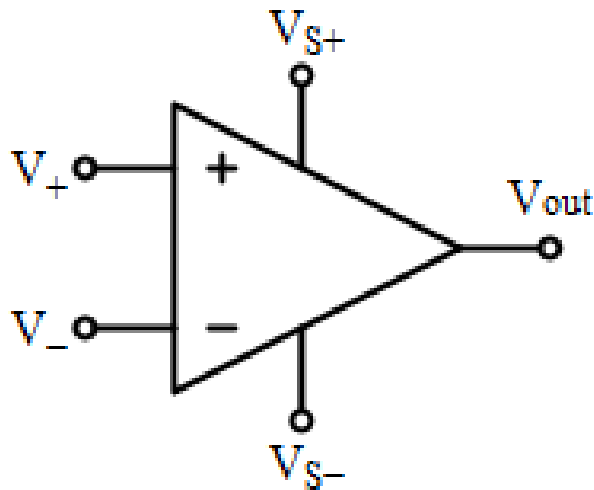

V_+ : non-inverting input

V_- : inverting input

V_{out} : output

V_{S+} : positive power supply

V_{S-} : negative power supply


$$V_{out} = K (V_+ - V_-)$$

- The difference between the two inputs voltages (V_+ and V_-) multiplied by the gain (K , “amplification factor”) of the Op-Amp gives you the output voltage
- The output voltage can only be as high as the difference between the power supply (V_{S+} / V_{S-}) and ground (0 Volts)




Saturation

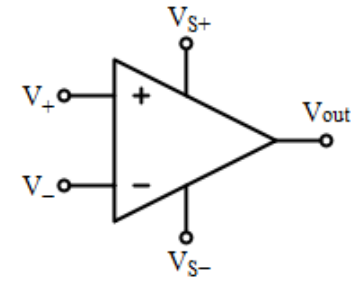Saturation is caused by increasing/decreasing the input voltage to cause the output voltage to equal the power supply's voltage*



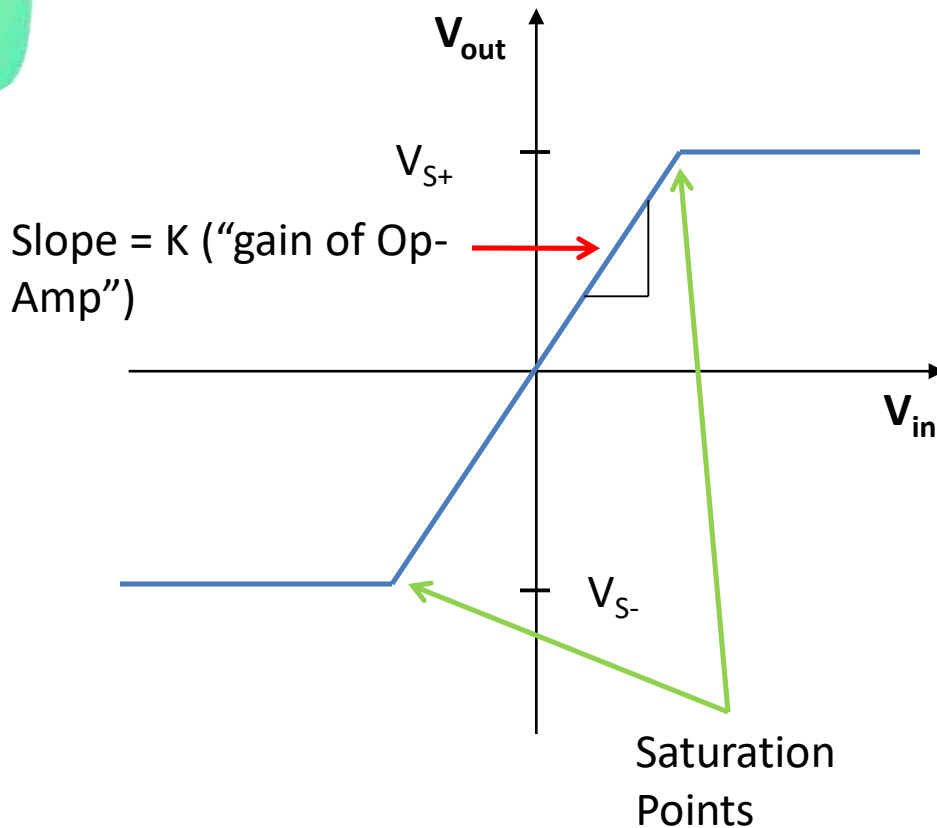The slope is normally much steeper than it is shown here. Potentially just a few millivolts (mV) of change in the difference between V_+ and V_- could cause the op-amp to reach the saturation level




* Note that saturation level of traditional Op-Amp is 80% of supply voltage with exception of CMOS op-amp which has a saturation at the power supply's voltage




Open Loop vs Closed Loop

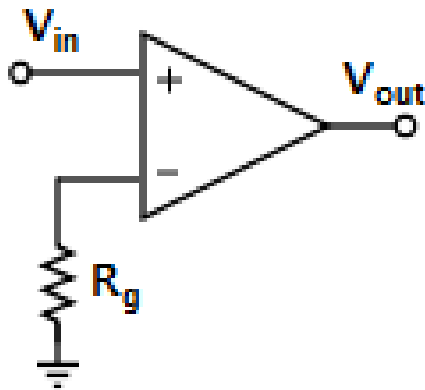- A closed loop op-amp has feedback from the output to the input, an open loop op-amp does not



Open Loop

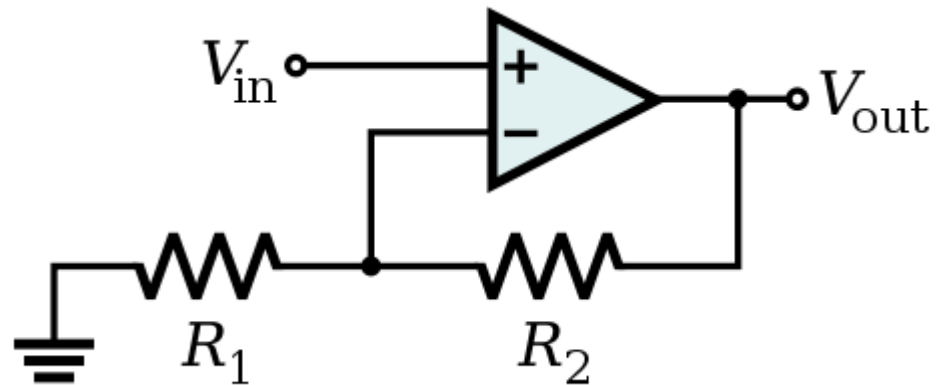


Closed Loop



NON-INVERTING OP-AMP

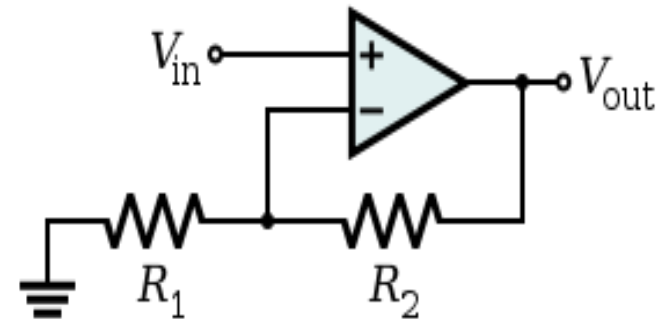- Amplifies the input voltage by a constant
- Closed loop op-amp
- Voltage input connected to non-inverting input
- Voltage output connected to inverting input through a feedback resistor
- Inverting input is also connected to ground
- Non-inverting input is only determined by voltage output





NON-INVERTING OP-AMP


$$V_o = K(V_+ - V_-) \text{ \& } R_2 = R_f$$

$R_1/(R_1+R_2) \leftarrow$ Voltage Divider

$$V_i = V_o (R_1/(R_1+R_2))$$

$$V_o/V_i = A_{cl} = [1 + (R_2/R_1)]$$


$$V_{out} = V_{in} (1 + (R_2/R_1))$$

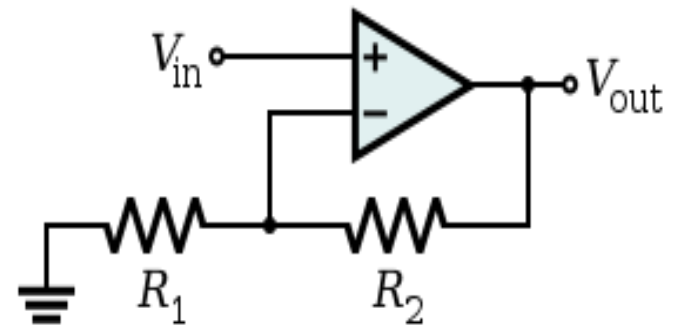



INVERTING OP-AMP

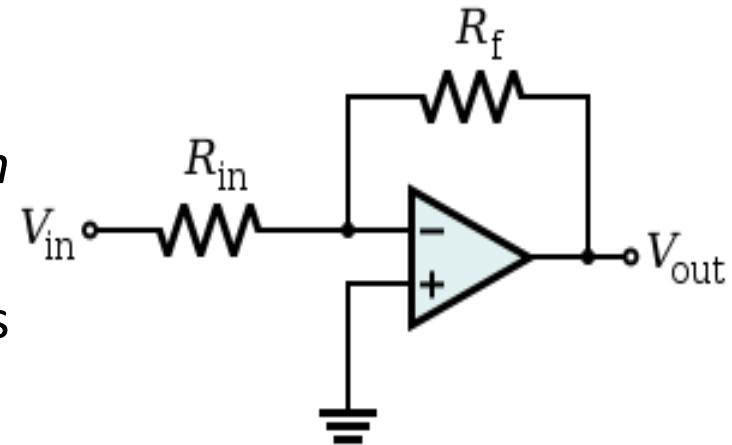- Amplifies and inverts the input voltage
- Closed loop op-amp
- Non-inverting input is determined by *both* voltage input and output
- The polarity of the output voltage is opposite to that of the input voltage
- Voltage input is connected to inverting input
- Voltage output is connected to inverting input through a feedback resistor
- Non-inverting input is grounded





INVERTING OP-AMP

$$V_{out} = K(V_{+} - V_{-})$$

Nodal equation at “a” (V_a) is

$$0 = ((V_a - V_i) / R_i) + ((V_a - V_o) / R_f)$$

Since V_a is virtual gnd = 0

$$0 = ((0 - V_i) / R_i) + ((0 - V_o) / R_f)$$

$$V_o / V_i = -R_f / R_i = A_{cl}$$

$$V_{out} = -V_{in} R_f / R_{in}$$

