



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19EEB102 / ELECTRIC CIRCUIT ANALYSIS

I YEAR / II SEMESTER



UNIT-III: AC CIRCUITS

POWER AND POWER FACTOR



TOPIC OUTLINE

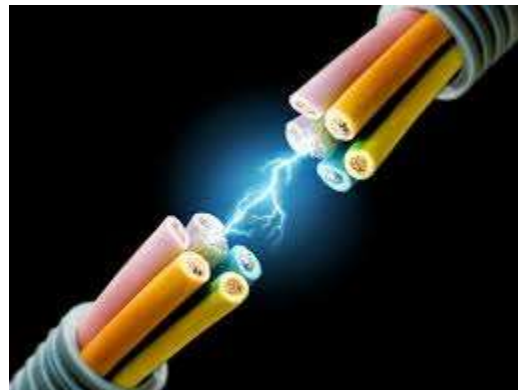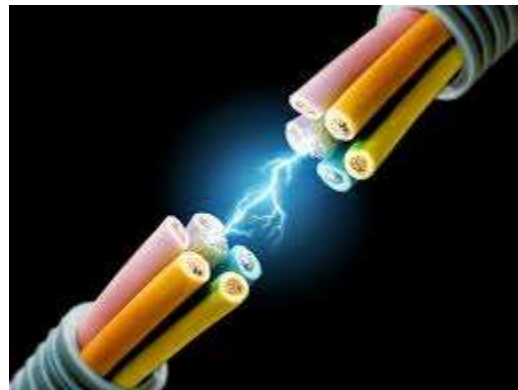- AC Power
- Types of Power
 - Power Factor





1. POWER IN RESISTOR

- Suppose a voltage $v = V_p \sin \omega t$ is applied across a resistance R . The resultant current i will be

$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R} = I_p \sin \omega t$$

- The result power p will be

$$p = vi = V_p \sin \omega t \times I_p \sin \omega t = V_p I_p (\sin^2 \omega t) = V_p I_p \left(\frac{1 - \cos 2\omega t}{2} \right)$$


- The average value of $(1 - \cos 2\omega t)$ is 1, so

$$\text{Average Power } P = \frac{1}{2} V_p I_p = \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} = VI$$

where V and I are the **RMS voltage and current**



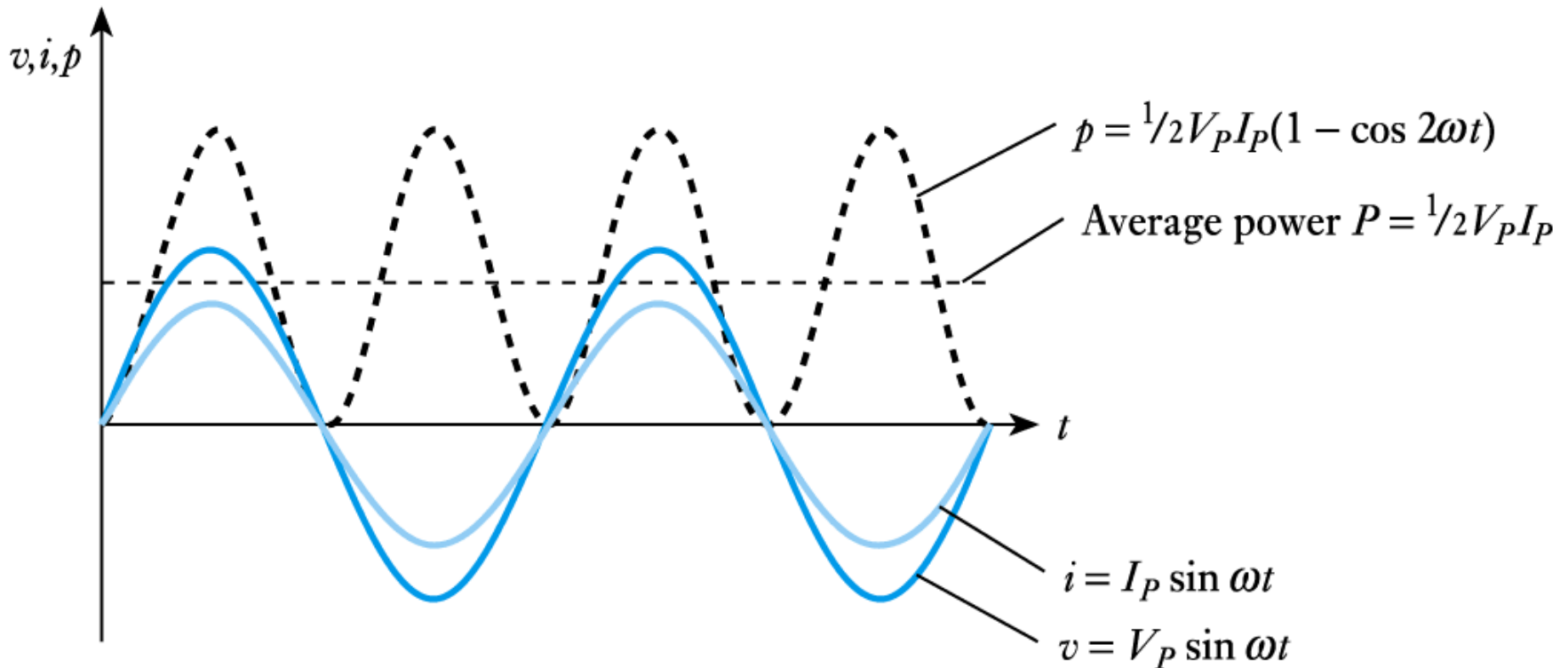RELATIONSHIP BETWEEN V , I AND P IN A RESISTOR





2. POWER IN CAPACITORS


- For capacitors we know that the current leads the voltage by 90° .
- Therefore, if a voltage $v = V_p \sin \omega t$ is applied across a capacitance C , the current will be

given by $i = I_p \cos \omega t$

- *Then*
$$\begin{aligned} &= V_p \sin \omega t \times I_p \cos \omega t \\ &= V_p I_p (\sin \omega t \times \cos \omega t) \\ &= V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$



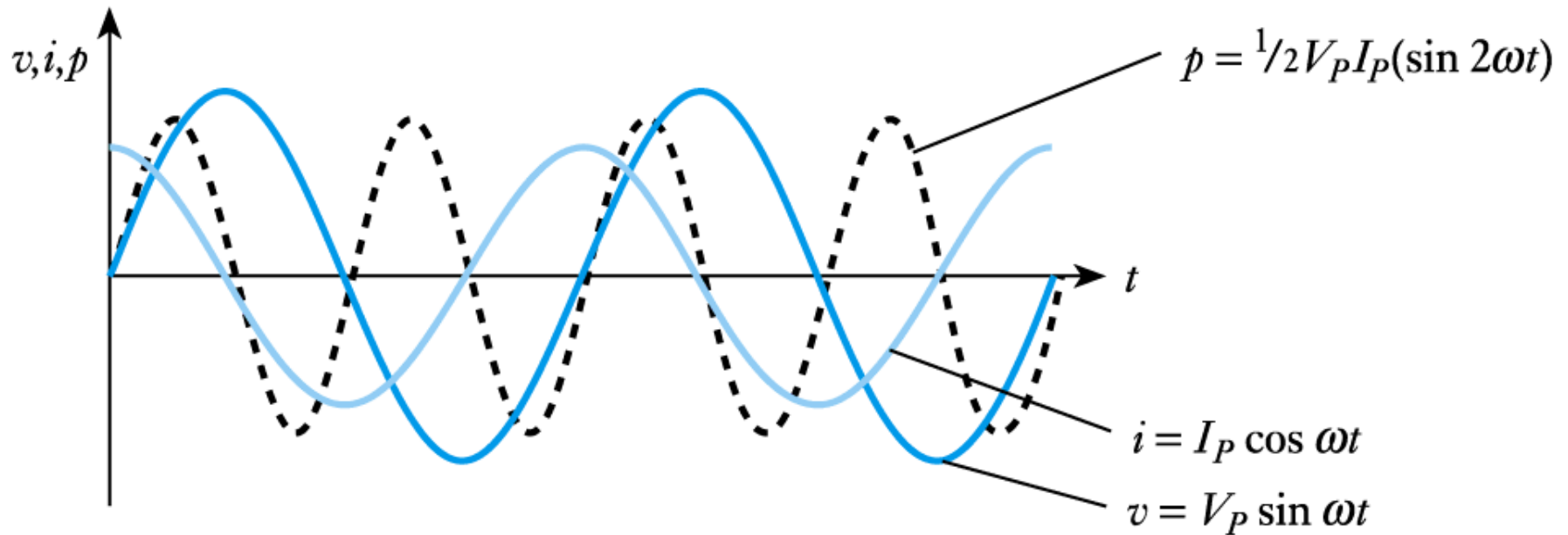RELATIONSHIP BETWEEN V , I AND P IN A CAPACITOR



3. POWER IN INDUCTORS



For inductors we know that the **current lags the voltage by 90°** .


• Therefore, if a voltage $v = V_p \sin \omega t$ is applied across an inductance L , the current will be given by $i = -I_p \cos \omega t$

• Then

$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times -I_p \cos \omega t \\ &= -V_p I_p (\sin \omega t \times \cos \omega t) \\ &= -V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$



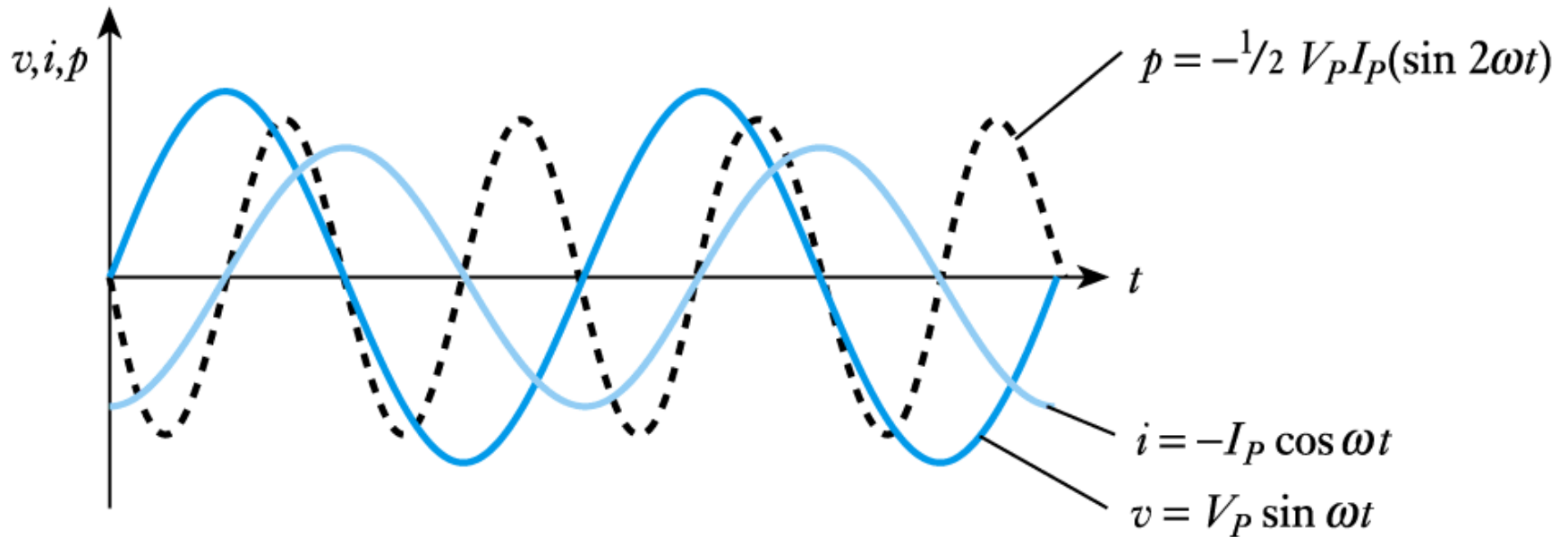RELATIONSHIP BETWEEN V , I AND P IN AN INDUCTOR







POWER

LOAD (POWER CONSUMED)

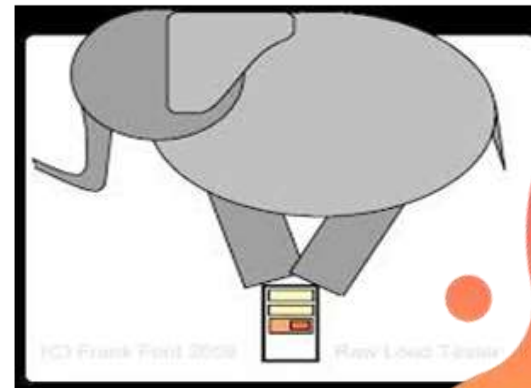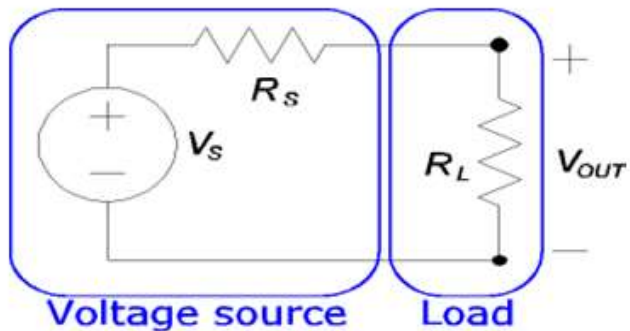- It is a any electric load on a circuit that does work.
- A device connected to the **output of a circuit**
 - **Example:** Power windows, light bulbs, motors.





POWER - TYPES

- **Real power** is the capacity of the circuit performing work in a particular time.
 - It is the product of V , I and cosine angle of voltage and current
- **Apparent power** is the product of the current and voltage of the circuit
- **Reactive power** is the product of V , I and sine angle of voltage and current




POWER

Real Power $P = VI \cos \phi$ watts or kW

Reactive Power $Q = VI \sin \phi$ var or kVAR

Apparent Power $S = VI$ VA or kVA

$$S^2 = P^2 + Q^2$$

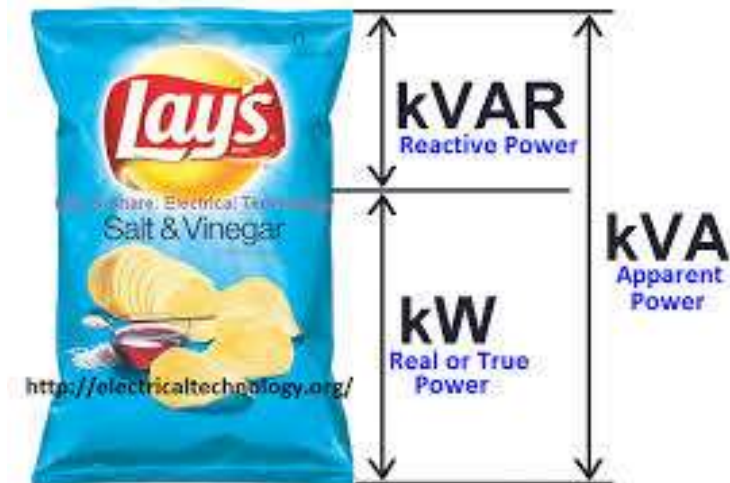



REAL AND REACTIVE POWER




If a circuit has resistive and reactive parts, the resultant power has 2 parts:

- The first is *dissipated* in the resistive element. This is the **real power, P**
- The second is *stored and returned* by the reactive element. This is the **reactive power, Q** , which has units of **volt amperes reactive** or **var**



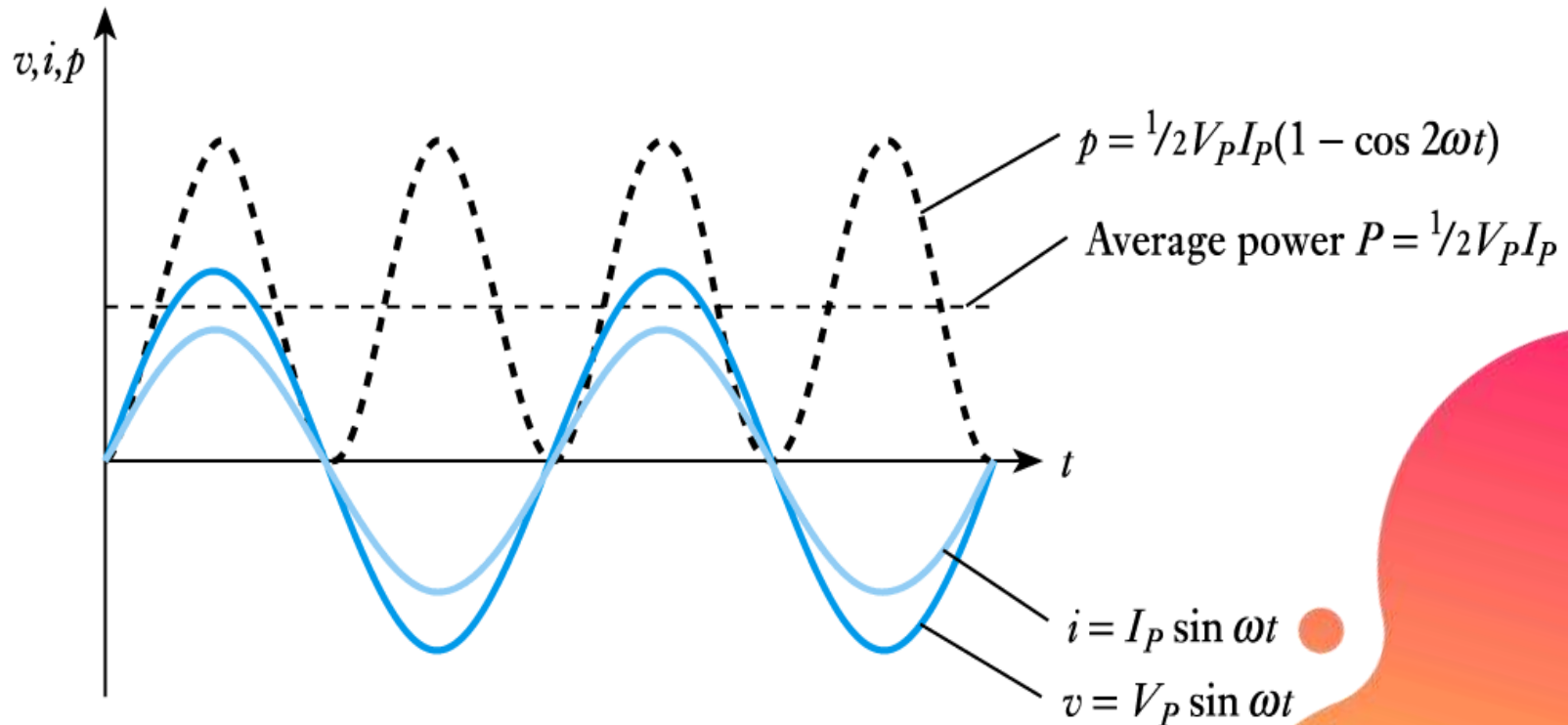RELATIONSHIP BETWEEN V , I AND P IN A RESISTOR






POWER TRIANGLE

The Power Triangle:



You pay for fuel for the **VERTICAL** portion of flight, as well as the fuel for the **HORIZONTAL** portion of flight.


Non-Working
(Reactive)
Power

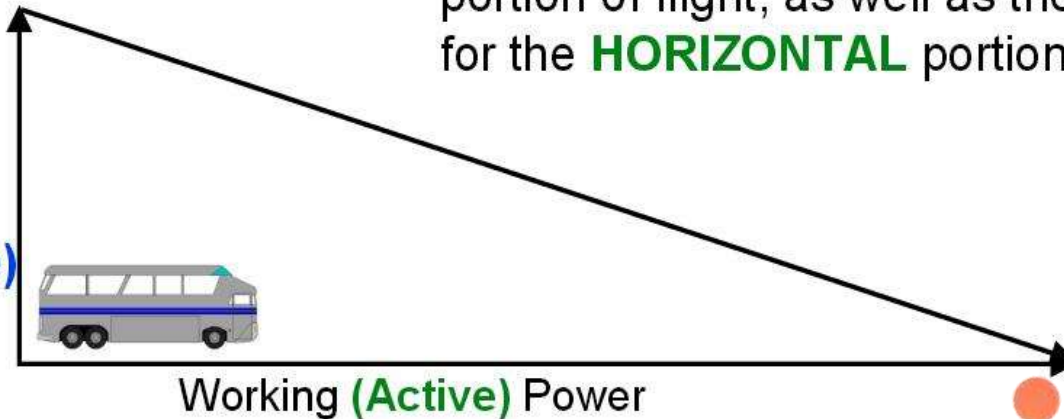



POWER FACTOR

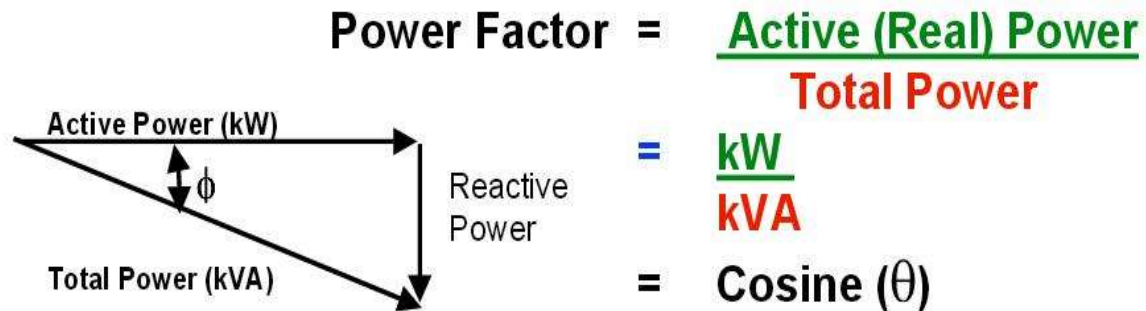
- Power Factor is the ratio of **Active Power** to **Total Power**:



- Power Factor is a measure of efficiency (Output/Imp)



RECAP...

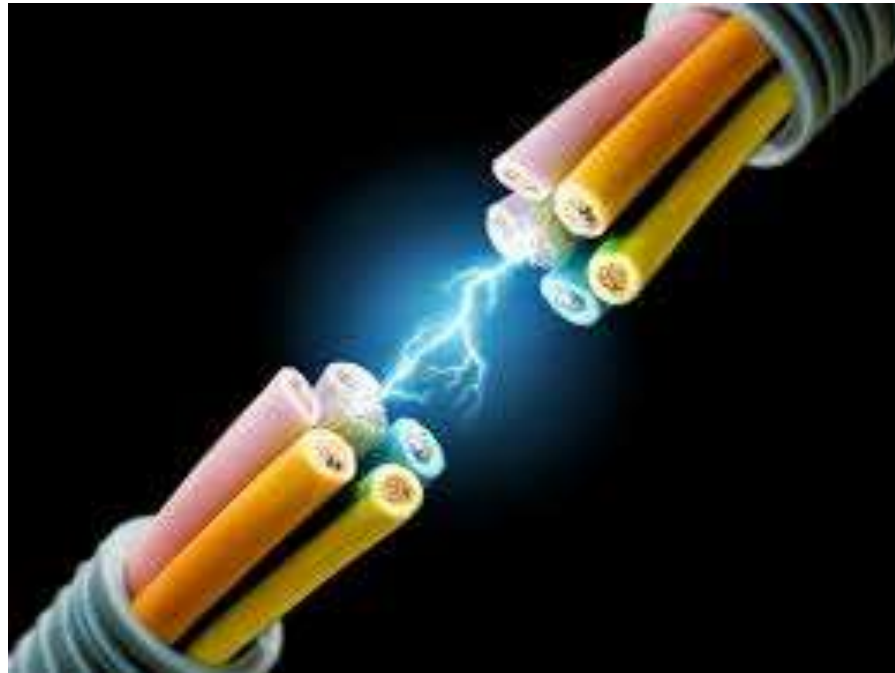

...THANK YOU