



SNS COLLEGE OF TECHNOLOGY


(Affiliated To Anna University, Approved by AICTE - New Delhi)

Accredited by NBA - AICTE and Recognized by UGC

ISO 9001 : 2000 Certified Institution





FUNDAMENTALS OF ELECTRICAL ENGINEERING

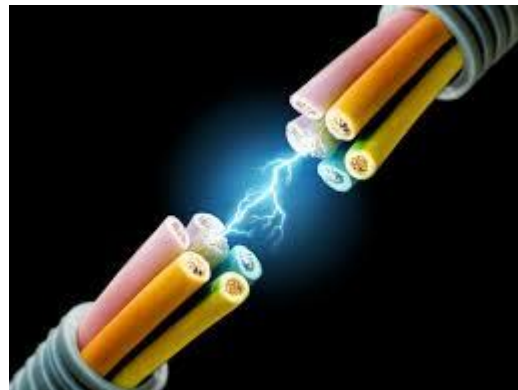

LOAD (POWER CONSUMED)

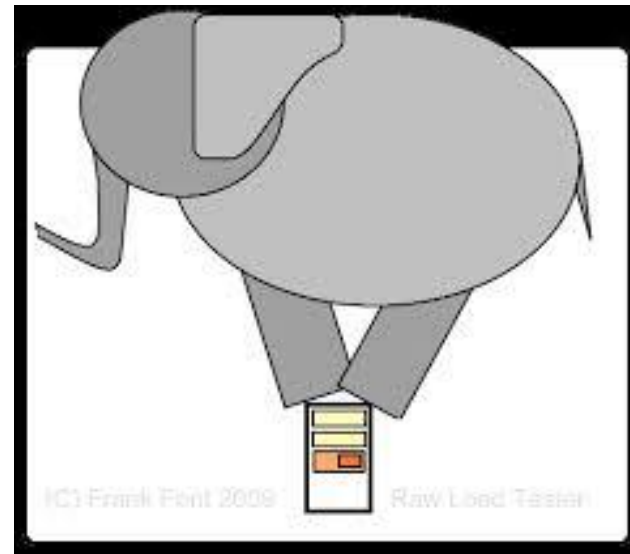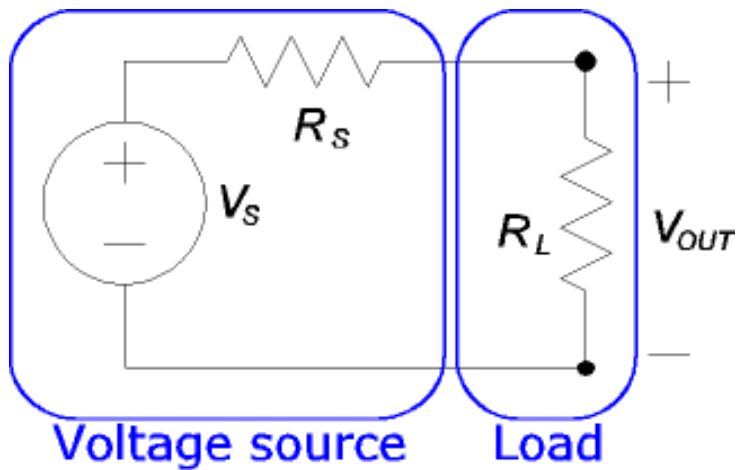- It is a any electric load on a circuit that does work.
- A device connected to the **output of a circuit**
 - **Example:** Power windows, light bulbs, motors.



CIRCUIT

- Source:

A Voltage or a Current source which delivers Electrical energy

- Sink:

A Element which consumes Electrical energy

- Circuit:

Consist of a source and a sink connected with some wires forming a closed loop

CIRCUIT DEFINITIONS

- **Node:**

Any point where 2 or more circuit elements are connected together

- **Branch:**

A circuit element between **two nodes**

- **Loop:**

Collection of branches that form a **closed path** returning to the same node without intersecting


Would This Work?




Would This Work?



Simple Circuits

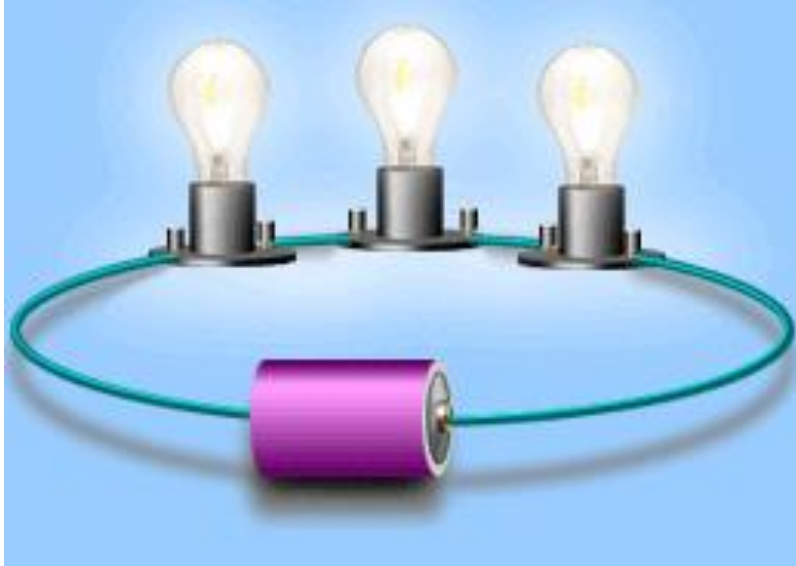

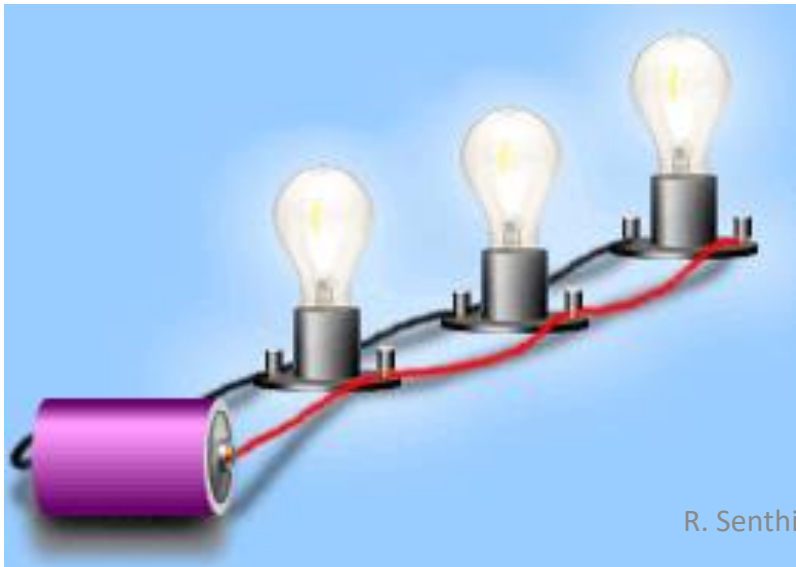- Series circuit
 - All in a row
 - **1 path** for electricity
 - 1 light goes out and the circuit is broken



- Parallel circuit
 - **Many paths** for electricity
 - 1 light goes out and the others stay on

DIFFERENT TYPES OF CIRCUIT


SERIES CIRCUIT

- One pathway for current to flow.
- Example: Old Christmas lights




PARALLEL CIRCUIT

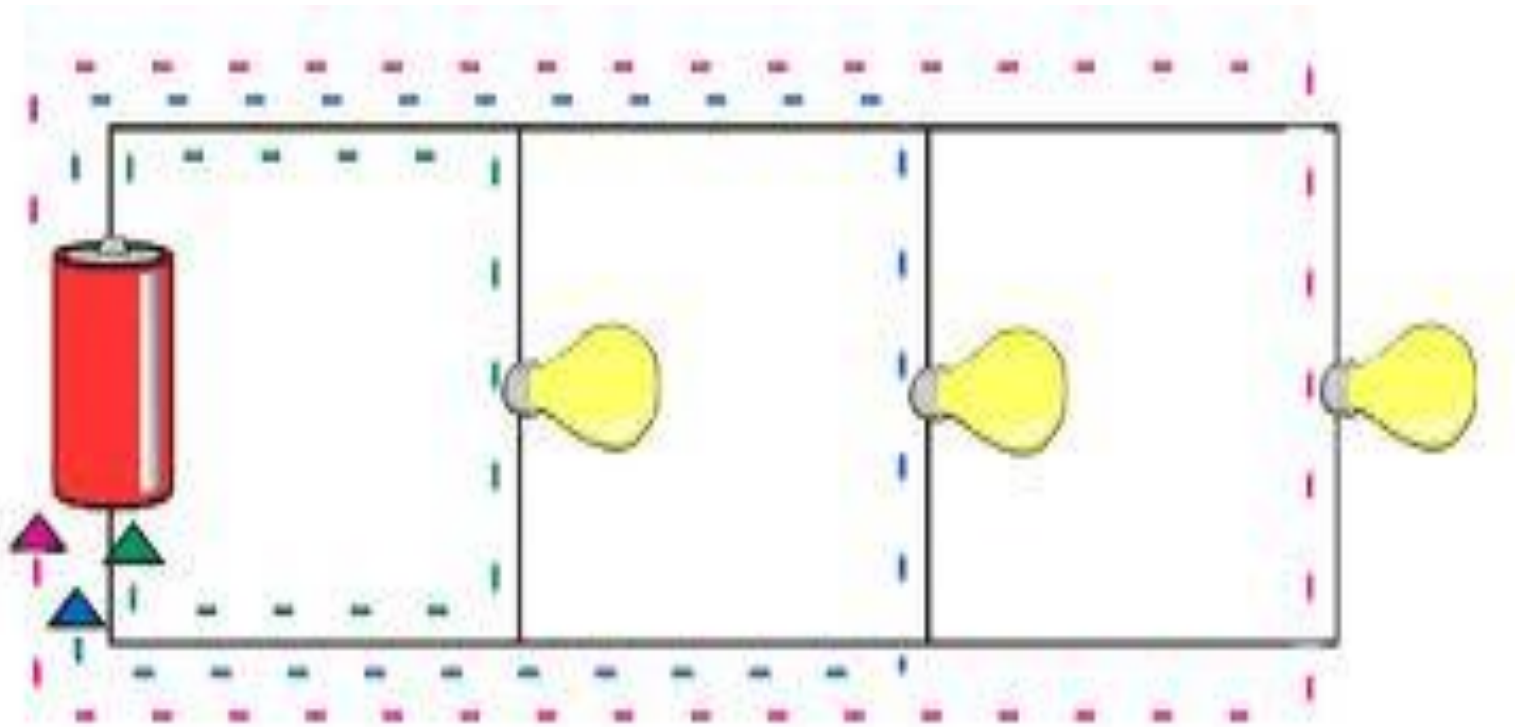- More than one path way for current to flow.
- Used in most **electrical vehicle** circuits.




SERIES RESISTANCE CIRCUIT

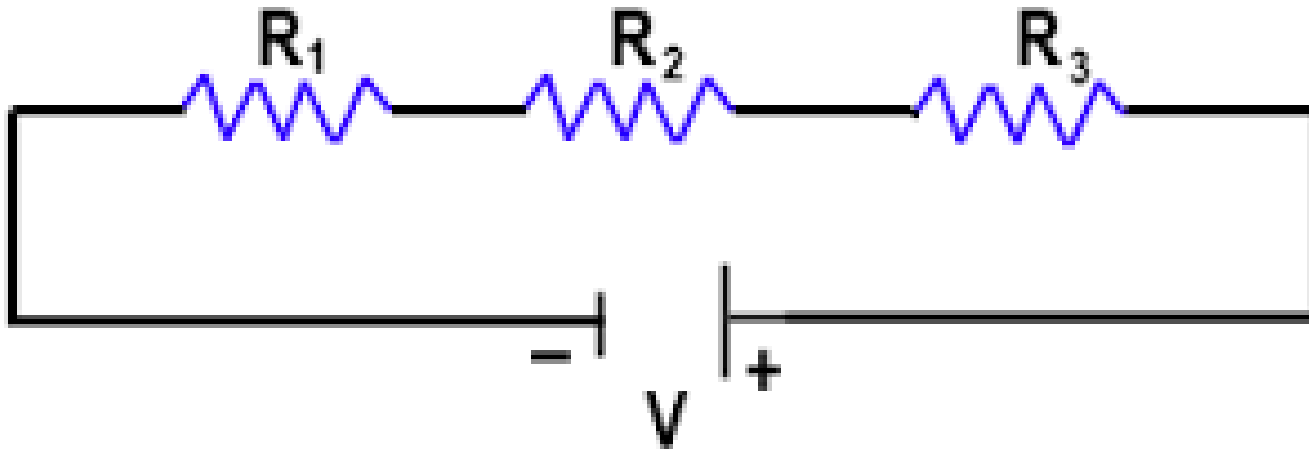

$$R_{\text{total}} = R_1 + R_2 + R_3 \dots$$

PARALLEL RESISTANCE CIRCUIT

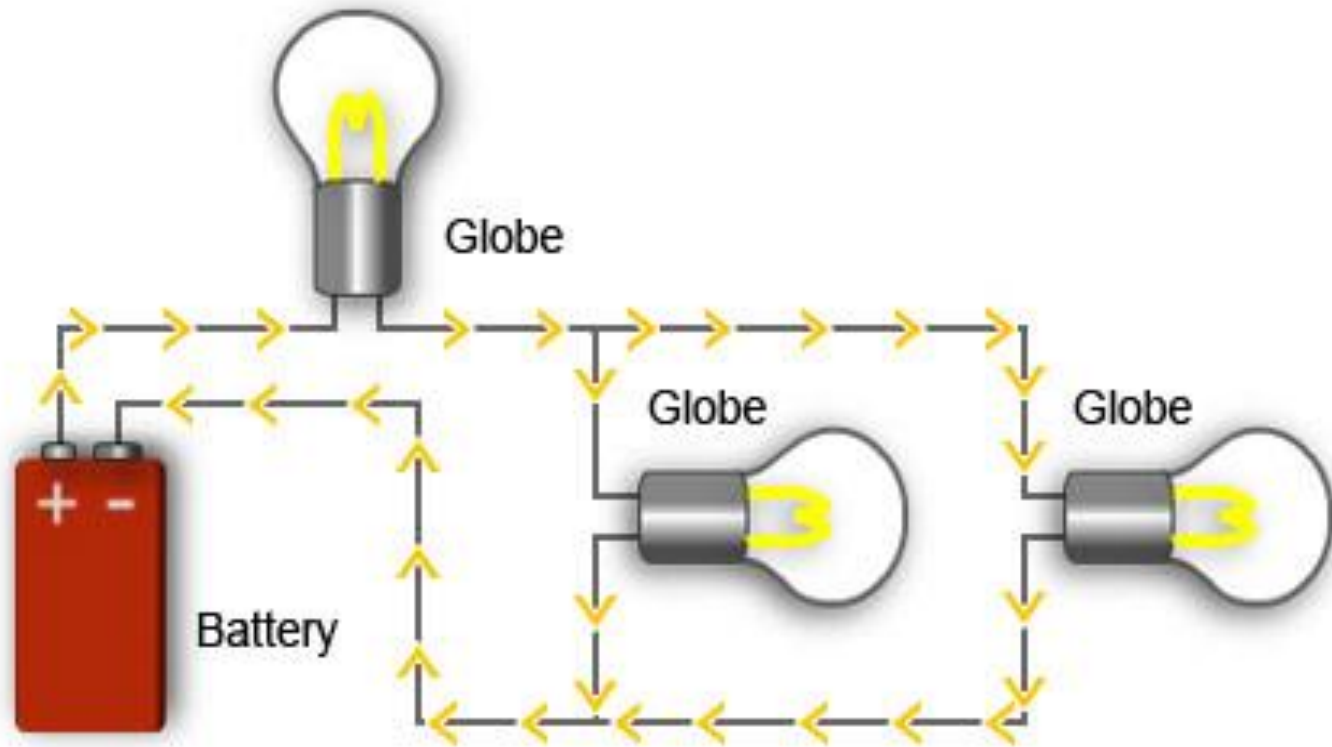


$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \text{etc.}$$

$$R_{TOT} = \frac{R_1 \times R_2}{(R_1 + R_2)}$$


EXAMPLE

- Three nodes

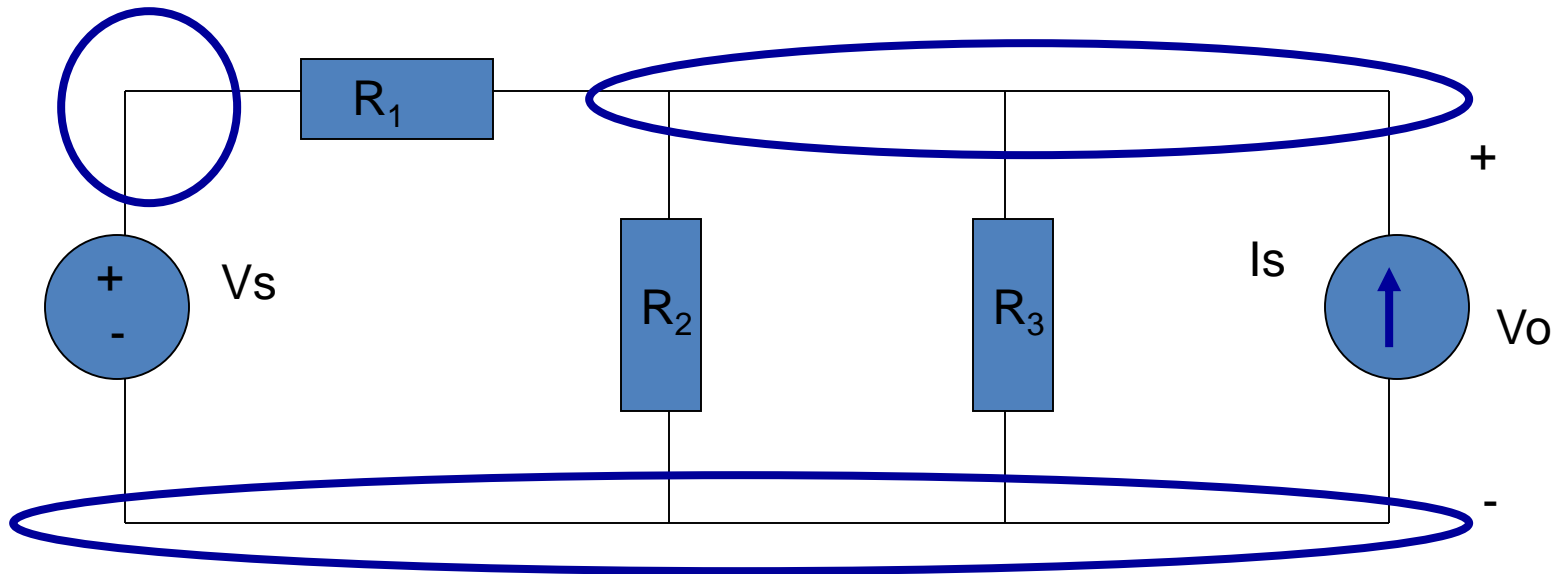


EXAMPLE

- 5 Branches

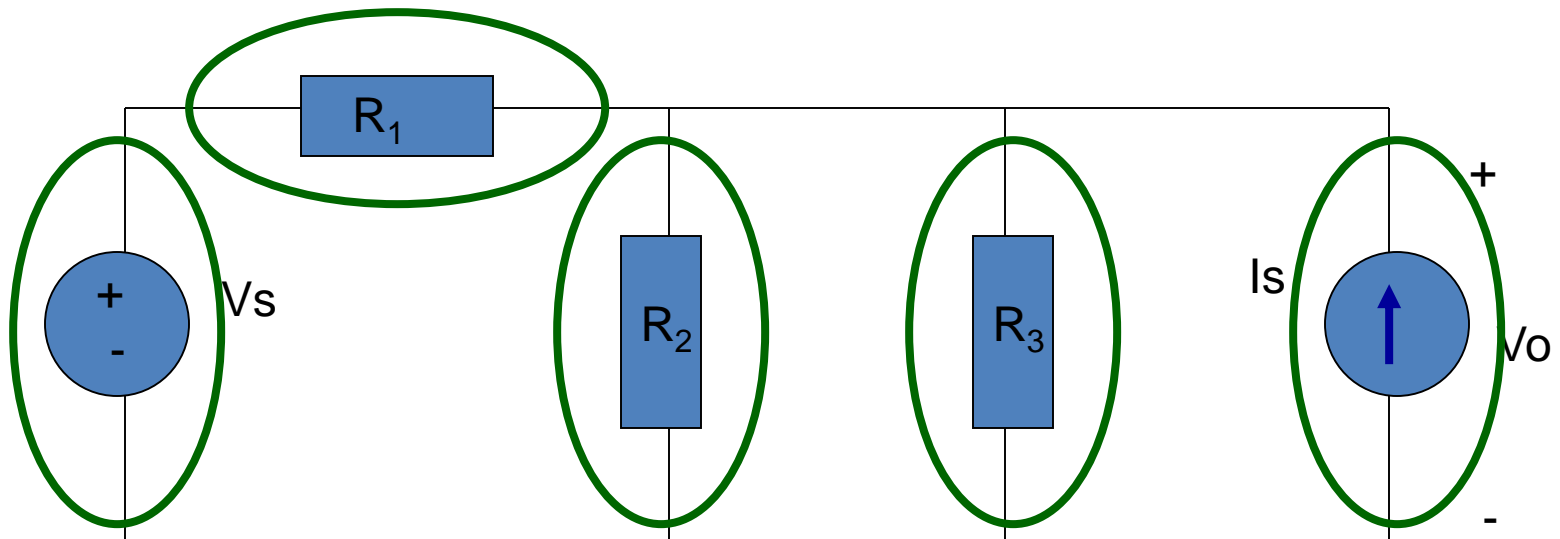

Example

- Three Loops, if starting at node A

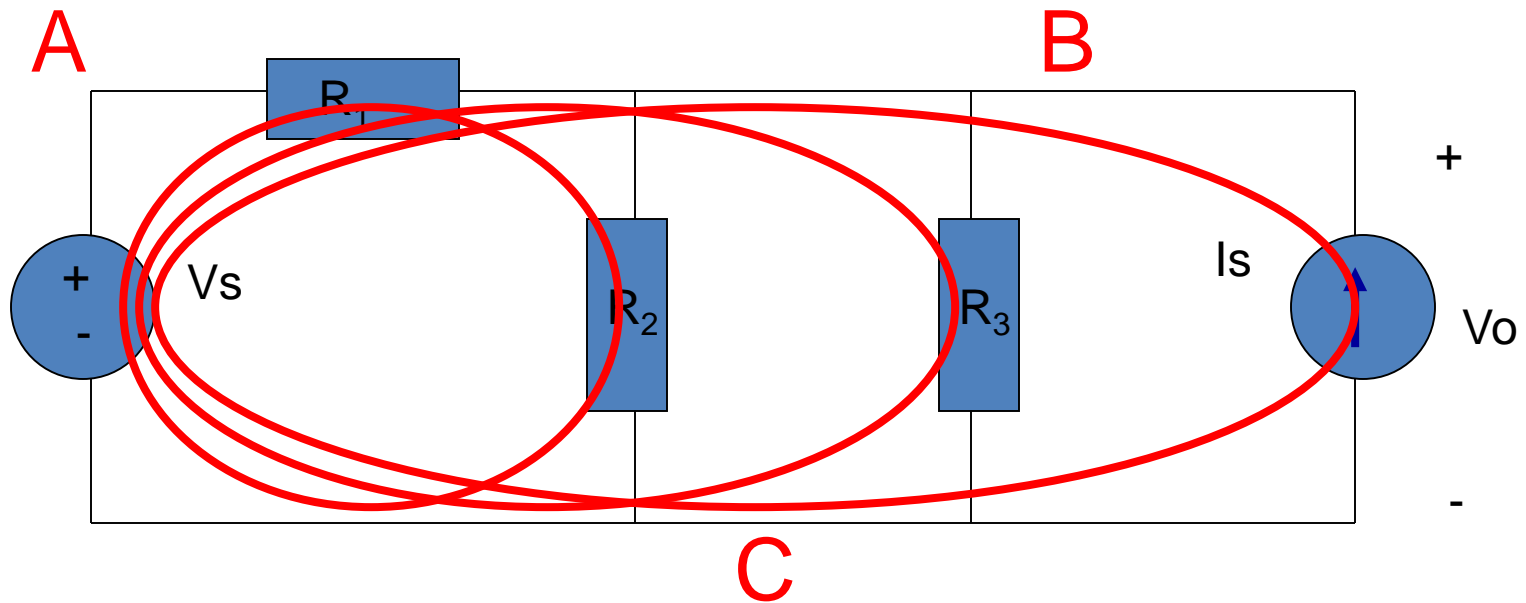

AC FUNDAMENTALS

PARAMETER VALUES:


- Instantaneous (e , i)
- Peak (V_m , I_m)
- Average (V_{ave} , I_{ave})
- RMS (V , I or V_{rms} , I_{rms})

Parameters V and I are in sine wave.

ROOT MEAN SQUARE (RMS)

Definition:

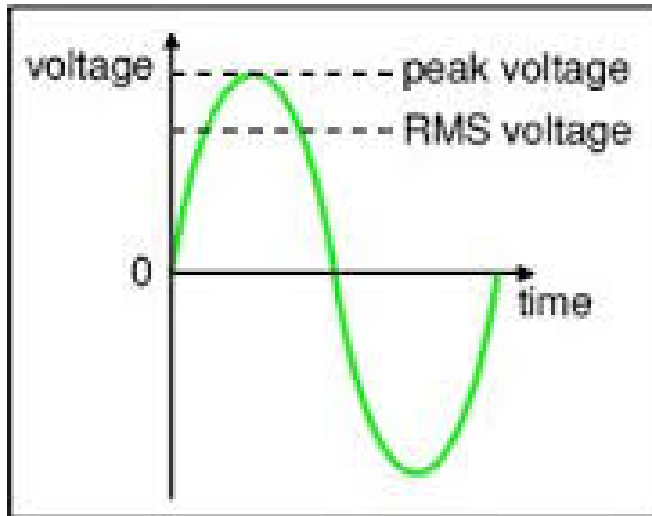The RMS value of a set of values (or a continuous-time waveform) is the **square root** of the arithmetic mean of the squares of the original values.



$$rms = \frac{V_{peak}}{\sqrt{2}} \text{ (for an undistorted sine wave)}$$
$$rms = \frac{V_{peak}}{\sqrt{3}} \text{ (for an undistorted triangle wave)}$$
$$rms = \frac{V_{peak}}{1} \text{ (for a symmetrical square wave)}$$

POWER

- The instantaneous **power** dissipated in a component is a **product of** the instantaneous **voltage** and the instantaneous **current**

$$p = vi$$

- In a **resistive circuit** the voltage and current are in **phase** – calculation of **p is straightforward**
- In **reactive circuits**, there will normally be some phase **shift between v and i** , and calculating the power becomes more complicated

1. POWER IN RESISTOR

- Suppose a voltage $v = V_p \sin \omega t$ is applied across a resistance R . The resultant current i will be

$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R} = I_p \sin \omega t$$

- The result power p will be


$$p = vi = V_p \sin \omega t \times I_p \sin \omega t = V_p I_p (\sin^2 \omega t) = V_p I_p \left(\frac{1 - \cos 2\omega t}{2} \right)$$

- The average value of $(1 - \cos 2\omega t)$ is 1, so

$$\text{Average Power } P = \frac{1}{2} V_p I_p = \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} = VI$$

where V and I are the **RMS voltage and current**

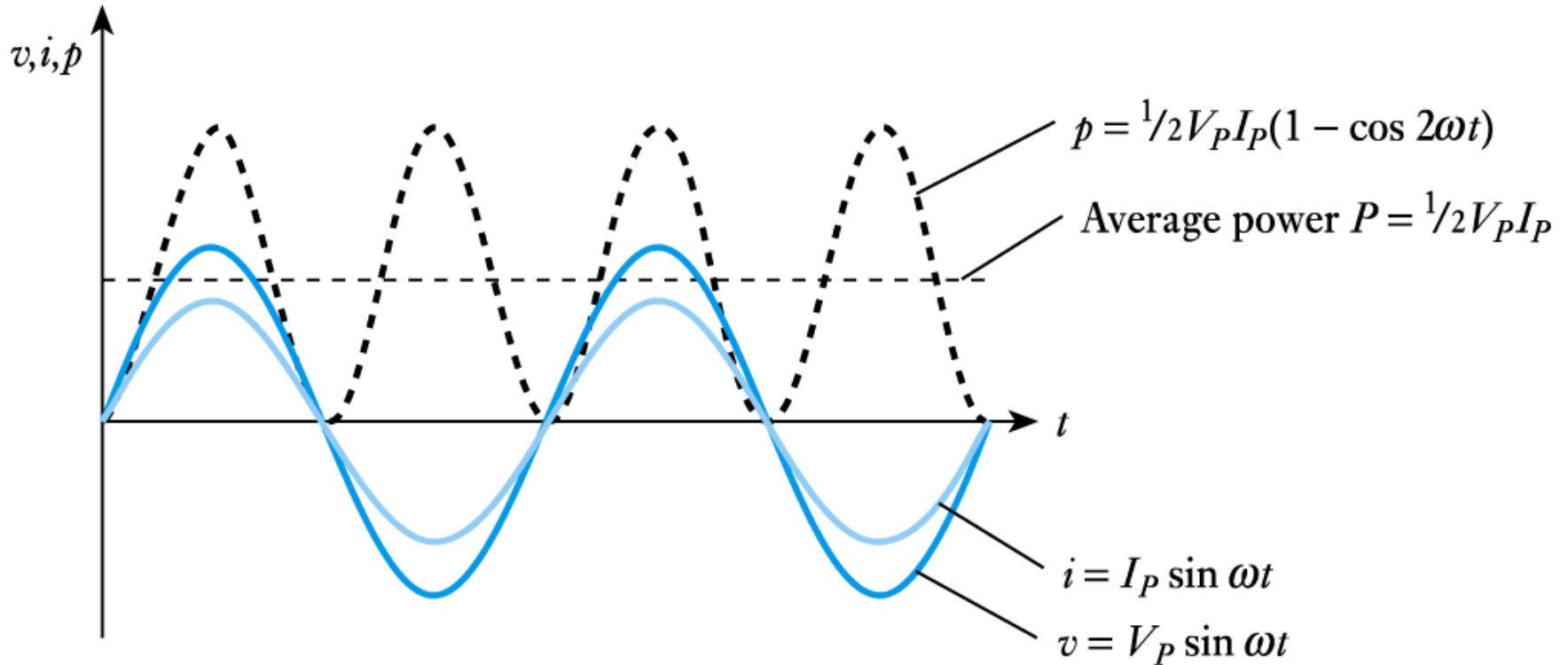RELATIONSHIP BETWEEN V , I AND P IN A RESISTOR




2. POWER IN CAPACITORS

- For capacitors we know that the current leads the voltage by 90° .
- Therefore, if a voltage $v = V_p \sin \omega t$ is applied across a capacitance C , the current will be given by $i = I_p \cos \omega t$

- *Then*
$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times I_p \cos \omega t \\ &= V_p I_p (\sin \omega t \times \cos \omega t) \\ &= V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$

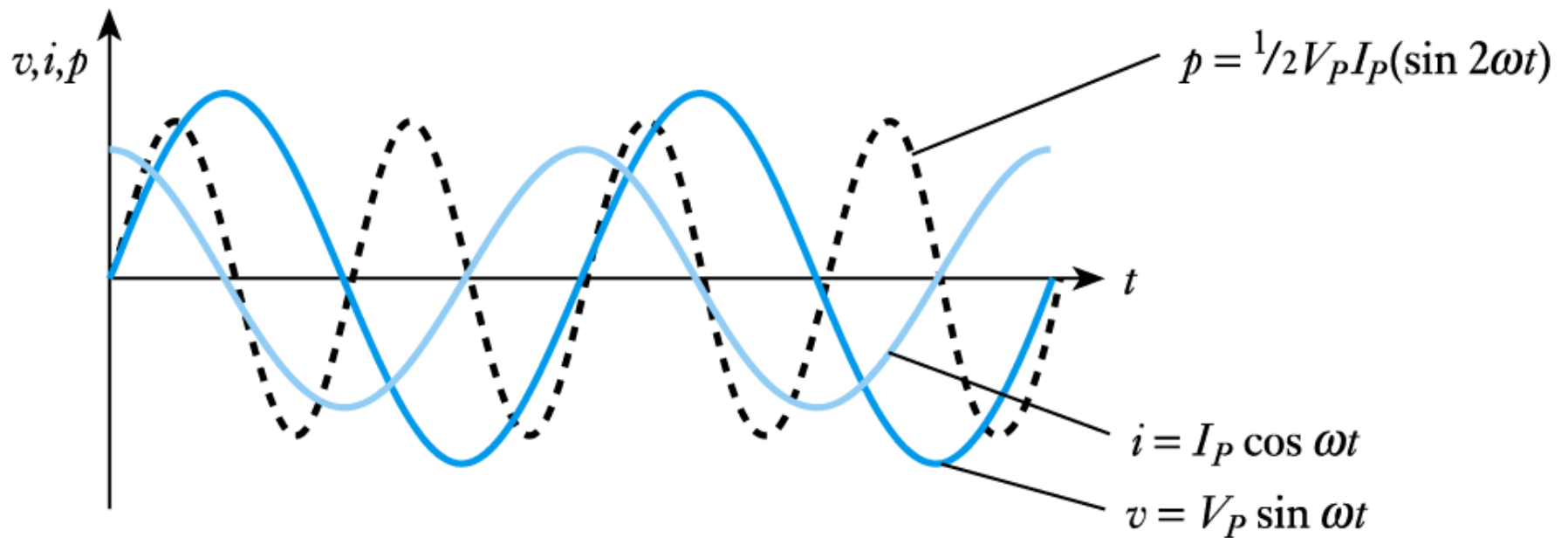RELATIONSHIP BETWEEN V , I AND P IN A CAPACITOR



3.POWER IN INDUCTORS


- For inductors we know that the **current lags the voltage by 90°** .

•Therefore, if a voltage $v = V_p \sin \omega t$ is applied across an inductance L , the current will be given by $i = -I_p \cos \omega t$

•Then


$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times -I_p \cos \omega t \\ &= -V_p I_p (\sin \omega t \times \cos \omega t) \\ &= -V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$

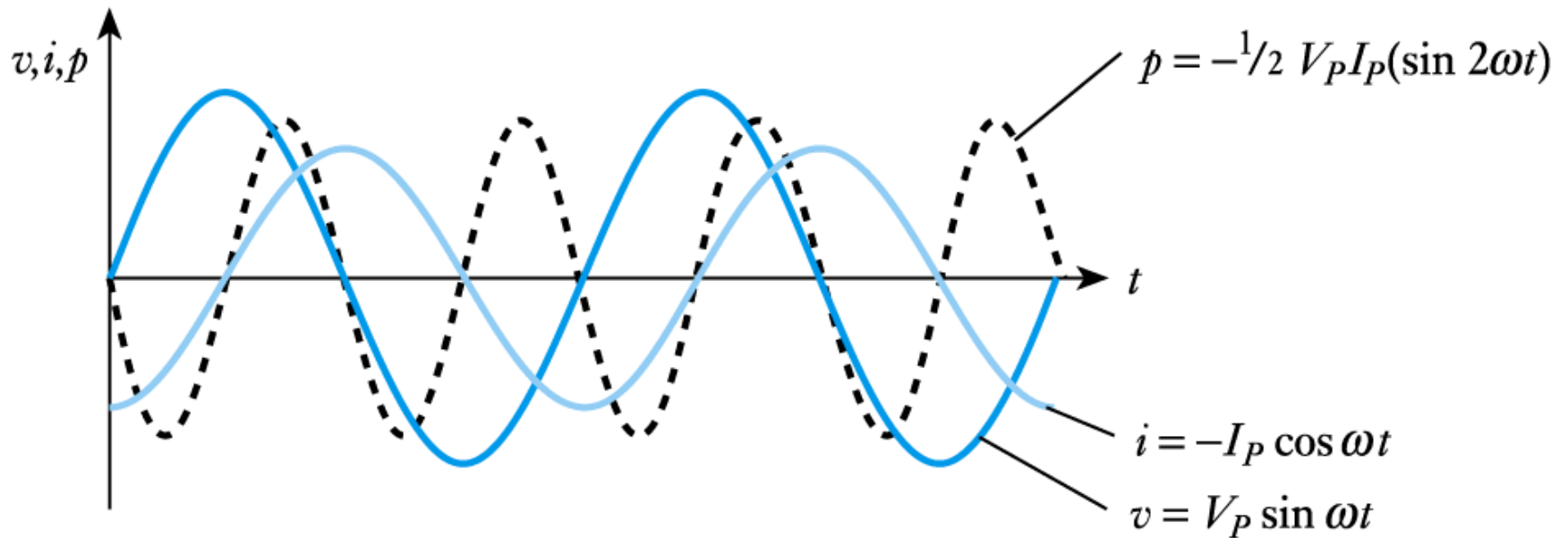RELATIONSHIP BETWEEN V , I AND P IN AN INDUCTOR



ACTIVE AND REACTIVE POWER

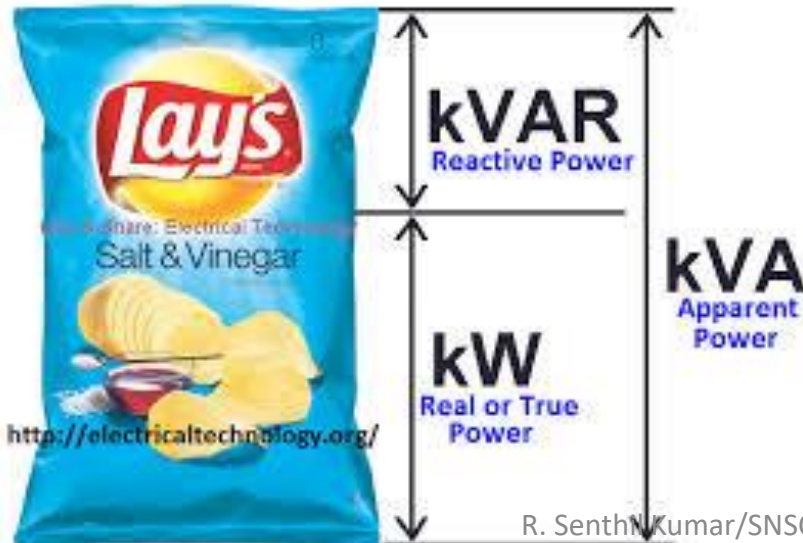- When a circuit has resistive and reactive parts, the resultant power has 2 parts:
 - The first is *dissipated* in the resistive element. This is the **active power, P**
 - The second is *stored and returned* by the reactive element. This is the **reactive power, Q** , which has units of **volt amperes reactive** or **var**



POWERS AND UNITS

Active Power $P = VI \cos \phi$ watts

Reactive Power $Q = VI \sin \phi$ var

Apparent Power $S = VI$ VA


$$S^2 = P^2 + Q^2$$

POWER TRIANGLE

The Power Triangle:



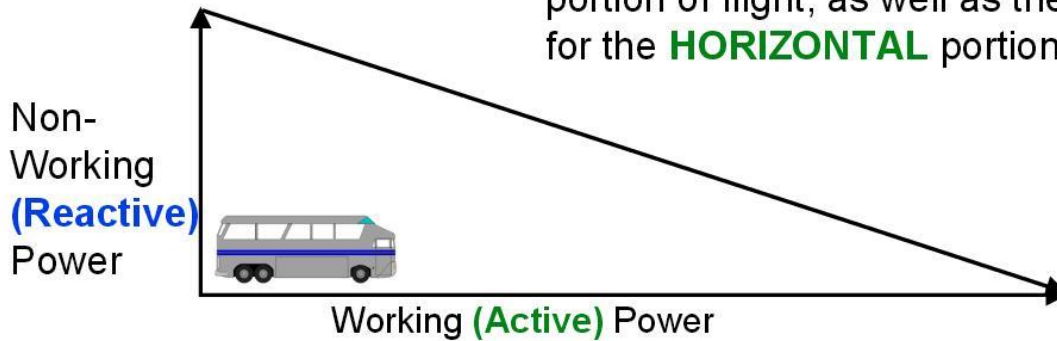You pay for fuel for the **VERTICAL** portion of flight, as well as the fuel for the **HORIZONTAL** portion of flight.



- Power Factor is the ratio of **Active Power** to **Total Power**:

$$\begin{aligned} \text{Power Factor} &= \frac{\text{Active (Real) Power}}{\text{Total Power}} \\ &= \frac{\text{kW}}{\text{kVA}} \\ &= \text{Cosine } (\theta) \end{aligned}$$

- Power Factor is a measure of efficiency (Output/Input)

POWER FACTOR

Definition:

It is the ratio of the **real power** flowing to the load, to the **apparent power** in the circuit (or) the cosine angle of voltage and current

- **Real power** is the capacity of the circuit for performing work in a particular time.
- **Apparent power** is the product of the current and voltage of the circuit

THANK YOU...