



# **SNS COLLEGE OF TECHNOLOGY**

(An Autonomous Institution)

**COIMBATORE-35**

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



**19EEB102 / ELECTRIC CIRCUIT ANALYSIS**

**I YEAR / II SEMESTER**


**UNIT-IV: RESONANCE and COUPLED CIRCUITS**

**COEFFICIENT OF COUPLING**


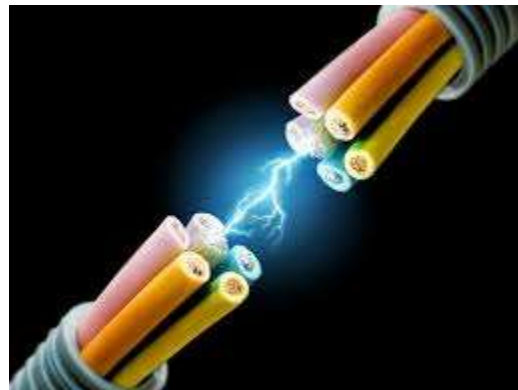
# TOPIC OUTLINE





- Dot Convention
- Coefficient of Coupling
- Problems



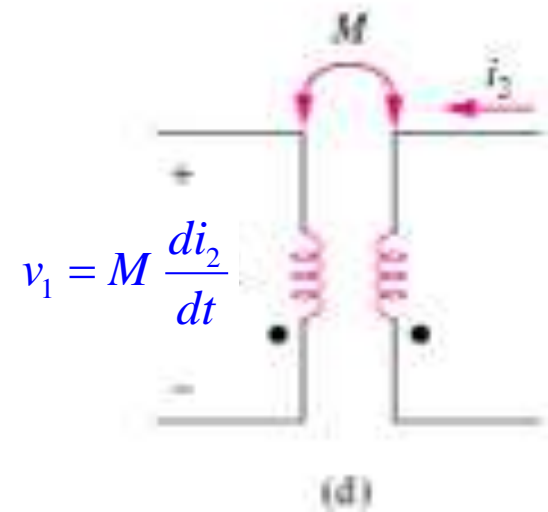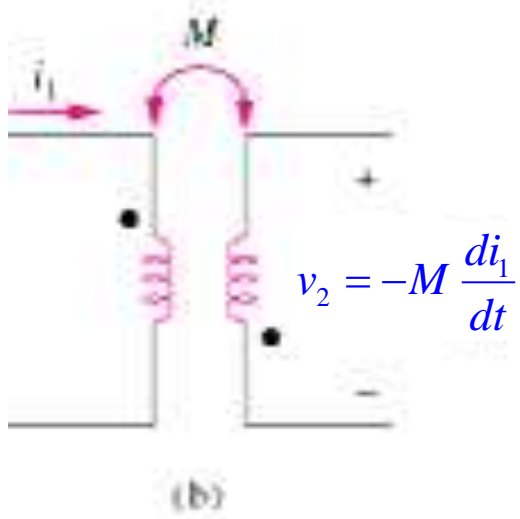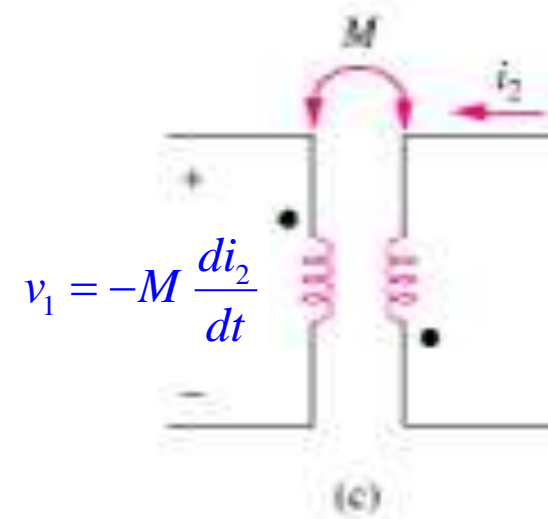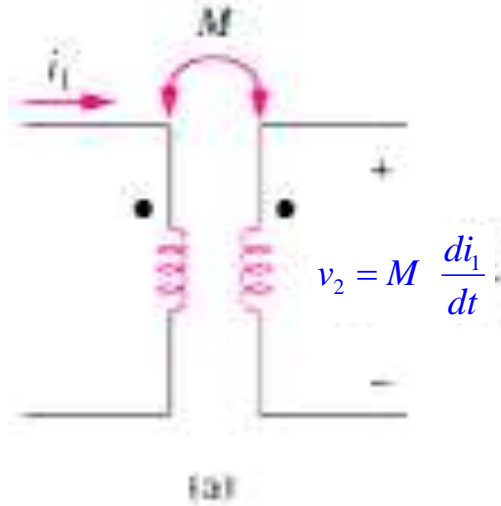
# Dot Convention

➤ If the current **ENTERS** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **POSITIVE** at the dotted terminal of the second coil.

If the current **LEAVES** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **NEGATIVE** at the dotted terminal of the second coil.



# Dot Convention

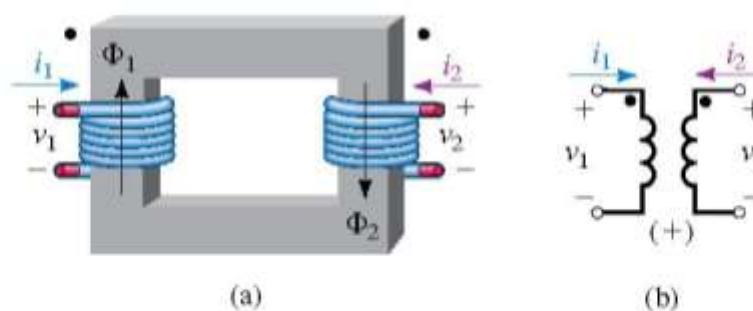

**FIGURE 24-52** When both currents enter dotted terminals, use the + sign for the mutual term in Equation 24-15.


therefore, the voltage across coil 1 is the sum of that produced by  $i_1$  and  $i_2$ . That is,

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad (24-15a)$$

Similarly, for coil 2,

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \quad (24-15b)$$

Now consider Figure 24-53. Here, the fluxes oppose and the flux linking each coil is the *difference* between that produced by its own current and that produced by the current of the other coil. Thus, the sign in front of the mutual voltage terms will be negative.

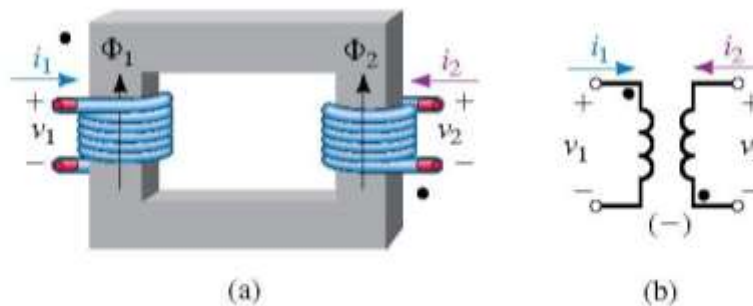


**FIGURE 24-53** When one current enters a dotted terminal and the other enters an undotted terminal, use the - sign for the mutual term in Equation 24-15.

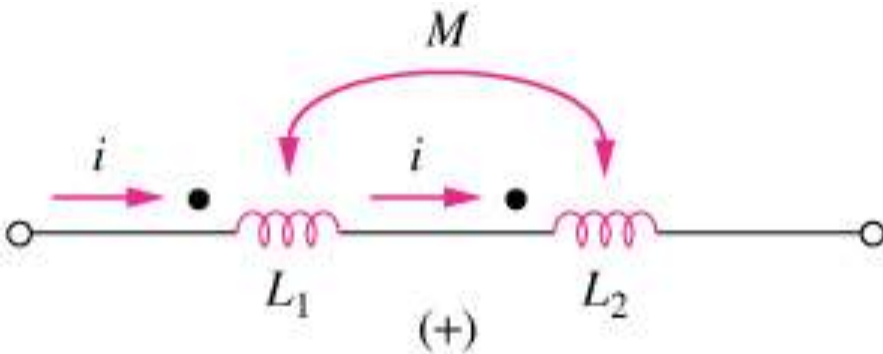


# Coils in Series

➤ The total inductance of two coupled coils in series depend on the placement of the dotted ends of the coils. The mutual inductances may add or subtract.




a) Series-aiding connection.

$$L=L_1+L_2+2M$$

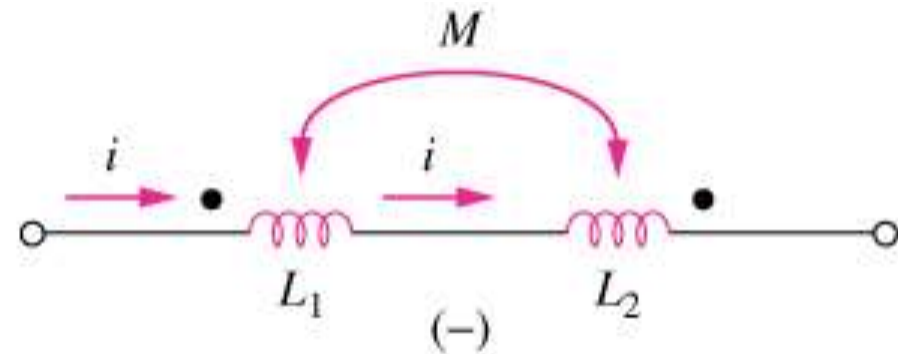


b) Series-opposing connection.

$$L=L_1+L_2-2M$$

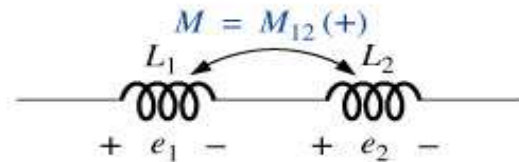


(a)

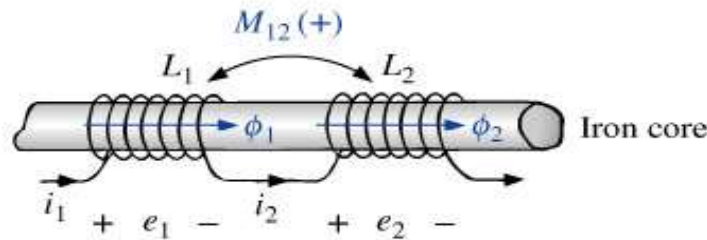

(b)


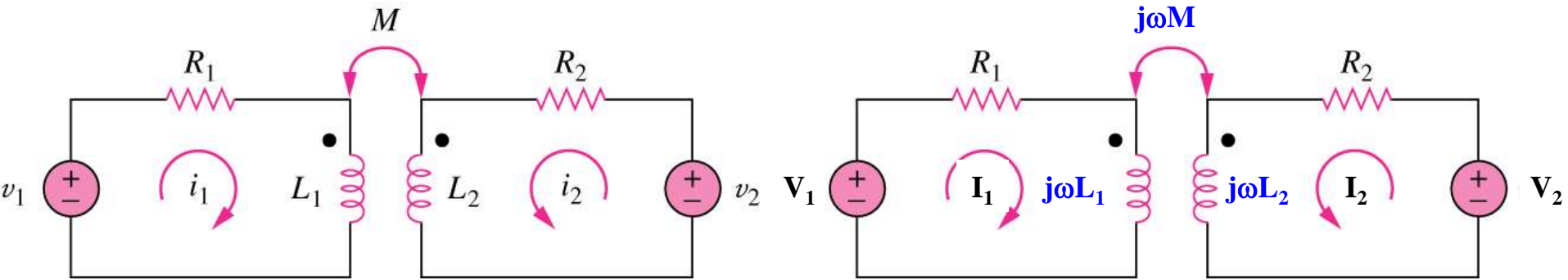
# Time-domain and Frequency-domain Analysis



a) Time-domain circuit

b) Frequency-domain circuit

## Time Domain

$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

## Frequency Domain

$$V_1 = (R_1 + j\omega L_1)I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + (R_2 + j\omega L_2)I_2$$



# Energy in a Coupled Circuit


- The total energy  $w$  stored in a mutually coupled inductor is:
- **Positive sign** is selected if both currents ENTER or LEAVE the dotted terminals.
- Otherwise we use Negative sign.

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$


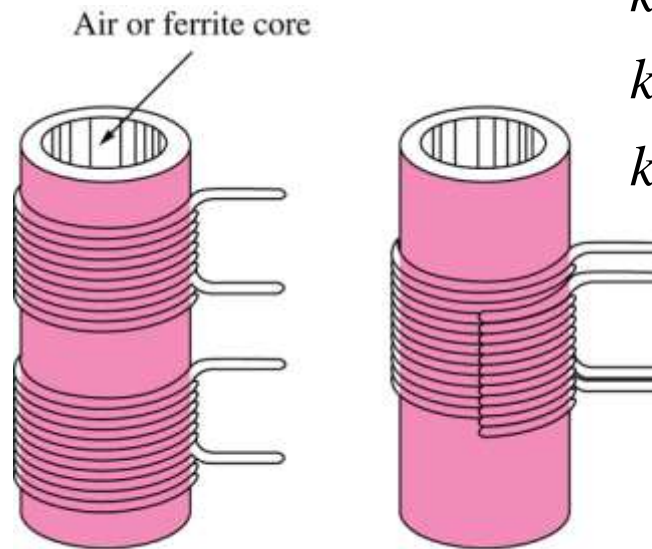
# Coupling Coefficient

- The Coupling Coefficient  $k$  is a measure of the magnetic coupling between two coils  
 $0 \leq k \leq 1$



$k = 1$  Perfect Coupling

$k < 0.5$  Loosly Coupling

$k > 0.5$  Tightly Coupling

a) Loosely coupled coil

b) Tightly coupled coil

$$0 \leq k \leq 1$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$







Circuits

# Thank you

