



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai





19EEB102 / ELECTRIC CIRCUIT ANALYSIS
I YEAR / II SEMESTER
UNIT-V: TRANSIENT CIRCUITS

RC , RLC TRANSIENT FOR DC INPUT



TOPIC OUTLINE

- RC Transient
- RLC Transient

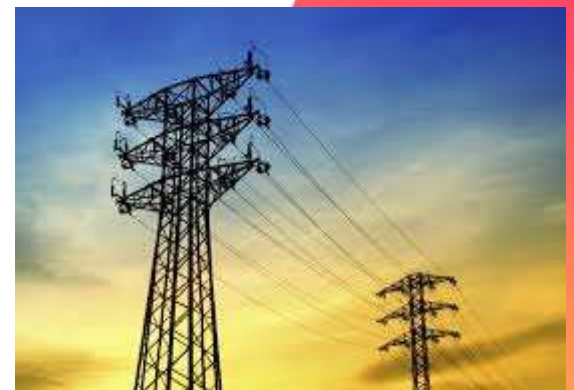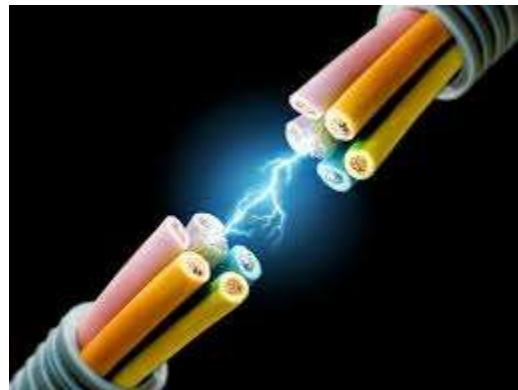

Follow these basic steps to analyze a circuit using Laplace techniques:

- 1 Develop the differential equation in the time-domain using Kirchhoff's laws and element equations.
- 2 Apply the Laplace transformation of the differential equation to put the equation in the s -domain.
- 3 Algebraically solve for the solution, or response transform.
- 4 Apply the inverse Laplace transformation to produce the solution to the original differential equation described in the time-domain.


Transient Analysis of series RC Circuit (Differential Approach)

Consider a series RC circuit as shown in Fig. 10.124. The switch is closed at time $t = 0$. The capacitor is initially uncharged.

Applying KCL to the circuit for $t > 0$,

$$\frac{V - V_s}{R} = -C \frac{dv}{dt}$$
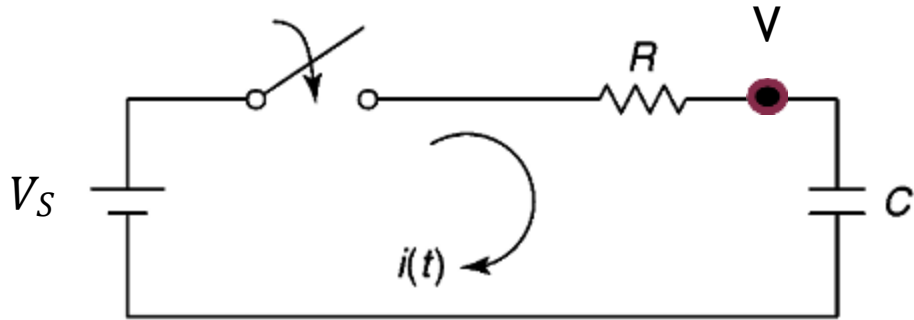
$$\frac{-1}{RC} \cdot dt = \frac{1}{V - V_s} dv$$



Integrating both sides =>

$$\frac{-1}{RC} \int_0^t (1) dt = \int_0^{V(t)} \frac{1}{V - V_s} dv$$

$$\frac{-1}{RC} [t - 0] = \ln(V - V_s) \Big|_0^{V(t)}$$

$$\frac{-t}{RC} = \ln[V(t) - V_s] - \ln[-V_s]$$



$$= \ln\left[\frac{V(t) - V_s}{-V_s}\right] = \ln\left[\frac{V_s - V(t)}{V_s}\right]$$

$$\frac{V_s - V(t)}{V_s} = e^{-t/RC}$$

$$V_s - V(t) = V_s e^{-t/RC}$$

$$V(t) = V_s [1 - e^{-t/RC}]$$
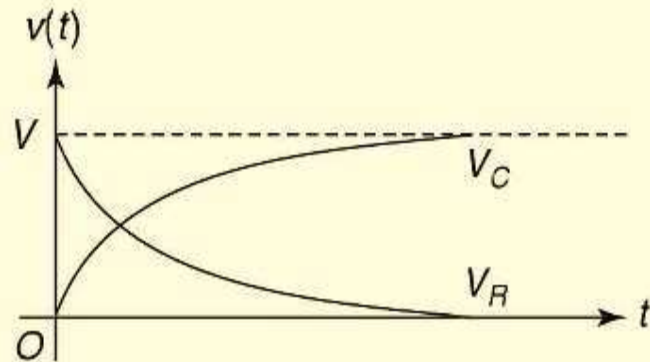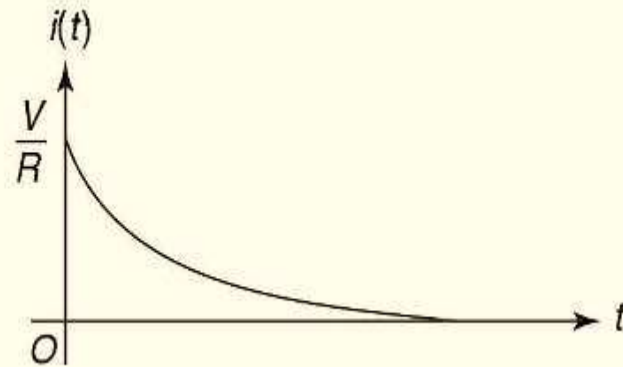
$$i = \frac{V_s}{R} e^{-\frac{1}{RC}t} \quad \text{for } t > 0$$




Transient Analysis of series RC Circuit (Laplace Approach)

Consider a series RC circuit as shown in Fig. 10.124. The switch is closed at time $t = 0$. The capacitor is initially uncharged.

Applying KCL to the circuit for $t > 0$,

$$\frac{V - V_s}{R} = -C \frac{dv}{dt}$$

$$V - V_s = -RC \frac{dv}{dt}$$

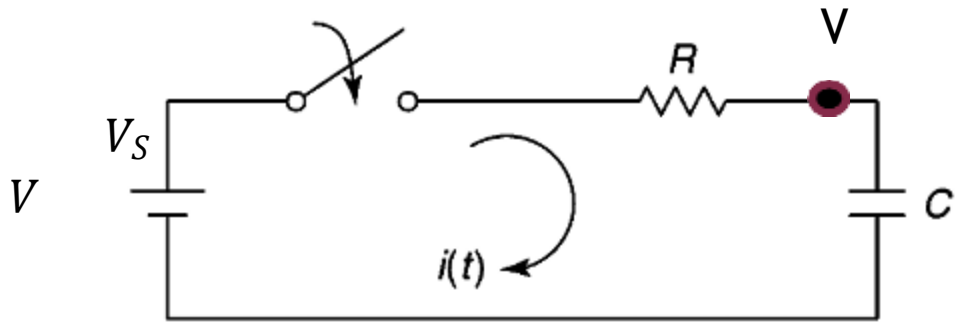

$$\text{Applying Laplace} \Rightarrow V(S) - \frac{V_s}{S} = -RC[S V(S)]$$



$$V(S)[1 + SCR] = \frac{V_s}{S}$$

$$V(S) = \frac{V_s}{S(1 + SCR)} = \frac{V_s}{RC} \frac{1}{S(S + \frac{1}{RC})}$$

$$= \left[\frac{1}{S} - \frac{1}{S + \frac{1}{RC}} \right]$$

$$= V_s \left[\frac{1}{S} - \frac{1}{S + \frac{1}{RC}} \right]$$
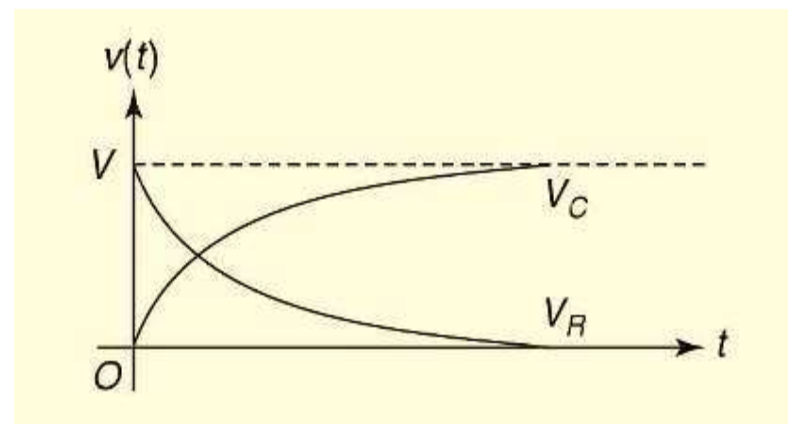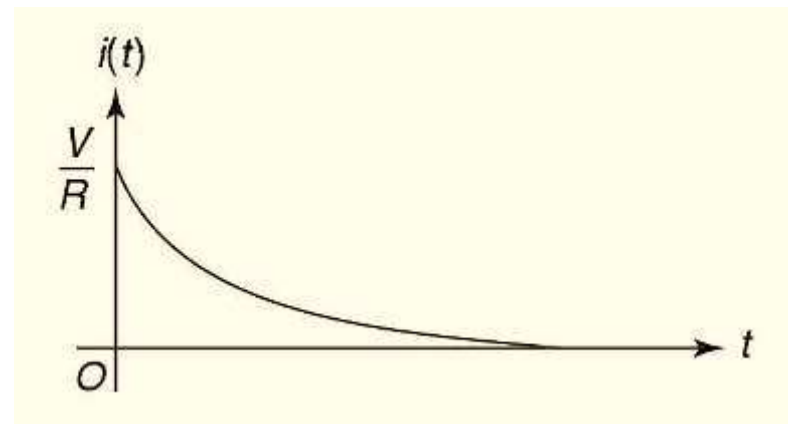
$$= V_s \left[\frac{1}{S} - \frac{1}{S + \frac{1}{RC}} \right]$$




$$V(t) = V_s [1 - e^{-t/RC}]$$

$$i = \frac{V}{R} e^{-\frac{1}{RC}t} \quad \text{for } t > 0$$

Transient Analysis of series RLC Circuit (Differential Approach)

Equation of RLC Circuit

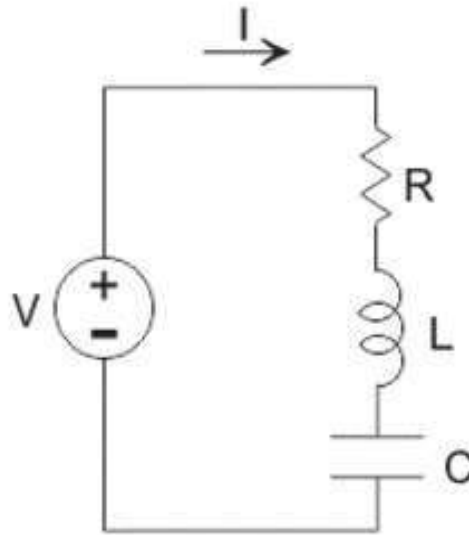Consider a **RLC circuit** having resistor R, inductor L, and capacitor C connected in series and are driven by a **voltage source** V. Let Q be the charge on the capacitor and the current flowing in the circuit is I. Apply **Kirchhoff's voltage law**



$$L.I'(t) + Q.I(t) + \frac{1}{C}Q(t) = V(t)$$

In this equation; resistance, **inductance**, **capacitance** and voltage are known quantities but current and charge are unknown quantities. We know that an current is a rate of electric charge flowing, so it is given by

$$\frac{dQ}{dt}(t) = I(t) \text{ or } I(t) = Q'(t)$$

Differentiating again $I'(t) = Q''(t)$

$$L.Q''(t) + R.Q'(t) + \frac{1}{C}Q(t) = V(t)$$

Differentiating the above equation with respect to 't' we get,

$$L.I''(t) + R.I'(t) + \frac{1}{C}I(t) = V'(t)$$

Now at time $t = 0$, $V(0) = 0$ and at time $t = t$, $V(t) = E_0 \sin \omega t$

Differentiating with respect to 't' we get $V'(t) = \omega E_0 \cos \omega t$

Substitute the value of $V'(t)$ in above equation

$$L.I''(t) + R.I'(t) + \frac{1}{C}I(t) = \omega E_0 \cos \omega t$$

Let us say that the solution of this equation is $I_p(t) = A \sin(\omega t - \phi)$ and if $I_p(t)$ is a solution of above equation then it must satisfy this equation,

$$L.I_p(t) + R.I_p(t) + \frac{1}{C}I_p(t) = \omega E_0 \cos \omega t$$

$$-L\omega^2 A \sin(\omega t - \phi) + R\omega A \cos(\omega t - \phi) + \frac{1}{C} A \sin(\omega t - \phi) = \omega E_o \cos \omega t$$

$$-L\omega^2 A \sin(\omega t - \phi) + R\omega A \cos(\omega t - \phi) + \frac{1}{C} A \sin(\omega t - \phi) = \omega E_o \cos(\omega t - \phi + \phi)$$

Apply the formula of $\cos(A + B)$ and combine similar terms we get,

$$\begin{aligned} & \left(\frac{1}{C} - L\omega^2 \right) A \sin(\omega t - \phi) + R\omega A \cos(\omega t - \phi) \\ & = \omega E_o \cos \phi \cos(\omega t - \phi) - \omega E_o \sin \phi \sin(\omega t - \phi) \end{aligned}$$

Match the coefficient of $\sin(\omega t - \phi)$ and $\cos(\omega t - \phi)$ on both sides we get,

$$\left(-\frac{1}{C} + 2L\omega \right) A = \omega E_o \sin \phi \text{ and } R\omega A = \omega E_o \cos \phi$$

Now we have two equations and two unknowns i.e ϕ and A , and by dividing the above two equations we get,

$$\tan \phi = \frac{-\frac{1}{C} + 2L\omega}{R\omega}$$

Squaring and adding above equation, we get

$$A \sqrt{\left(-\frac{1}{C} + 2L\omega\right)^2 + (R\omega)^2} = \omega E_0$$

$$\text{or } A = \frac{\omega E_0}{\sqrt{\left(-\frac{1}{C} + 2L\omega\right)^2 + (R\omega)^2}}$$

Analysis of RLC Circuit Using Laplace Transformation

Step 1 : Draw a phasor diagram for given circuit.

Step 2 : Use Kirchhoff's voltage law in RLC series circuit and current law in RLC parallel circuit to form differential equations in the time-domain.


Step 3 : Use **Laplace transformation** to convert these differential equations from time-domain into the s-domain.

Step 4 : For finding unknown variables, solve these equations.

Step 5 : Apply inverse Laplace transformation to convert back equations from s-domain into time domain.



RECAP....

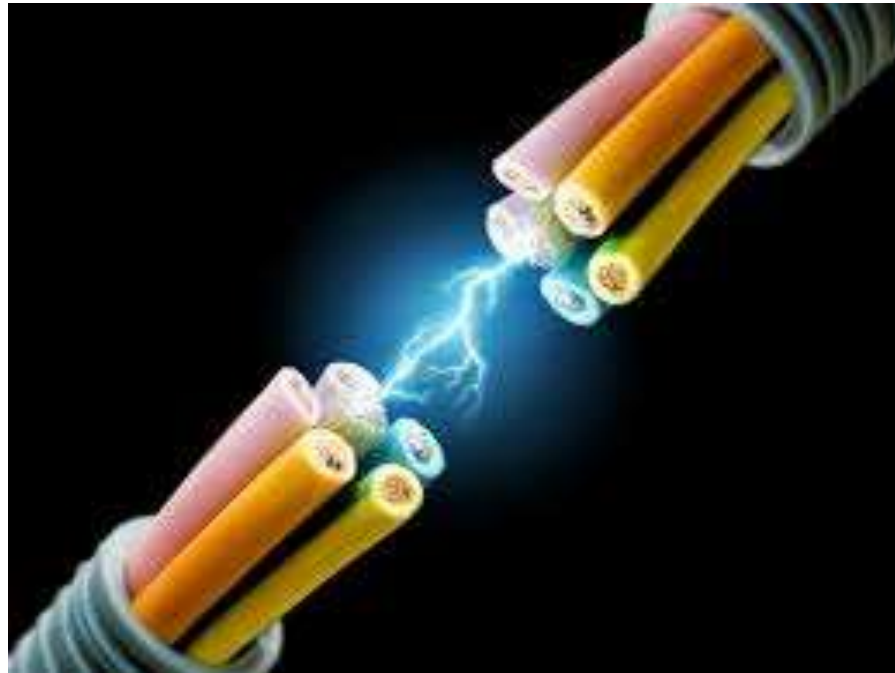

...THANK YOU