



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

**Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai**



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COURSE NAME: 19EET302/ Power System 1

III YEAR / V SEMESTER

Unit 2 – POWER SYSTEM MODELLING


Topic 1: Modelling of medium transmission lines-Nominal T method






What We'll Discuss

TOPIC OUTLINE

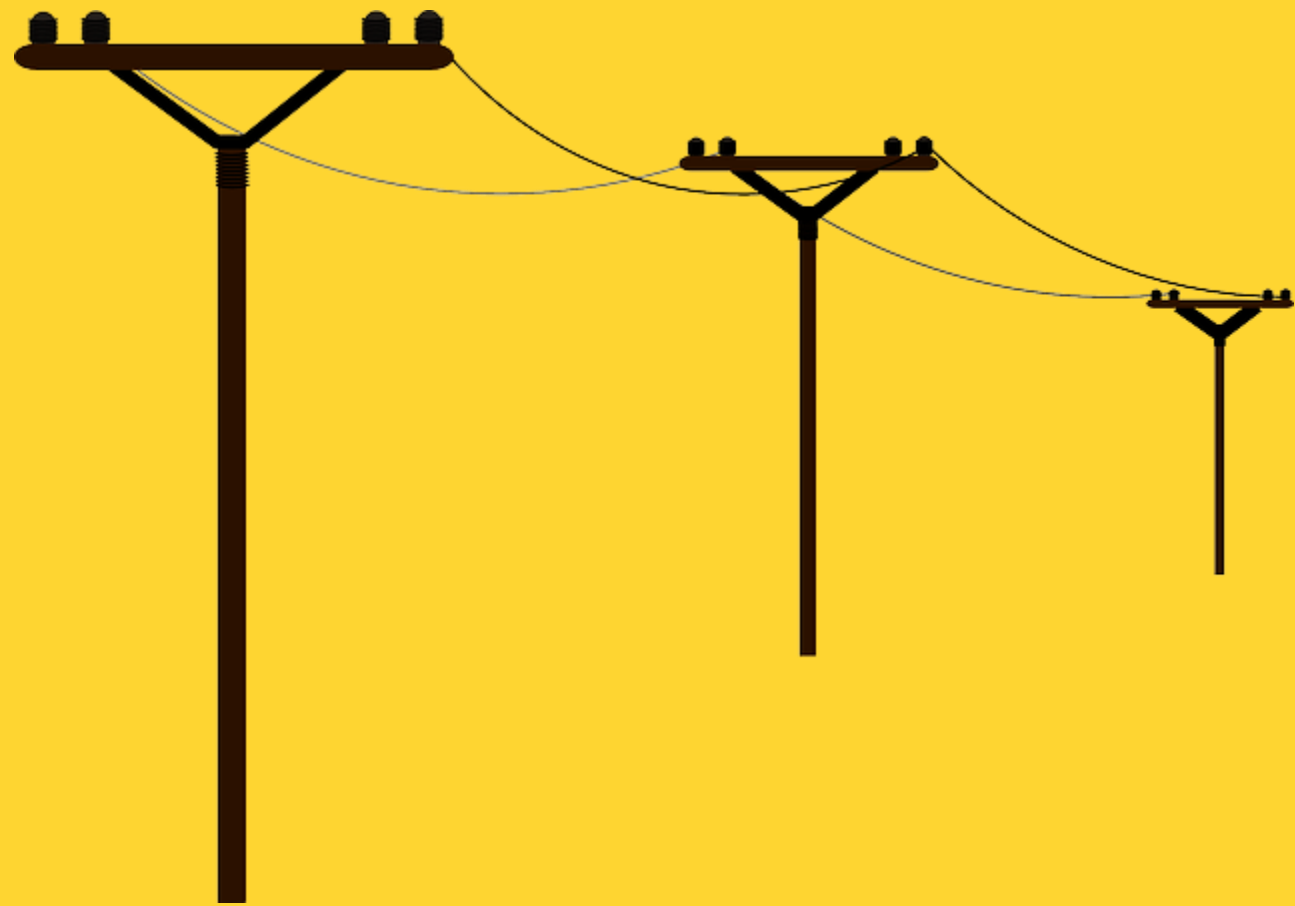

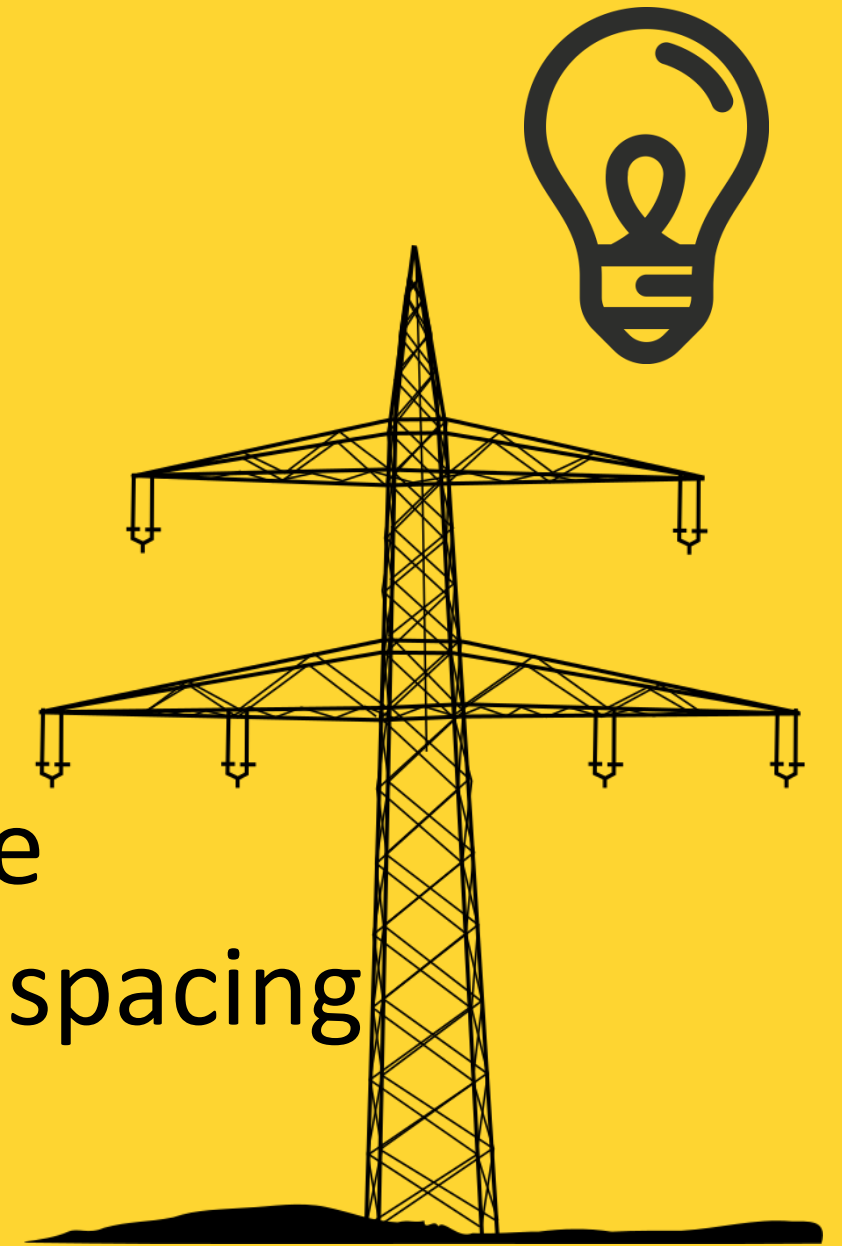- Guess the topic
- Inductance of Three phase overhead line Symmetrical spacing
- Applications






Medium Lines - Nominal T Model




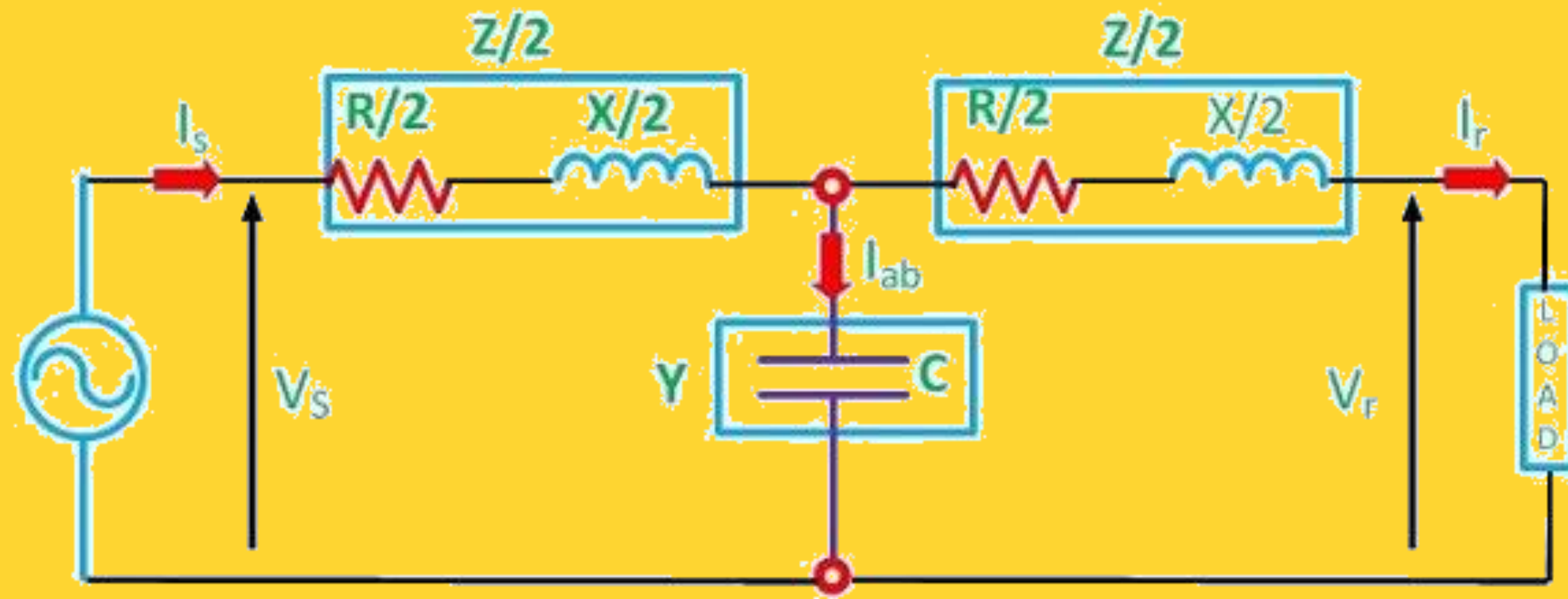In a nominal T model of a medium transmission line, the series impedance is divided into two equal parts, while the shunt admittance is concentrated at the centre of the line.



Nominal T model of a Medium Line

Circuit Globe

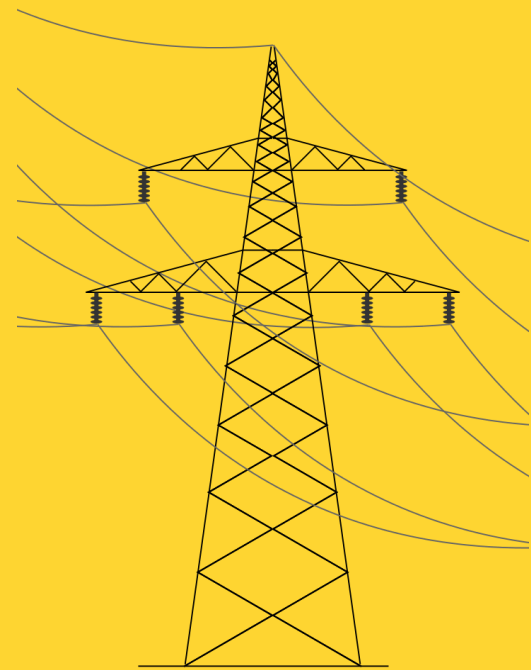



Medium Lines - Nominal T Model



Sending end voltage and current can be obtained by application of KVL and KCL. to the circuit shown below

$$V_{ab} = V_r + \frac{Z}{2} I_r$$

Current in the capacitor can be given as,


$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = Y Z_{ab}$$

$$I_s = I_r + I_{ab}$$

By Kirchoff's current law at node a,

$$I_s = I_r + Y V_{ab}$$
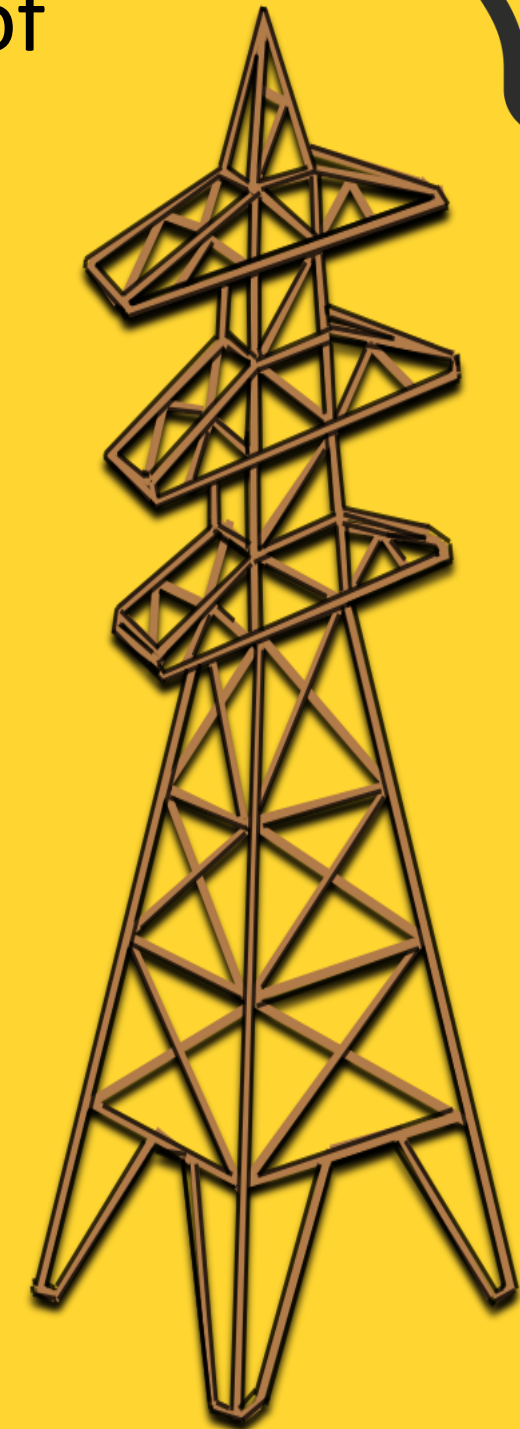
$$I_s = I_r + Y \left(V_r + \frac{Z}{2} I_r \right)$$





Medium Lines - Nominal T Model



By Kirchoff's voltage law

$$V_s = V_{ab} + \frac{Z}{2} I_s$$

$$V_s = V_r + \frac{Z}{2} I_r + \frac{Z}{2} \left[Y V_r + \left(1 + \frac{ZY}{2} \right) I_r \right]$$

Equation of Sending end voltage V_s and current I_s can be written in the matrix form

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \left(1 + \frac{ZY}{4} \right) \\ Y & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_r \\ I_r \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$A = D = 1 + \frac{ZY}{2}$$

$$B = Z \left(1 + \frac{ZY}{4} \right)$$

$$C = Y$$


Hence, the ABCD constant of the nominal T-circuit model of a medium line are



Phasor Diagram - Nominal T Model




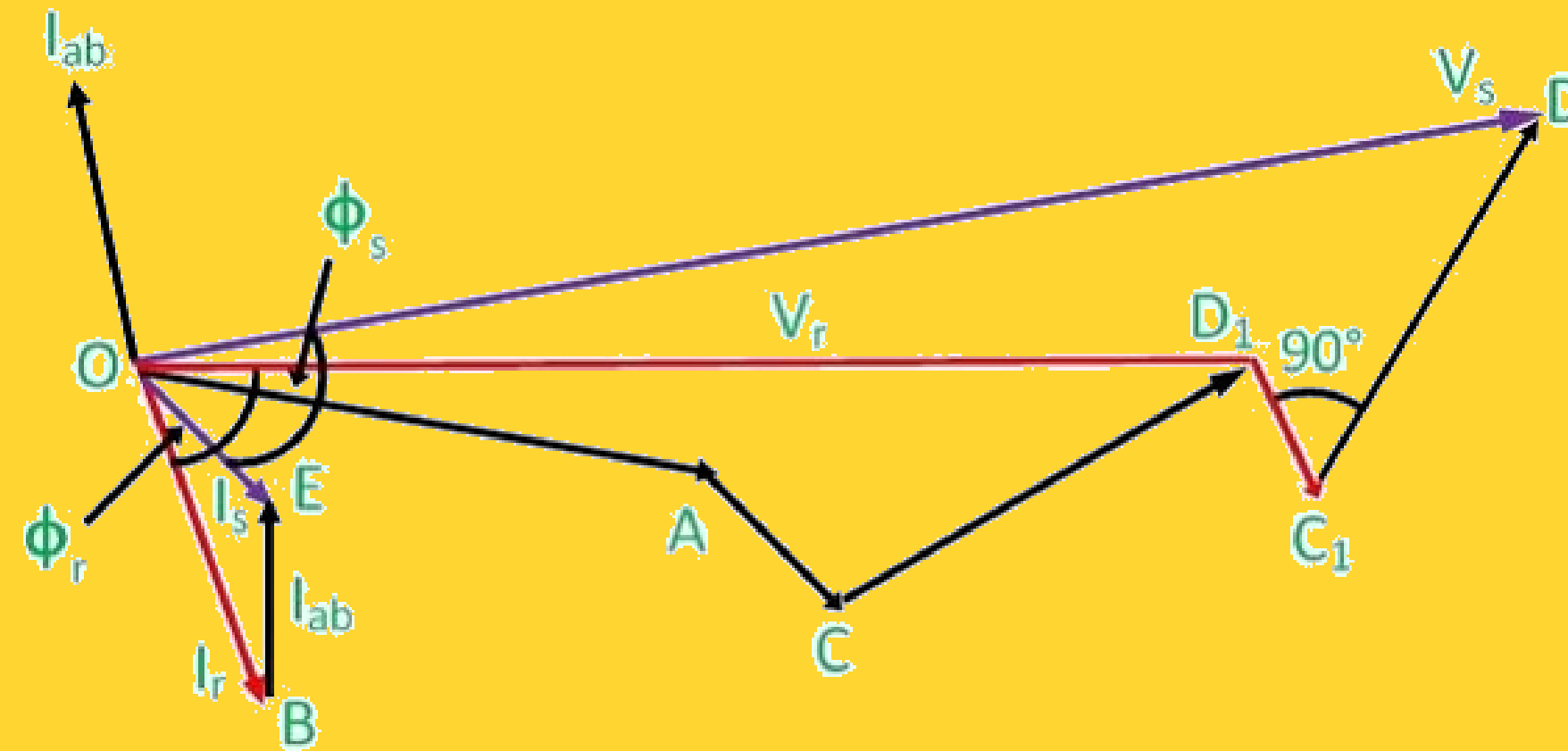The phasor diagram of the nominal T-circuit is shown below. It is drawn for a lagging power factor.



Phasor diagram of a nominal T network

Circuit Globe

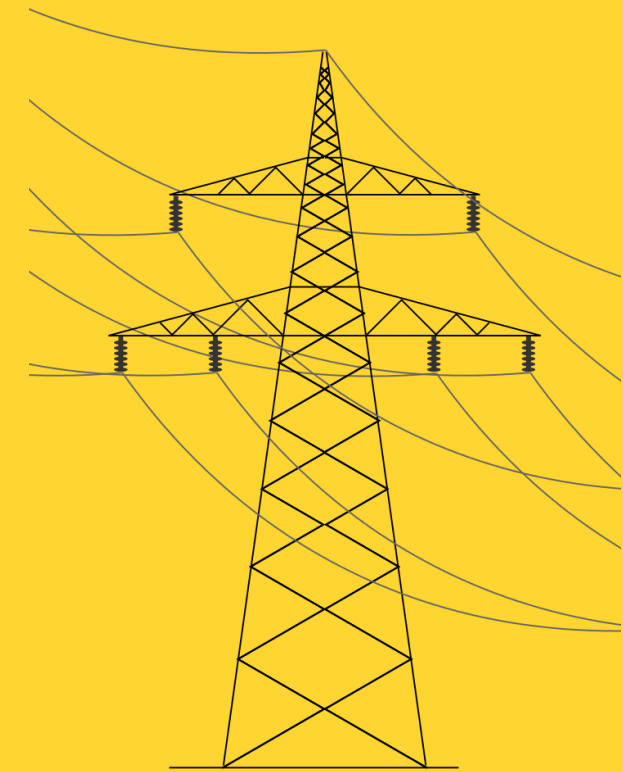



Phasor Diagram Parameters



$OA = V_r$ – receiving end voltage to neutral. taken as a reference phasor.

$OB = I_r$ – load current lagging behind V_r by an angle ϕ .

$AC = I_r R/2$ – Voltage drop in the reactance of the right-hand half of the line.

$OD1 = V_{ab}$ – voltage at the midpoint of the line across the capacitance C .

$BE = I_{ab}$ – current in the capacitor. It leads the voltage V_{ab} by 90°

$OE = I_s$ -sending-end current, the phasor sum of load current and capacitor current.



Phasor Diagram Parameters




$D1C1 = I_s R/2$ – voltage drop in the resistance on the left-hand side of the lines

$C1D = I_s X/2$ – voltage drop in the reactance in the left half of the line.



$OD = V_s$ – sending end voltage. It is the phasor sum of the of V_{ab} and the impedance voltage drop in the left-hand half of the line

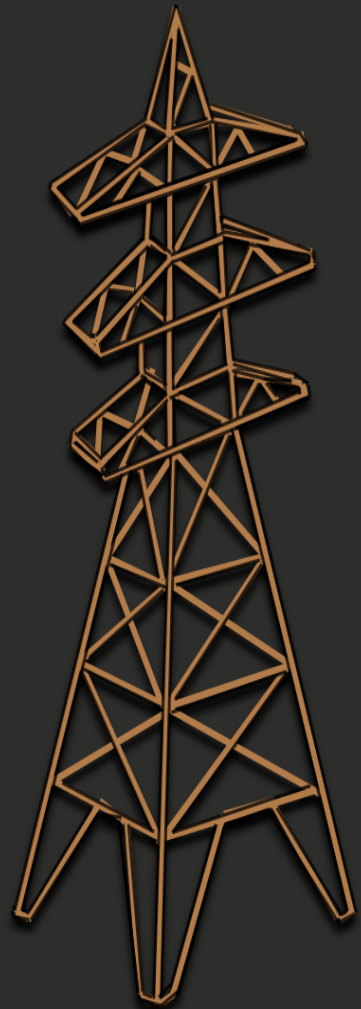ϕ_s – phase angle at the sending end. $\cos\phi_s$ is the power factor at the sending end of the line..





FROM THEORY TO PRACTICE

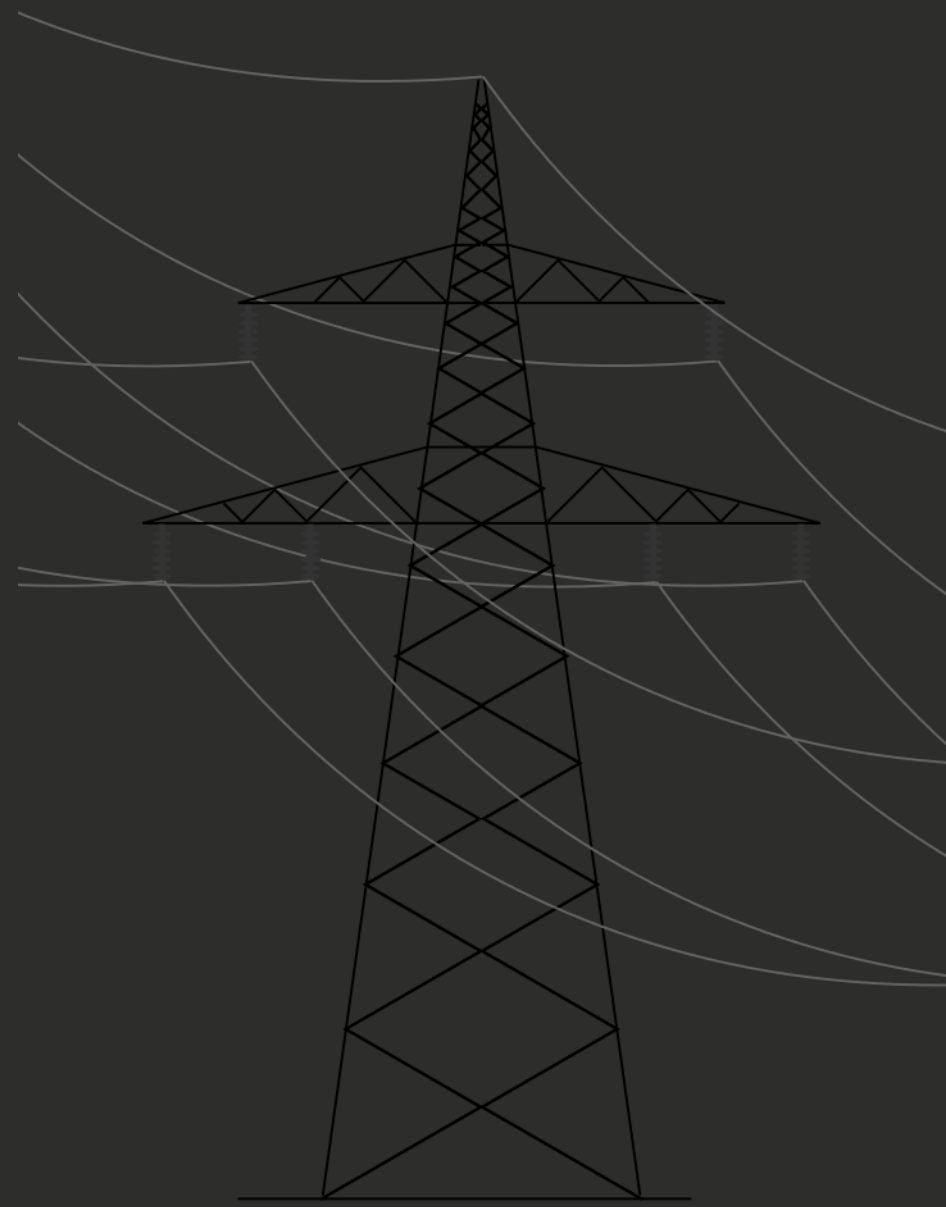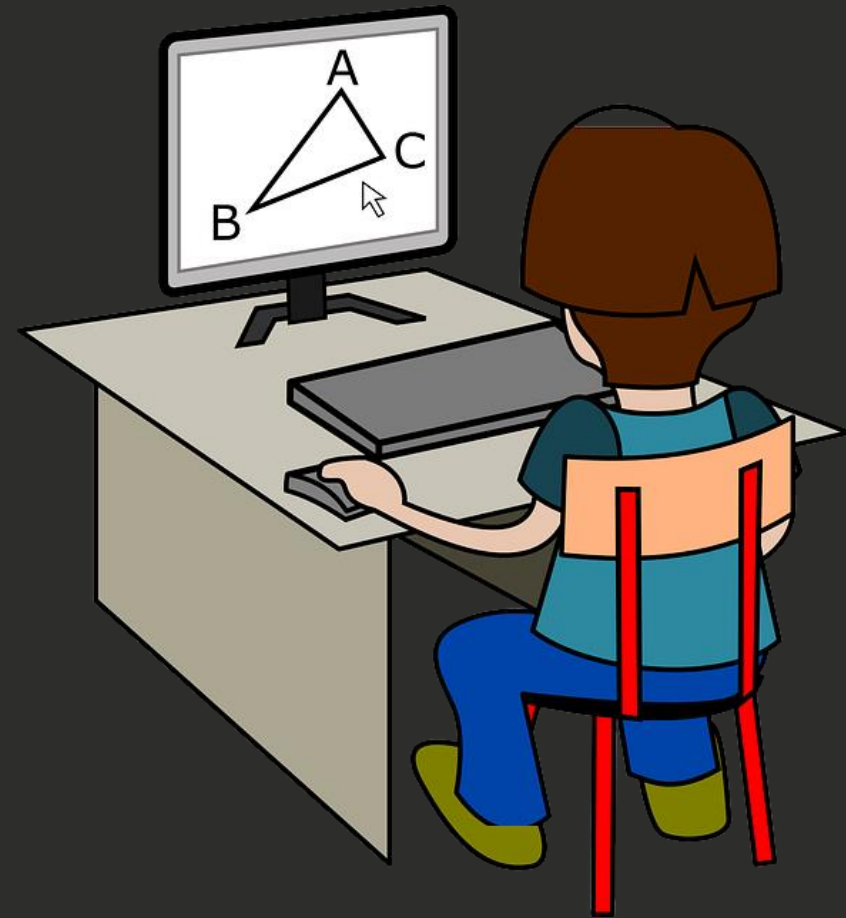


Practical
Applications



RECALL TIME



ASSESSMENT
TIME

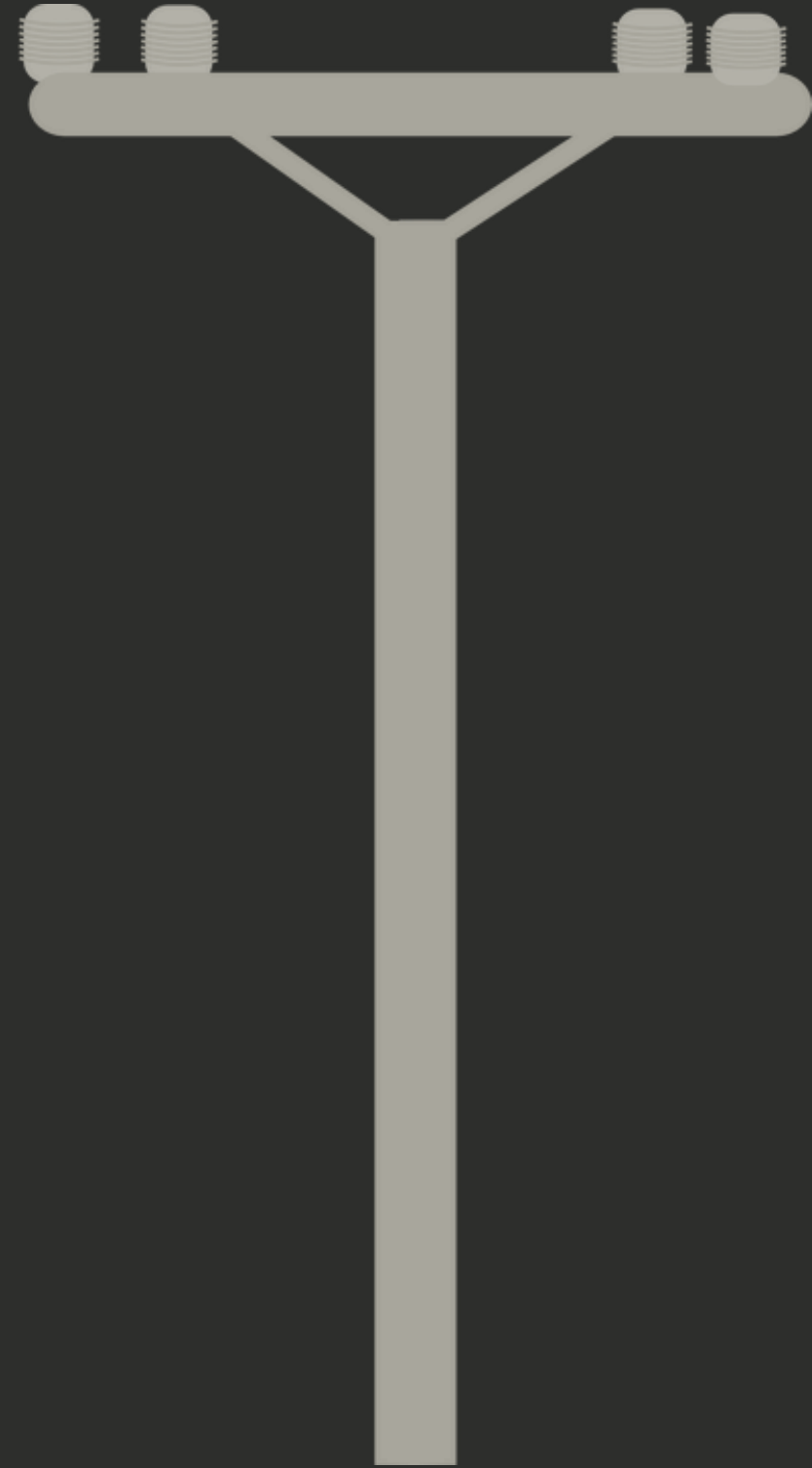

THANK YOU

