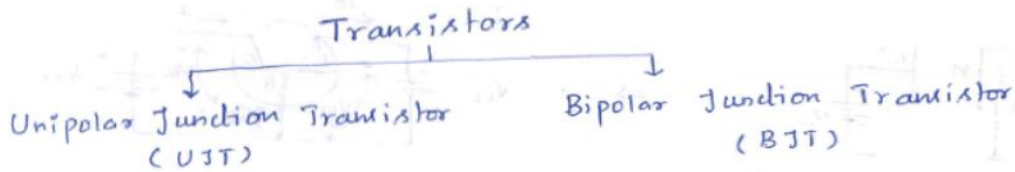


UNIT-I

Biasing of Discrete BJT and MOSFET




The current conduction is only due to one type of carriers i.e. majority carriers.

The current conduction in bipolar transistor is due to both minority and majority carriers.

Bipolar Junction Transistor (BJT)

Construction :

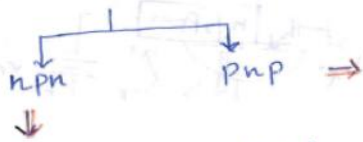- * It's a 3 terminal device → Emitter (E), Base (B) & collector (C)
- * Two Basic types







2 layers of n-type material sandwiching a thin p-type layer is called npn Transistor

2 layer of p-type material sandwiching a thin n-type layer is called pnp Transistor.

* The Emitter terminal is heavily doped while the base & collector are lightly doped.



* The Thickness of the base layer is ~ 0.001 of that of the emitter (or) collector layer.

Symbols :

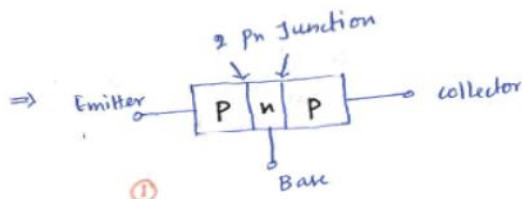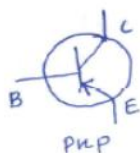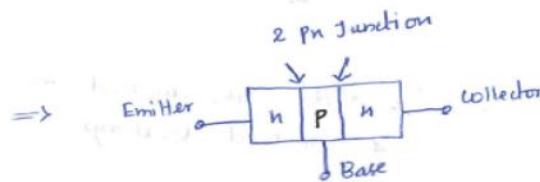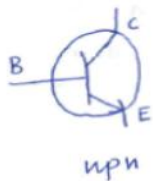

Operations:

npn

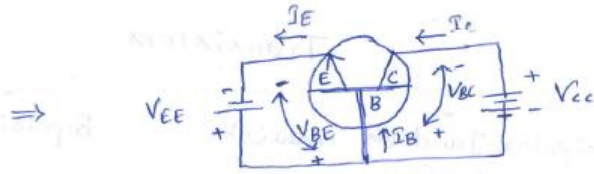
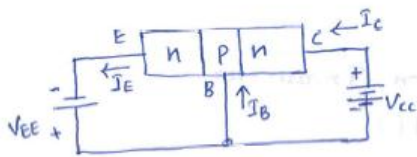


* The arrow at each Terminal points in the direction of conventional current.

* The current flow out of the E Terminal is referred as Emitter current, which is denoted as I_E .

* The current flow into the B terminal is referred as Base current, which is denoted as I_B & collector terminal current is denoted as I_C .

pnp

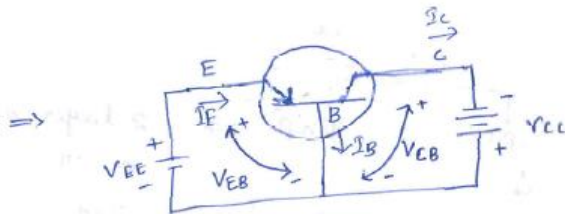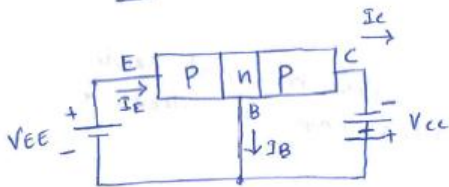

* The current flow into the E Terminal is referred as Emitter current, which is denoted as I_E .

* The current flow out of the B & C terminals are referred as base & collector currents, which are denoted as I_B & I_C .

For current flow through the BJT is 2 PN junctions (2 diodes back to back) must be properly biased.

One Junction is forward bias while the other is Reverse Bias.


1. Forward Bias

When the P side is applied +ve and n side is applied -ve in a junction & applied voltage is greater than a threshold 0.65V for Si

2. Reverse Bias

When the P side is applied -ve and n side is applied +ve in a junction & applied voltage is between 0 to a breakdown voltage.

For PNP Transistor

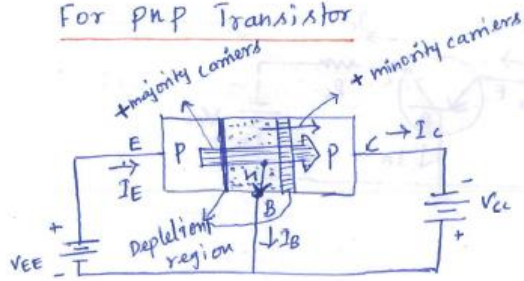

- * The Emitter-Base Junction is forward biased while the collector-Base junction is Reverse biased.
- * The majority carriers will flow from E to B across forward biased junction.

* Because the Base layer is very thin & has a high resistance, most of these carriers will diffuse across the reverse biased junction into the collector in the same direction of the minority charges & only tiny amount of current will flow out of the Base Terminal.

* Typically collector currents are of the order of mA while Base currents are μA .

* Applying Kirchhoff's current law:

$$I_E = I_C + I_B$$


- * The collector current is comprised of 2 components \rightarrow majority & minority carriers.
- * The minority current component is called leakage current, I_{CO} (I_C with Emitter terminal open).
- * So the collector current is

$$I_C = I_{C_{majority}} + I_{C_{minority}}$$


Transistor Configurations:

1. Common Base (CB) configuration
2. Common Emitter (CE) configuration
3. Common Collector (CC) configuration


1. Common Base configuration

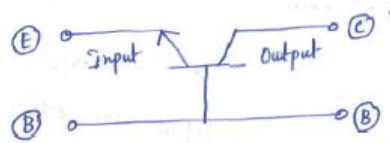

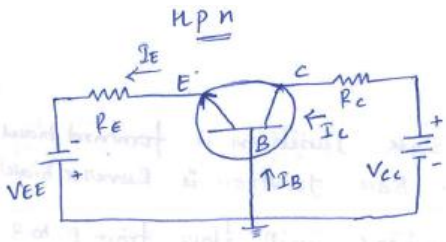
- * The Base terminal is common to both i/p & o/p.
- * The i/p is applied b/w the Emitter & the base & o/p is taken from collector & Base.



Considers npn

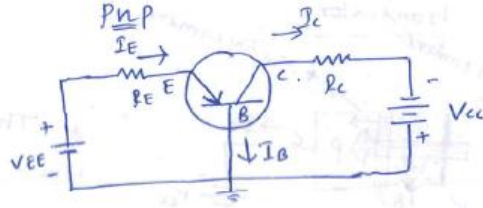


1. Input characteristics

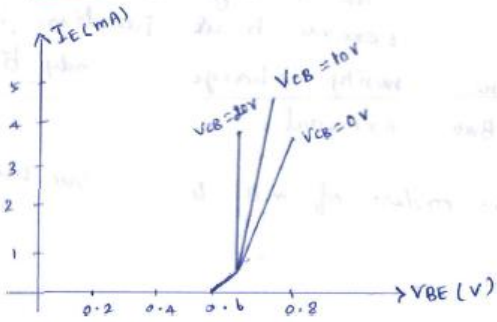

- * It shows the relation b/w input current I_E & input voltage V_{BE} for different values of output voltage V_{CB} .
- * It resembles the characteristics of forward bias diode.

- * I_E increases as V_{BE} increases for a fixed value of V_{CB} .
- * As V_{CB} increases, the width of the depletion layer in the Base increases.
- * Hence, the width of the Base available for conduction decreases.
- * The reduction in the width of the Base due to increase in Reverse bias is known as Early Effect.
- * Due to Early effect, the chance of recombination of electrons with holes in the Base decreases.
- * As V_{CB} further increases, at one stage the depletion region completely occupies the Base at which the collector-Base junction breaks down.
- * This phenomenon is known as punch-through.

2. Output characteristics

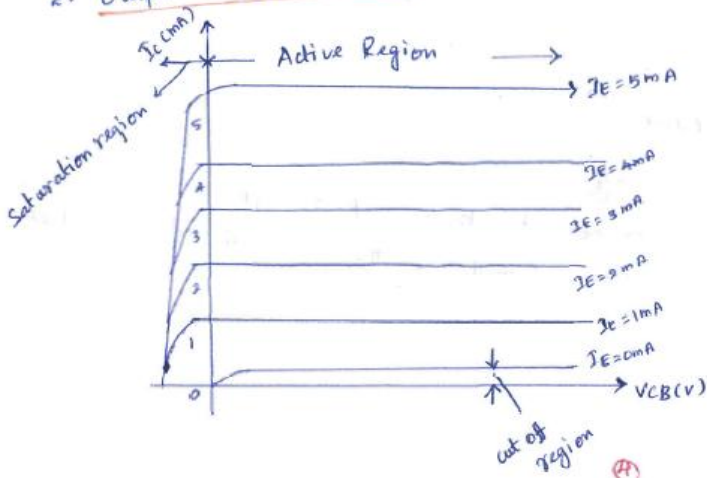

- * It shows the relationship b/w the o/p voltage V_{CB} & o/p current I_C for different values of input current I_E .

i) Cut-off Region

- * Both the junctions are reverse biased.
- * When the emitter-base junction is reverse biased, the current due to majority carrier i.e. I_E is zero.
- * When the collector-base junction is reverse biased, the current due to minority carriers flows from the collector to the base is represented as I_{CBO} .

ii) Active Region

- * The emitter-base junction is forward biased & the collector-base junction is reverse biased.
- * Once the V_{CB} reaches a value large enough to ensure a large portion of electrons enter the collector, I_C remains constant as shown by horizontal lines.
- * As I_E increases, I_C increases.

iii) Saturation Region

- * Both junctions are forward biased.
- * When V_{CB} is -ve, the collector-base junction is actually forward biased.
- * Thus, graphs are drawn on the -ve side of V_{CB} .

Current Amplification factor (α)


- * It's the ratio of change in collector current to the change in emitter current at constant collector-base voltage V_{CB} .

$$\alpha_{AC} = \frac{\Delta I_C}{\Delta I_E} \Big|_{V_{CB} = \text{constant}}$$


- * If only DC values are considered

$$\alpha_{DC} = \frac{I_C}{I_E}$$


2. Common - Emitter Configuration

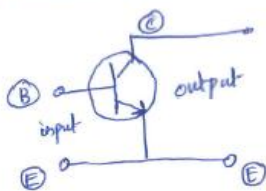

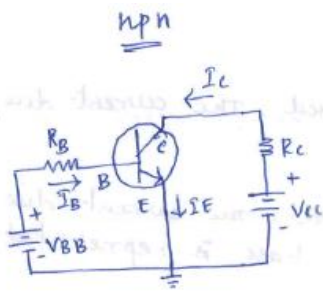
- * Input is applied b/w base & emitter and output is taken b/w collector & the emitter.



Consider npn

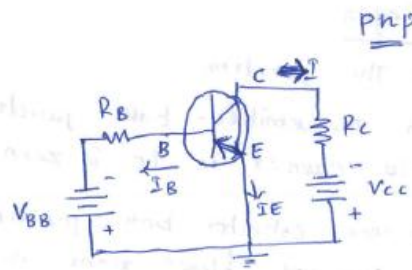


1. Input characteristics

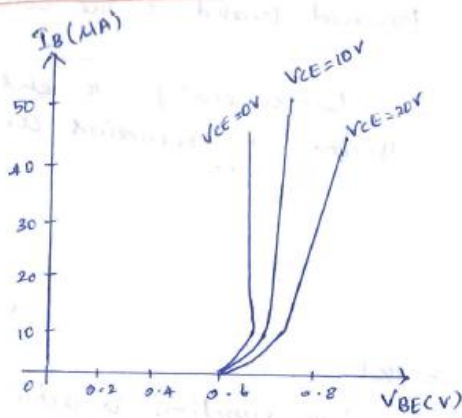

- * It shows the relationship b/w the i/p current I_B & i/p voltage V_{BE} for different values of o/p voltage V_{CE} .
- * It resembles the characteristics of forward bias diode.
- * I/p current I_B increases as i/p voltage V_{BE} increases for fixed value of V_{CE} .
- * As V_{CE} increases, the depletion region in the collector base increases which decreases the width of the base available for conduction.
- * Hence I_B decreases due to early effect & the graph shifts towards the x-axis.

2. Output characteristics

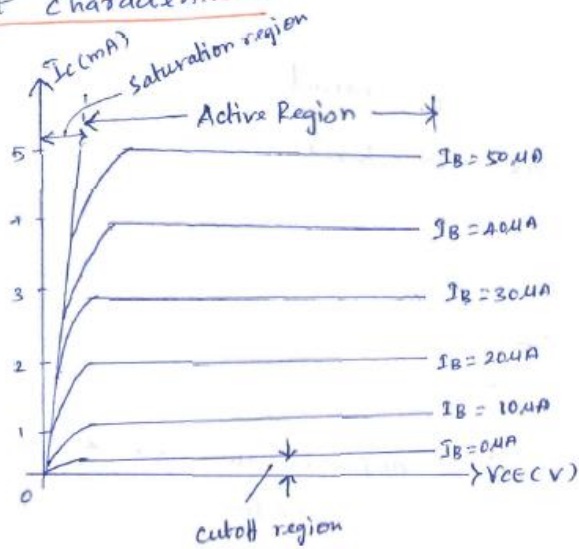

- * It shows the relation b/w o/p current I_C & o/p voltage V_{CE} for different values of i/p current I_B .

i) Cut-off Region

- * Both the junctions are reverse biased.
- * When the emitter-base junction is reverse biased, the current due to majority carriers i.e. I_B is zero.
- * When the collector-base junction is reverse biased, the current due to minority carriers flows from the collector to emitter which is represented as I_{CEO} .

ii) Active Region

- * The emitter-base junction is forward biased & the collector-base junction is reverse biased.
- * As I_B is maintained constant, current I_C increases as reverse-biased voltage V_{CE} increases.

iii) Saturation Region

- * Both junctions are forward biased.
- * When V_{CE} is reduced to a small value such as 0.2 V, the collector-base junction is actually forward biased.
- * In this region, there is a large change in I_C with small change in V_{CE} .

Current Amplification factor (β)

- * It's defined as the change in collector current to the change in base current at constant collector-emitter voltage V_{CE} .

$$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE} = \text{constant}}$$

- * If only DC values are considered

$$\beta_{DC} = \frac{I_C}{I_B}$$

Relation between α and β

$$I_E = I_C + I_B \quad \text{--- (1)}$$

Also,

$$\beta_{DC} = \frac{I_C}{I_B} \quad \text{--- (2)}$$

From (1) $I_B = I_E - I_C$ --- (3)

sub (3) in (2) $\beta_{DC} = \frac{I_C}{I_E - I_C}$ --- (4)

* Divide eqn (4) by I_E both Numerator & Denominator

$$(4) \Rightarrow \beta_{DC} = \frac{I_C / I_E}{\frac{I_E - I_C}{I_E}} = \frac{I_C / I_E}{1 - \frac{I_C}{I_E}} \quad \text{--- (5)}$$

W.K.T $\alpha_{DC} = \frac{I_C}{I_E}$

Sub α_{DC} in eqn (5)

$$(5) \Rightarrow \beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$$

* If subscript DC is ignored

$$\beta = \frac{\alpha}{1 - \alpha}$$

Collector Current (I_C):

* Apply KCL to the transistor

$$I_E = I_B + I_C \quad \text{--- (A)}$$

* The collector current has 2 components

$$I_C = I_{C \text{ majority}} + I_{C \text{ minority}}$$

$$I_C = \alpha I_E + I_{CO} \quad \text{--- (B)}$$

* For general purpose Transistors $\rightarrow I_C$ is measured in mA & I_{CO} is measured in μA (or) nA.

sub eq (A) in (B)

$$I_C = \alpha (I_B + I_C) + I_{CO}$$

$$= \alpha I_B + \alpha I_C + I_{CO}$$

$$I_C - \alpha I_C = \alpha I_B + I_{CO}$$

$$I_C (1 - \alpha) = \alpha I_B + I_{CO}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CO}$$


$$= \beta I_B + \frac{1}{1 - \alpha} I_{CO}$$

$$\therefore \beta = \frac{\alpha}{1 - \alpha}$$

sub $\frac{1}{1 - \alpha} = (\beta + 1)$ so we get


$$I_C = \beta I_B + (\beta + 1) I_{CO}$$

3. Common-Collector Configuration

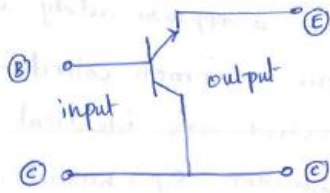


* The i/p is applied b/w base & collector & o/p is taken b/w emitter & collector.

npn

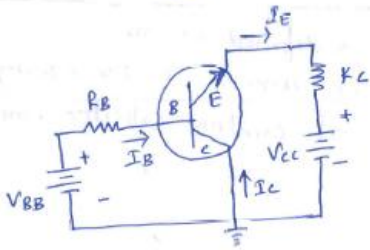


Consider npn

pnp

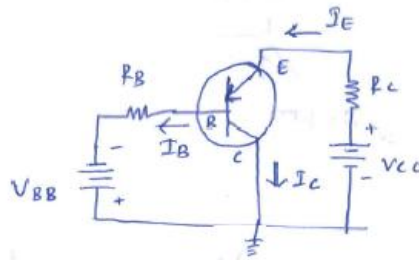

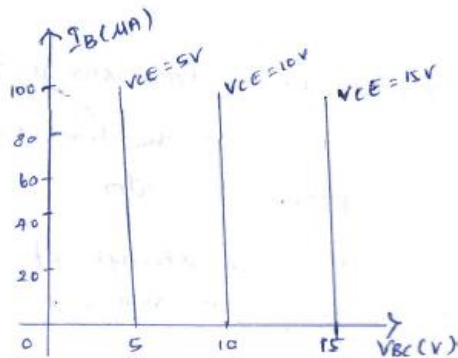1) Input characteristics

- * It shows the relation b/w i/p current I_B & i/p voltage V_{BC} for different values of o/p voltage V_{CE} .
- * The i/p voltage V_{BC} is largely determined by the o/p voltage V_{CE} .



* The i/p current I_B decreases to 0 as i/p voltage V_{BC} increases slightly for fixed values of V_{CE} .

$$V_{CE} = V_{BE} + V_{BC}$$


$$V_{BE} = V_{CE} - V_{BC}$$

* When V_{BC} is increased by keeping V_{CE} constant, V_{BE} decreases which decreases I_B .

* \therefore If the value of V_{BE} is allowed to increase to a point where it's near to the value of V_{CE} , the value of V_{BE} approaches 0 & no base current will flow.

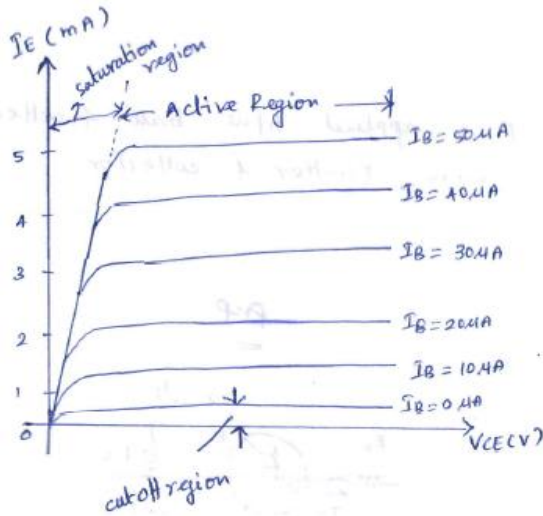2) Output characteristics

* It shows the relation b/w o/p current I_E & o/p voltage V_{CE} for different values of i/p current I_B .



* Since I_C is approximately equal to I_E , the common collector characteristics are identical to the common emitter op characteristics.

Current Amplification factor (γ)


* It's defined as the ratio of change in Emitter current to the change in base current at constant collector-emitter voltage V_{CE} .

$$\gamma_{AC} = \frac{\Delta I_E}{\Delta I_B} \Big|_{V_{CE} = \text{constant}}$$

* If only DC values are considered

$$\gamma_{DC} = \frac{I_E}{I_B}$$

Load Line Analysis

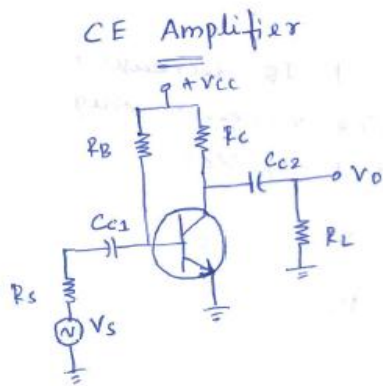

- * The basic function of a transistor is to do amplification.
- * The weak signal is given to the transistor & amplified output is obtained from the collector.
- * The process of raising the strength of weak signal without any change in its general shape is known as Amplification.
- * A Transistor must be properly biased to operate as an amplifier.

- * In CE amplifier the capacitor C_{c1} is a DC blocking capacitor & couples AC input signal to the base of the Transistor.
- * The capacitor C_{c2} is used to couple AC output of the amplifier to load R_L .

DC Analysis:

For DC, $f=0$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{0} = \infty$$

* The DC equivalent circuit is obtained by replacing all capacitors by open circuit.

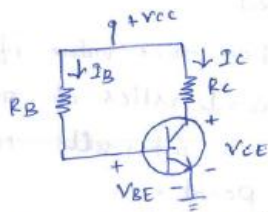


Fig: DC Equivalent circuit

Load line:

* Applying KVL to the collector-emitter circuit

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CC} - V_{CE} = I_C R_C$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \quad \text{--- (1)}$$

* The eqn (1) represent the DC load line with slope is $-\frac{1}{R_C}$ & y-intercept of $\frac{V_{CC}}{R_C}$.

* When $I_C = 0$ i.e. the transistor is in cutoff region

$$(1) \Rightarrow 0 = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C}$$

$$\frac{V_{CE}}{R_C} = \frac{V_{CC}}{R_C}$$

$$V_{CE} = V_{CC}$$

* When $V_{CE} = 0$ i.e. the transistor is in saturation region

$$(1) \Rightarrow I_C = -\frac{1}{R_C} (0) + \frac{V_{CC}}{R_C}$$

$$I_C = \frac{V_{CC}}{R_C}$$

* The two endpoints are $(V_{CC}, 0)$ & $(0, \frac{V_{CC}}{R_C})$.

* A line passing through these points is called DC load line as the slope of this line depends on the DC load R_C .

Quiescent point

* Applying KVL to the base-emitter circuit

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$V_{CC} - V_{BE} = I_B R_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

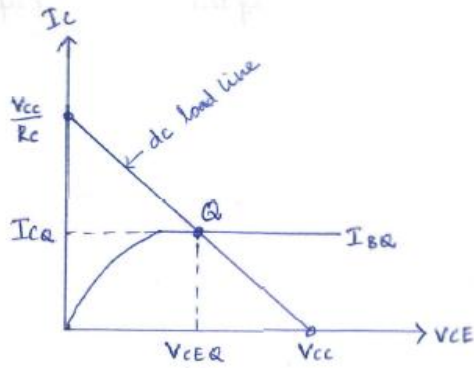


Fig: Load line and Q point

* This equation gives the value of base current.

* For this value of base current, o/p characteristics of the amplifier is plotted which intersects the DC load line at Q-point.

* Hence, Q point indicates quiescent (inactive, still) value of collector-emitter voltage V_{CE} + collector current I_C .

Need for Biasing

* The Transistor can be operated in 3 regions: cutoff, active + saturation by applying proper biasing conditions

| Region of operation | Emitter-Base Junction | collector-Base junction |
|---------------------|-----------------------|-------------------------|
| cutoff | Reverse biased | Reverse biased |
| Active | forward biased | Reverse biased |
| Saturation | forward biased | Forward biased |

* In order to operate Transistor in the desired region we have to apply external dc voltage of correct polarity + magnitude to the 2 junctions of the Transistor. This is called biasing of the Transistor.

* Dc biasing is used to establish proper values of I_C + V_{CE} called the Dc operating point (or) quiescent point (or) Q point.

* The value of I_C + V_{CE} is expressed in terms of operating point (or) Q point.

* For faithful amplification, Q point must be selected properly.

* The fulfilment of the below condition is known as transistor biasing


1. proper zero signal collector current I_C
2. proper base-emitter voltage V_{BE}
3. proper collector-emitter voltage V_{CE}

Selection of operating point:

* While fixing the Q-point it has to be seen that the o/p of the amplifier is a proper sinusoidal waveform for sinusoidal input without distortion.


- * If an amplifier is not biased properly, it can go into saturation (or) cutoff when an i/p signal is applied.
- * By fixing the Q-point at different positions, we can observe the variation in I_c & V_{CE} corresponding to a given variation of I_B .

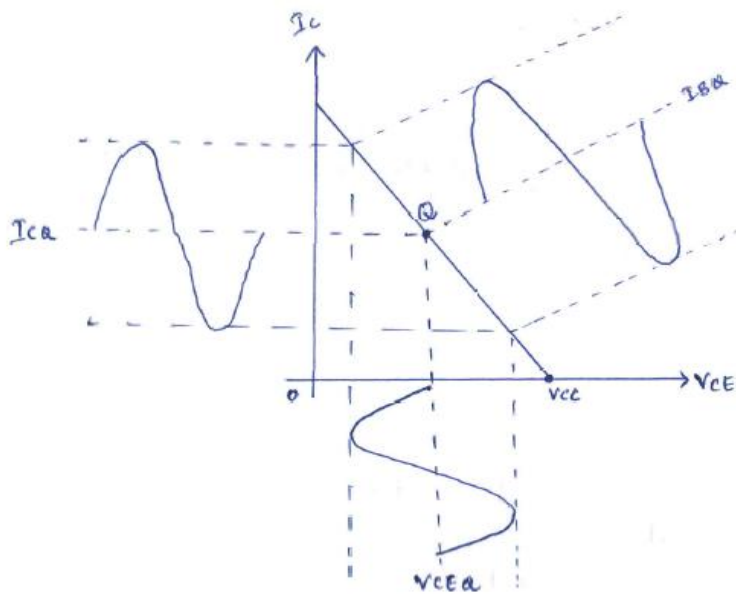Case 1: When the Q point is located in the middle of the DC load line (or) center of the Active region




- * The Q point is fixed at point Q.
- * The o/p signal is sinusoidal waveform without any distortion.
- * Thus the point Q is the best operating point.

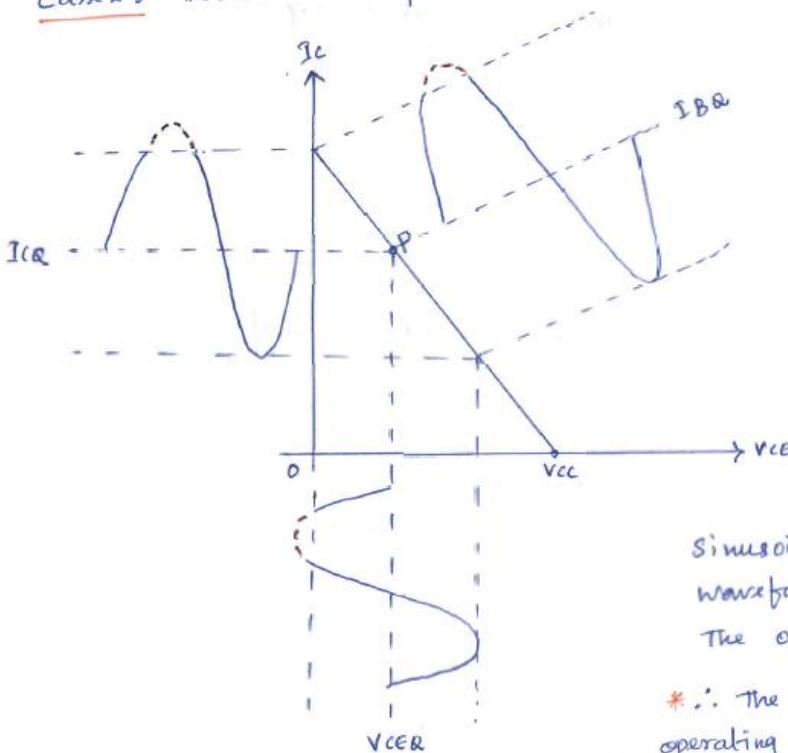Case 2: When the Q point is located near the saturation region.



- * The Q point is fixed at point P.
- * The point P is very near to saturation region.
- * The collector current I_c is clipped only at the positive half cycle.
- * Even though the I_B varies sinusoidally, I_c is not a sinusoidal waveform i.e. distortion is present at the o/p.
- * \therefore The point P is not a suitable operating point.

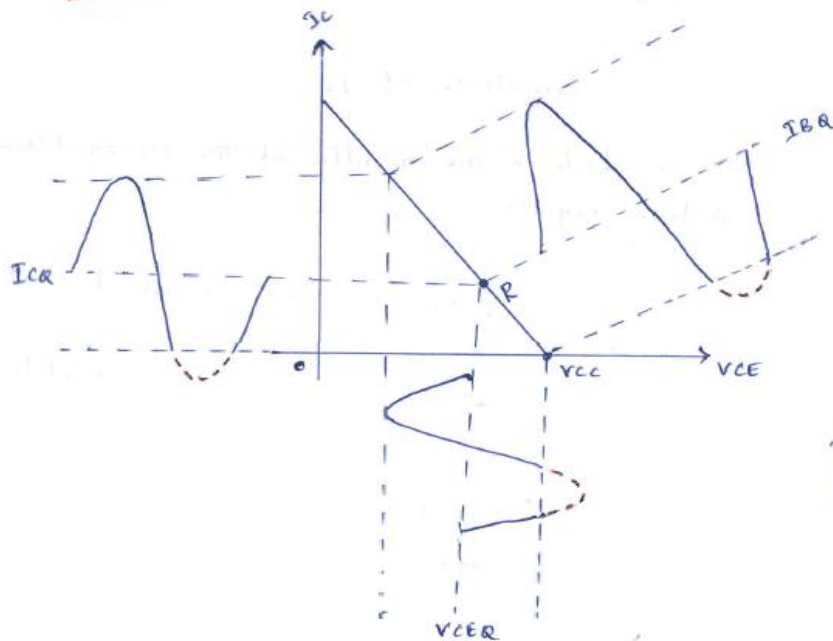Case 3: When the Q-point is located near the cut-off region



- * The Q point is fixed at point R.
- * The point R is very near to the cut off region.
- * The I_c is clipped at the negative half cycle.
- * So point R is also not a suitable Q point (or) operating point.

Variation of Q-point (or) Factors Affecting stability of Q-point

- * The biasing circuit should be designed to fix the operating point (or) Q-point at the center of the active region.
- * But only fixing of the operating point is not sufficient.
- * While designing the biasing circuit, care should be taken so that the Q-point will not shift into an undesirable region (i.e. cut off or saturation).
- * Designing the bias circuit to stabilize the Q-point is taken as bias stability.

Temperature

1) I_{CO}

- * The flow of current in the circuit produces heat at the junctions.
- * This heat increases the temperature at the junctions.
- * We know that the minority carriers are temperature dependent.
- * They increase with temperature.
- * The increase in the minority carriers increases the leakage current I_{CBO} .

$$\therefore I_{CEO} = (1 + \beta) I_{CBO}$$

- * I_{CBO} doubles for every 10°C rise in temperature.

* Increase in I_{CE0} in turn increases the collector current.

$$\therefore I_C = \beta I_B + I_{CE0}$$

* The increase in I_C further raises the temperature at the collector junction & the same cycle repeats.

* The excessive increase in I_C shifts the Q-point into the saturation region, changing the operating condition set by biasing circuit.

* The power dissipation at collector base junction is

$$P_D = V_C I_C$$

* The increase in the I_C increases the power dissipated at the collector junction.

* This in turn further increases the temperature of the junction & hence increases the I_C .


* The power is cumulative.

* The excess heat produced at the collector base junction may even burn & destroy the transistor.

* This situation is called Thermal runaway of the transistor.

* For any transistor the maximum power dissipation is always a fixed value.

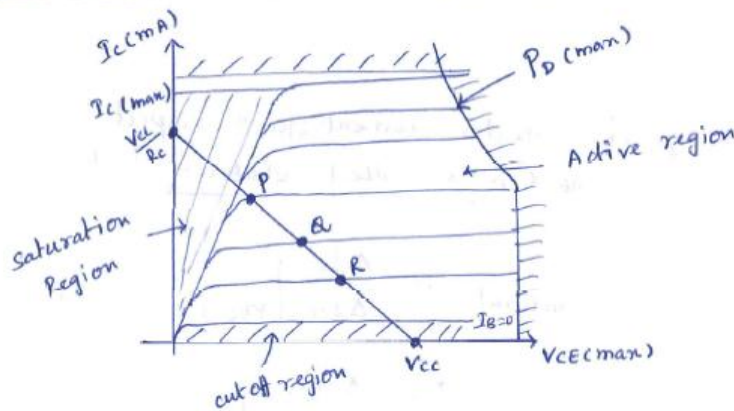* This known as maximum power dissipation rating of a transistor.



* The hyperbola give the maximum power dissipation for transistor.

* If this limit is crossed the device will fail.

2) V_{BE}

* V_{BE} changes with temperature at the rate of $2.5 \text{ mV}/^\circ\text{C}$

* I_B depends upon V_{BE}

* I_B depends on V_{BE} & I_C depends on I_B , I_C depends on V_{BE} .

* $\therefore I_C$ changes with temperature due to change in V_{BE}


* The change in I_C changes the Q-point.

3) β_{dc}

- * It's also temperature dependent.
- * As β_{dc} varies, I_c also varies, since $I_c = \beta I_B$
- * The change in I_c change the Q-point.

Transistor current gain $h_{FE} | \beta$

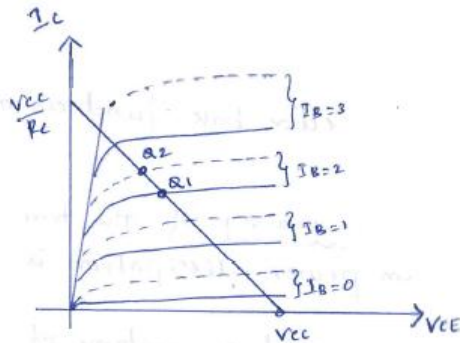- * There are changes in the Transistor parameters among different units of the same type, same number.
- * If we take 2 transistor units of same type & use them in the circuit, there is change in the β value in actual practice.
- * The biasing circuit is designed according to the required β value.
- * But due to change in β from unit to unit, the Q-point may shift.



- * This fig: shows the CE o/p characteristics for 2 Transistor of the same type.
- * The dashed characteristics are for a Transistor whose β is much larger than that of the Transistor represented by solid curves.

Stability Factors

S:

- * The rate of change of collector current (I_c) with respect to collector leakage current (I_{co}) at constant V_{BE} & β is called stability factor.

$$S = \left. \frac{\partial I_c}{\partial I_{co}} \right|_{V_{BE} \text{ \& } \beta \text{ constant}} = \left. \frac{\Delta I_c}{\Delta I_{co}} \right|_{V_{BE} \text{ \& } \beta \text{ constant}}$$

$$= \left. \frac{\Delta I_{c2} - \Delta I_{c1}}{\Delta I_{co2} - \Delta I_{co1}} \right|_{V_{BE} \text{ \& } \beta \text{ constant}}$$

S':

- * The rate of change of collector current (I_c) with respect to V_{BE} at constant I_{co} & β is called stability factor S'.

$$S' = \left. \frac{\partial I_c}{\partial V_{BE}} \right|_{I_{co} \text{ \& } \beta \text{ constant}} = \left. \frac{\Delta I_c}{\Delta V_{BE}} \right|_{I_{co} \text{ \& } \beta \text{ constant}} = \left. \frac{\Delta I_{c2} - \Delta I_{c1}}{\Delta V_{BE2} - \Delta V_{BE1}} \right|_{I_{co} \text{ \& } \beta \text{ constant}}$$