



SNS COLLEGE OF TECHNOLOGY



Coimbatore-35.

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

**COURSE NAME : 19ITT202 – COMPUTER ORGANIZATION AND
ARCHITECTURE**

II YEAR/ III SEMESTER

UNIT – II Arithmetic Operations

Topic: Design of Fast Adders

Mrs. M. Lavanya


Assistant Professor

Department of Computer Science and Engineering



HALF ADDER

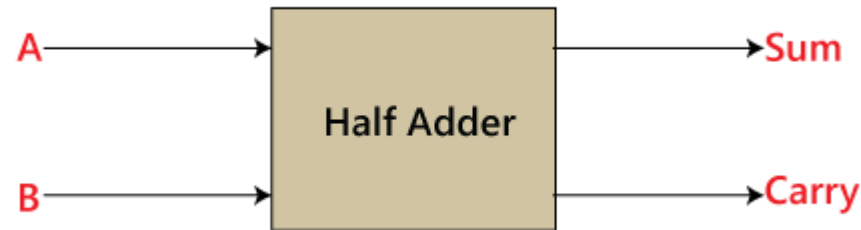- A half adder is a combinational circuit that performs addition / subtraction operation for two input values and gives the output SUM and CARRY.
- The carry of previous operation is not carried for next operation.



- The addition of 2 bits is done using a combination circuit called a Half adder.
- The input variables are augend and addend bits and output variables are sum & carry bits. A and B are the two input bits.



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = A \cdot B$$

A \ B	0	1
0	0	1
1	1	0

$$\text{Sum} = A \text{ XOR } B$$

A \ B	0	1
0	0	0
1	0	1

$$\text{Carry} = A \text{ AND } B$$




Half-Adder

A	B	S	C

INPUT


A
B

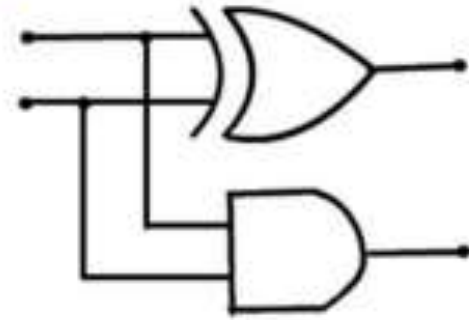

OUTPUT

$$S = A \oplus B$$


$$C = A \cdot B$$

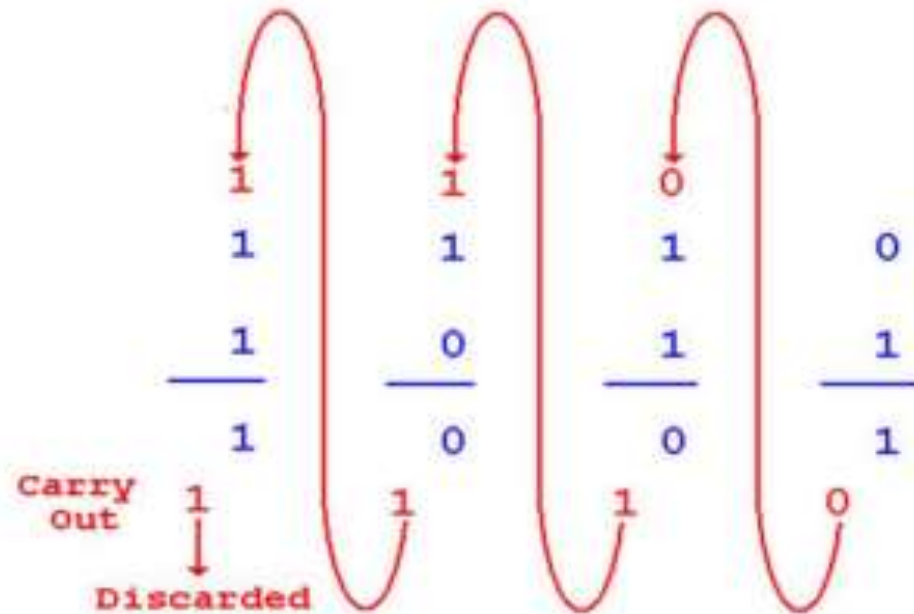



FULL ADDER

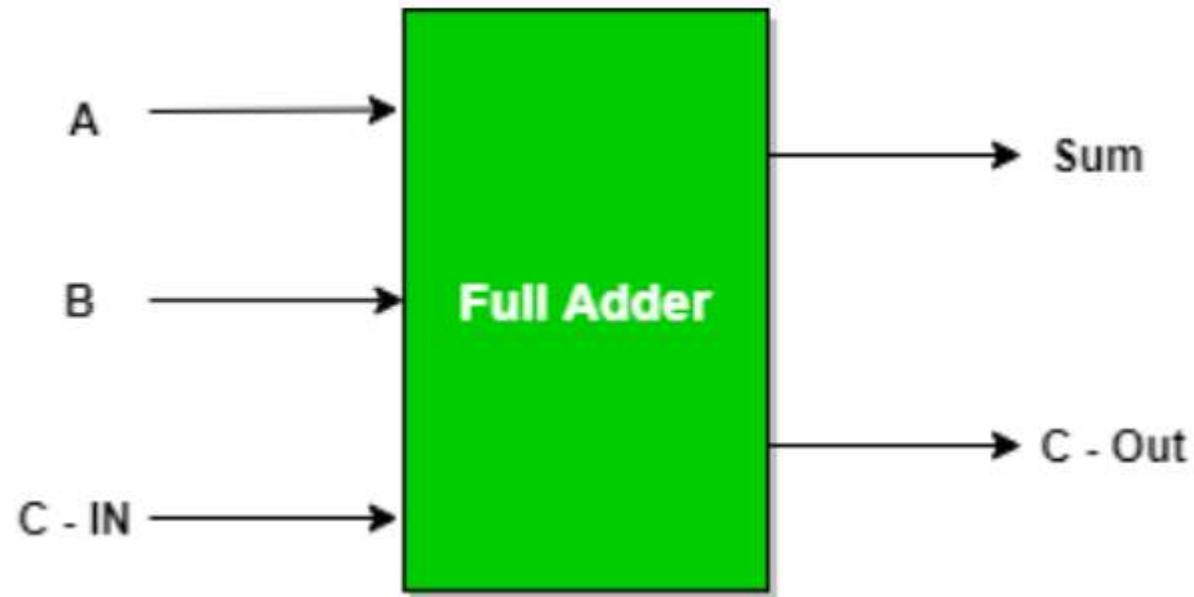- A complete circuit to perform a single stage of addition is called as a full adder (FA).
- It is used to add 3 values.






x_i	y_i	Carry-in c_i	Sum s_i	Carry-out c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$
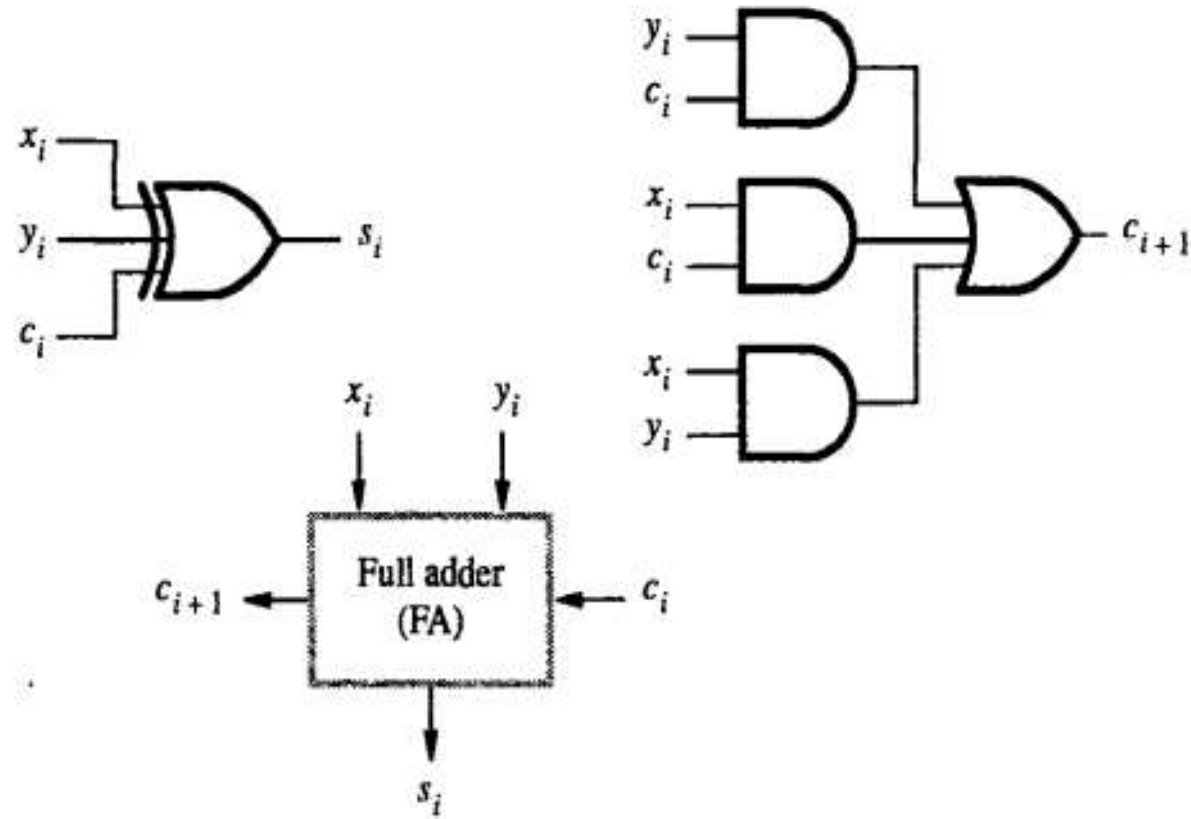
$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$




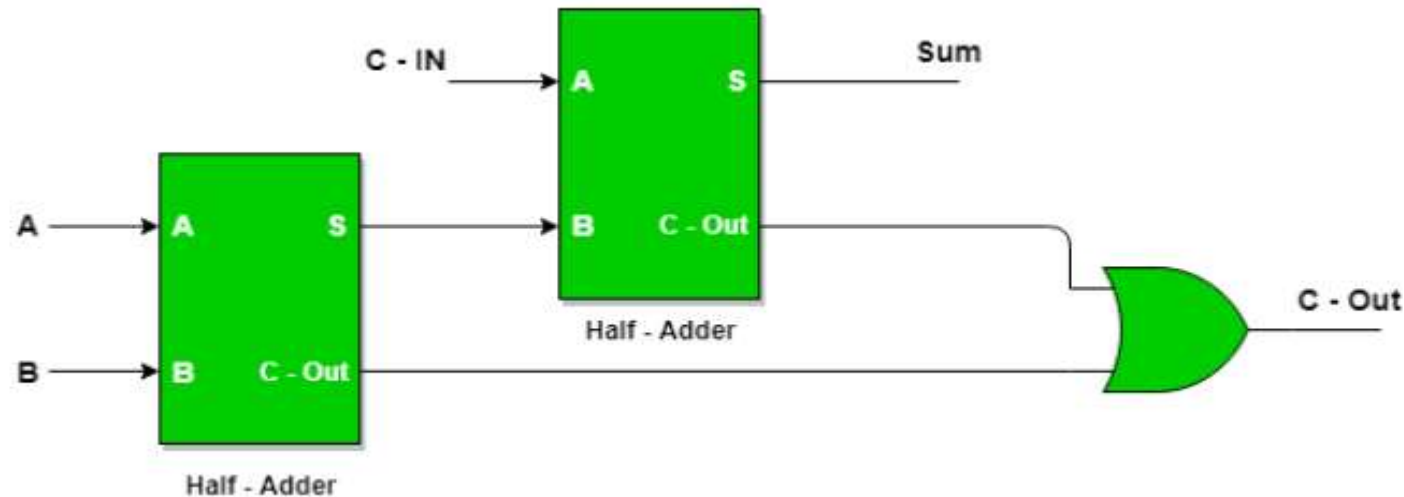(a) Logic for a single stage



Construction of Full Adder from 2 Half Adder

- A full adder can be constructed with the help of two half adder (HA)
- The difference is that the carry of the previous sum can be given as input for the next addition/operation in full adder.







Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B)C_{in}$$

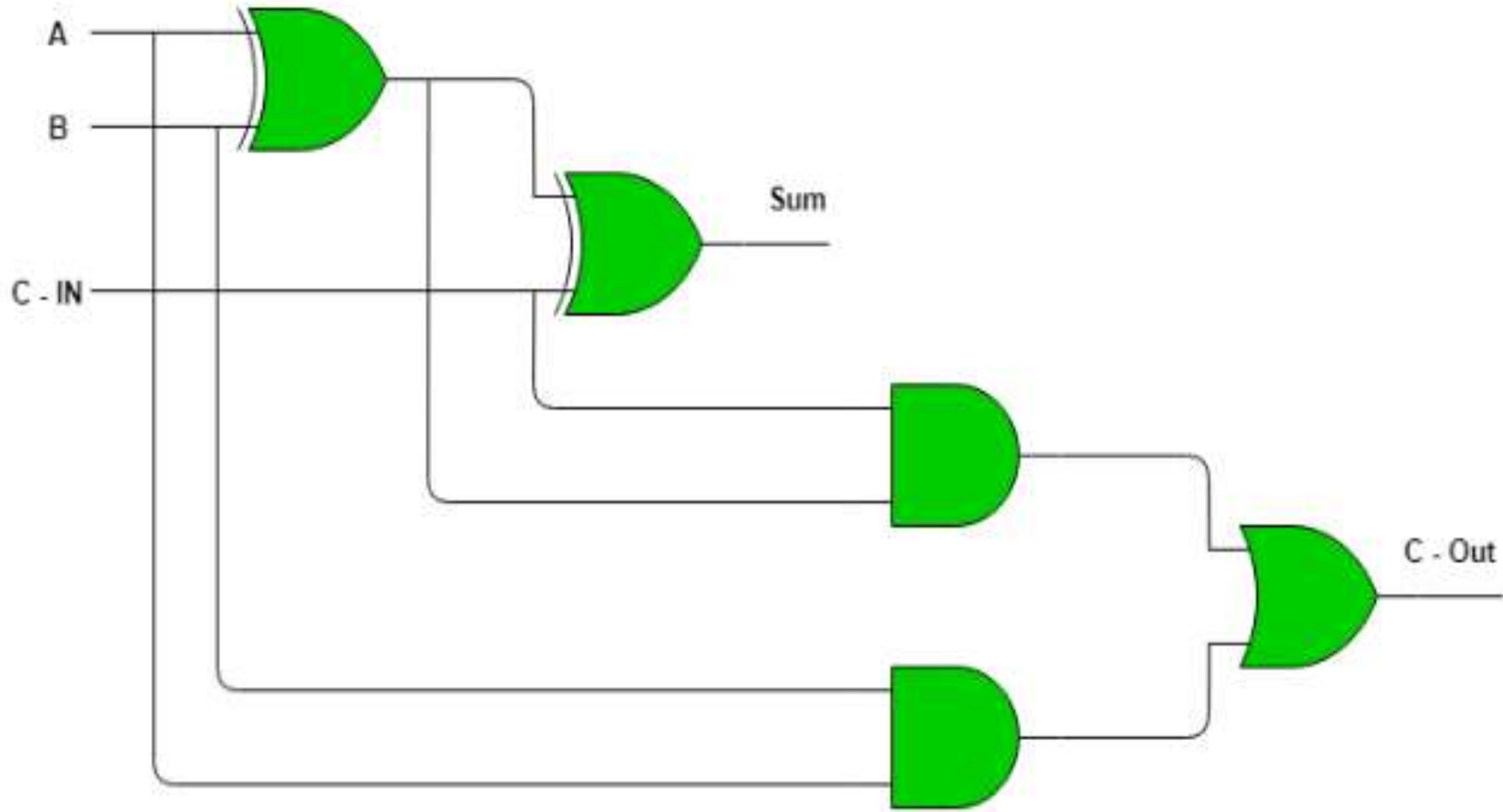

Full Adder logic circuit.

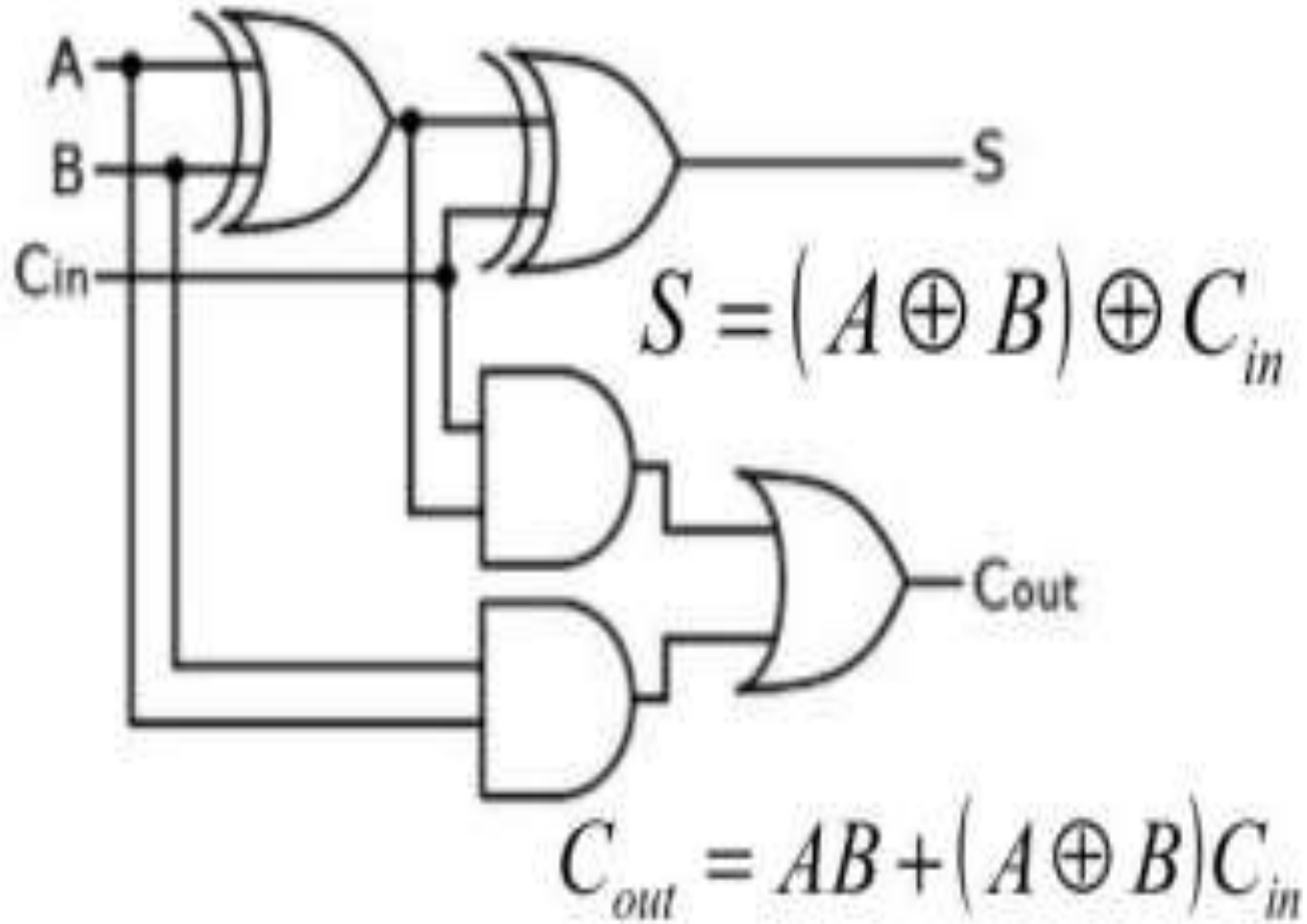



CARRY-LOOK AHEAD ADDITION

A fast adder circuit must speed up the generation of the carry signals. The logic expressions for s_i (sum) and c_{i+1} (carry-out) of stage i (see Figure 6.1) are

$$s_i = x_i \oplus y_i \oplus c_i$$

and

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Factoring the second equation into

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

we can write

$$c_{i+1} = G_i + P_i c_i$$

where

$$G_i = x_i y_i \quad \text{and} \quad P_i = x_i + y_i$$

The expressions G_i and P_i are called the *generate* and *propagate* functions for stage i .



Expanding c_i in terms of $i - 1$ subscripted variables and substituting into the c_{i+1} expression, we obtain

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} c_{i-1}$$

Continuing this type of expansion, the final expression for any carry variable is

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0 \quad [6.1]$$


Let us consider the design of a 4-bit adder. The carries can be implemented as

$$c_1 = G_0 + P_0 c_0$$


$$c_2 = G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$
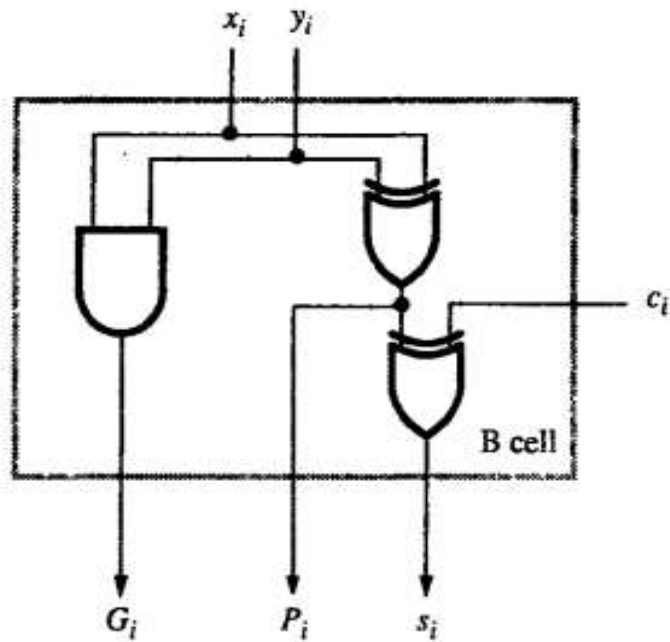
$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$



(a) Bit-stage cell

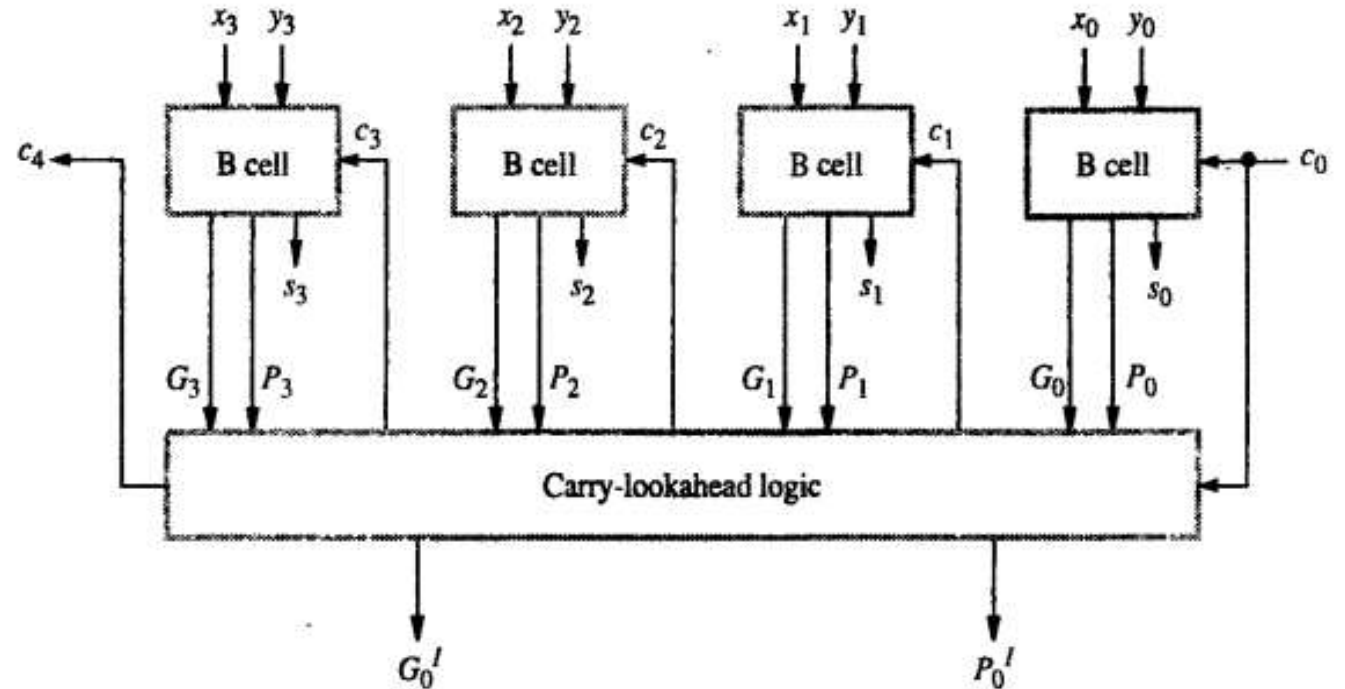

(b) 4-bit adder

Figure 6.4 4-bit carry-lookahead adder.

The complete 4-bit adder is shown in Figure 6.4b. The carries are implemented in the block labeled carry-lookahead logic. An adder implemented in this form is called a *carry-lookahead adder*.

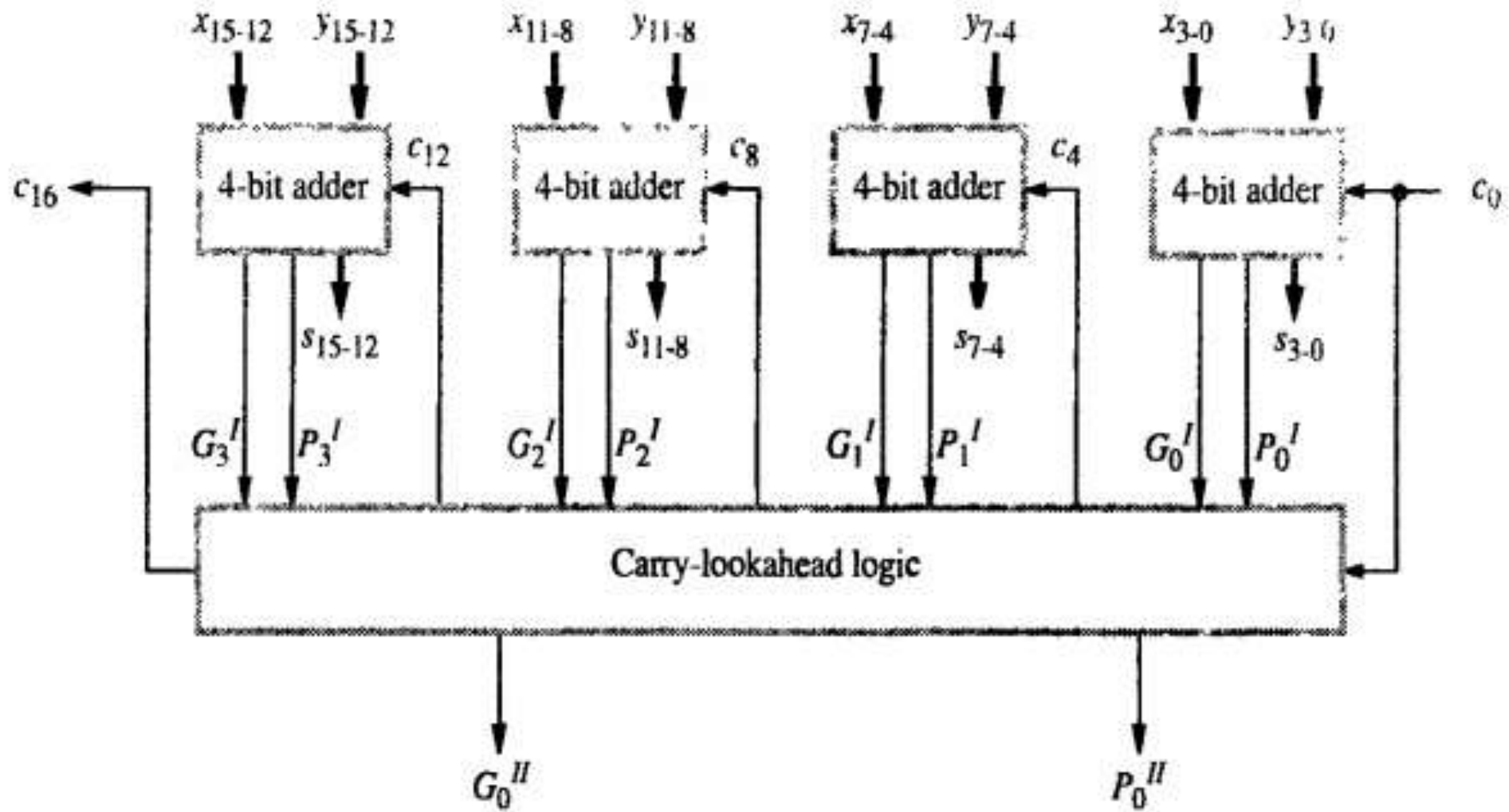


Figure 6.5 16-bit carry-lookahead adder built from 4-bit adders (see Figure 6.4b).

