



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)



COIMBATORE-35

**Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai**

DEPARTMENT OF BIOMEDICAL ENGINEERING

COURSE NAME: 19EIB201/ ELECTRONIC DEVICES

II YEAR / III SEMESTER

Unit 1 – Transistors

Topic 2: Bipolar Junction Transistors






Transistors

- When a p-type semiconductor is joined with the n-type semiconductor, a p-n junction is formed between them. This p-n junction forms a most popular device known as a semiconductor diode.
- An addition of another layer to a p-n junction diode forms a three terminal device called a transistor that amplifies the electronic signals. The term transistor normally refers to a Bipolar Junction Transistor (BJT).
- The transistor that is made up of one p-type and two n-type semiconductor layers is known as n-p-n transistor whereas the transistor that is made up of one n-type and two p-type





Transistors

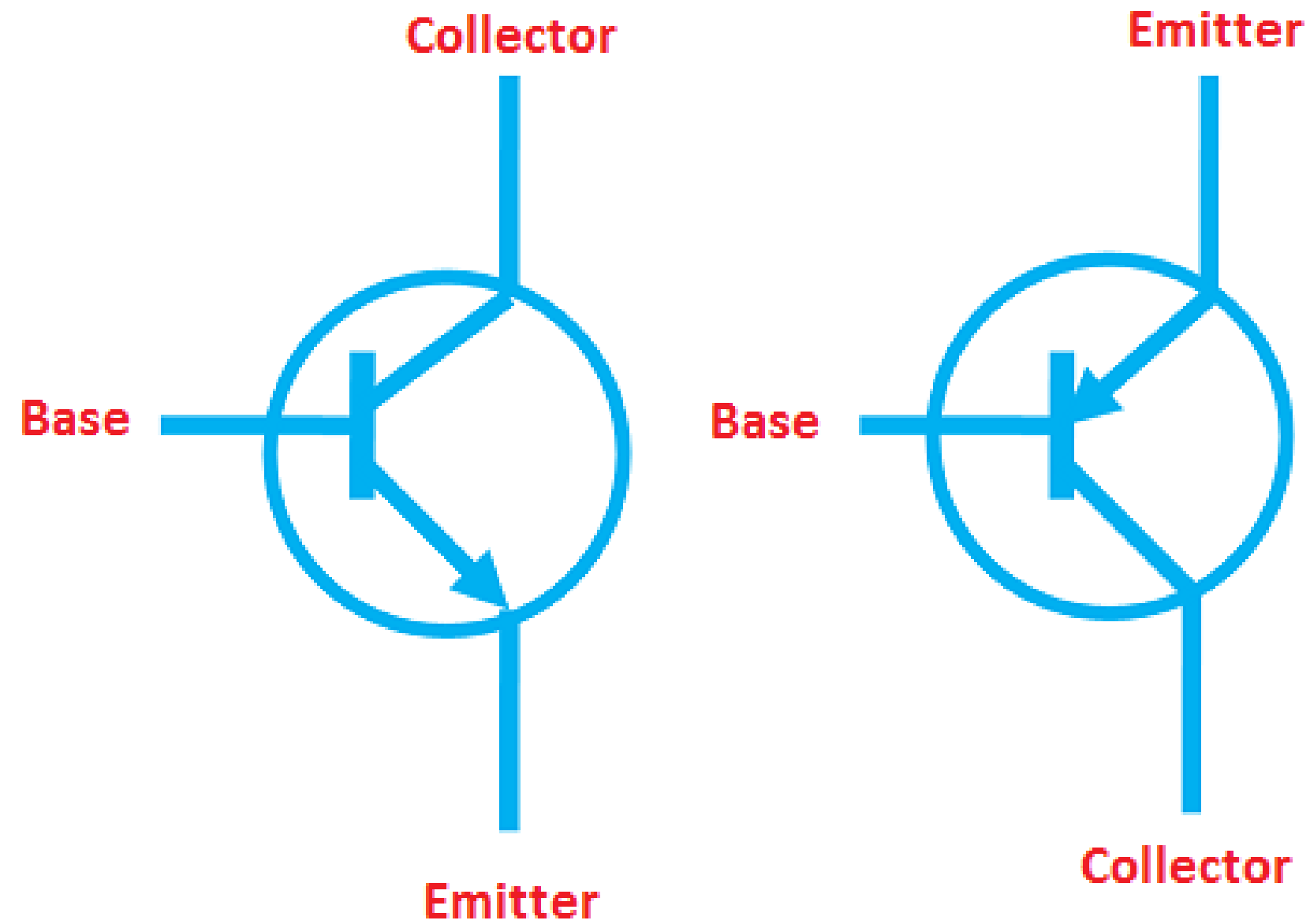


NPN Transistor

PNP Transistor

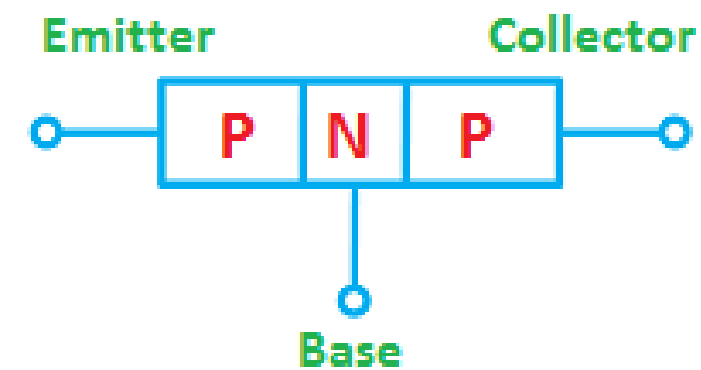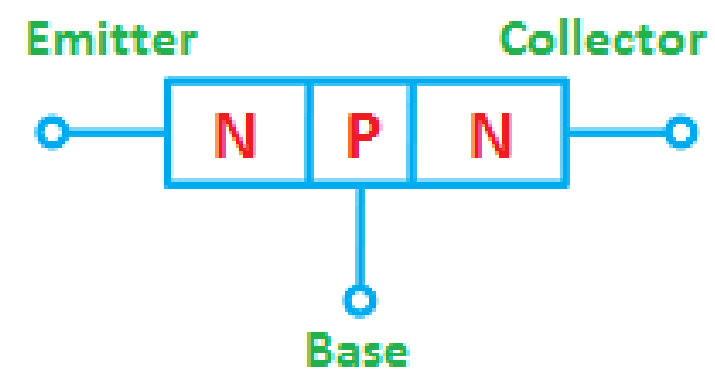



Classification of Transistors

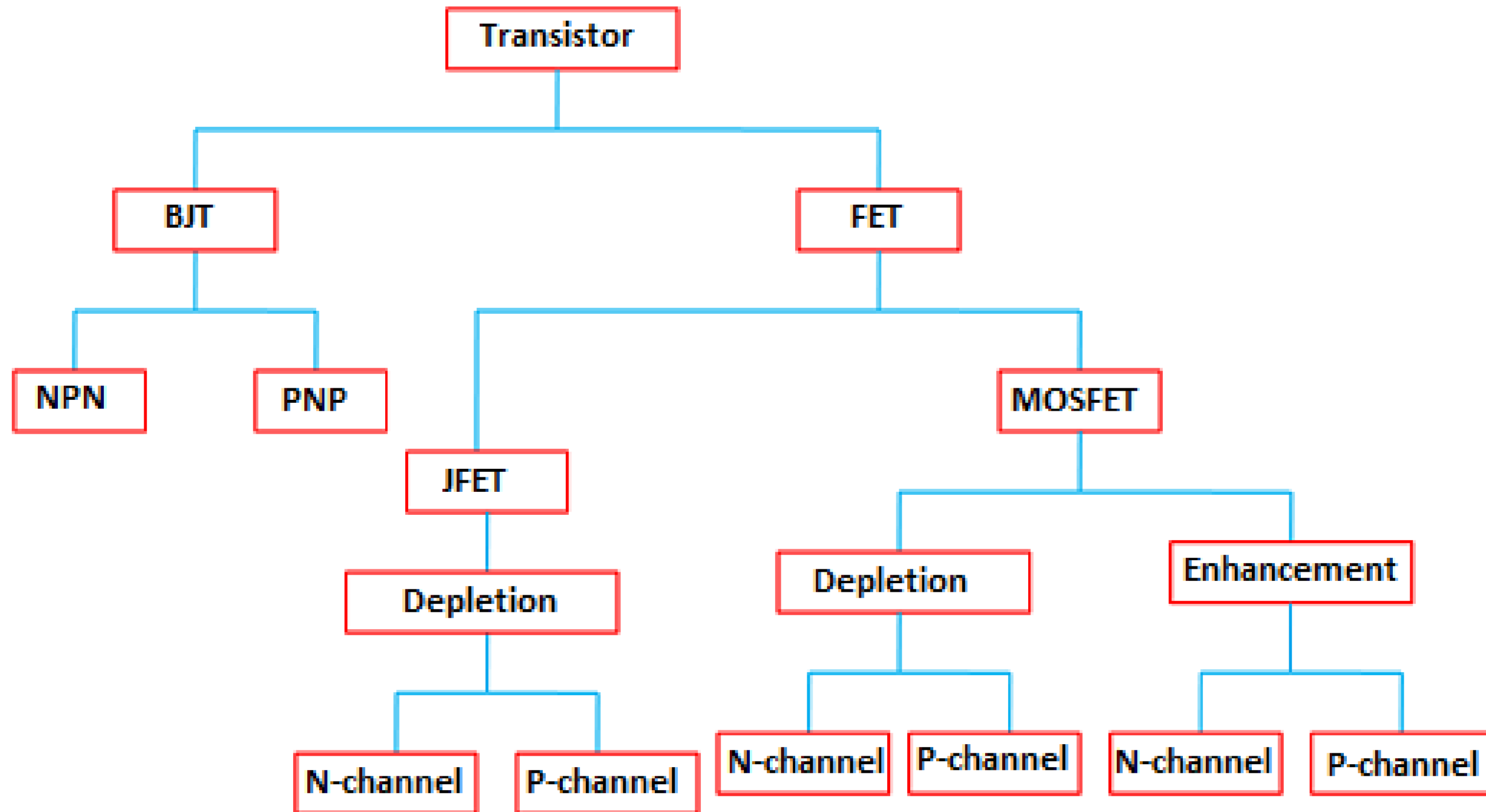

Classification of transistors




Bipolar Junction Transistor



- A bipolar junction transistor or BJT is a three terminal electronic device that amplifies the flow of current.
- It is a current controlled device. In bipolar junction transistor, electric current is conducted by both free electrons and holes.
- Bipolar junction transistors are classified into two types based on their construction: They are
 - ✓ NPN transistor
 - ✓ PNP transistor





Bipolar Junction Transistor

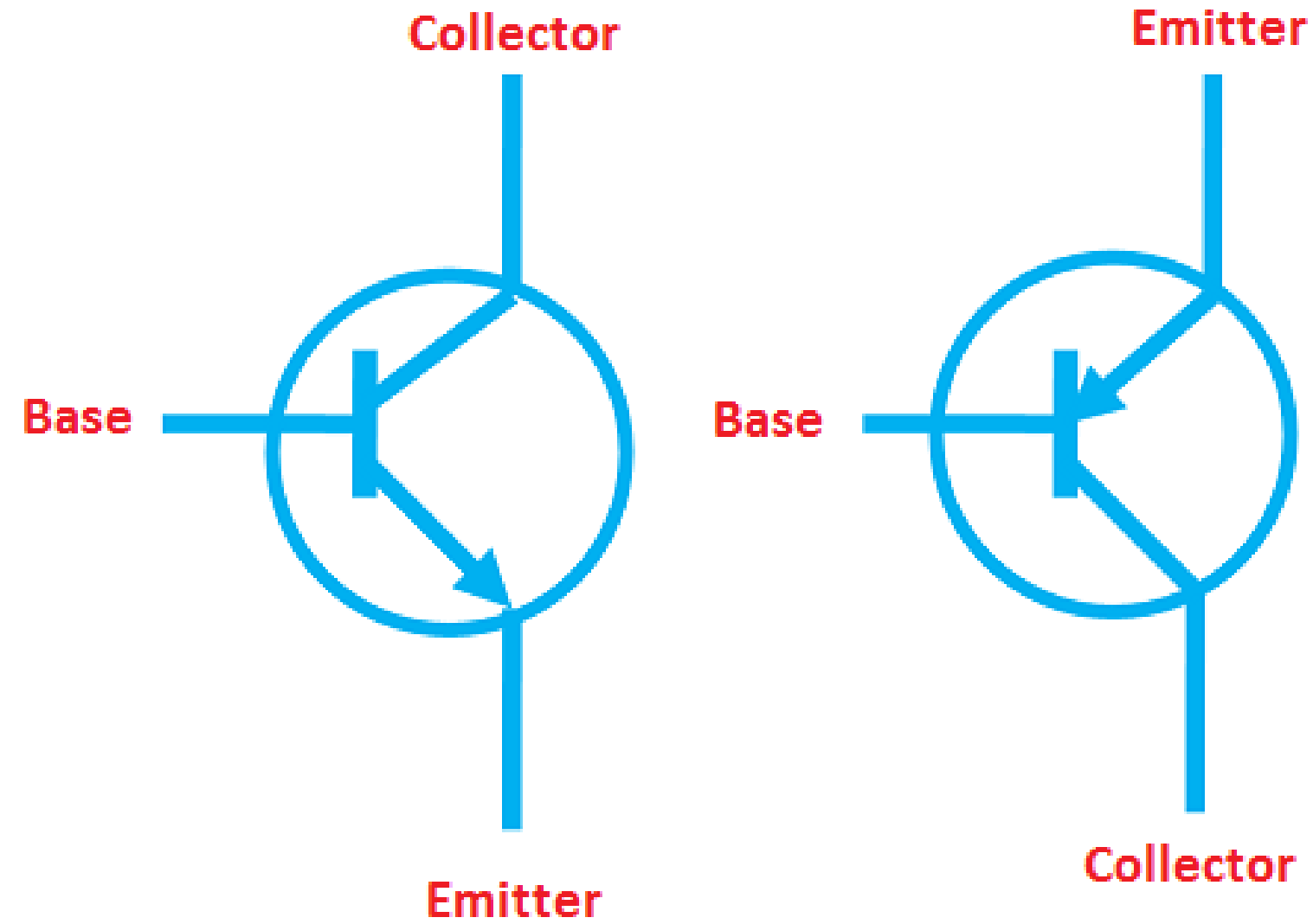

NPN Transistor

PNP Transistor

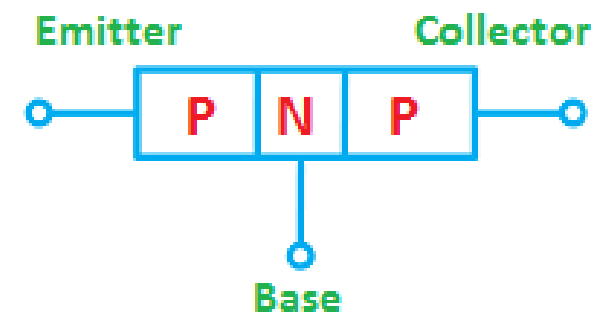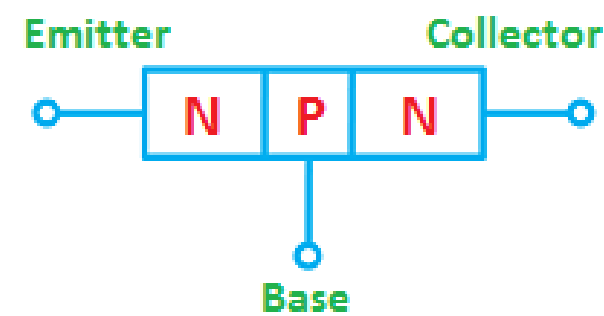



Bipolar Junction Transistor



- **Emitter:** As the name suggests, the emitter section supplies the charge carriers. The emitter section is heavily doped so that it can inject a large number of charge carriers into the base. The size of the emitter is always greater than the base.
- **Base:** The middle layer is called base. The base of the transistor is very thin as compared to emitter and collector. It is very lightly doped.
- **Collector:** The function of the collector is to collect charge carriers. It is moderately doped. The size of the collector is always greater than emitter and base.





BJT operation modes

- **The transistor can be operated in three modes:**
 - ✓ **Cut-off mode**
 - ✓ **Saturation mode**
 - ✓ **Active mode**
- Applying dc voltage to the transistor is nothing but the biasing of transistor.
- In order to operate transistor in one of these regions, we have to supply dc voltage to the npn or pnp transistor.
- Based on the polarity of the applied dc voltage, the transistor operates in any one of these regions.





Cut-off mode

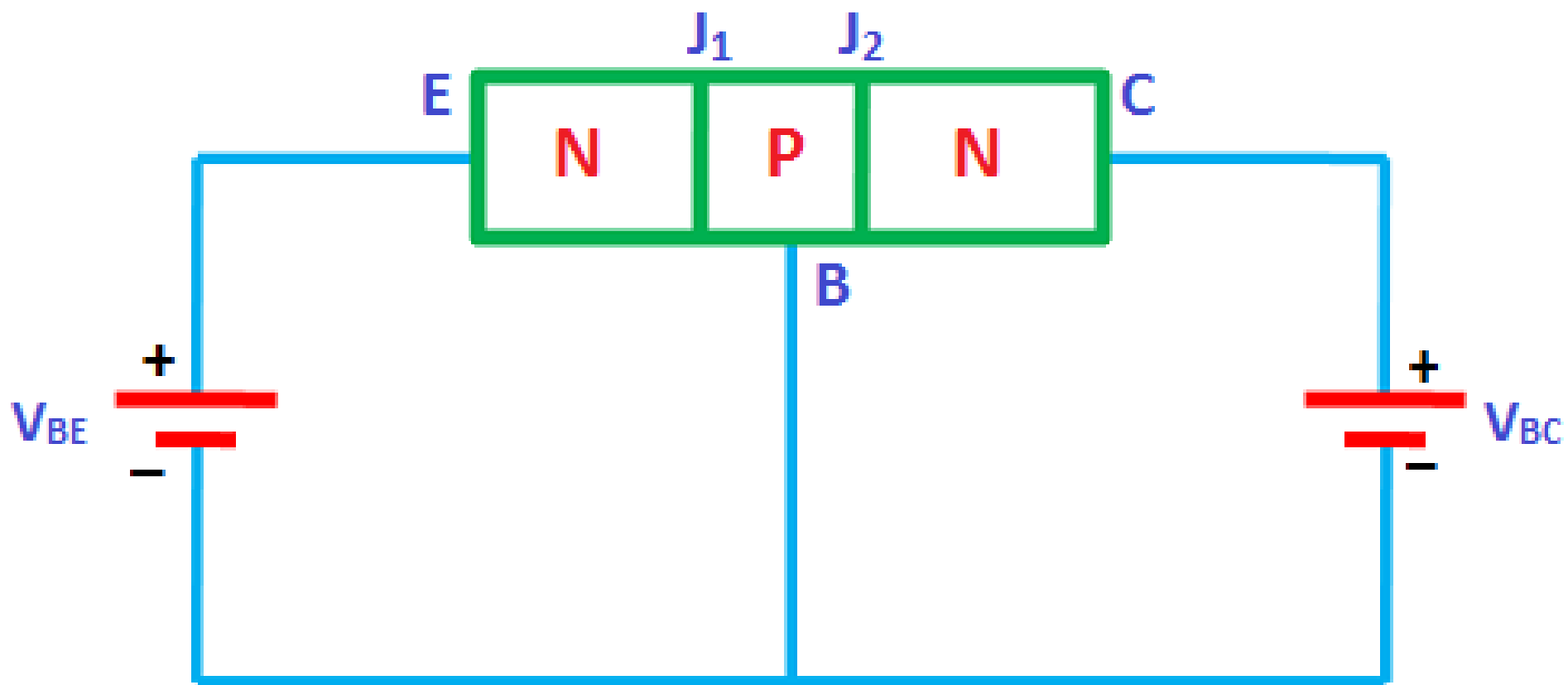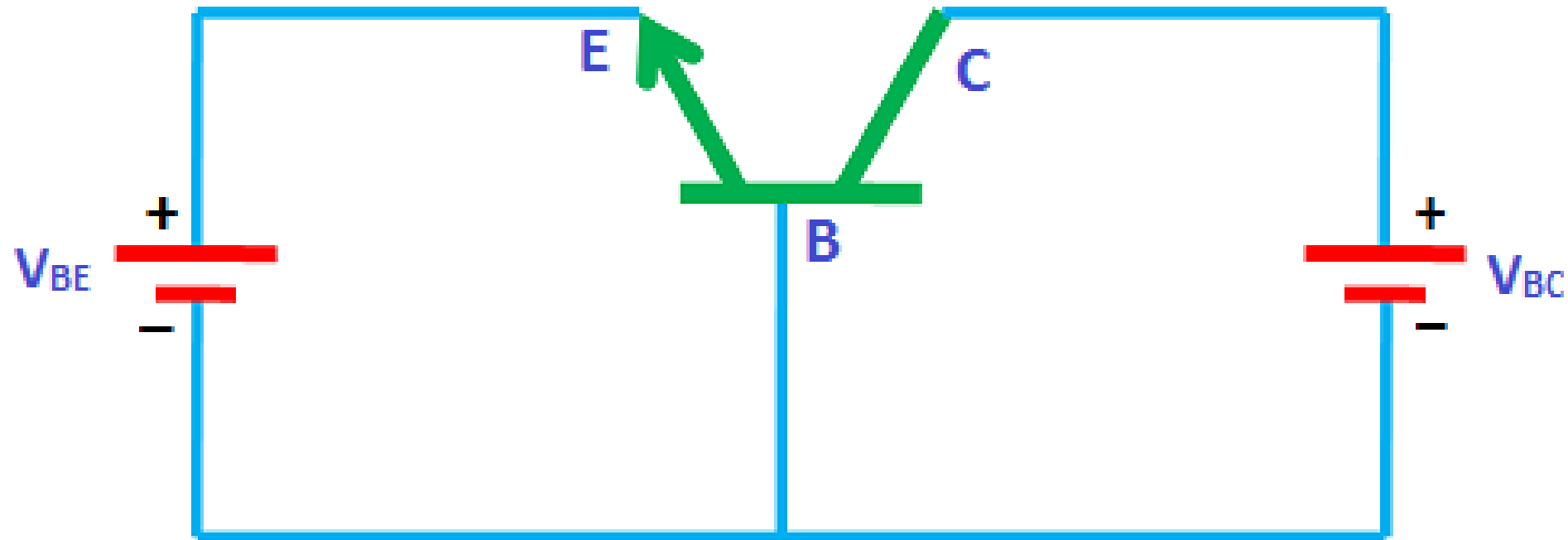

Cutoff mode





Saturation mode

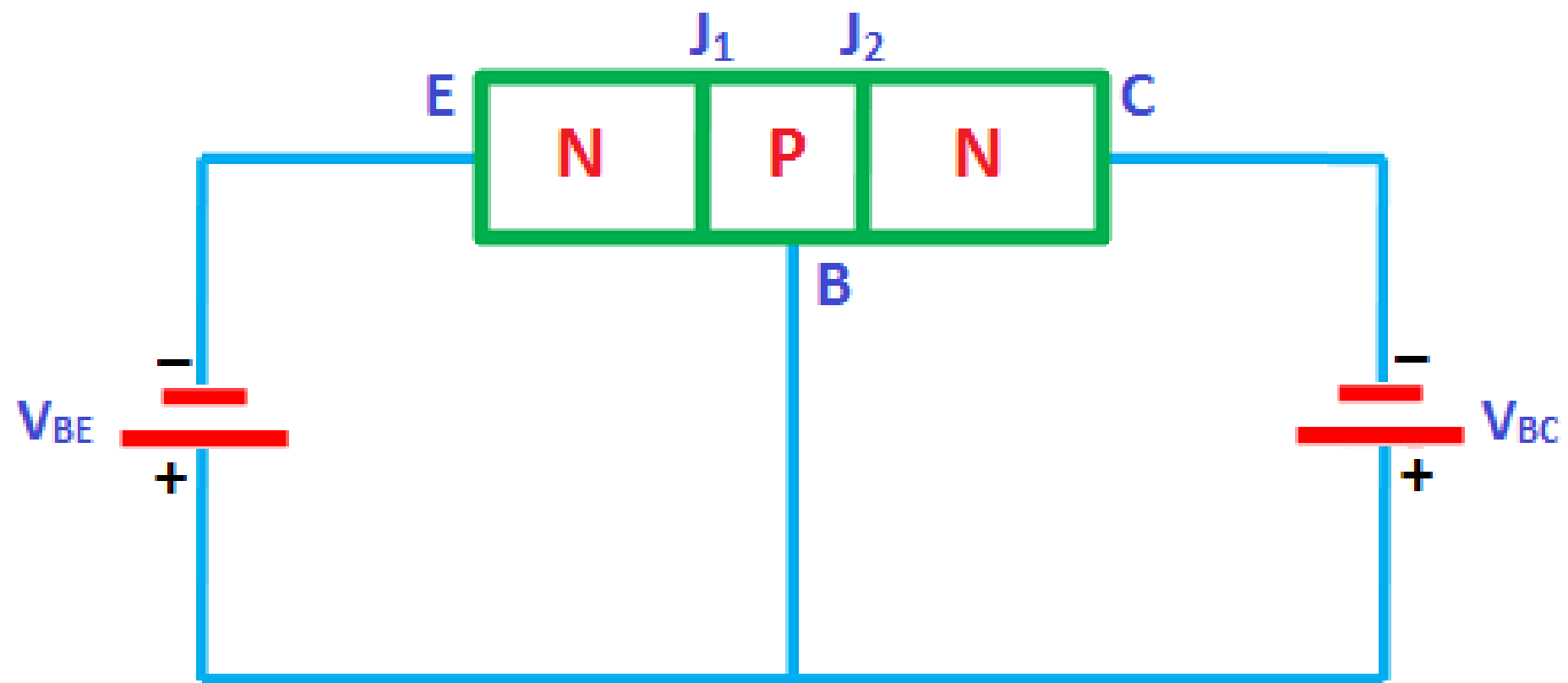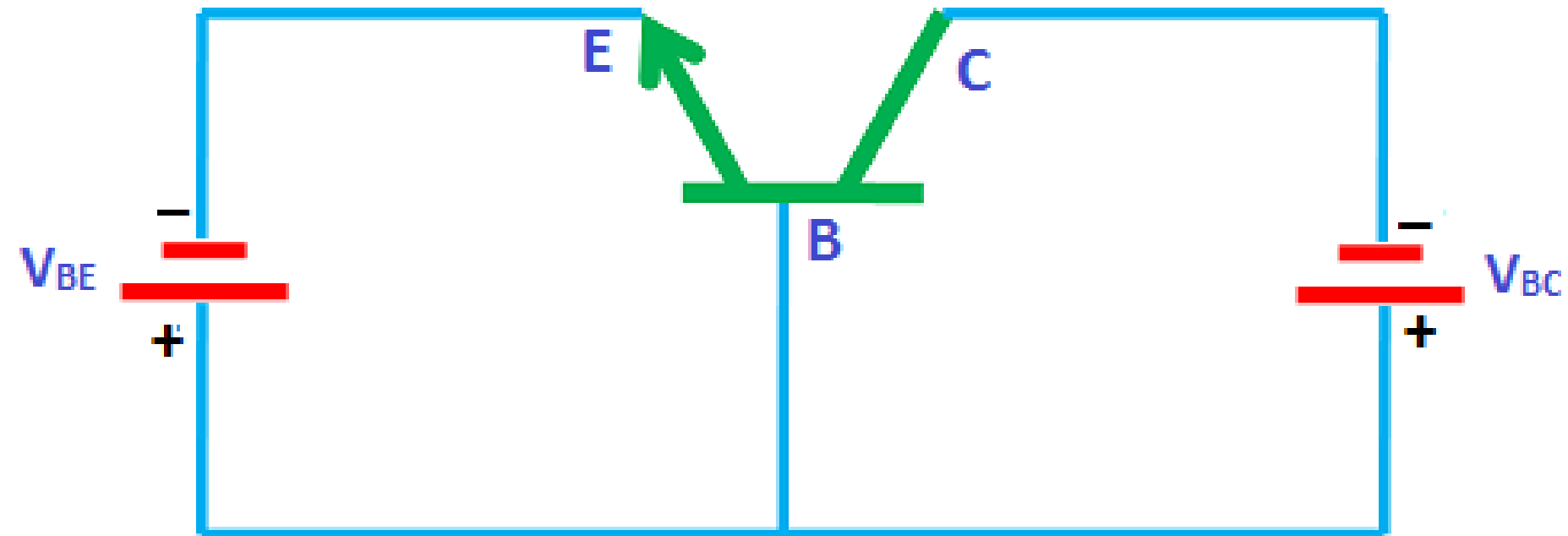

Saturation mode




Active mode

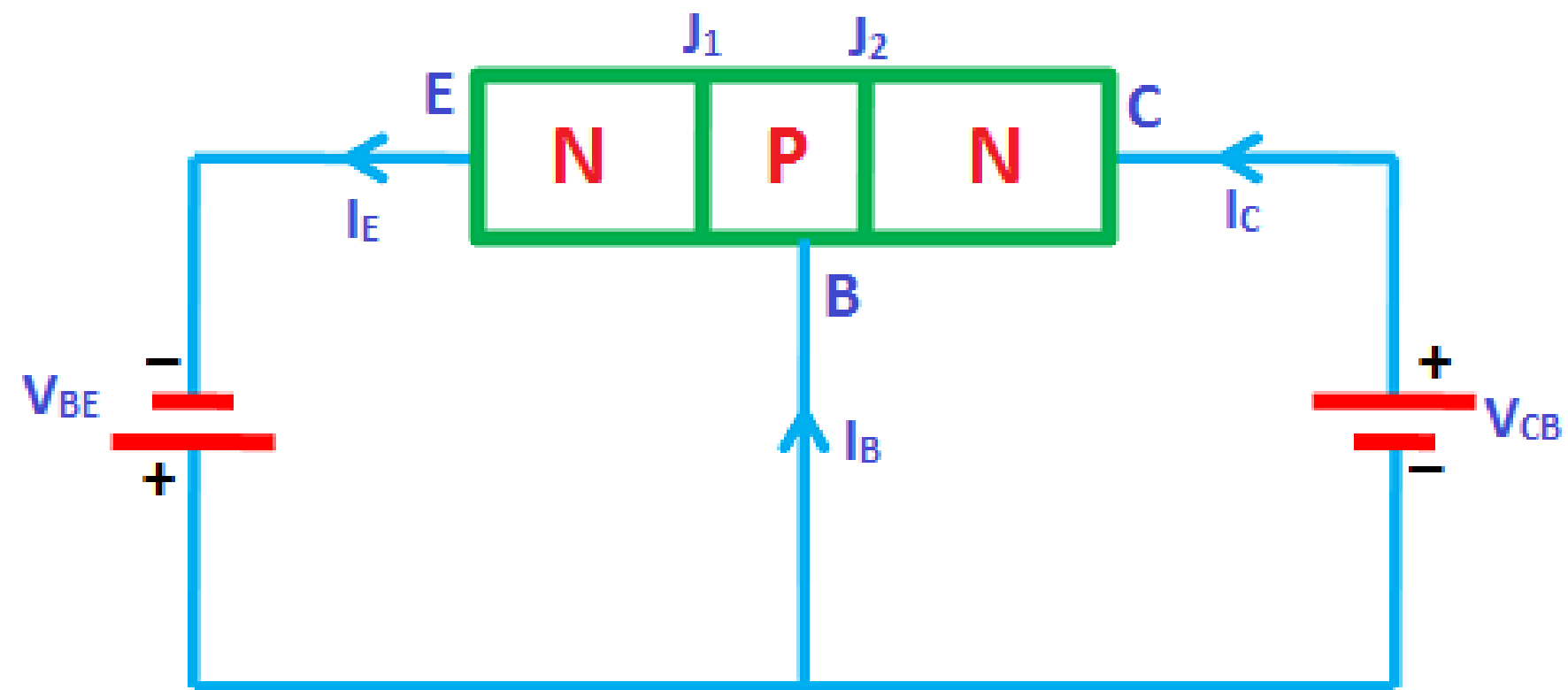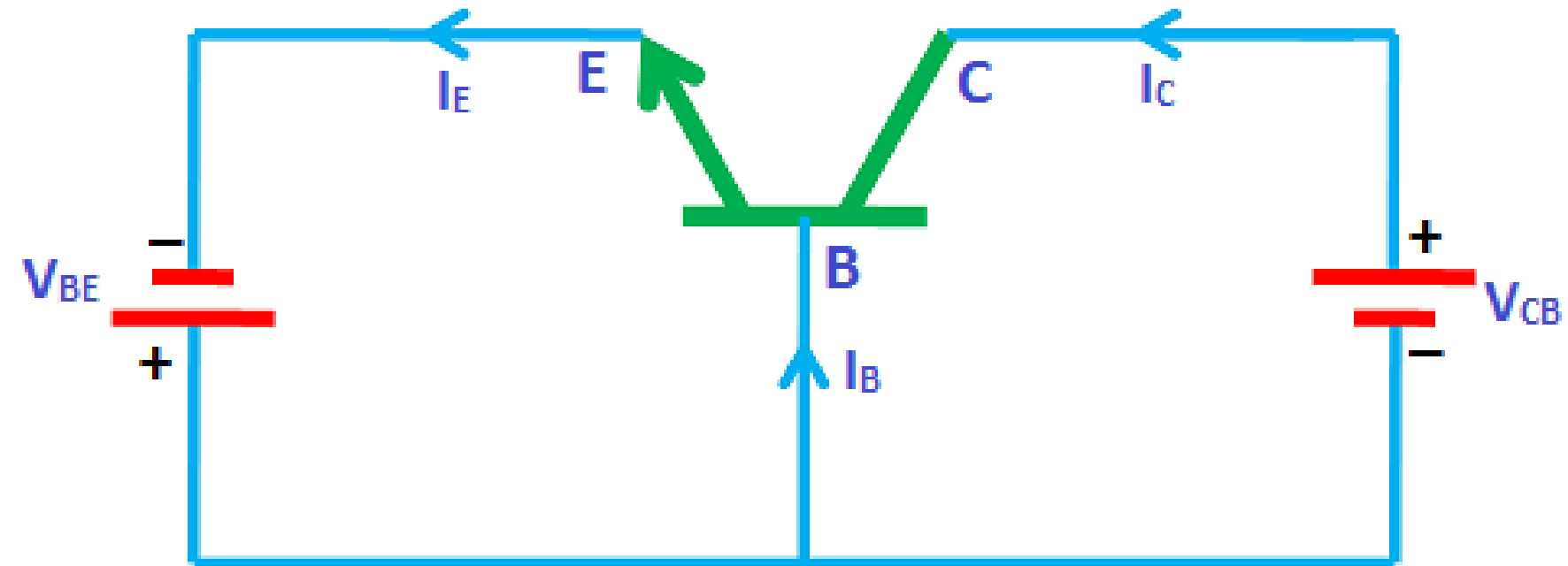

Active mode




NPN transistor

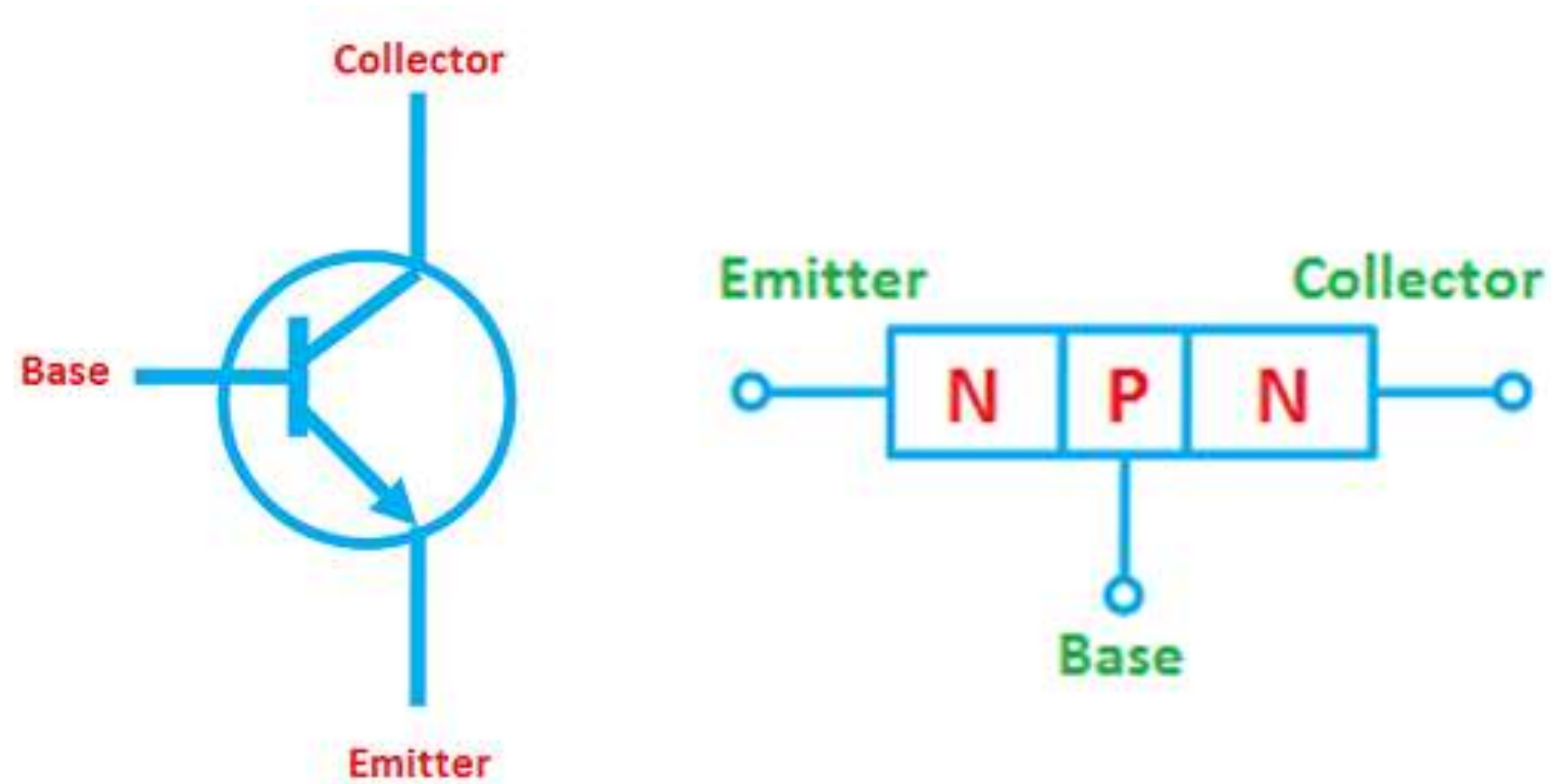

NPN transistor symbol




Working of NPN transistor- Unbiased

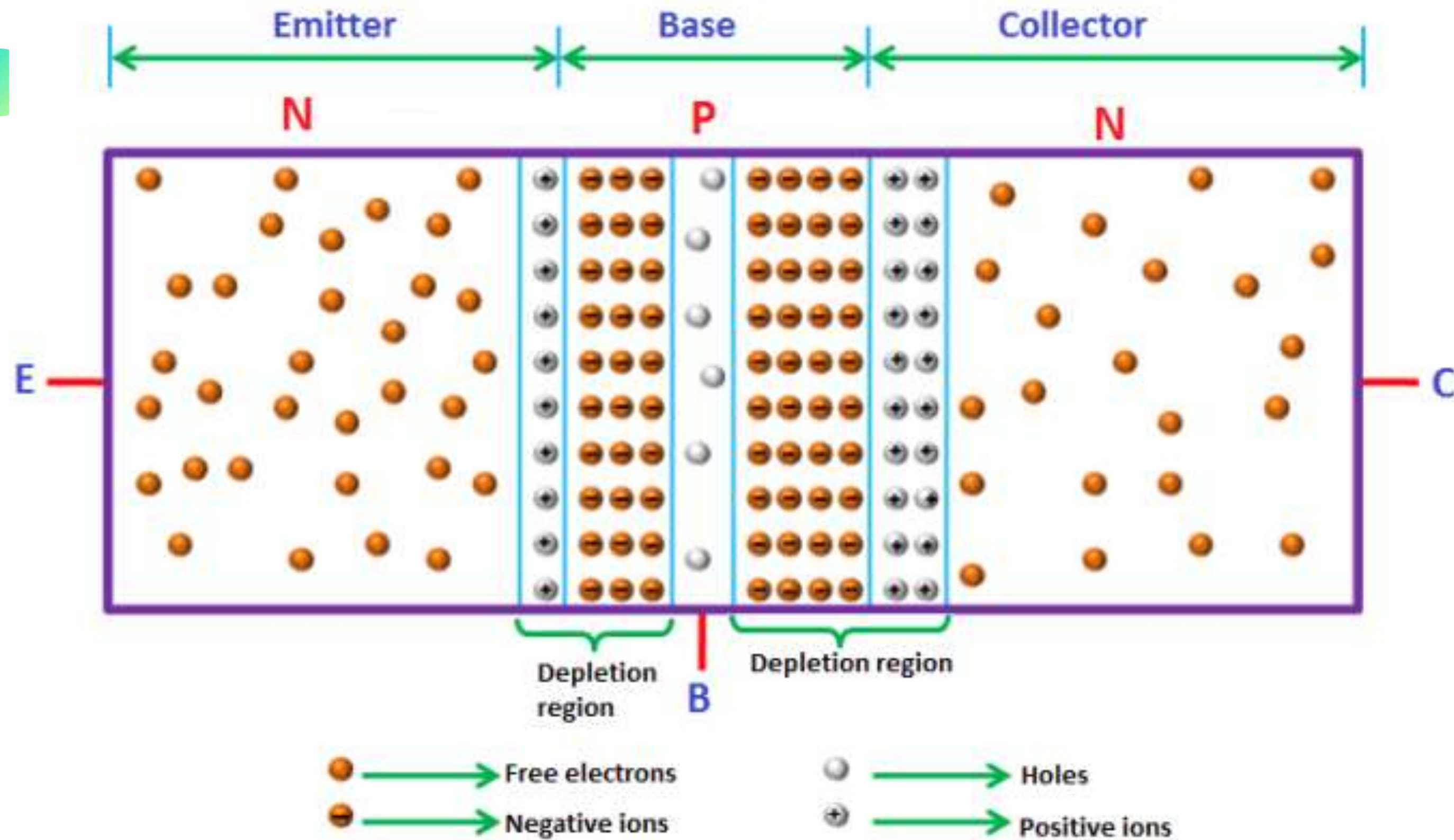





Working of NPN transistor- Biased

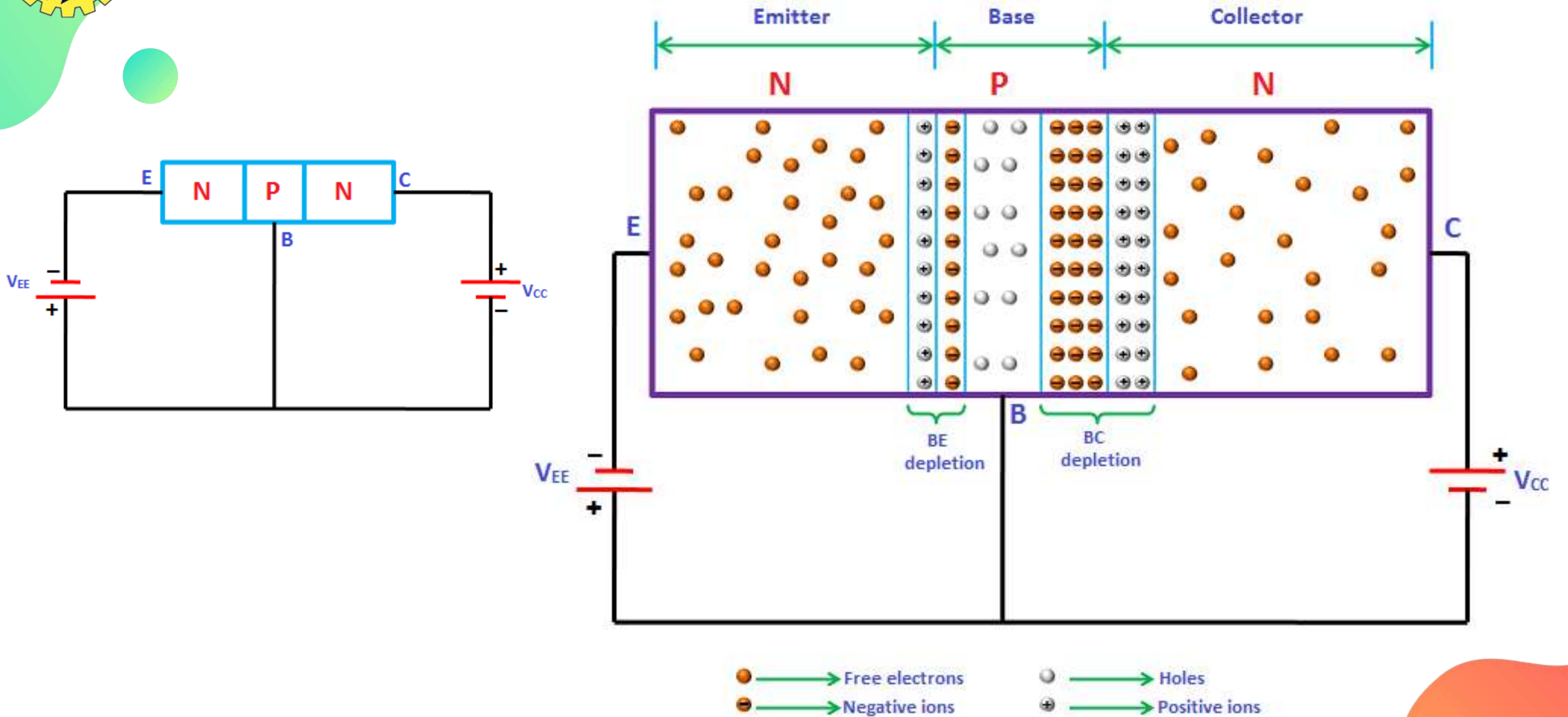




Current direction in NPN transistor

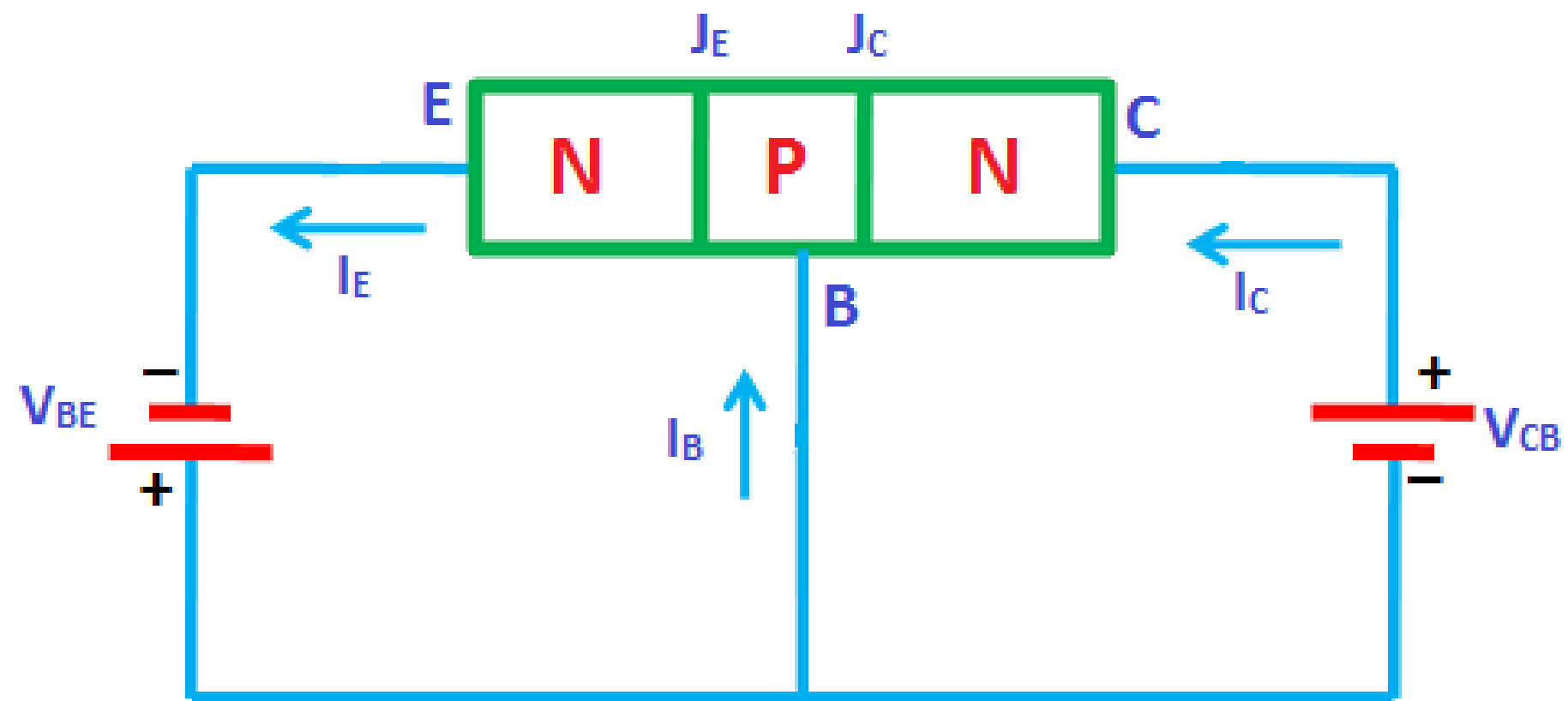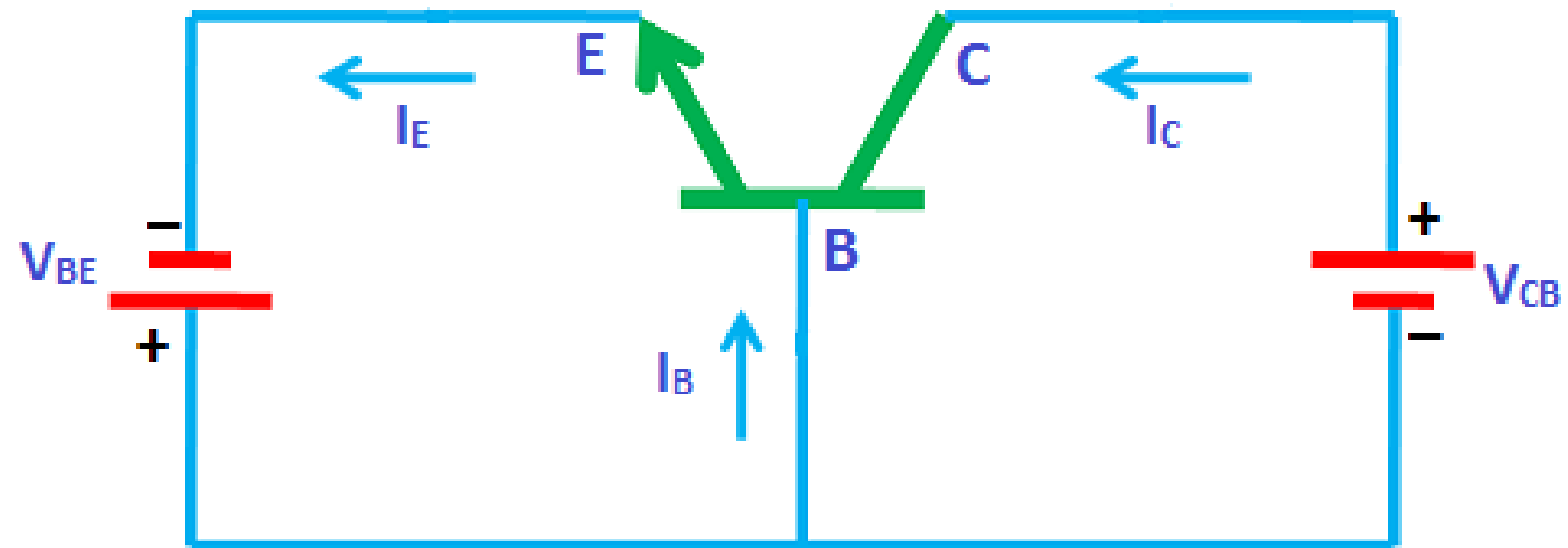




PNP Transistor

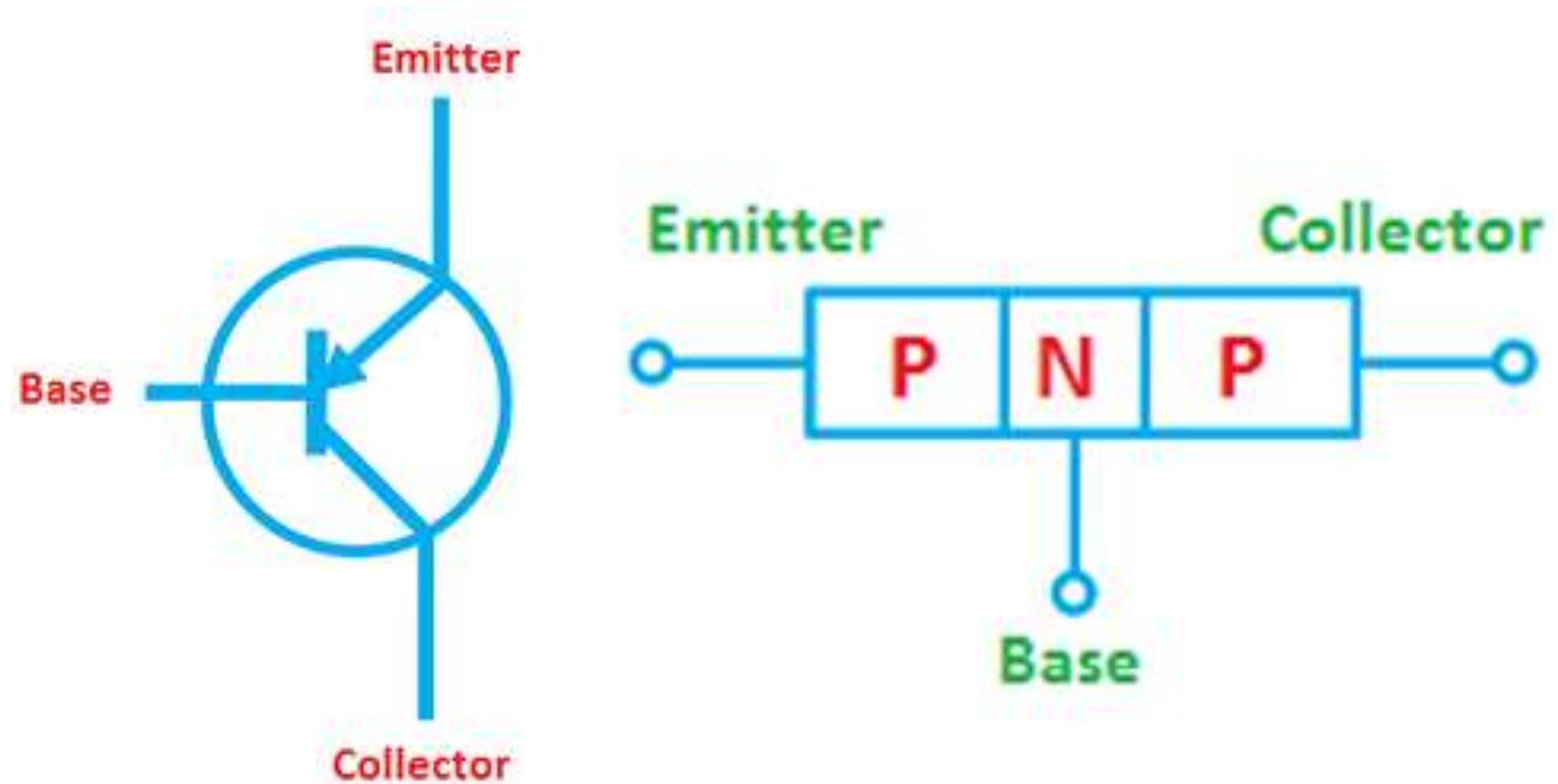

PNP transistor symbol




Working of NPN transistor- Unbiased

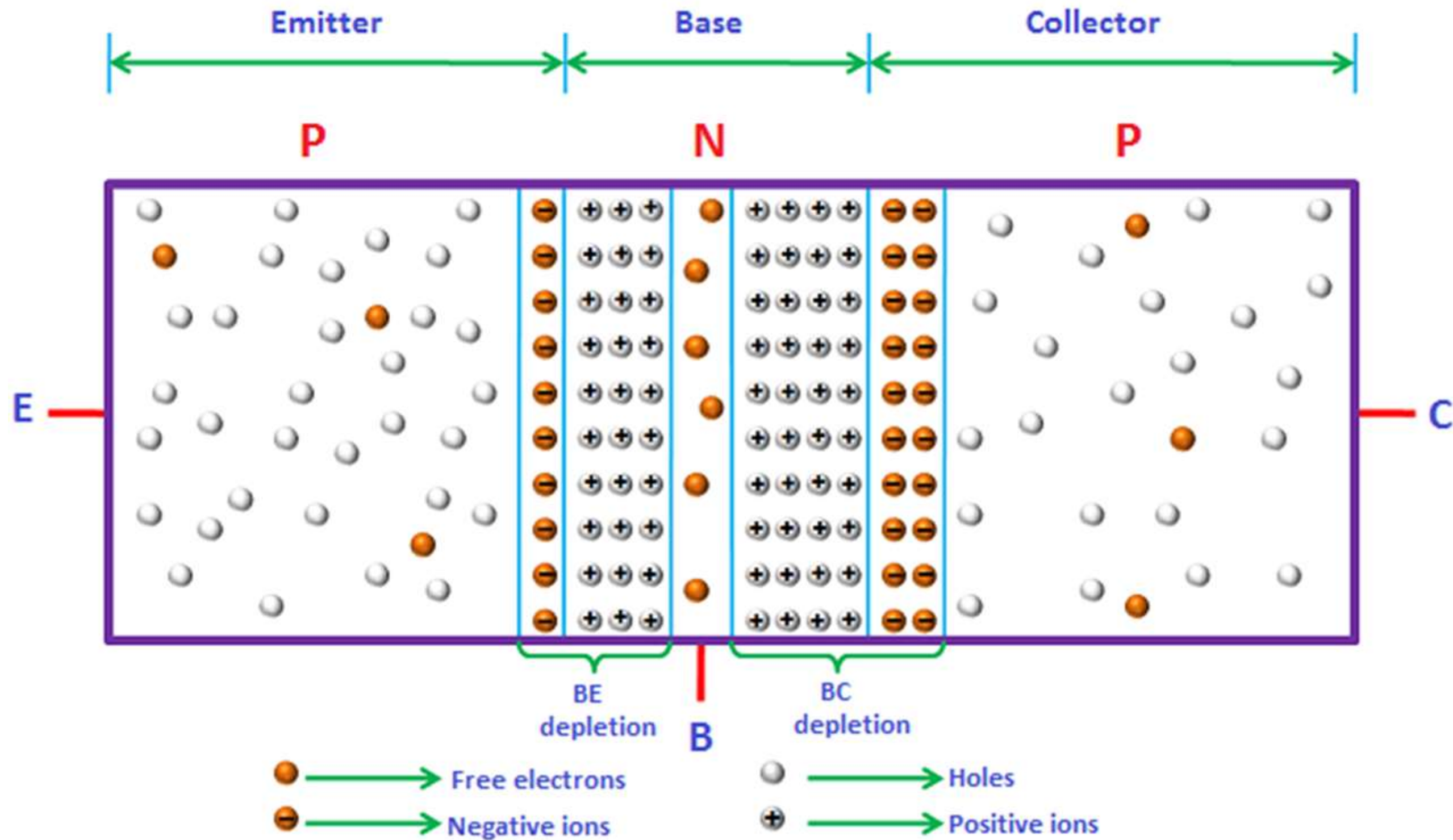





Working of NPN transistor- Biased

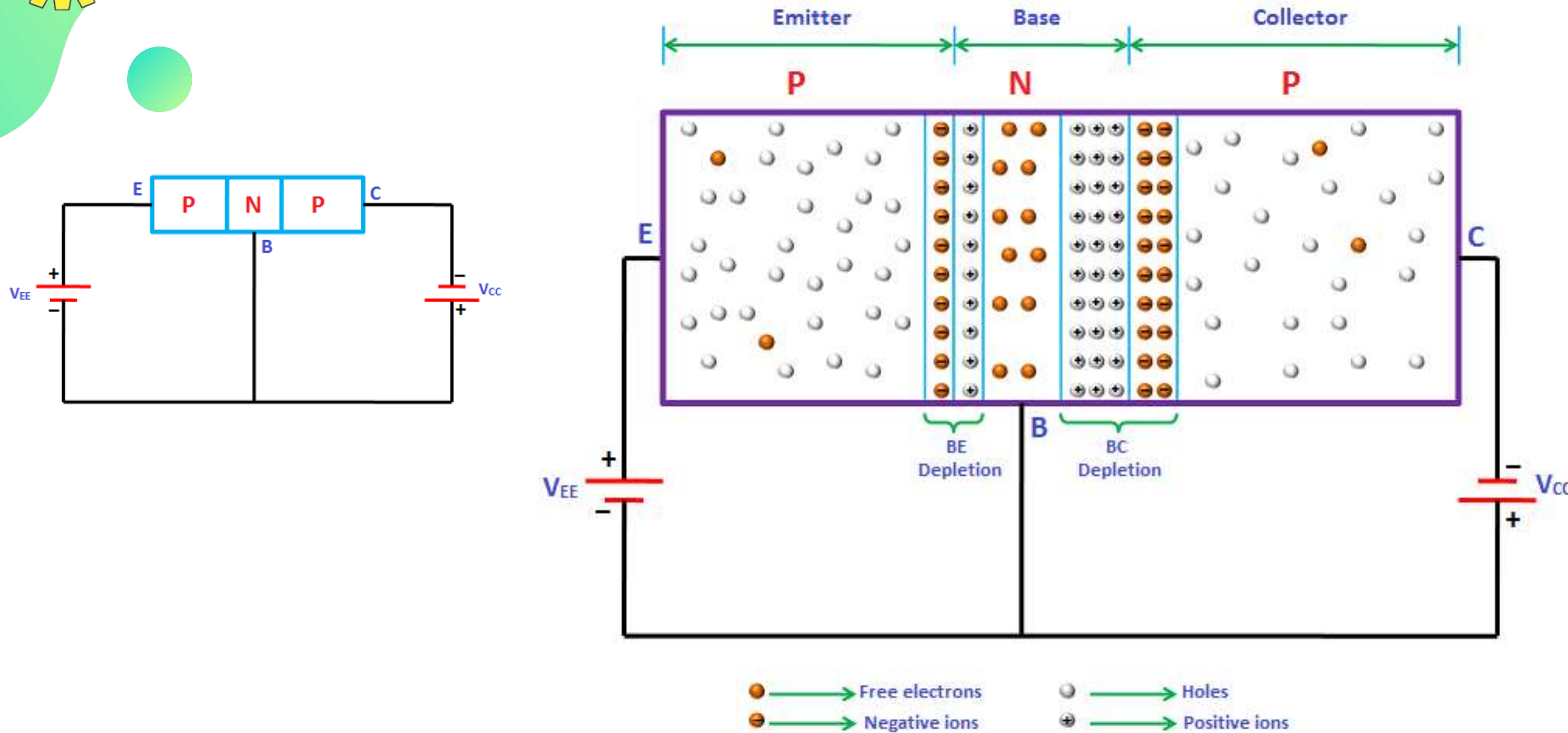



Current direction in PNP transistor

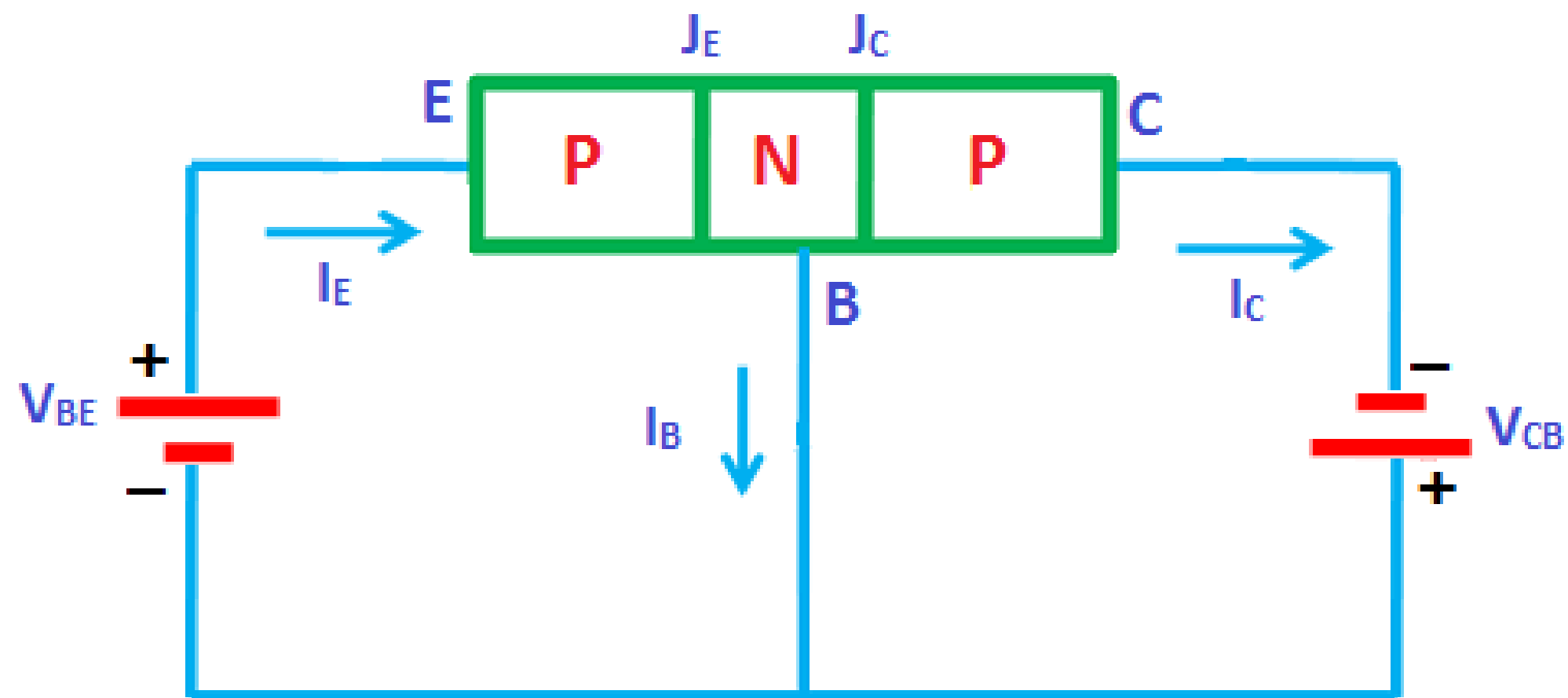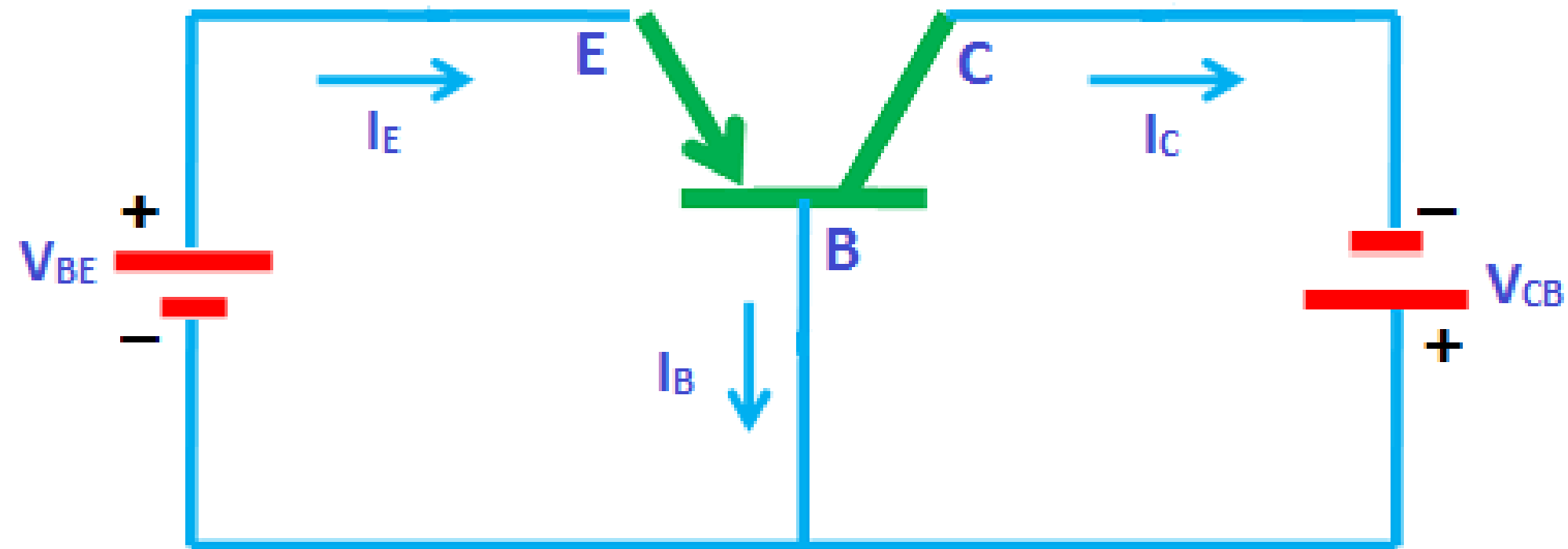



Types of Transistor Configuration




- We know that transistor has three terminals namely emitter (E), base (B), and collector (C). But to connect a transistor in the circuit, we need four terminals: two terminals for input and other two terminals for output.
- When a transistor is to be connected in a circuit, one terminal is used as the input terminal, the other terminal is used as the output terminal and the third terminal is common to the input and output.
- Depending upon the terminal which is used as a common terminal to the input and output terminals, the transistor can be connected in the following three configurations.

They are:


- ✓ Common base (CB) configuration
- ✓ Common emitter (CE) configuration
- ✓ Common collector (CC) configuration



Common base (CB) configuration

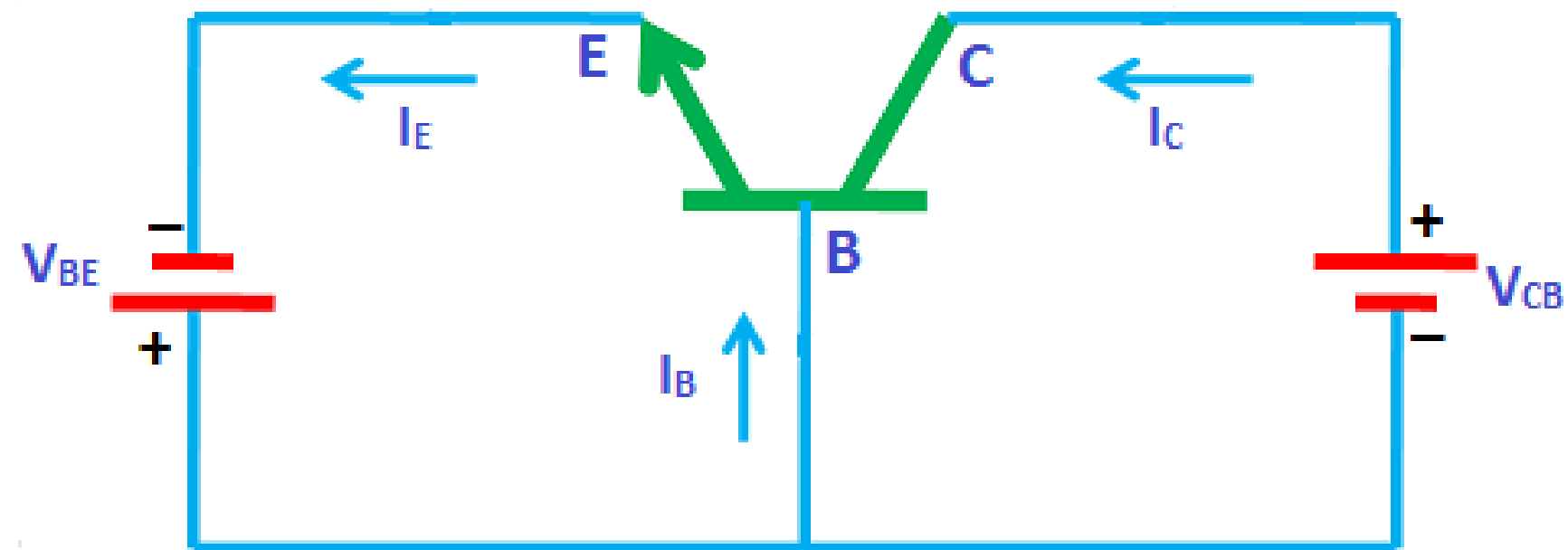


$$I_E = I_B + I_C$$

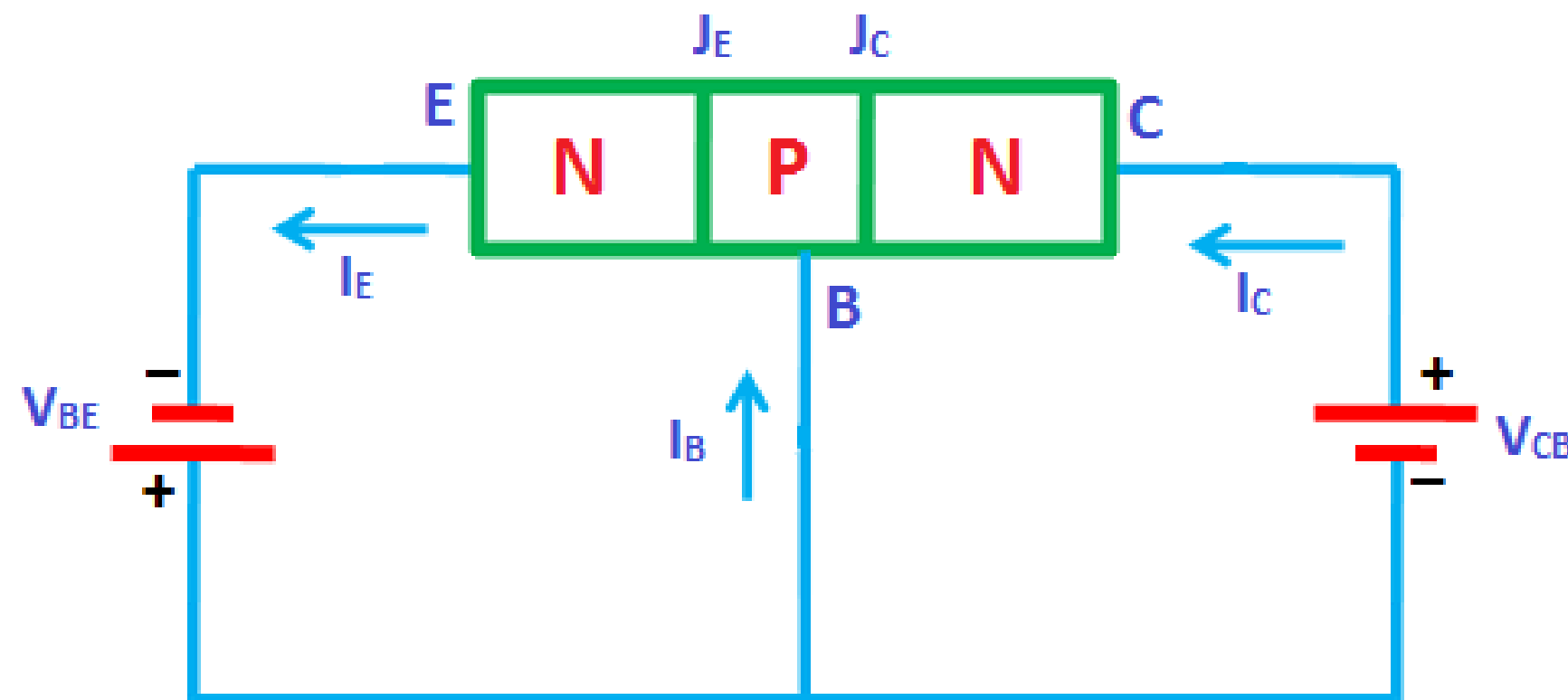


Common base configuration



Transistor Characteristics

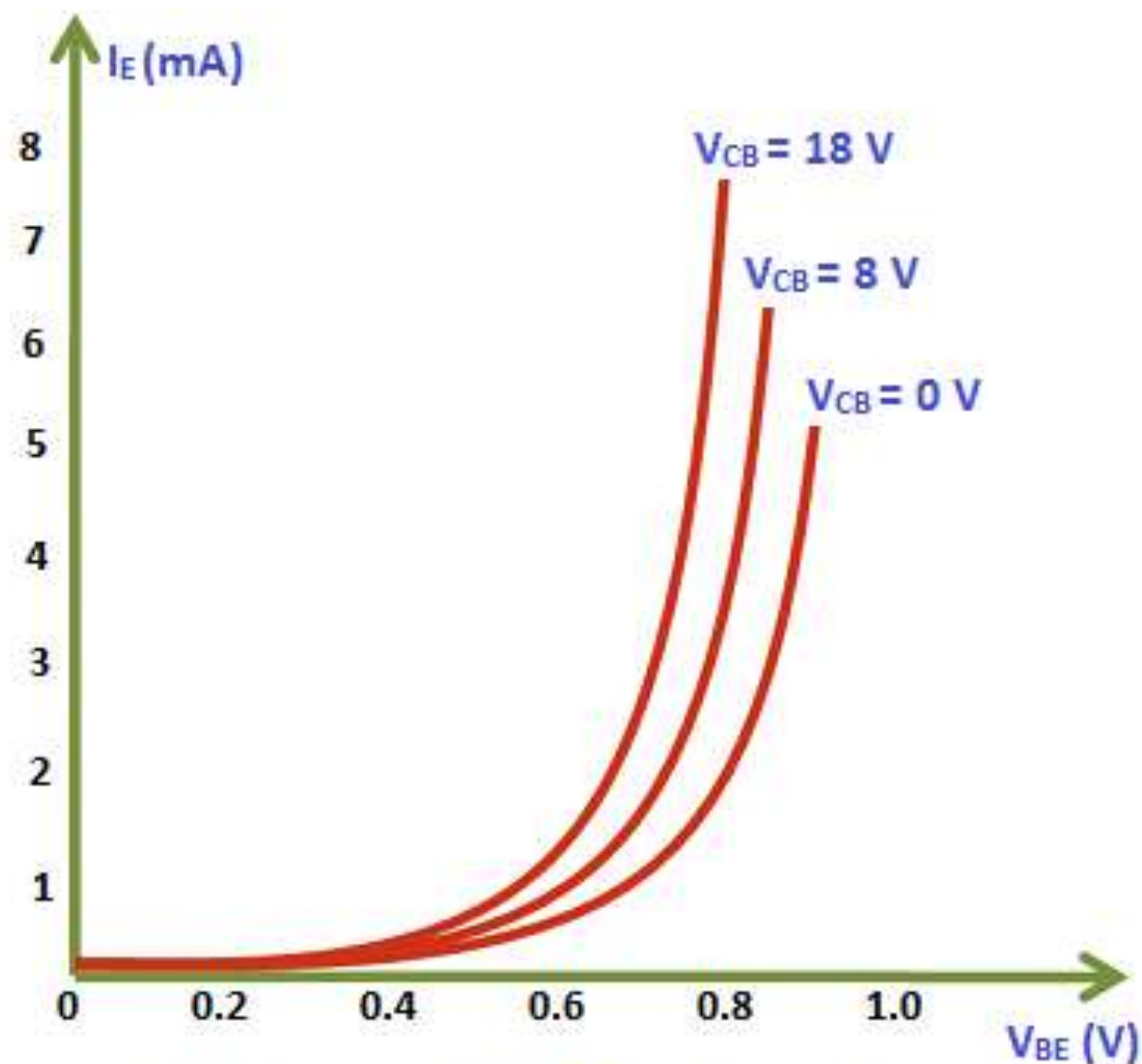

I/p characteristics CB configuration

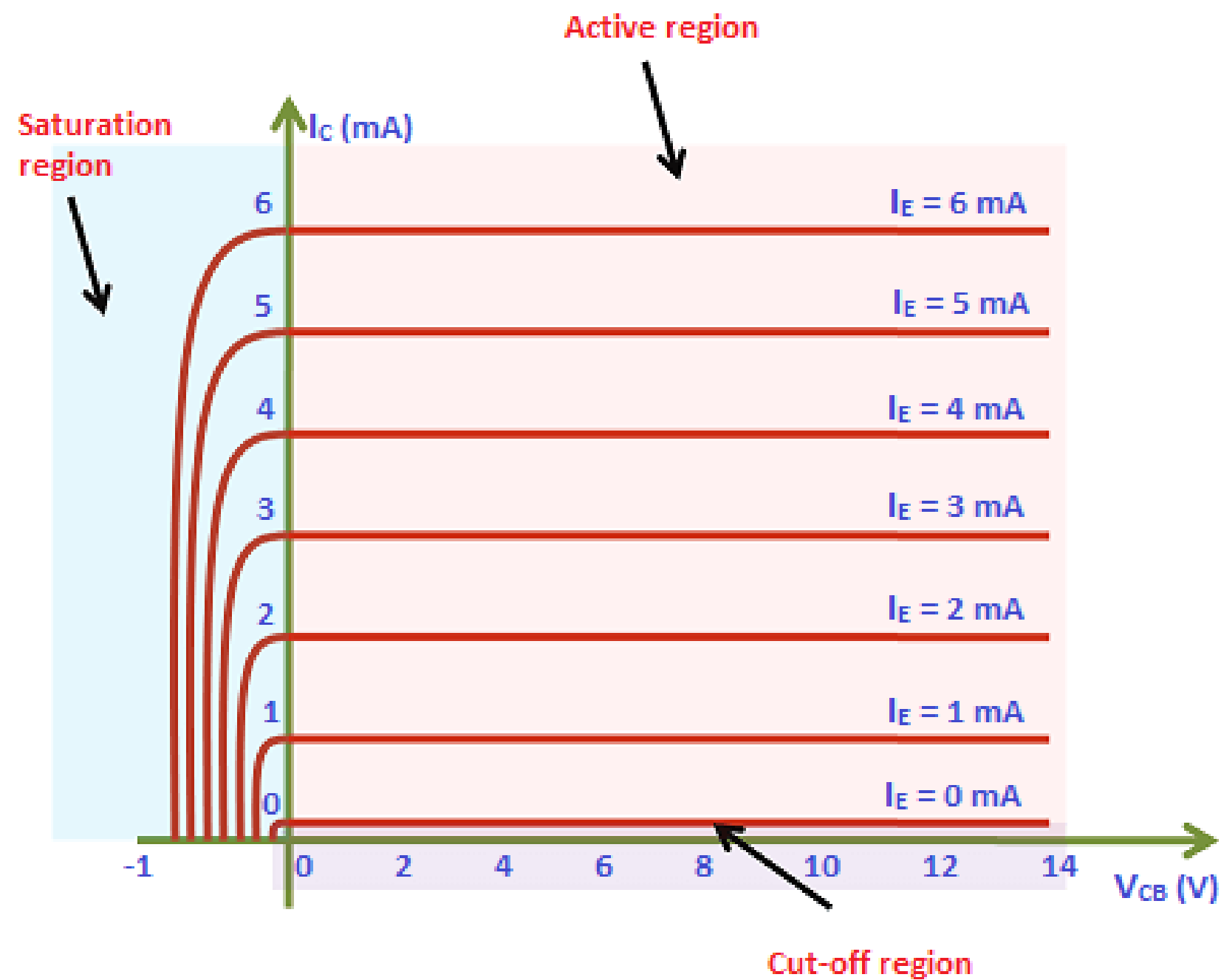

O/P characteristics CB configuration




Transistor Parameters




| Dynamic input resistance (r_i) | Dynamic output resistance (r_o) | Current gain (α) |
|---|---|--|
| <p>Dynamic input resistance is defined as the ratio of change in input voltage or emitter voltage (V_{BE}) to the corresponding change in input current or emitter current (I_E), with the output voltage or collector voltage (V_{CB}) kept at constant.</p> $r_i = \frac{\Delta V_{BE}}{\Delta I_E},$ $V_{CB} = \text{Constant}$ | <p>Dynamic output resistance is defined as the ratio of change in output voltage or collector voltage (V_{CB}) to the corresponding change in output current or collector current (I_C), with the input current or emitter current (I_E) kept at constant.</p> $r_o = \frac{\Delta V_{CB}}{\Delta I_C},$ $I_E = \text{Constant}$ | <p>The current gain of a transistor in CB configuration is defined as the ratio of output current or collector current (I_C) to the input current or emitter current (I_E).</p> $\alpha = \frac{I_C}{I_E}$ |



Common Emitter Configuration

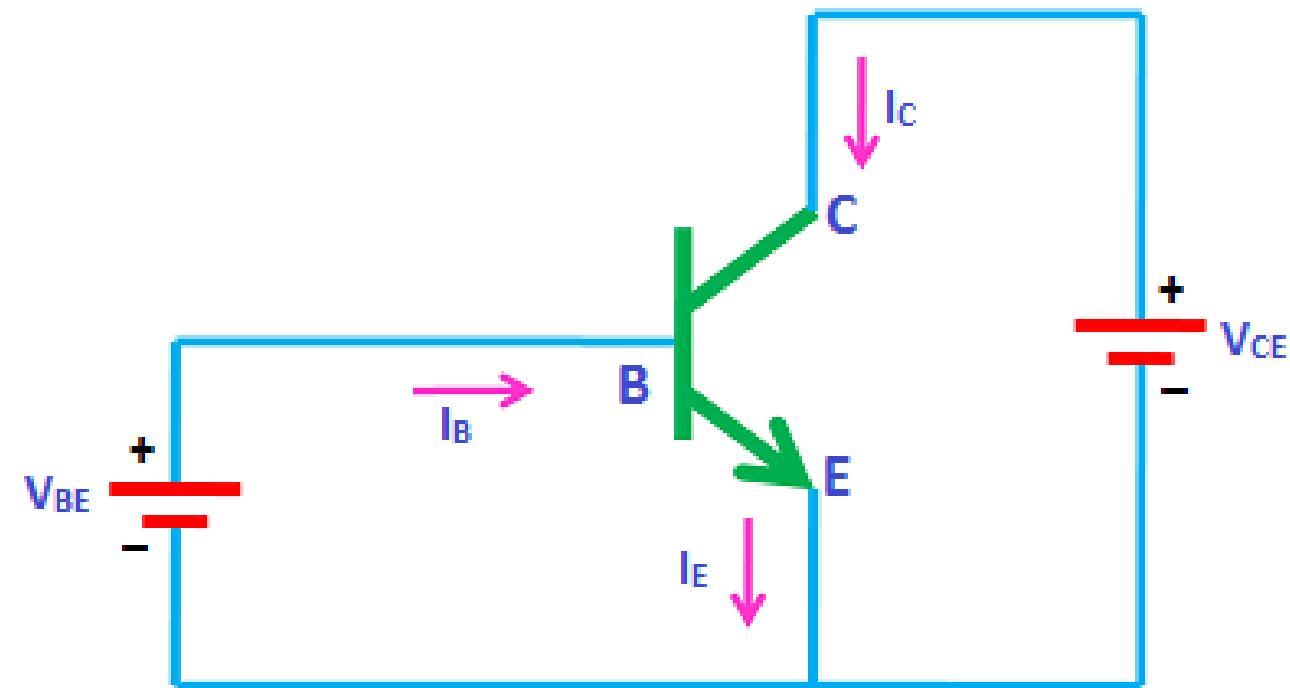


$$I_E = I_B + I_C$$

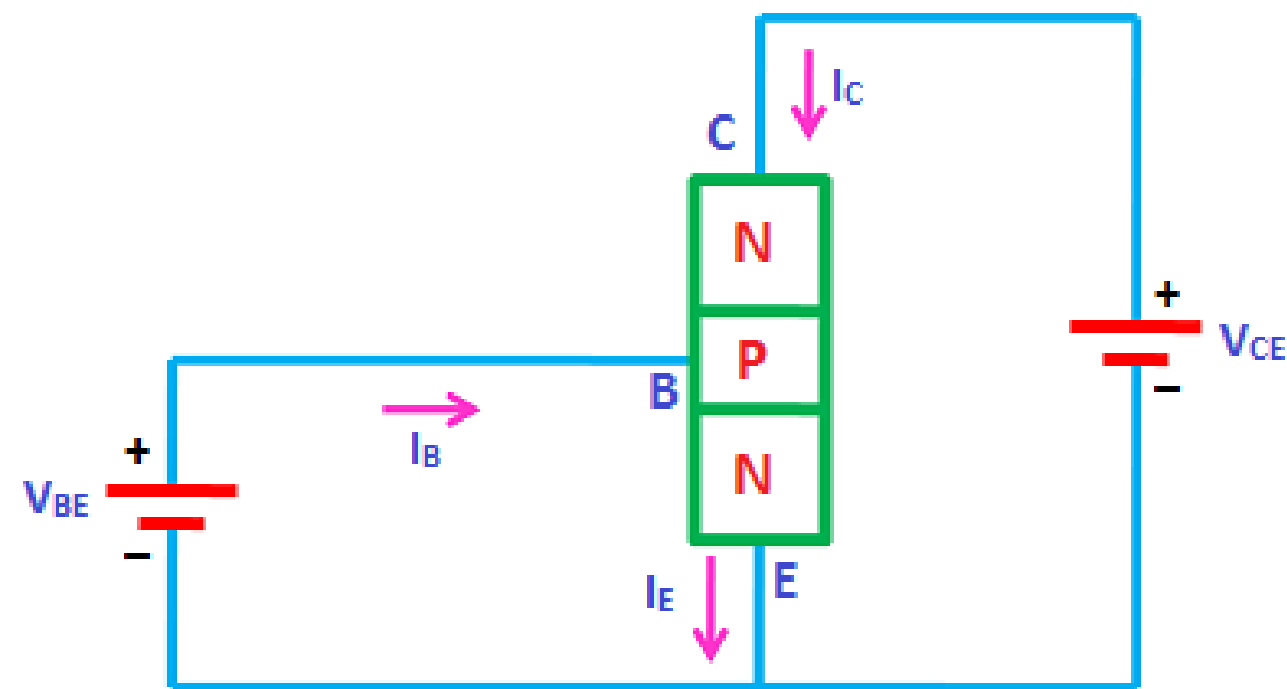


Common emitter configuration



Transistor Characteristics

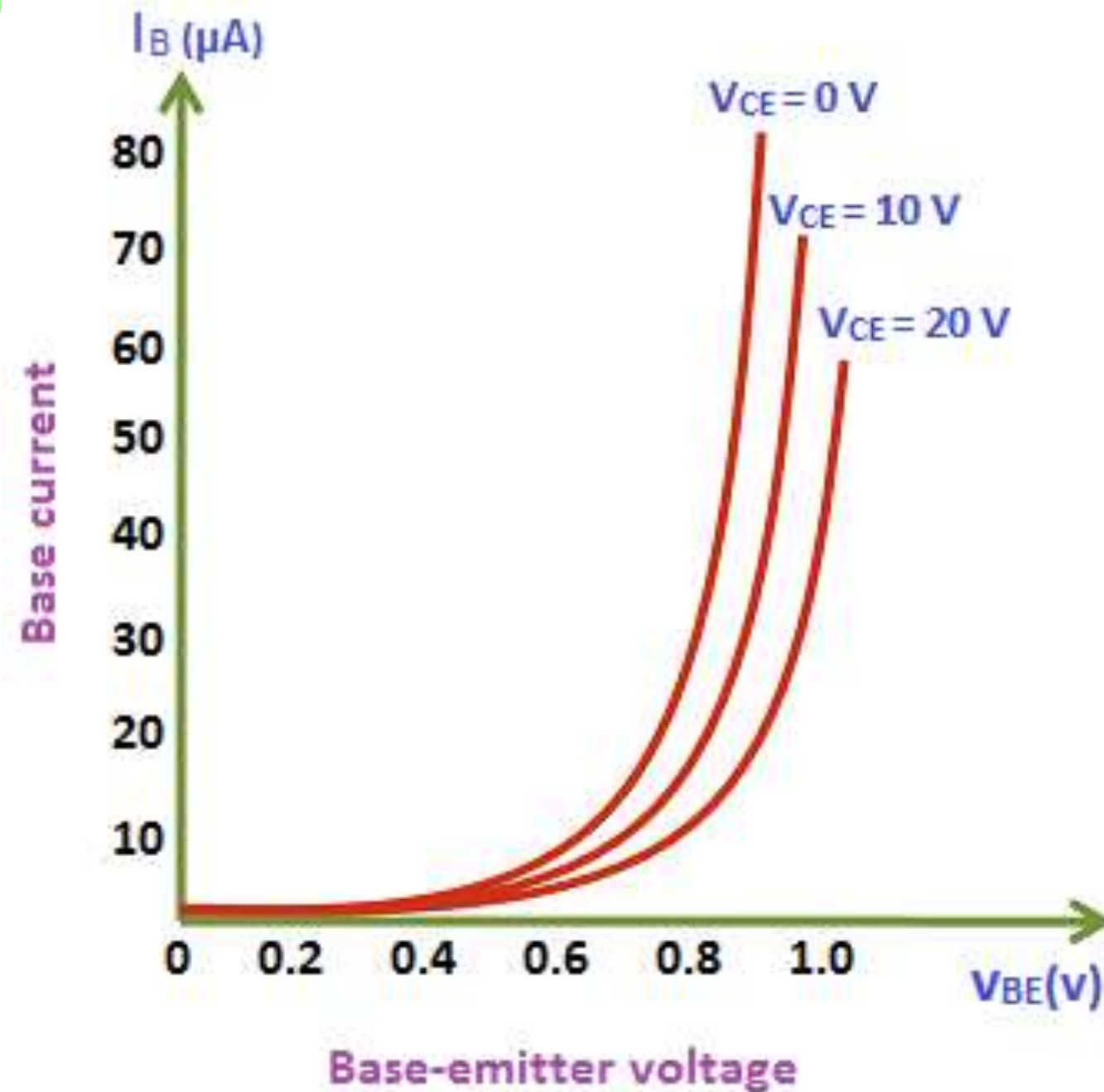

I/P characteristics CE configuration

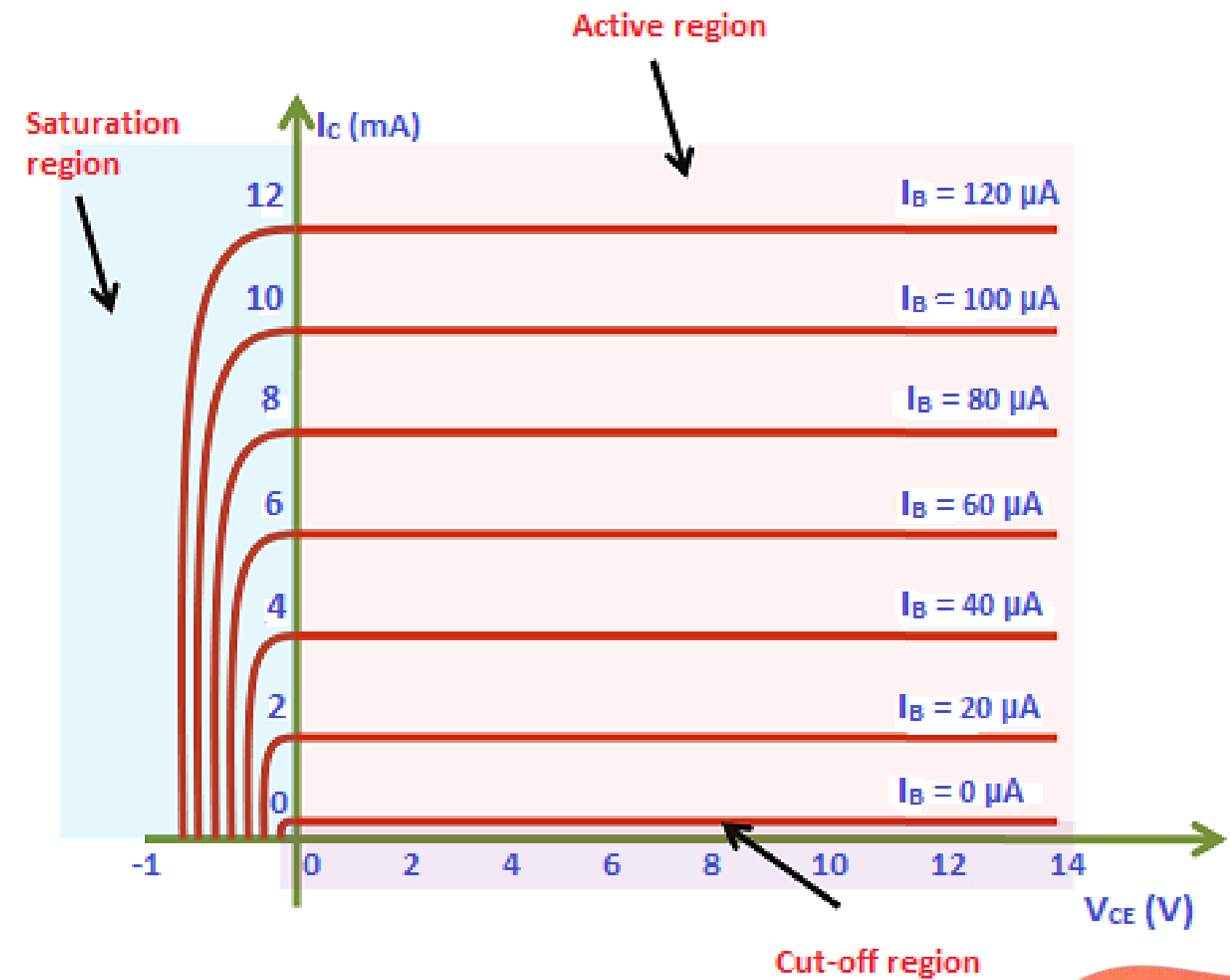

O/P Characteristics CE Configuration





Transistor Parameters



| Dynamic input resistance (r_i) | Dynamic output resistance (r_o) | Current gain (α) |
|---|--|---|
| <p>Dynamic input resistance is defined as the ratio of change in input voltage or base voltage (V_{BE}) to the corresponding change in input current or base current (I_B), with the output voltage or collector voltage (V_{CE}) kept at constant.</p> $r_i = \frac{\Delta V_{BE}}{\Delta I_B},$ $V_{CE} = \text{Constant}$ | <p>Dynamic output resistance is defined as the ratio of change in output voltage or collector voltage (V_{CE}) to the corresponding change in output current or collector current (I_C), with the input current or base current (I_B) kept at constant.</p> $r_o = \frac{\Delta V_{CE}}{\Delta I_C},$ $I_B = \text{Constant}$ | <p>The current gain of a transistor in CE configuration is defined as the ratio of output current or collector current (I_C) to the input current or base current (I_B).</p> $\alpha = \frac{I_C}{I_B}$ |




Common Collector Configuration

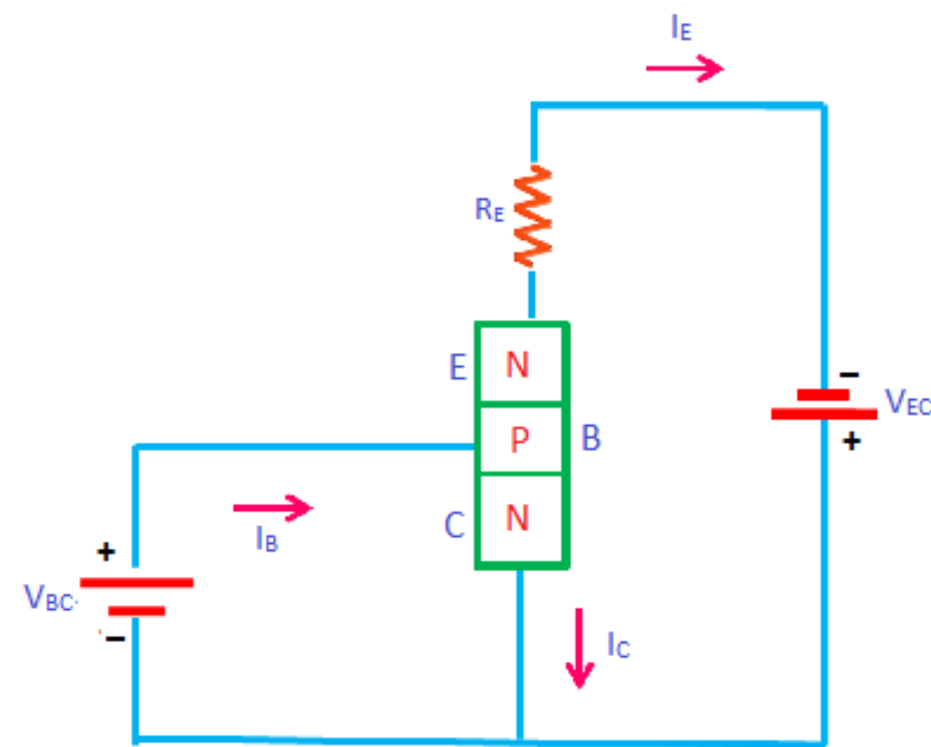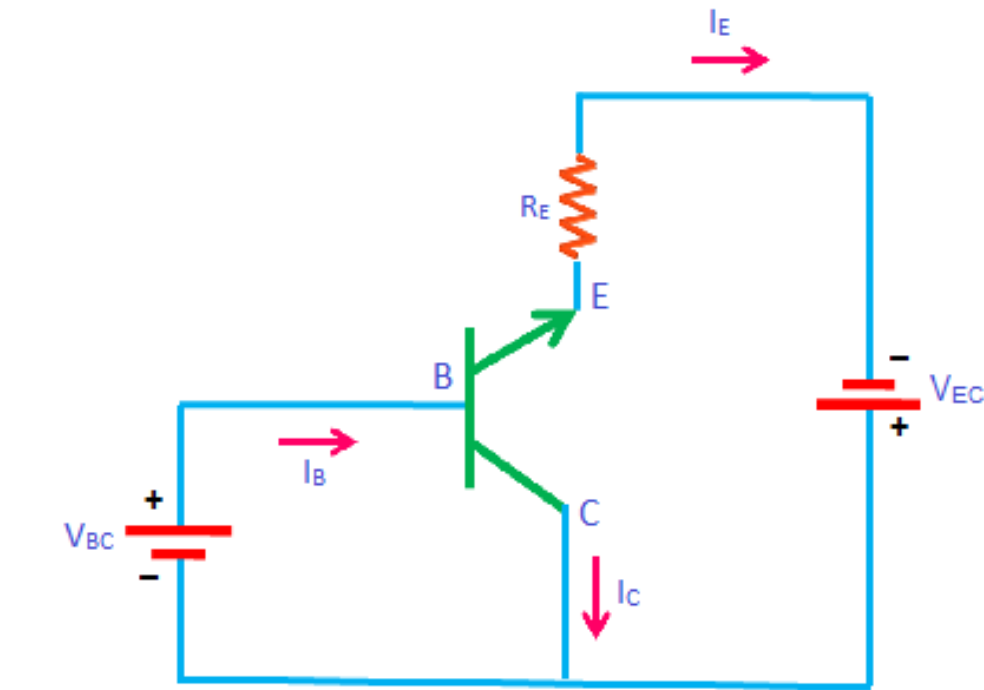


Common collector configuration



Transistor Characteristics

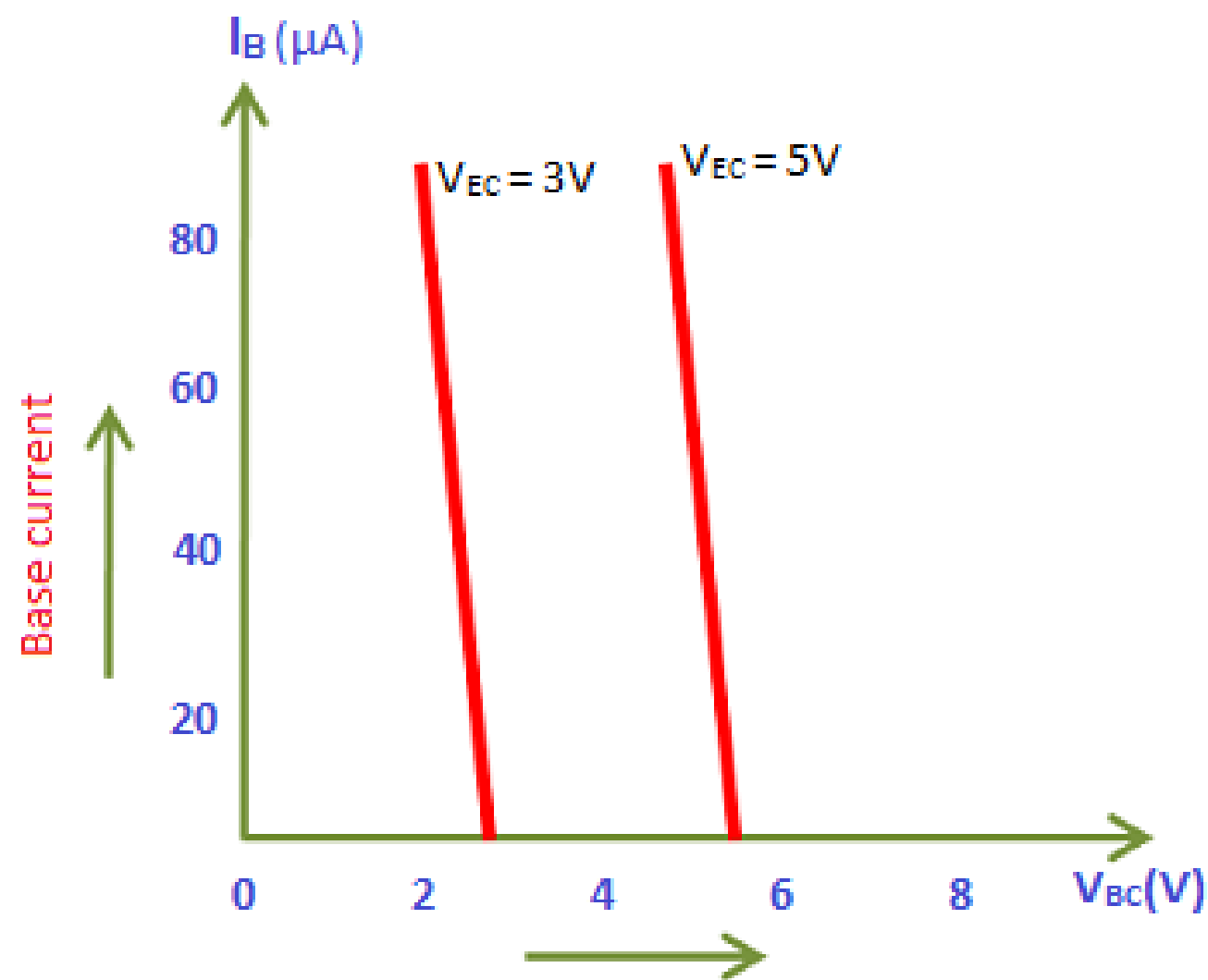

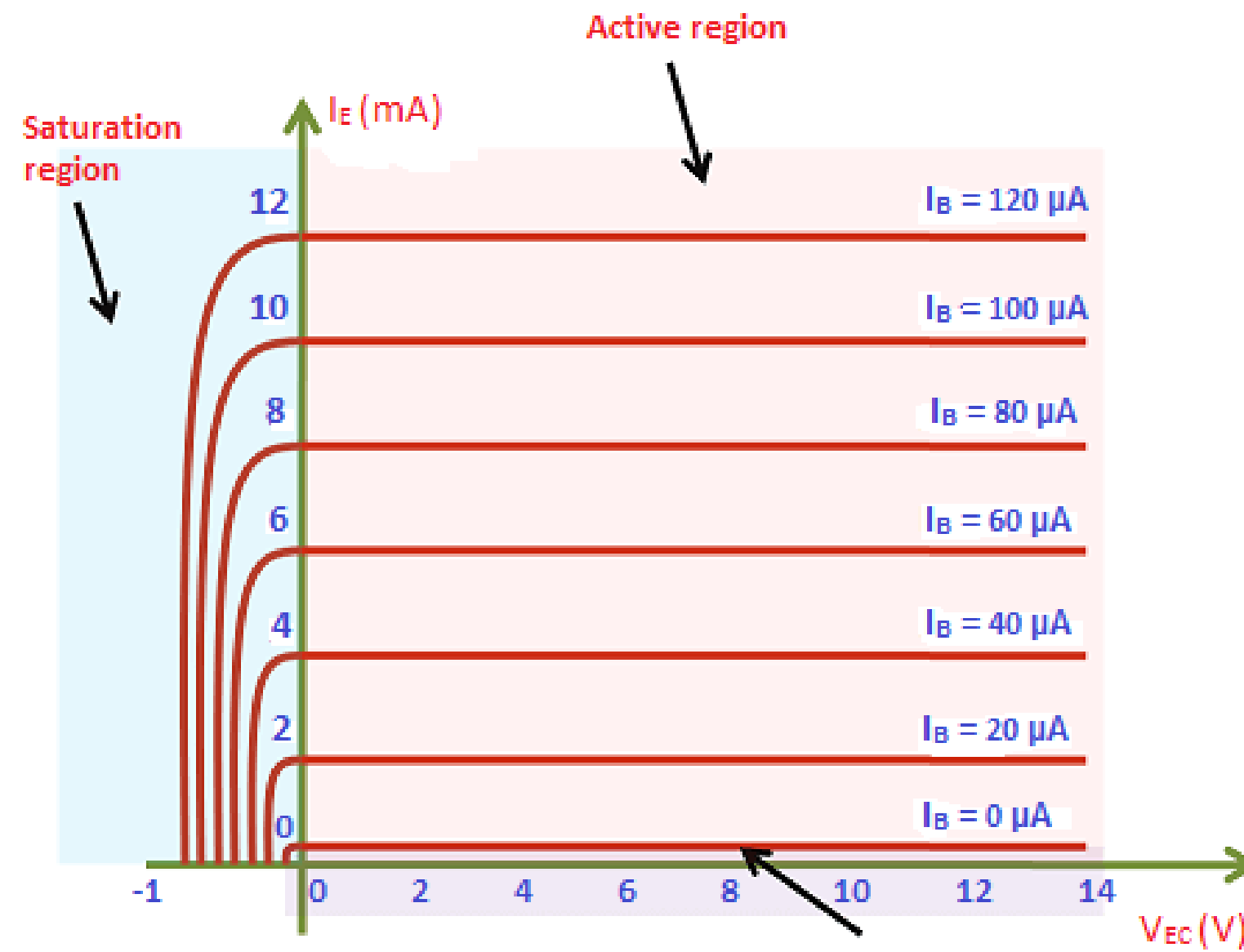Base-collector voltage
Input characteristics



Output characteristics



Transistor Parameters

| Dynamic input resistance (r_i) | Dynamic output resistance (r_o) | Current gain (α) |
|---|--|---|
| <p>Dynamic input resistance is defined as the ratio of change in input voltage or base voltage (V_{BC}) to the corresponding change in input current or base current (I_B), with the output voltage or emitter voltage (V_{EC}) kept at constant.</p> $r_i = \frac{\Delta V_{BC}}{\Delta I_B},$ $V_{CE} = \text{Constant}$ | <p>Dynamic output resistance is defined as the ratio of change in output voltage or emitter voltage (V_{EC}) to the corresponding change in output current or emitter current (I_E), with the input current or base current (I_B) kept at constant.</p> $r_o = \frac{\Delta V_{CE}}{\Delta I_E},$ $I_B = \text{Constant}$ | <p>The current gain of a transistor in CE configuration is defined as the ratio of output current or collector current (I_C) to the input current or base current (I_B).</p> $\gamma = \frac{\Delta I_E}{\Delta I_B}$ |



SUMMARY



ASSESSMENT

Dear student,

Quiz is posted in your Google class room

Allotted time for quiz is 5 min

No of Questions is 10





KEEP
LEARNING..
Thank u

SEE YOU IN NEXT CLASS