

# **SNS COLLEGE OF TECHNOLOGY**

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

# DEPARTMENT OF MECHATRONICS

## 19MCB302- INDUSTRIAL ELECTRONCIS & APPLICATION

III YEAR V SEM

**UNIT 1 – PHASE CONTROLLED CONVERTERS** 

**TOPIC** -Single Phase controlled Rectifier

Mr. M.Anand., M.E.,(Ph.D.,)

ASSISTANT PROFESSOR,

DEPARTMENT OF MECHATRONICS,

SNSCT, Coimbatore.



#### **APPLICATION**






Ammeter




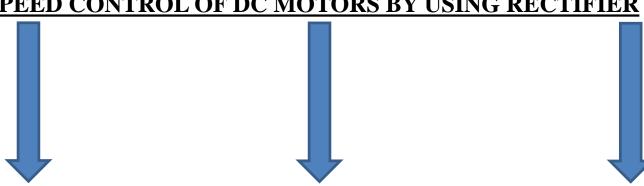
#### SPEED CONTROL OF DC MOTORS BY USING RECTIFIER



By changing the voltage or current value in the *field or armature* of the DC Motor

DC Series Motor DC Shunt Motor

Rectifier is a device which is used to convert the Fixed AC into Variable (Controlled DC)






#### **RECTIFIER-Single Phase**




#### **RECTIFIER-Three Phase**

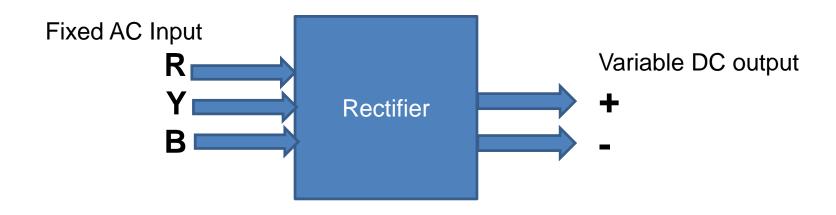






#### **Bridge Full Wave Rectifier**

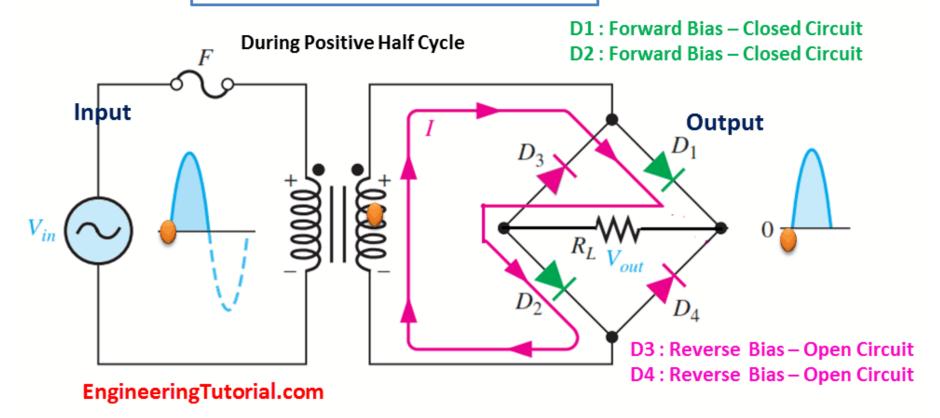





# Single phase controlled Converter



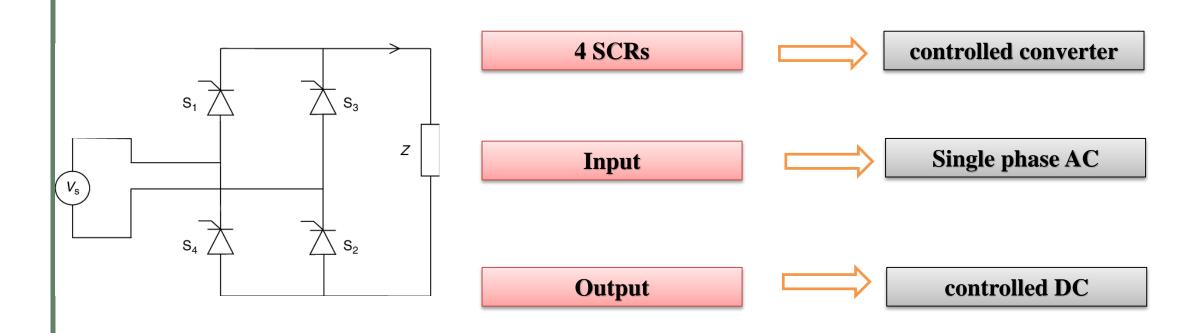



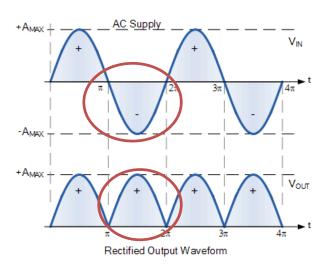

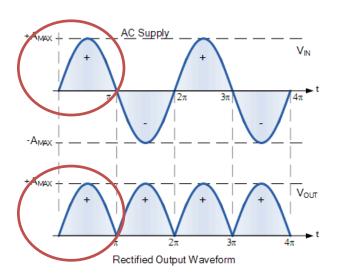


### **Uncontrolled Rectifier**



#### **Controlled Rectifier**


# Waveforms

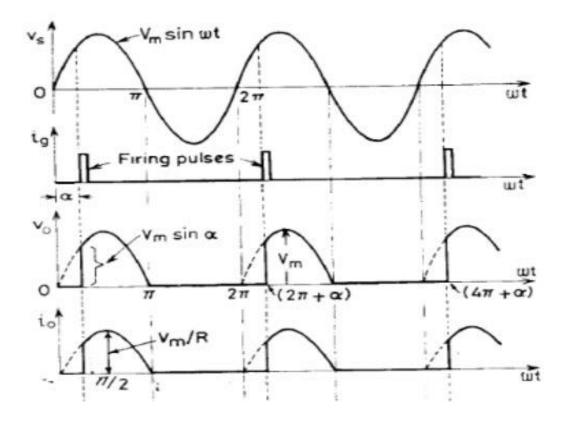


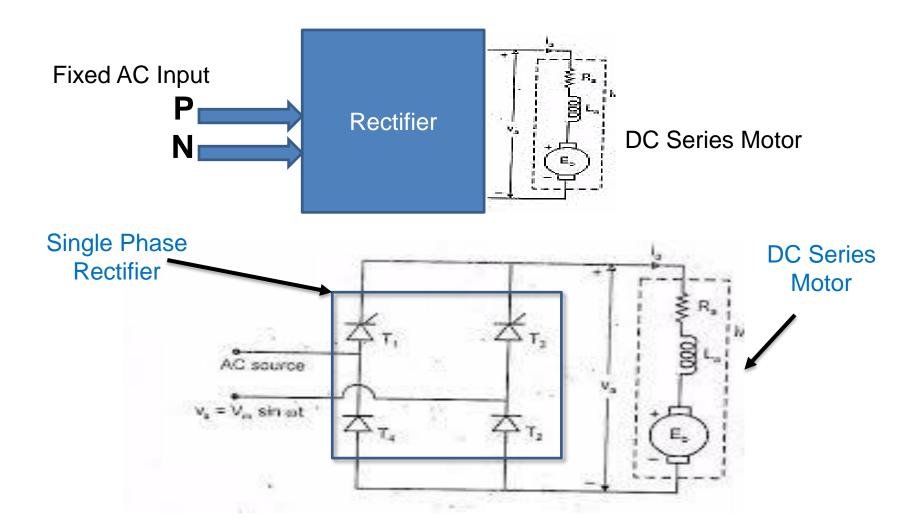
#### **Speed control of DC Motor (Series) by Single phase RECTIFIER**










#### **Speed control of DC Motor (Series) by Single phase RECTIFIER**

#### Firing Angle

0 to 90 degree phase shit rectangle pulse – Generated by Function generator

Input 230 V AC Supply 50 Hz P, N

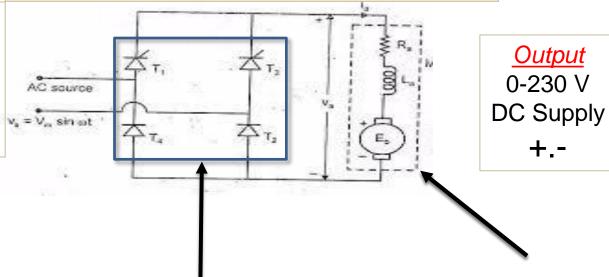

#### How SCR Works

For SCR operation, We have to give the Firing angle (Small amount of voltage) Given to the SCR


- Single Phase Rectifier consist of 4 SCRs named T1, T2, T3 and T4
- It Converts the AC Volt into DC Volt (As Like Bridge Diode Rectifier Principle)
- Output Voltage controlled by changing the firing input given to the 4 SCR

Speed of the DC Series Motor can be vary by the changing the firing angle given to the SCR




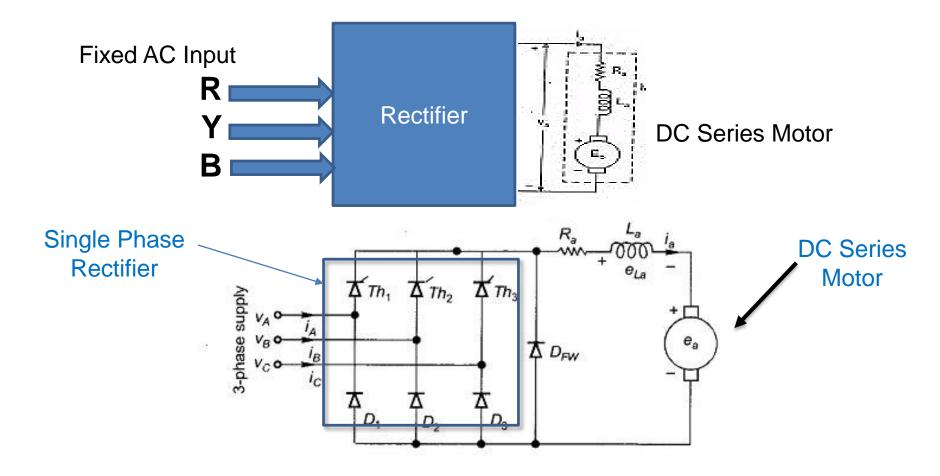
#### **Speed control of DC Motor (Series) by Three phase RECTIFIER**






#### **ASSESSMENT**


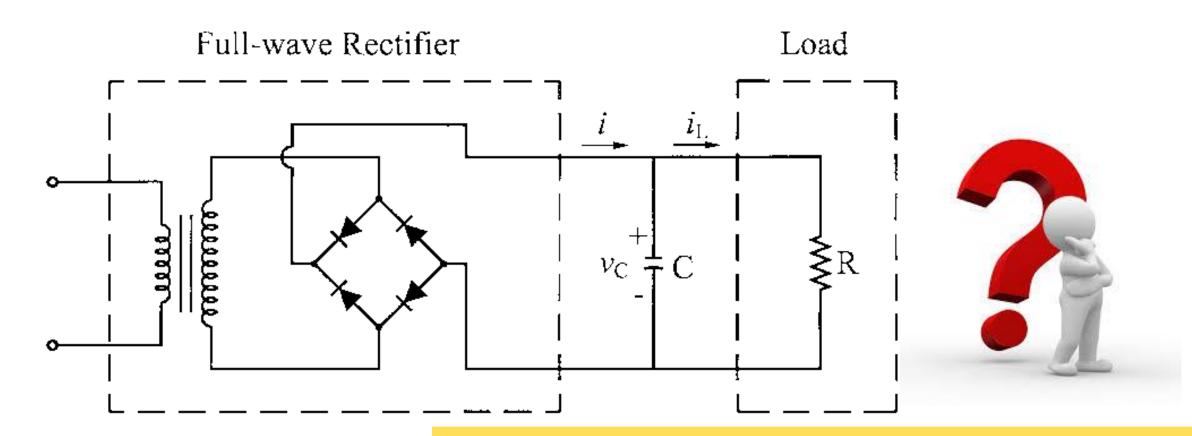
# Find the Input & output of the following Circuit.





#### References



- 1. <a href="https://www.sakthistabilizer.in/phase-converter.html">https://www.sakthistabilizer.in/phase-converter.html</a>
- 2. <a href="https://en.wikipedia.org/wiki/Phase\_converter">https://en.wikipedia.org/wiki/Phase\_converter</a>
- 3. <a href="https://www.youtube.com/watch?v=3-9YBY9Xzfs">https://www.youtube.com/watch?v=3-9YBY9Xzfs</a>

