



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF MECHATRONICS

### **19MCB302 – INDUSTRIAL ELECTRONICS & APPLICATION** III YEAR V SEM

#### UNIT 3 – DC TO DC CONVERTER

#### TOPIC – Step Up Chopper

Mr. M.Anand., M.E.,(Ph.D.,)

ASSISTANT PROFESSOR,

DEPARTMENT OF MECHATRONICS,

SNSCT, Coimbatore.





## APPLICATION





## Intro-Chopper


The DC **Choppers** convert the input DC voltage into fixed or variable DC output. Hence DC **chopper** is also called as dc to dc converter.




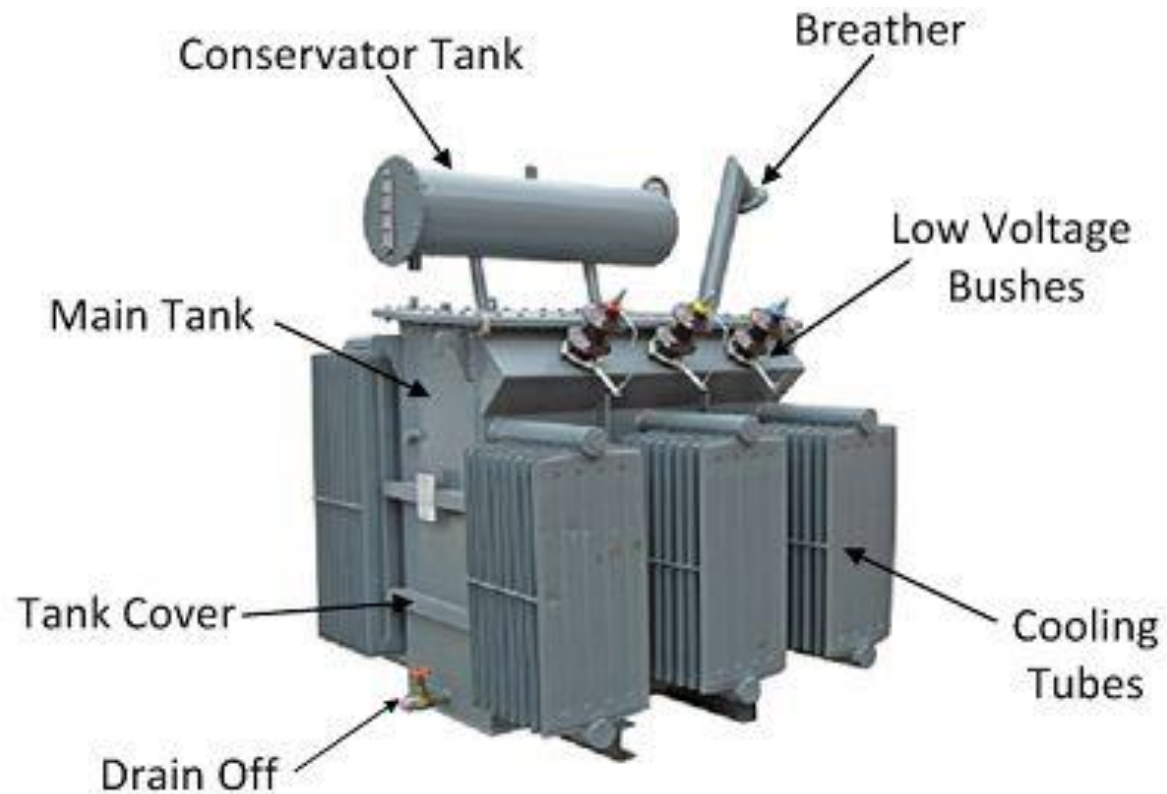
## Chopper

Chopper can increase or decrease the DC voltage level at its opposite side. So, chopper serves the same purpose in DC circuit transfers in case of ac circuit. So it is also known as DC transformer.



**Transformer**

Circuit Globe Application -



# Chopper




Devices used in Chopper

Low power application: GTO, IGBT, Power BJT, Power MOSFET etc.

High power application: Thyristor or SCR.

These devices are represented as a switch in a dotted box for simplicity. When it is closed current can flow in the direction of arrow only.

chopper switch

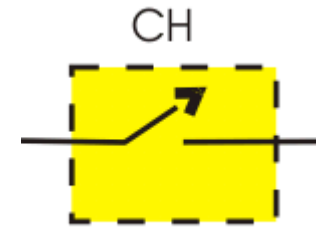




# Chopper
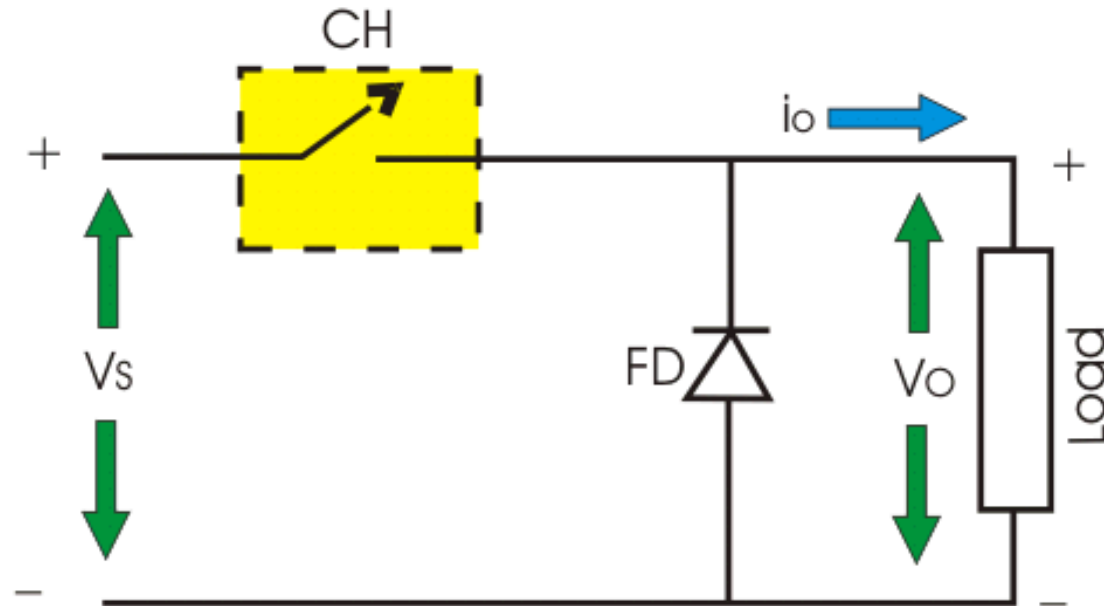
## 1) Step down Chopper :


Step down chopper as Buck converted is used to reduce the i/p voltage level at the output side




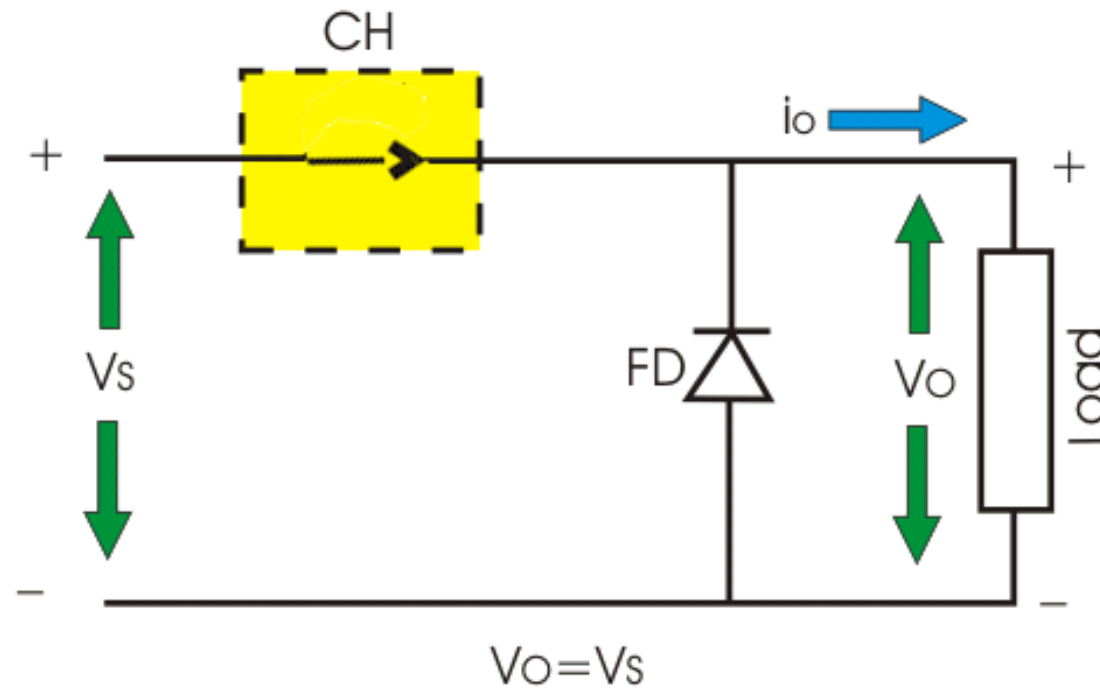
## Chopper


When CH is turned ON,  $V_s$  directly appears across the load as shown in figure. So  $V_o = V_s$ .




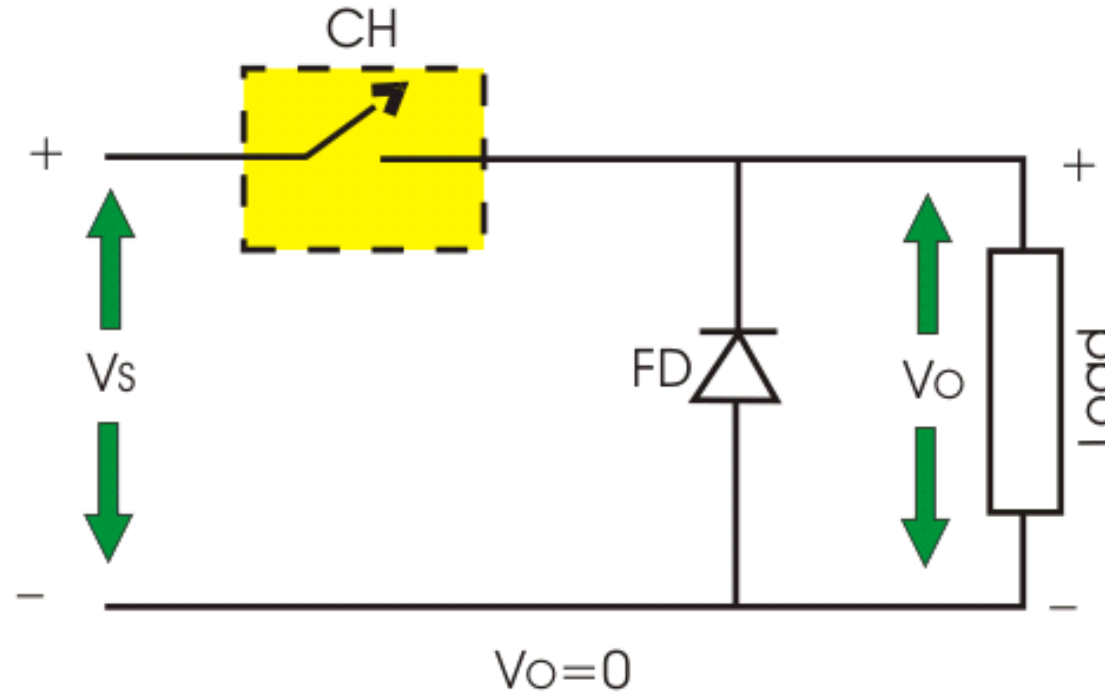
## Chopper

When CH is turned off,  $V_s$  is disconnected from the load. So output voltage  $V_o = 0$ .







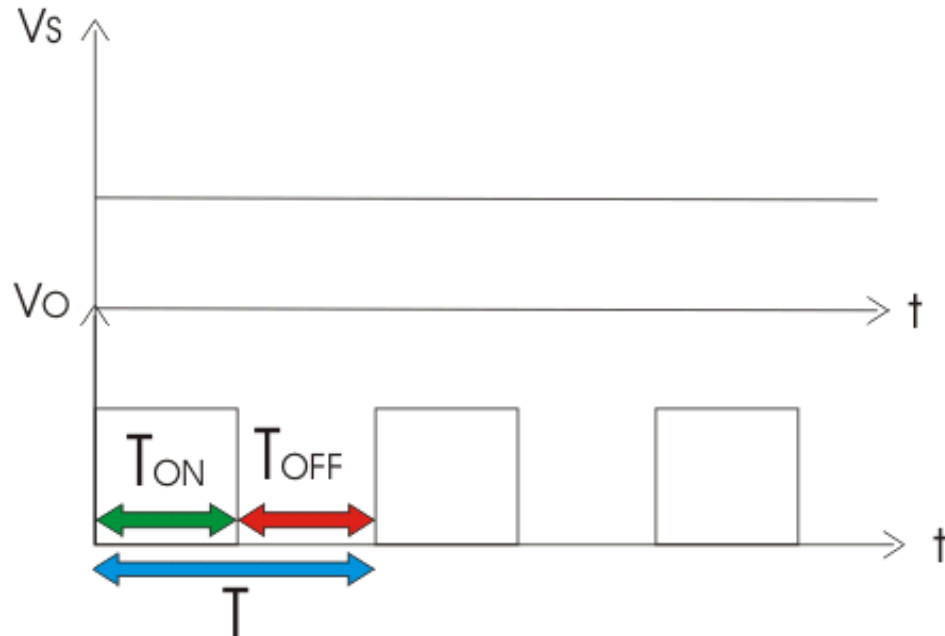
# Chopper



The voltage waveform of step down chopper is shown below:



$T_{ON}$  → It is the interval in which chopper is in ON state.

$T_{OFF}$  → It is the interval in which chopper is in OFF state.

$V_S$  → Source or input voltage.

$V_o$  → Output or load voltage.

$T$  → Chopping period =  $T_{ON} + T_{OFF}$



# Chopper



During ON time of Chopper

$$V_s = V_L + V_o \Rightarrow V_L = V_s - V_o \Rightarrow L \frac{di}{dt} = V_s - V_o \Rightarrow L \frac{\Delta I}{T_{ON}} = V_s - V_o$$

Therefore, peak to peak load current,

$$\Delta I = \frac{V_s - V_o}{L} T_{ON} \dots \dots \dots (i)$$



## Chopper



### During OFF Time of Chopper

If inductance value of  $L$  is very large, so load current will be continuous in nature. When CH is OFF inductor reverses its polarity and discharges. This current freewheels through diode FD.

$$\text{Therefore, } L \frac{di}{dt} = V_o$$
$$L \frac{\Delta I}{T_{OFF}} = V_o \Rightarrow \Delta I = V_o \frac{T_{OFF}}{L} \dots \dots \dots (ii)$$

By equating (i) and (ii)

$$\frac{V_s - V_o}{L} T_{ON} = \frac{V_o}{L} T_{OFF}$$
$$\frac{V_s - V_o}{V_o} = \frac{T_{OFF}}{T_{ON}}$$
$$\frac{V_s}{V_o} = \frac{T_{ON} - T_{OFF}}{T_{ON}}$$
$$\text{Therefore, } V_o = \frac{T_{ON}}{T} V_s = DV_s$$




## Single phase Uncontrolled Converter

**DC Fixed Voltage**




**DC Output Voltage  
(Step up)**

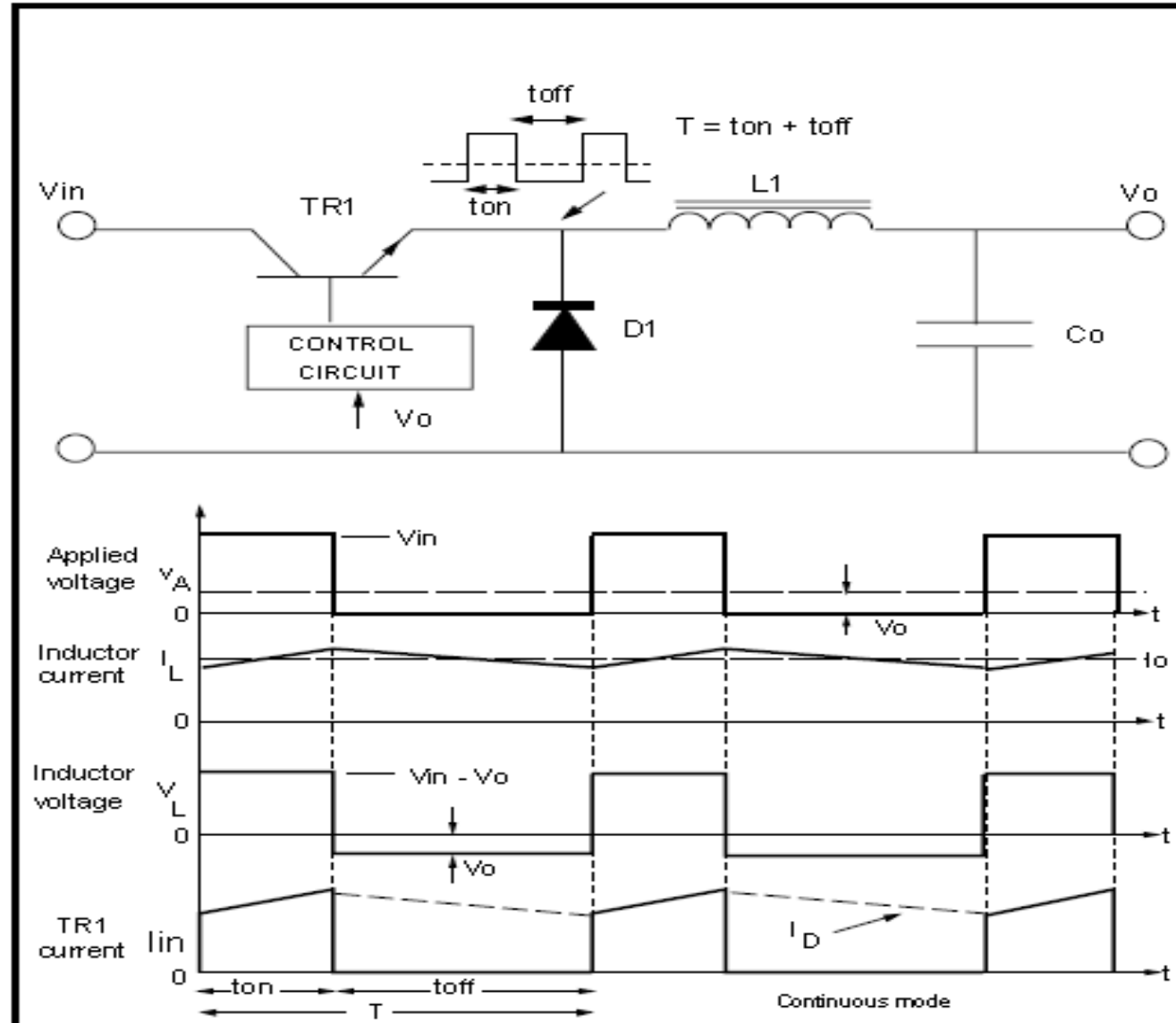




## Output Waveform

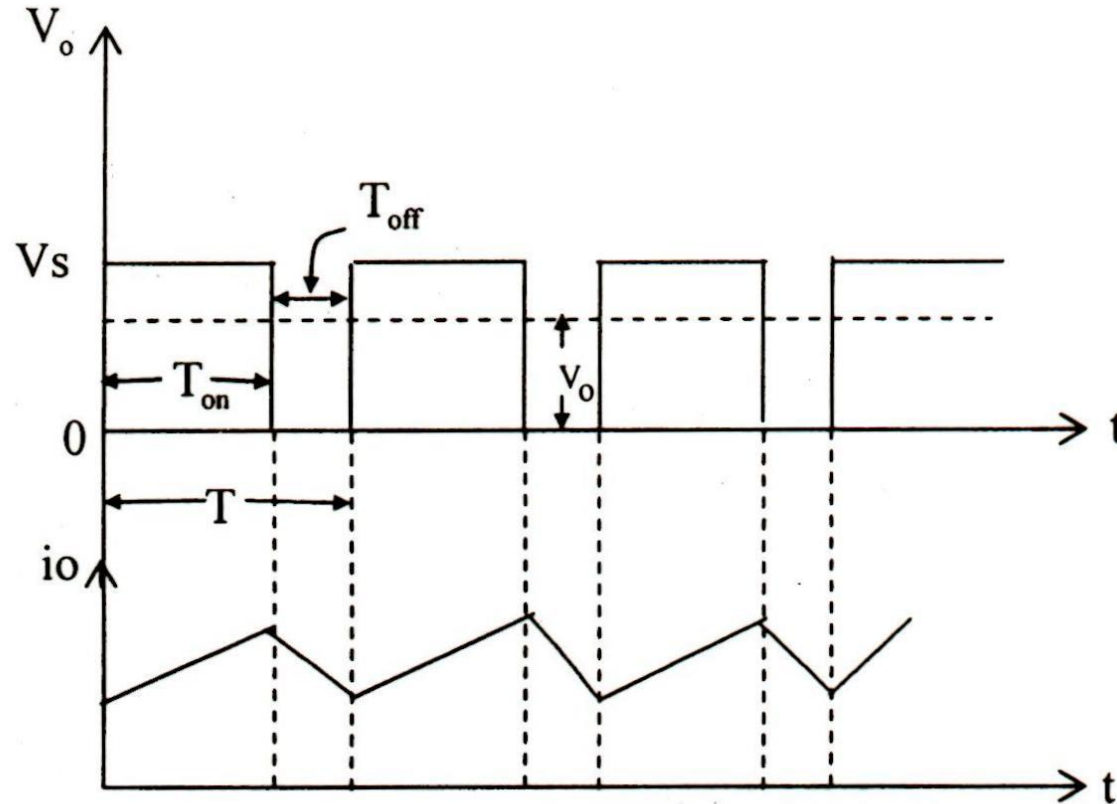



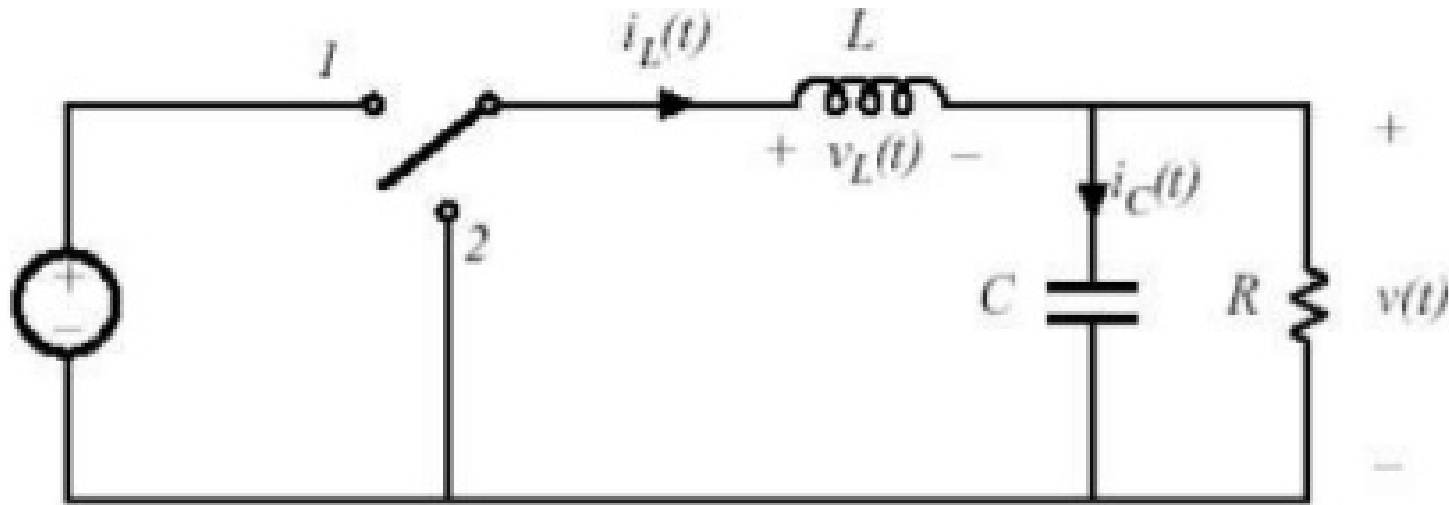
## Assessment - Draw the equivalent circuit for the Following.





# Buck converter (Step-down converter)

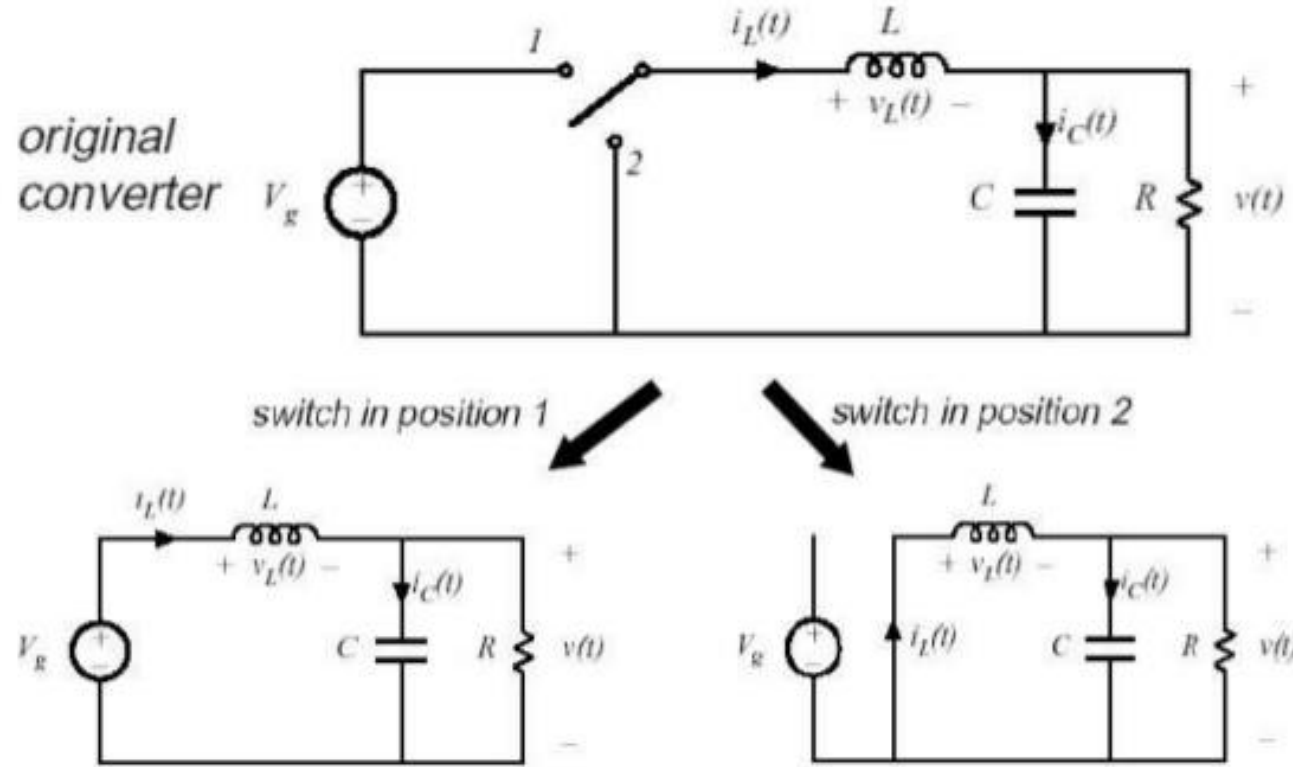

A. K. Gautam







## References

1. [https://www.tutorialspoint.com/power\\_electronics/power\\_electronics\\_introduction.htm#:~:text=Power%20Electronics%20refers%20to%20the,efficiency%20and%20reliability%20is%20100%25.](https://www.tutorialspoint.com/power_electronics/power_electronics_introduction.htm#:~:text=Power%20Electronics%20refers%20to%20the,efficiency%20and%20reliability%20is%20100%25.)
2. <http://www.egr.unlv.edu/~eebag/EE-442-642%20Introduction%20F14.pdf>
3. <https://www.youtube.com/watch?v=djbJm-xWo2w>
4. <https://www.youtube.com/watch?v=jx5l2Fbil8U>

