

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COURSE NAME: 19EEB201 DC Machines and Transformers

II YEAR / III SEMESTER

Unit 2 – DC Motor

Topic 5: Starters for DC Motor





(S)

What We'll Discuss

TOPIC OUTLINE

Necessity of starter
Two Point Starter
Three Point Starter
Four Point Starter
Assessment



Necessity of Starter



- Let us consider a case of 230 V, 5 kW DC motor having armature resistance of 0.5 W and full load current of 27.0 A.
- If this DC motor is directly connected to supply mains, it will draw a starting current of 17 times its
 full load current.


```
(IfL = 5000 / ( 230 × 0.8 )
= 27.17 Amp
Assume efficiency = 80%
```

IL = 230 / 0.4 = 460.0 Amp

Starting current drawn by motor

= 460 / 27.17

= 17 times full load current

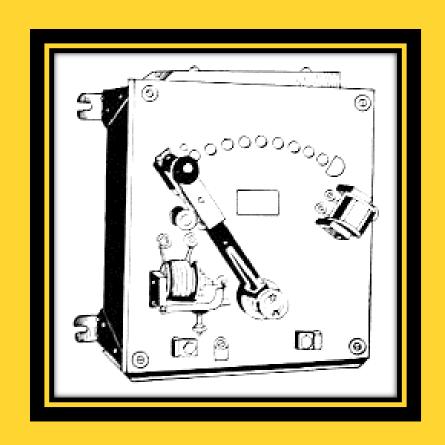



Necessity of Starter





- (I) Blow out the fuses
- (II) Damage the commutator, brushes and also armature winding and
- (III) Produces large voltage drops in the supply voltage line.




Therefore the motor must be protected against the flow of excessive current during starting period (say 5 to 10 seconds).



Two Point Starter






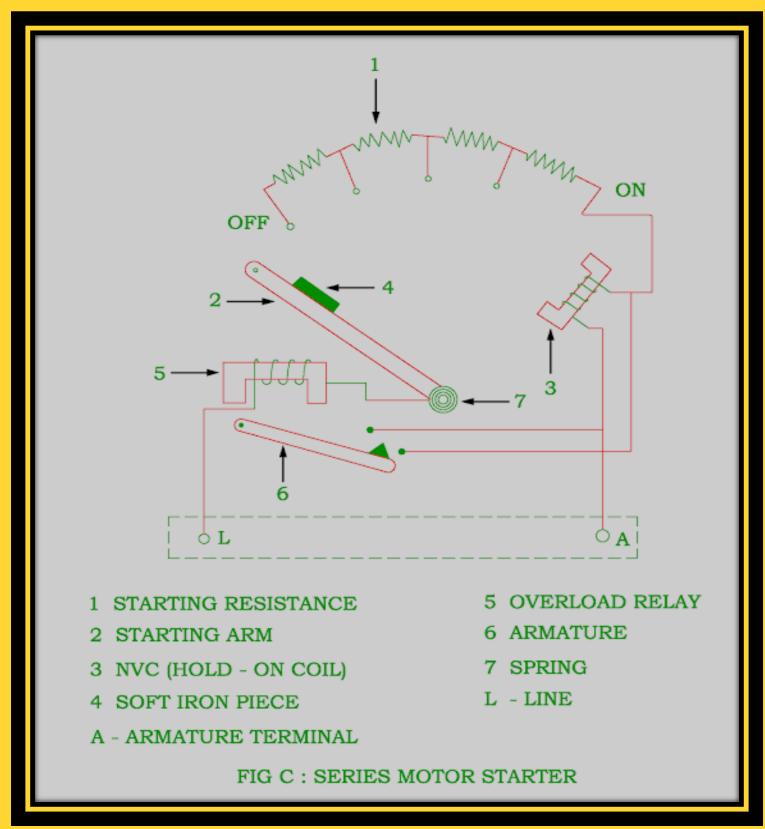



Three Point Starter



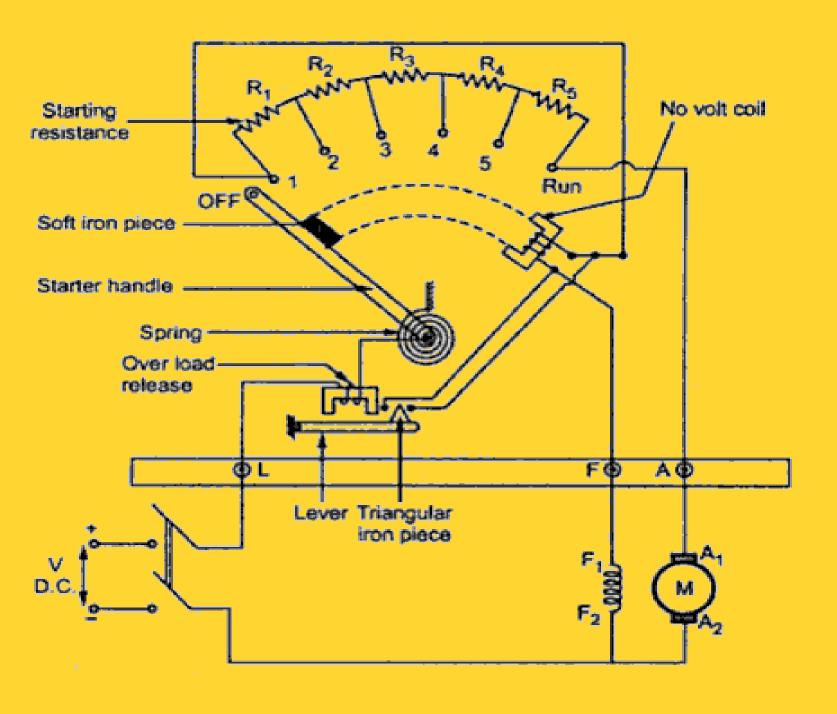


3 point Starter



Four Point Starter



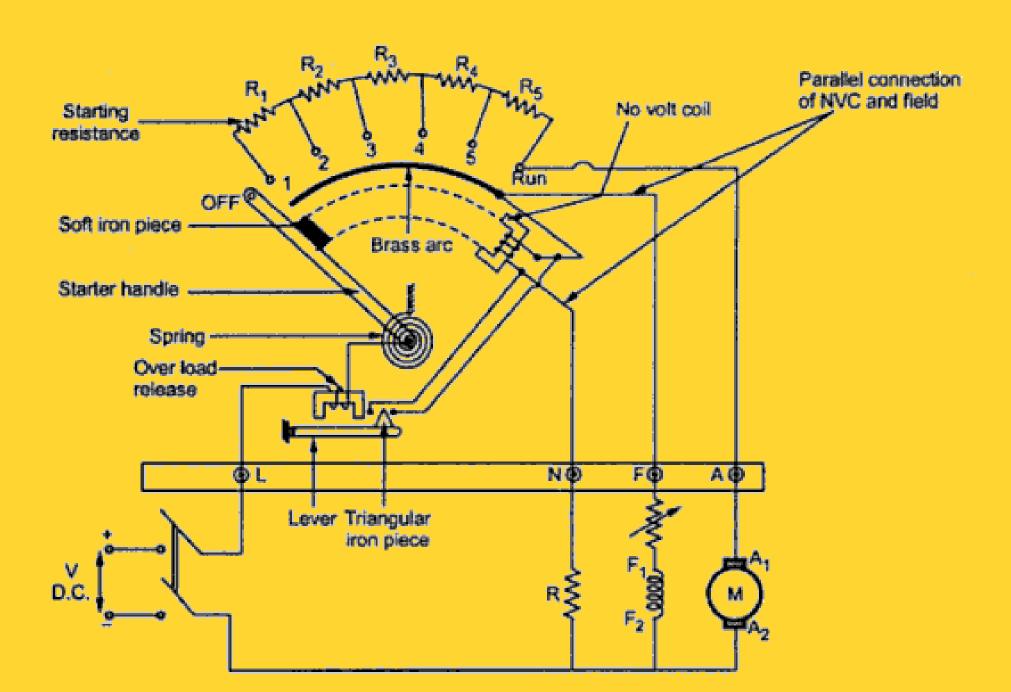







RECALL



1. List the Three types of DC Motor Starters





THANK YOU