



# **SNS COLLEGE OF TECHNOLOGY**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## **DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

**COURSE NAME : 19ECB201-ANALOG ELECTRONIC CIRCUITS**

**II YEAR /III SEMESTER**

**Unit 4- OSCILLATORS & MULTIVIBRATOR CIRCUITS**

**Topic 1 : Mechanism for start of oscillation and stabilization of  
amplitude**



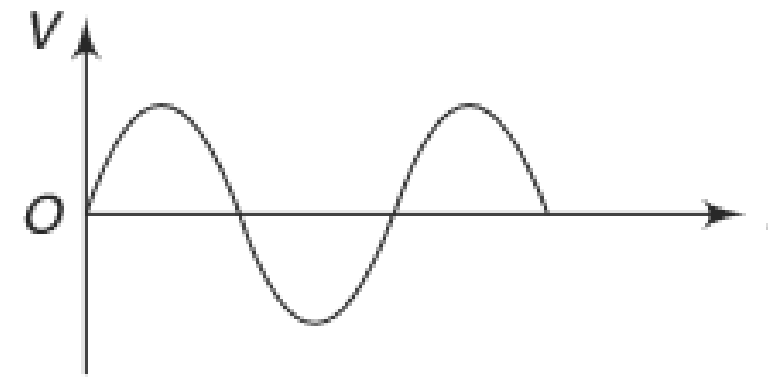
# Classification of oscillators




According to the waveform generated


- Harmonic oscillator
- Relaxation oscillator




(a)

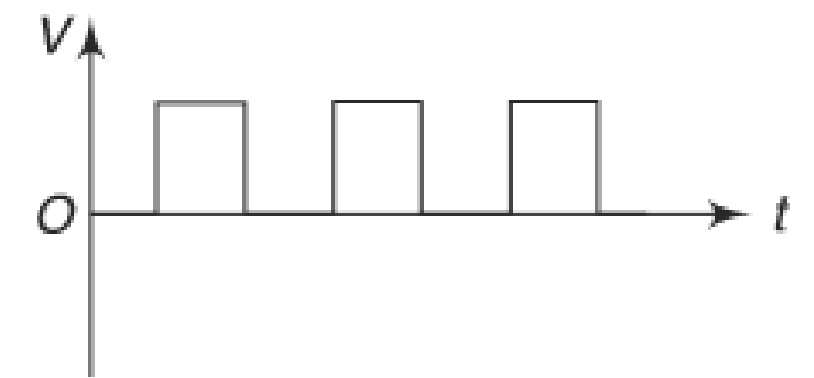

(b)

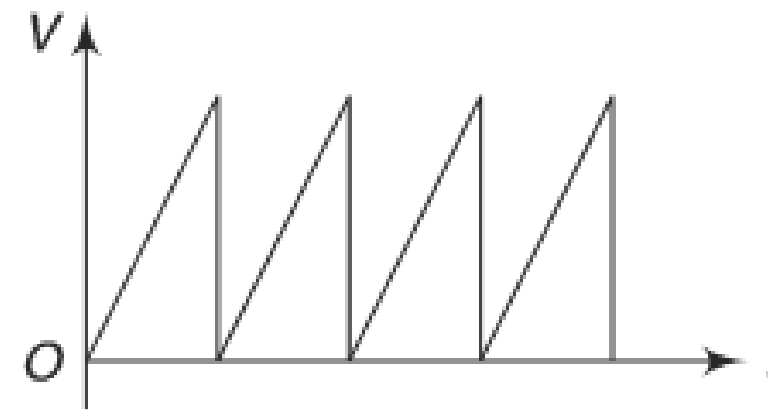


(c)


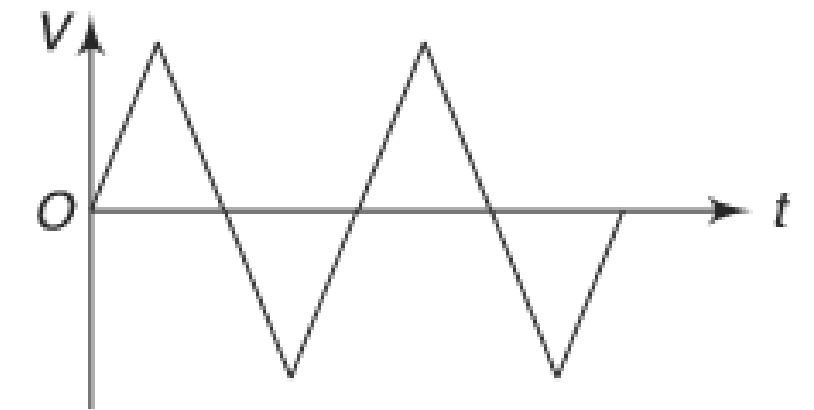



(d)



# Classification of oscillator

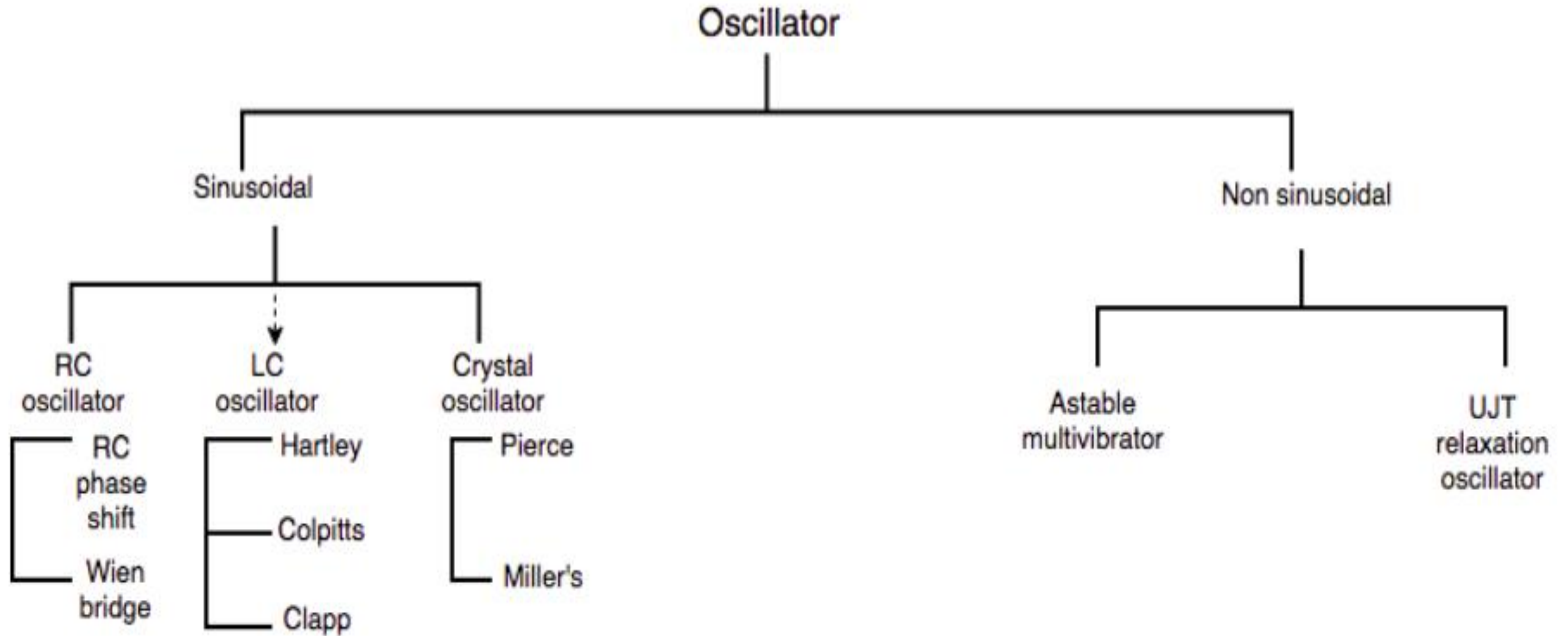


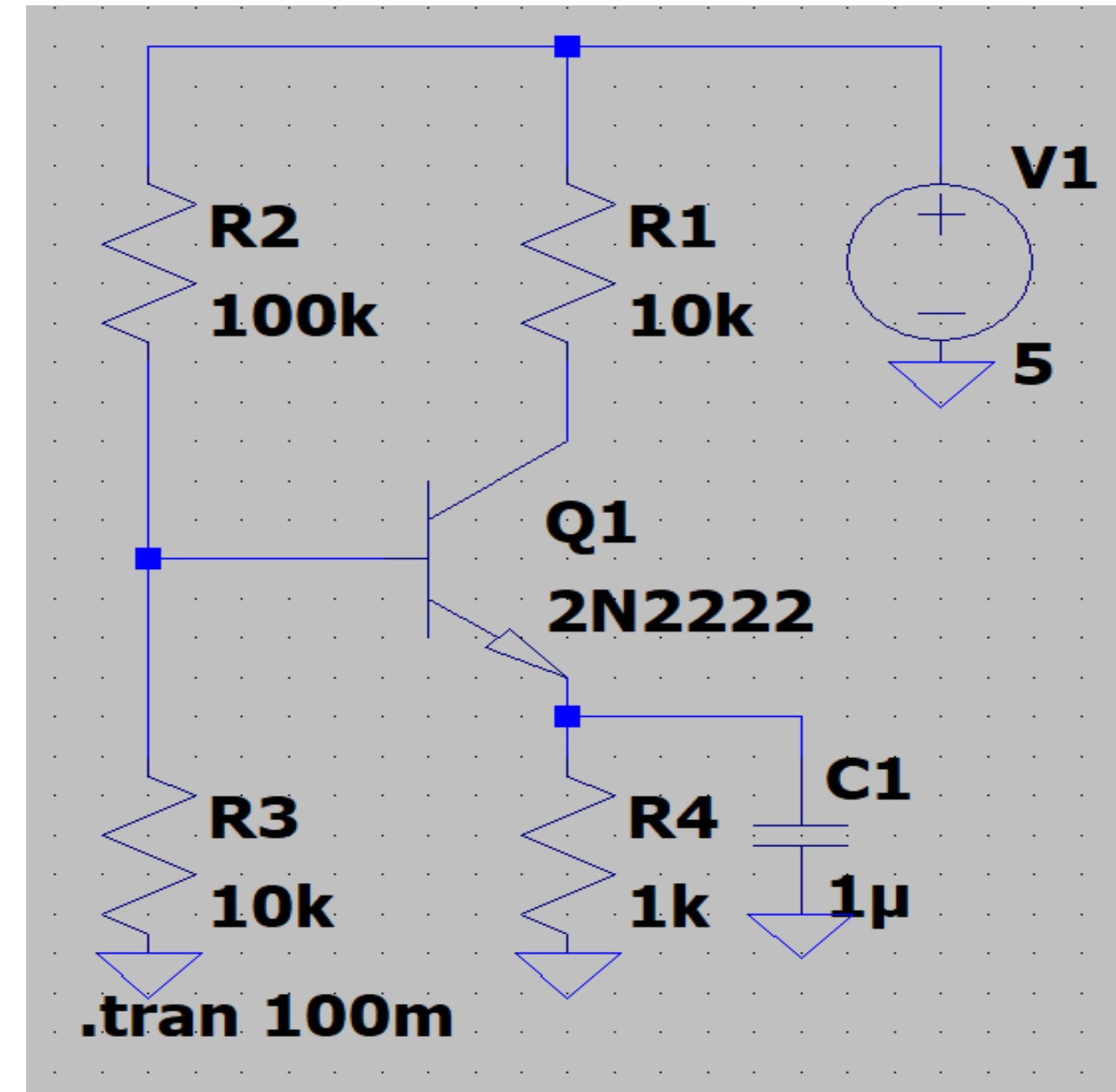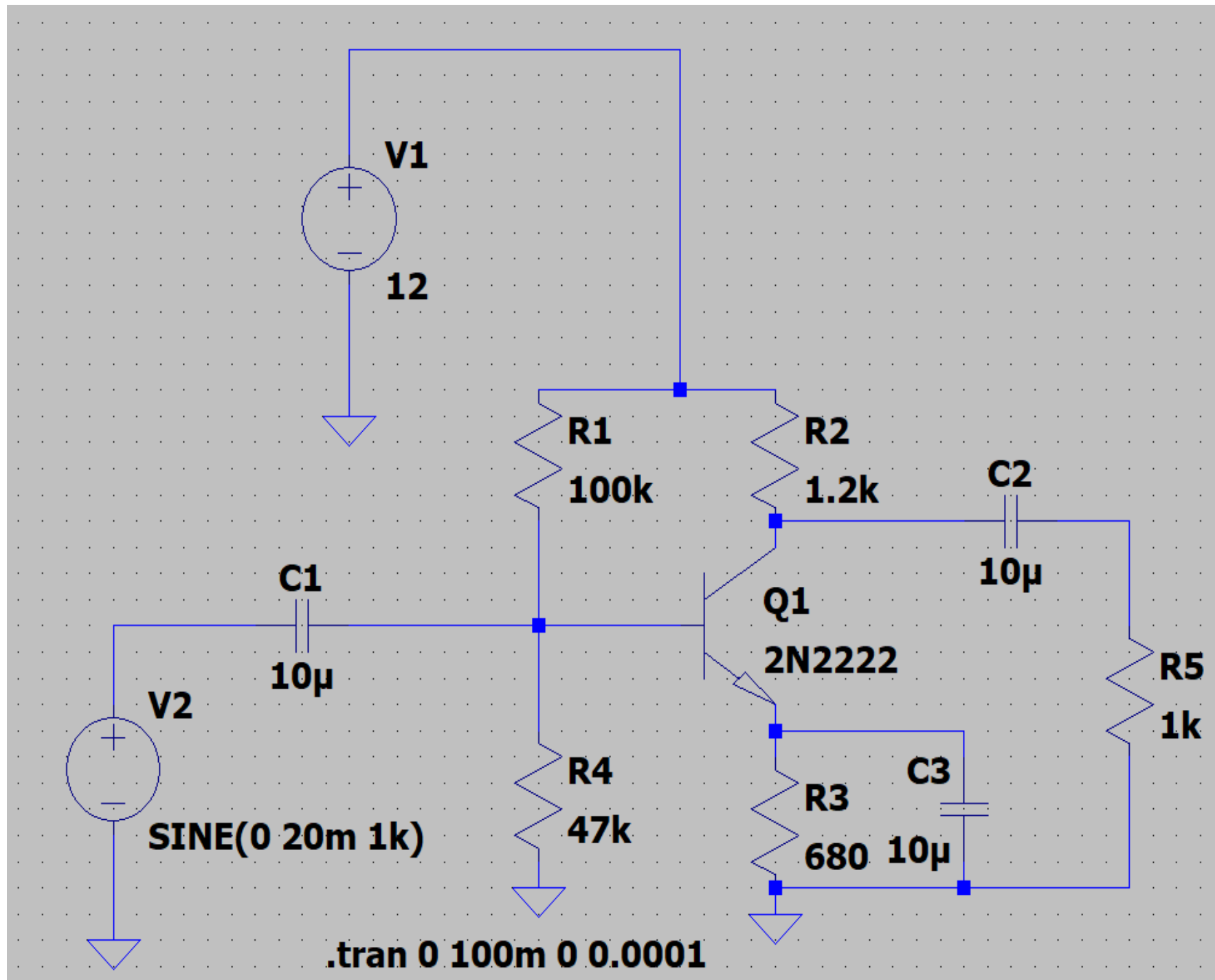

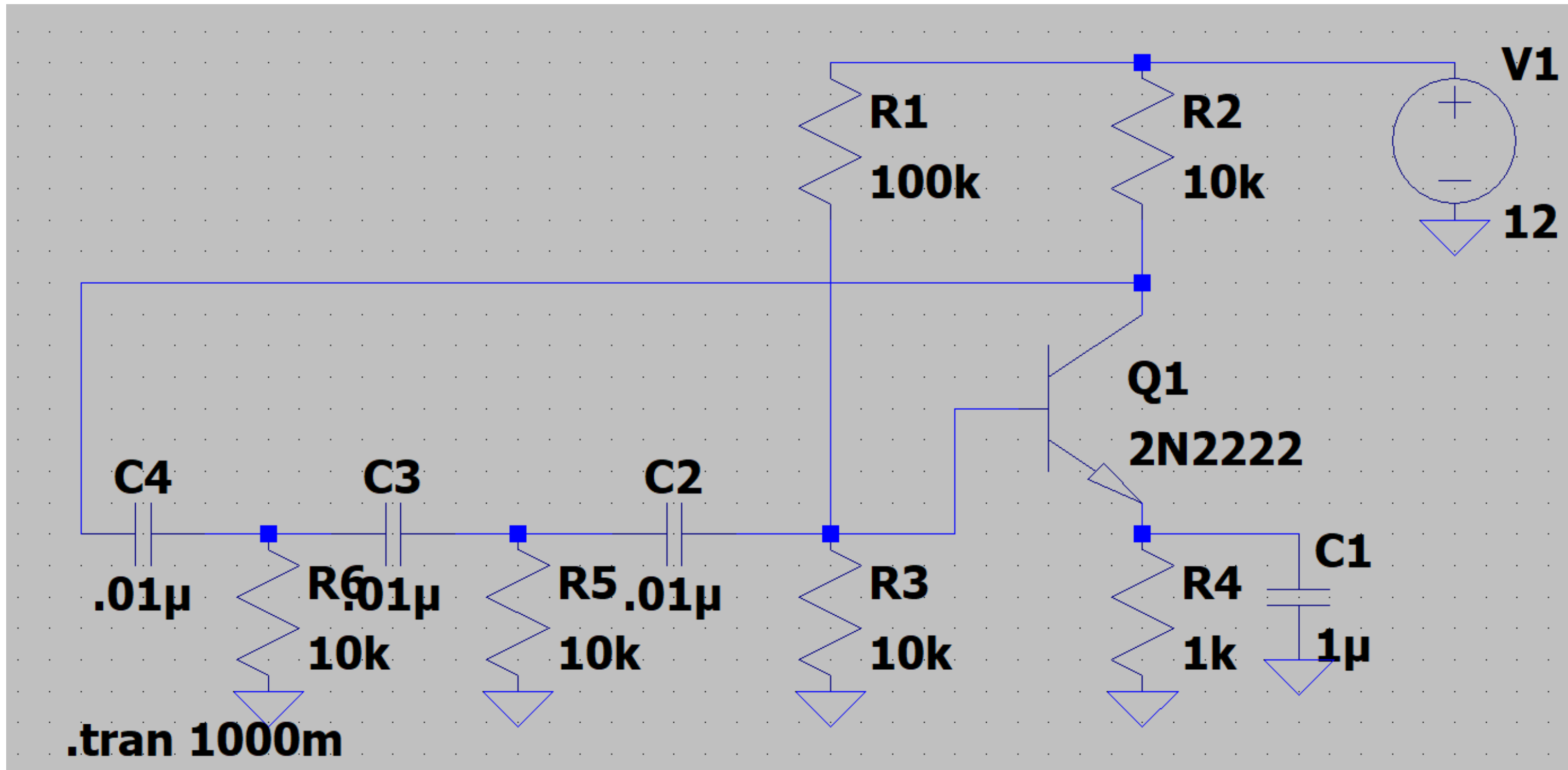



# Block diagram of sinusoidal oscillator

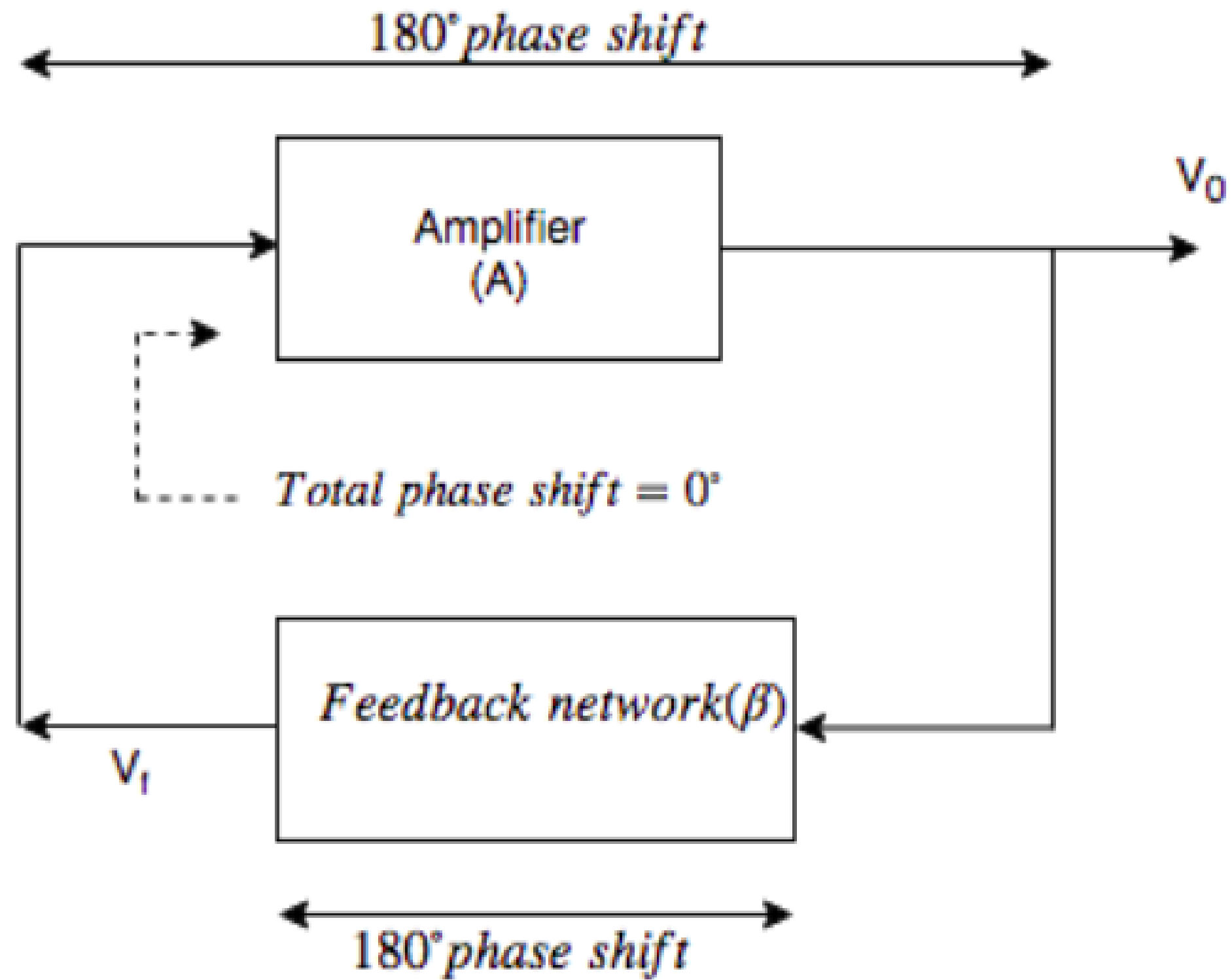





# Classification of oscillators



According to frequency generated


- Audio Frequency Oscillator: Upto 20kHz
- Radio Frequency Oscillator: 20 kHz to 30 MHz
- Very High Frequency Oscillator: 30 MHz to 300 MHz
- Ultra High Frequency Oscillator: 300 MHz to 3 GHz
- Microwave Frequency Oscillator: Above 3 GHz



# Mechanism for Start of Oscillations



**IDEATE**

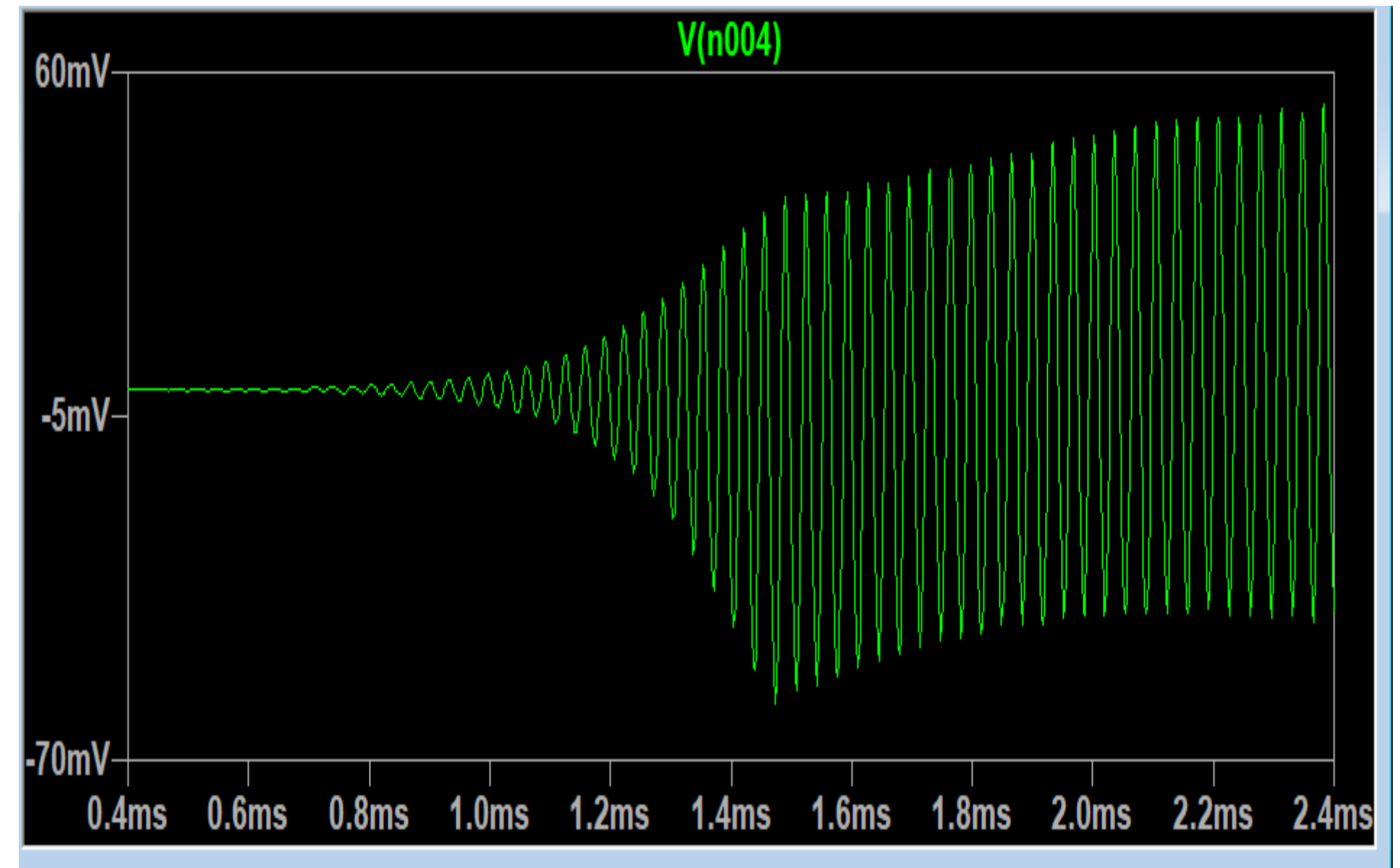






# Barkhausen Criterion



The essential conditions for maintaining oscillations are:

1.  $|A\beta| = 1$ , i.e. the magnitude of loop gain must be unity.
2. The total phase shift around the closed loop is zero or 360 degrees.

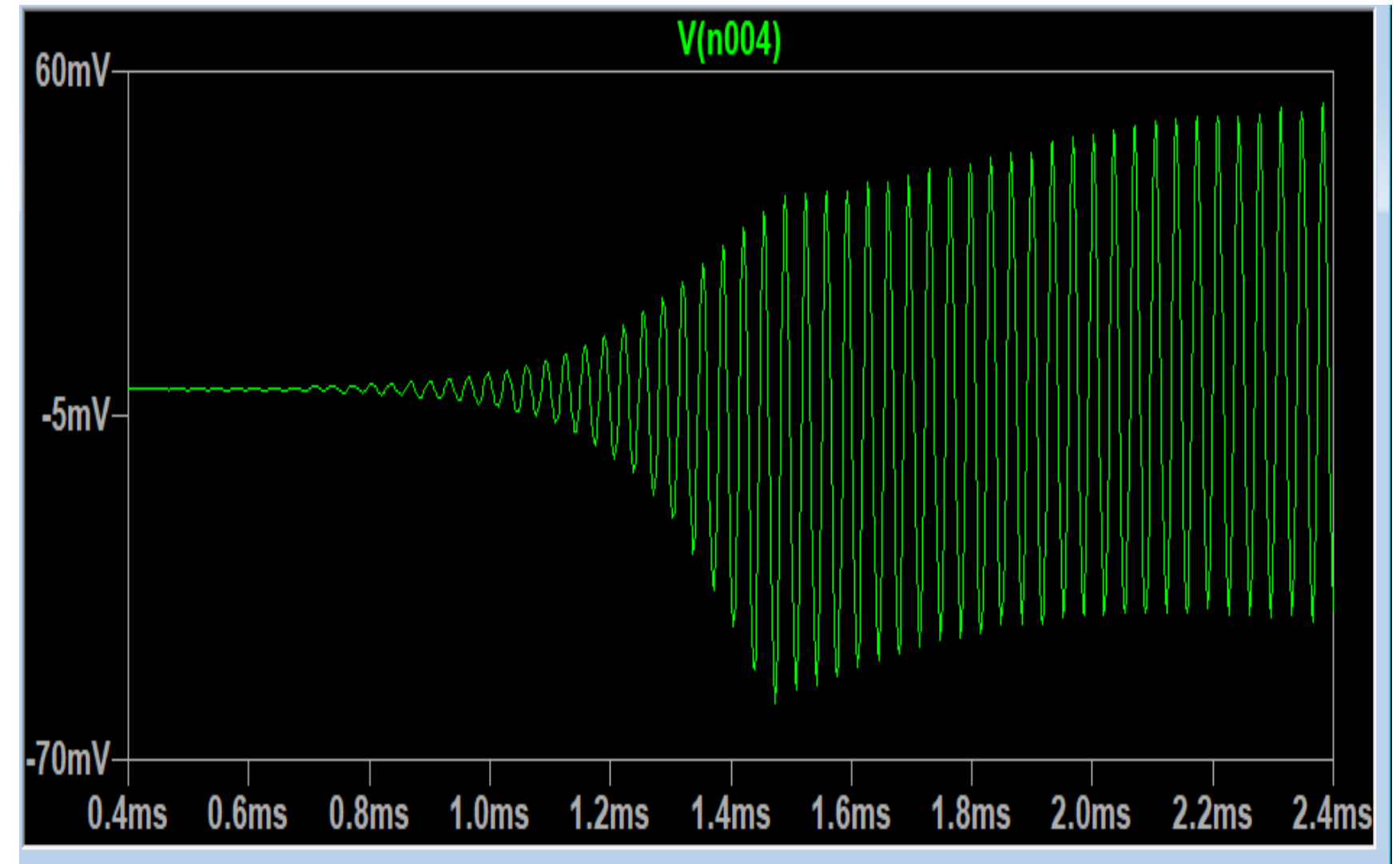



# Amplitude Stability of Oscillators

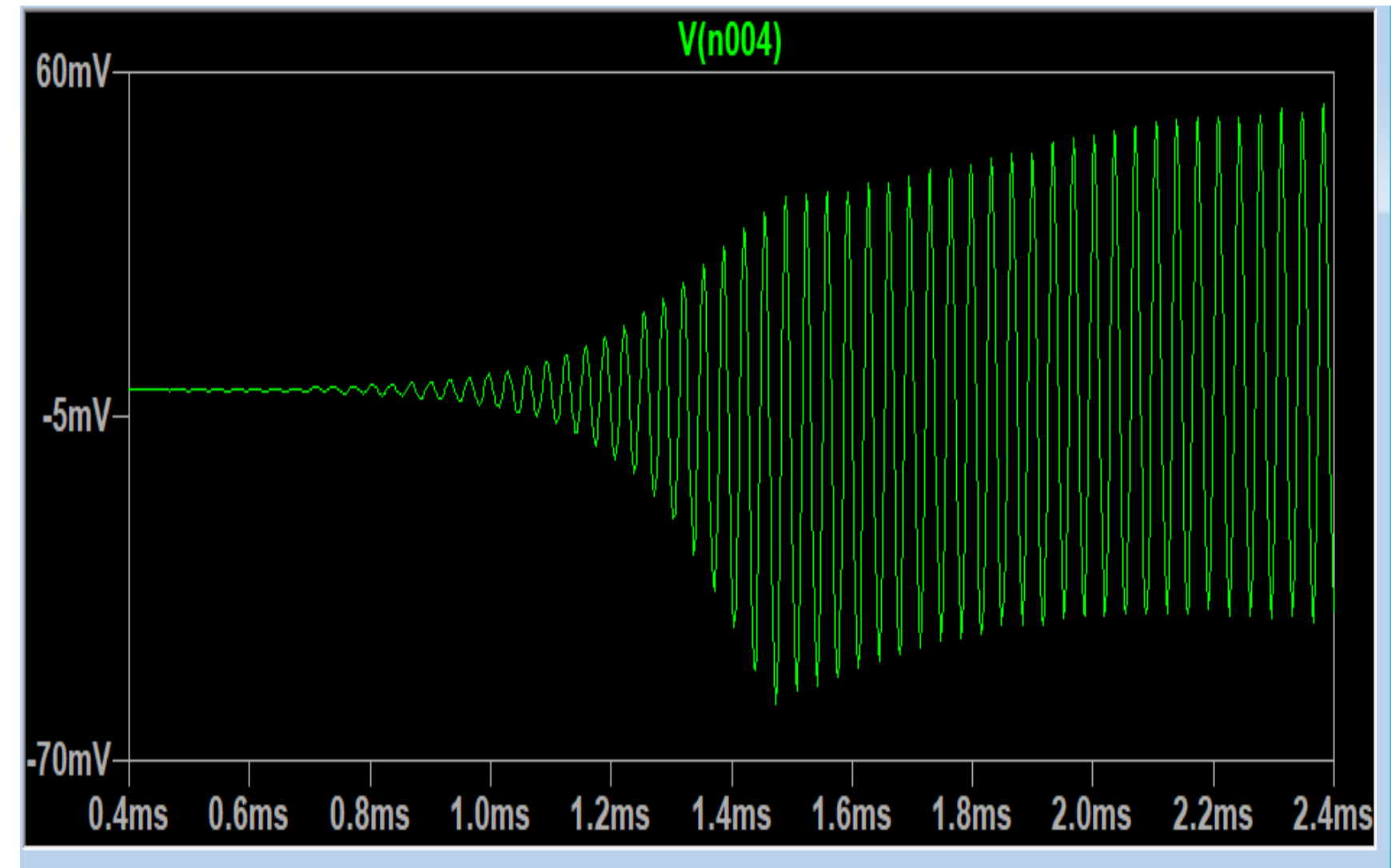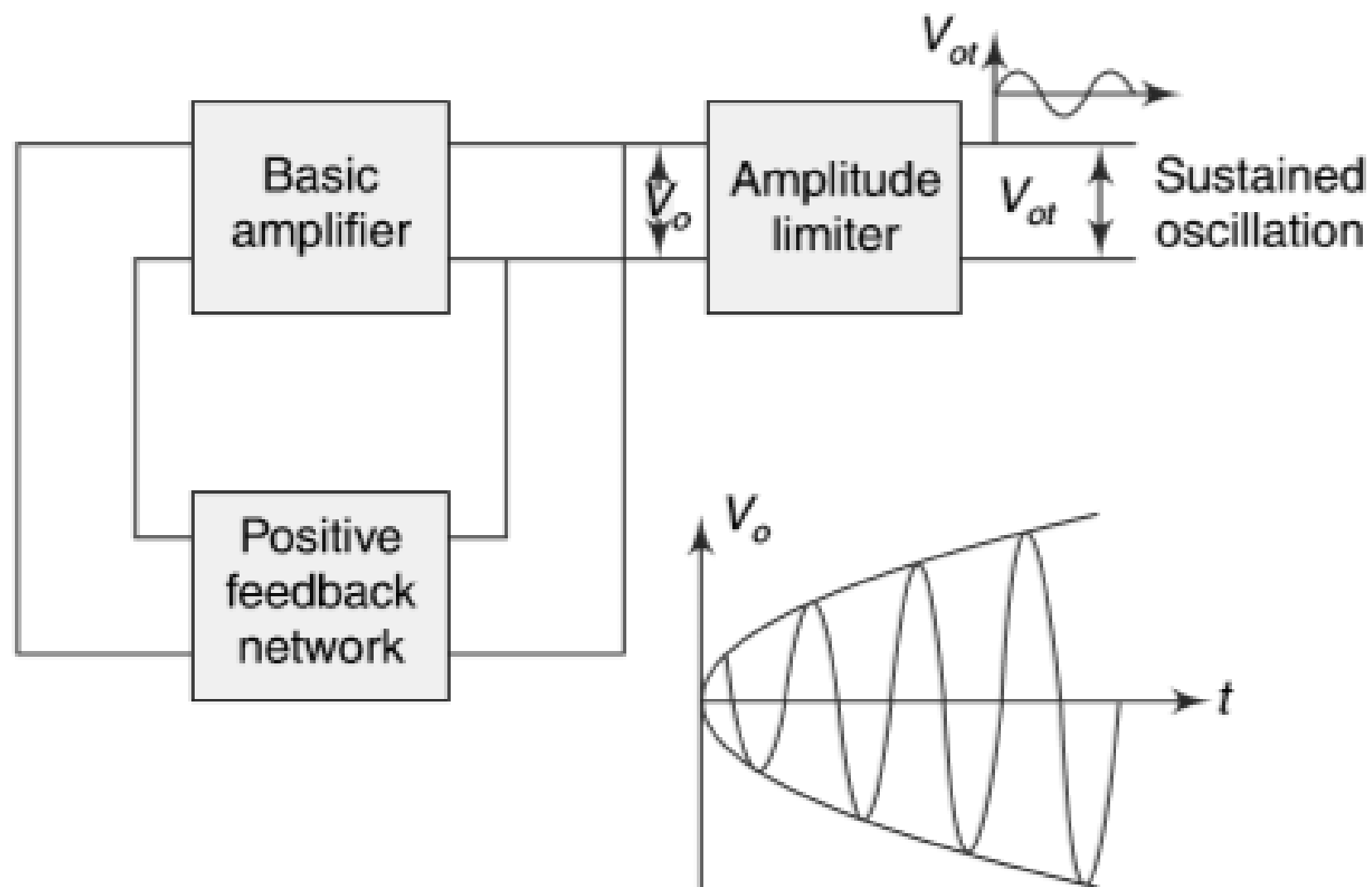



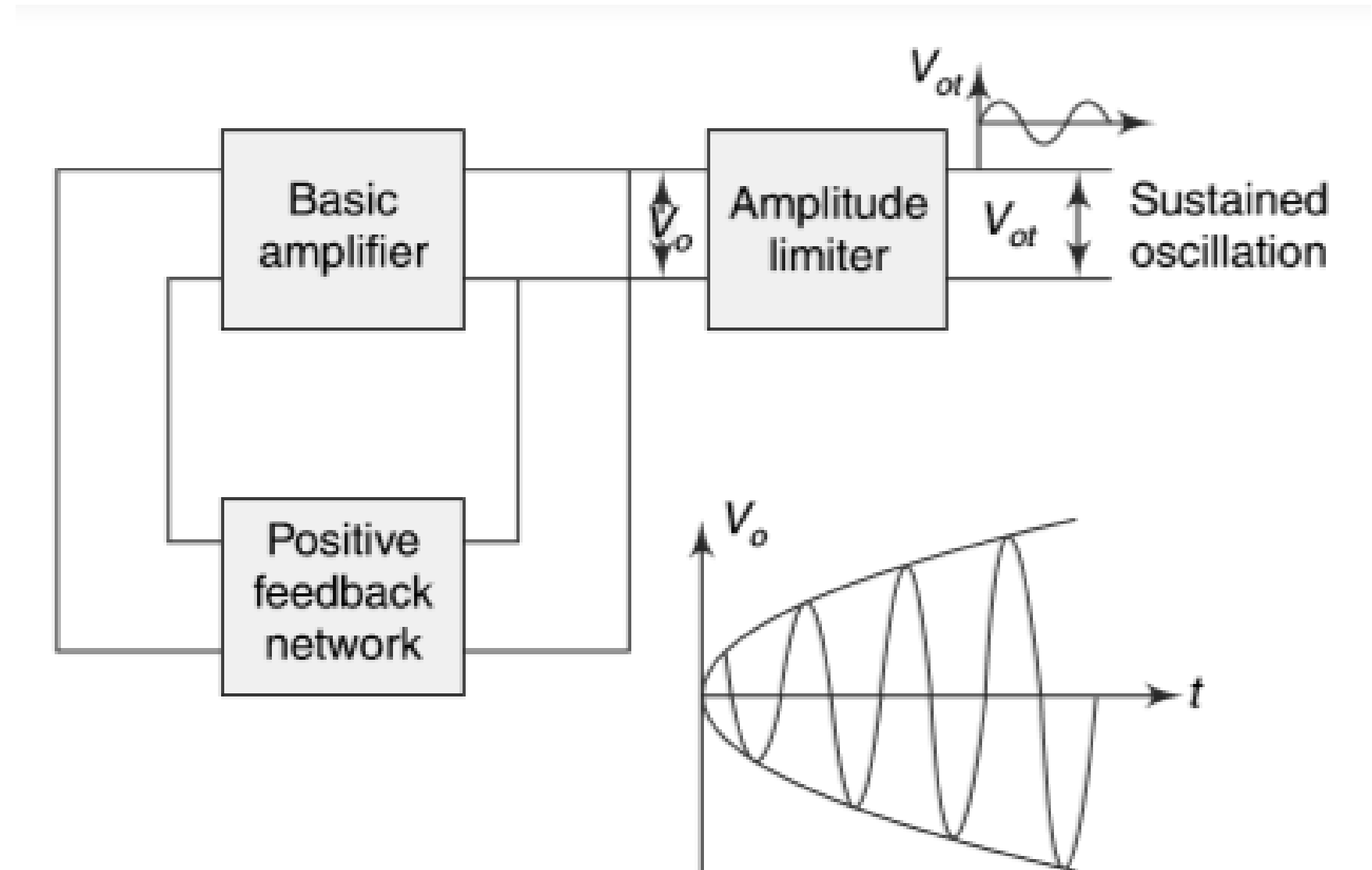
# General Form of an Oscillator





- ❖ Basic Amplifier
- ❖ Amplitude Limiter
- ❖ Positive feedback network





# Why Positive Feedback in Oscillators?

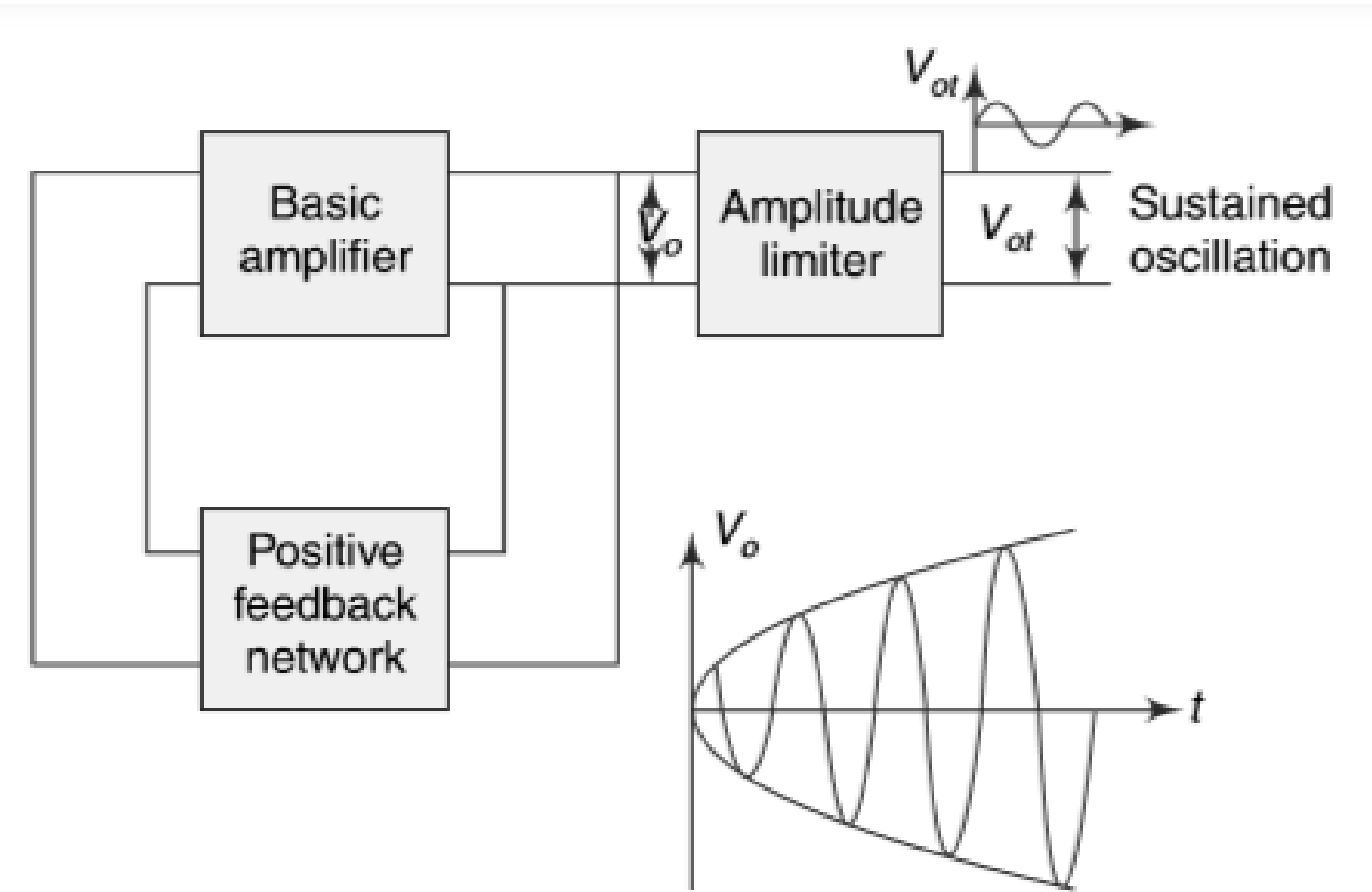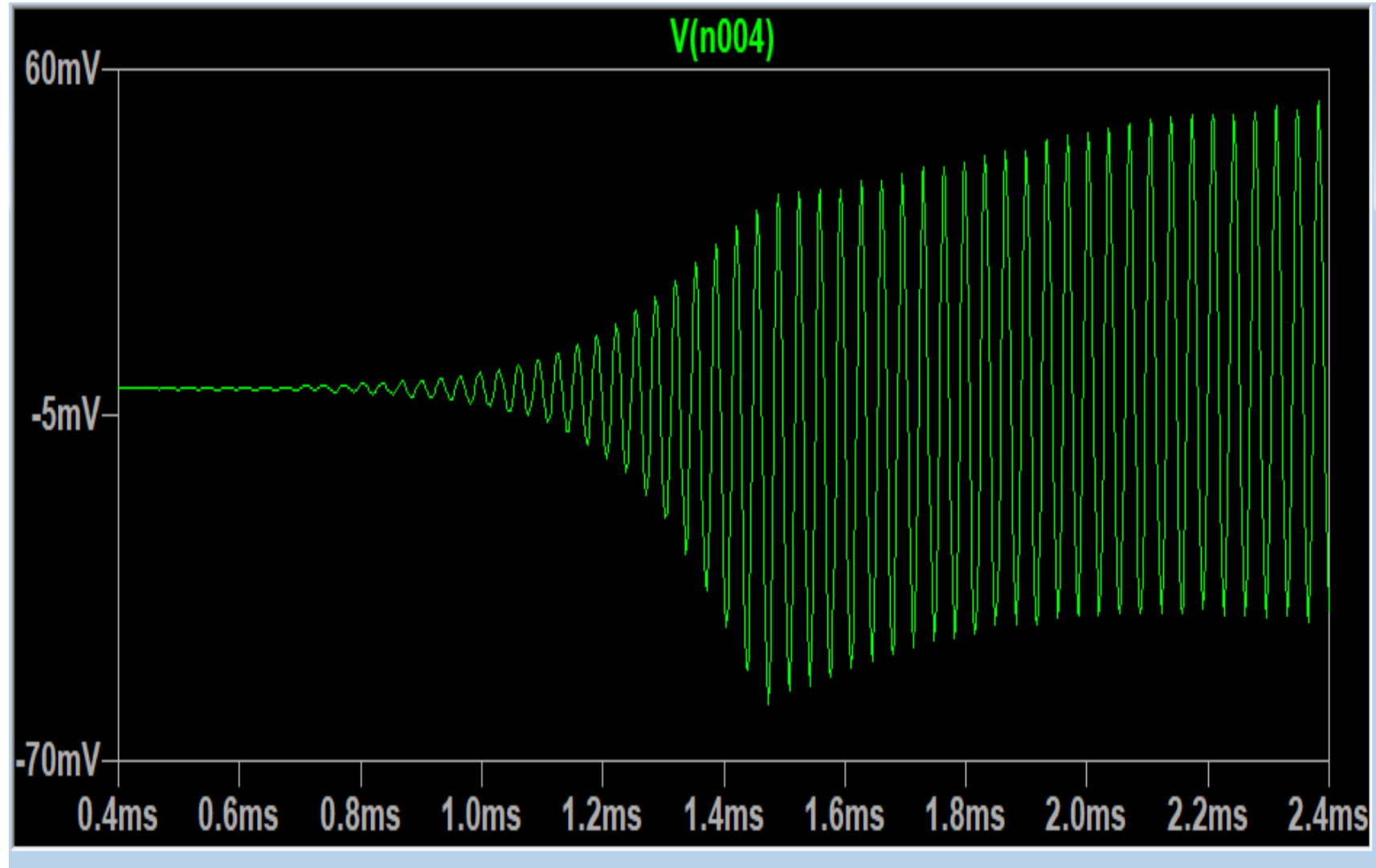




# Equivalent Circuit



Load Impedance

$$\frac{1}{Z'} = \frac{1}{Z_1} + \frac{1}{h_{ie}}$$

$$Z' = \frac{Z_1 h_{ie}}{Z_1 + h_{ie}}$$

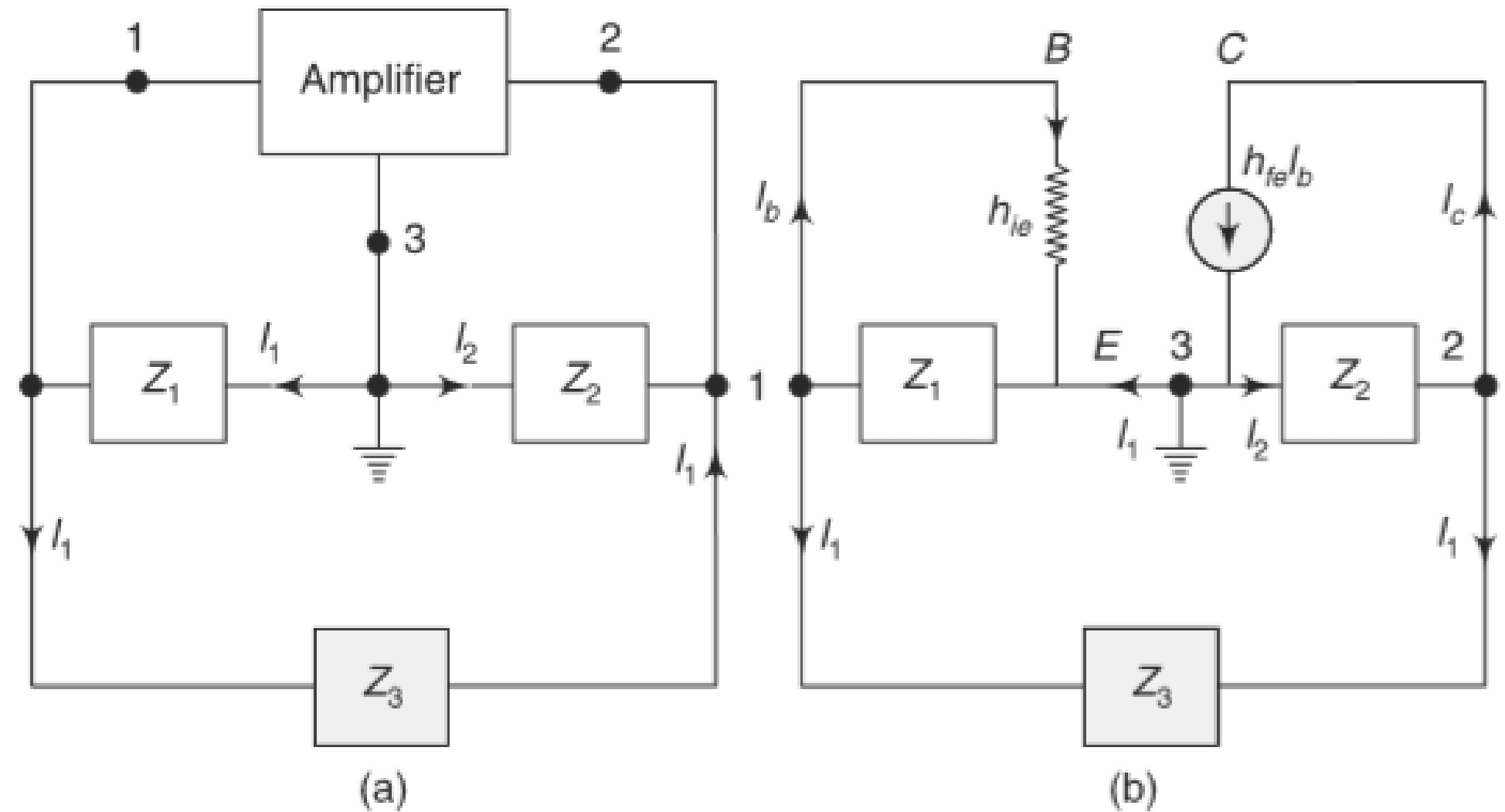




# Calculation of Load Impedance



$$\frac{1}{Z_L} = \frac{1}{Z_2} + \frac{1}{Z' + Z_3}$$

Derive
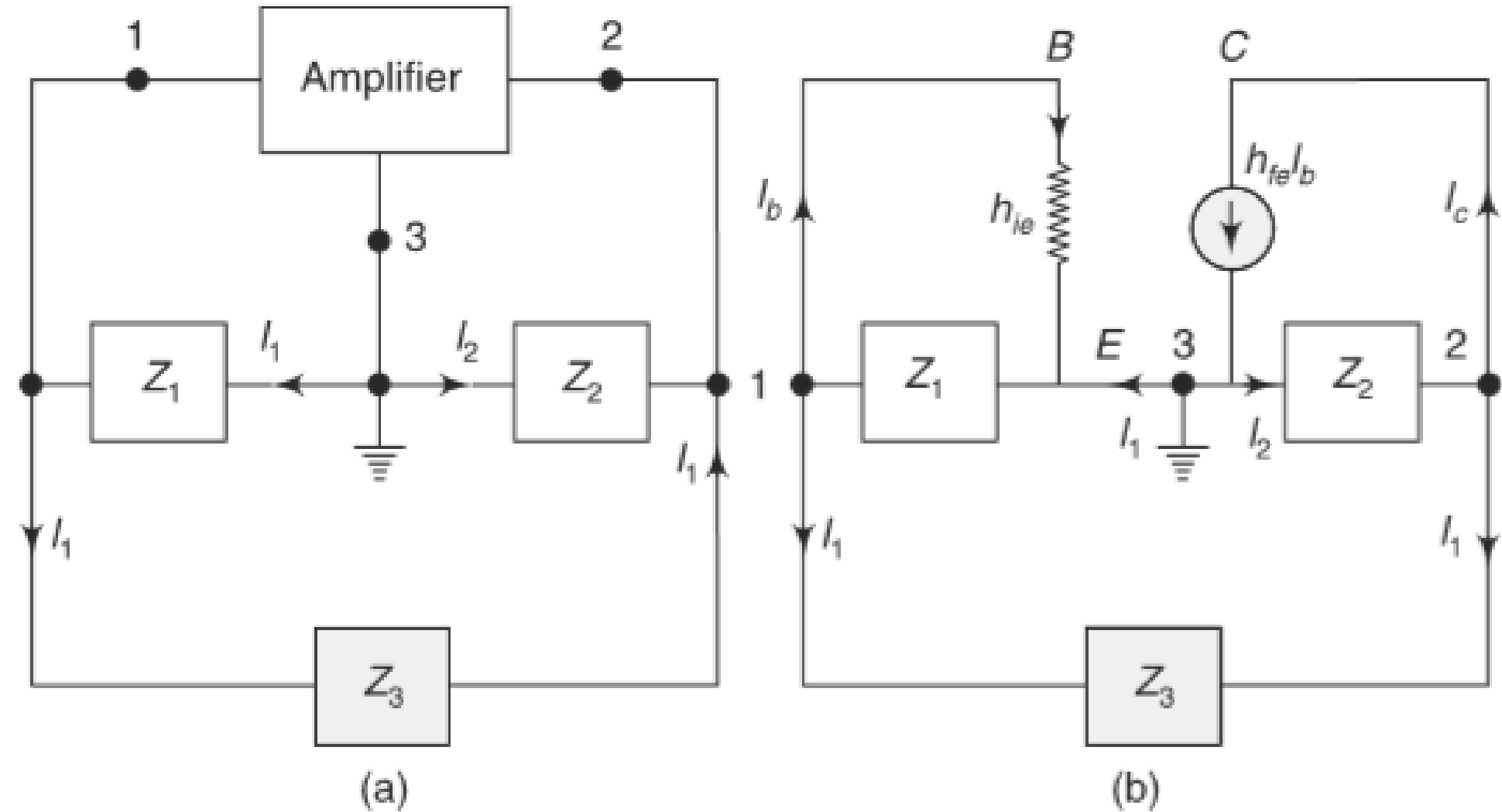
$$Z_L = \frac{Z_2[h_{ie}(Z_1 + Z_3) + Z_1 Z_3]}{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3}$$







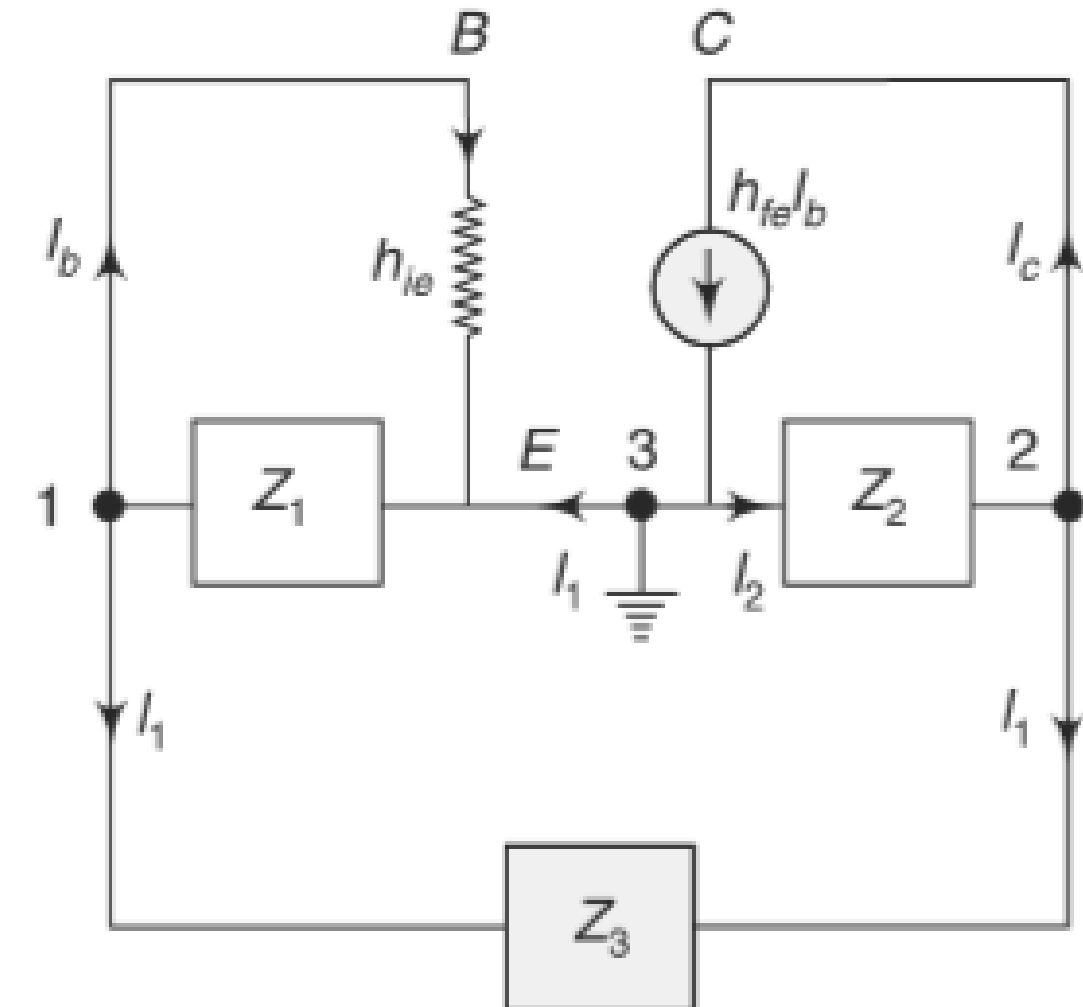
# Load Impedance



$$\begin{aligned} &= \frac{1}{Z_2} + \frac{1}{\frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3} \\ &= \frac{1}{Z_2} + \frac{Z_1 + h_{ie}}{Z_1 h_{ie} + Z_1 Z_3 + h_{ie} Z_3} \\ &= \frac{1}{Z_2} + \frac{Z_1 + h_{ie}}{h_{ie} (Z_1 + Z_3) + Z_1 Z_3} \end{aligned}$$





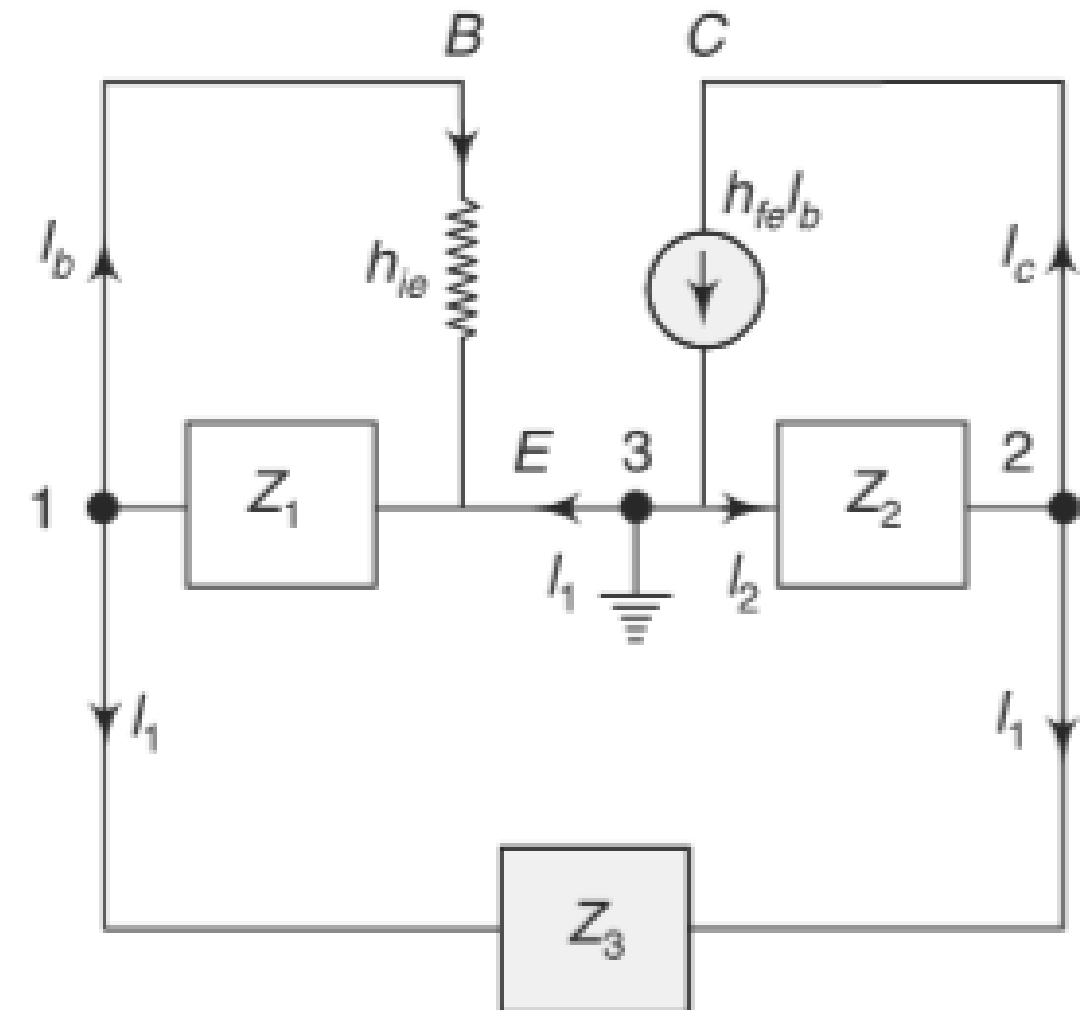
# Load Impedance



$$\begin{aligned} &= \frac{h_{ie}(Z_1 + Z_3) + Z_1 Z_3 + Z_2(Z_1 + h_{ie})}{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]} \\ &= \frac{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3}{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]} \\ Z_L &= \frac{Z_2 [h_{ie}(Z_1 + Z_3) + Z_1 Z_3]}{h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_1 Z_3} \end{aligned}$$






# Voltage Gain Without Feedback



$$A_{ve} = -\frac{h_{fe} Z_L}{h_{ie}}$$

$$V_0 = -I_1 (Z' + Z_3) = -I_1 \left( \frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3 \right)$$
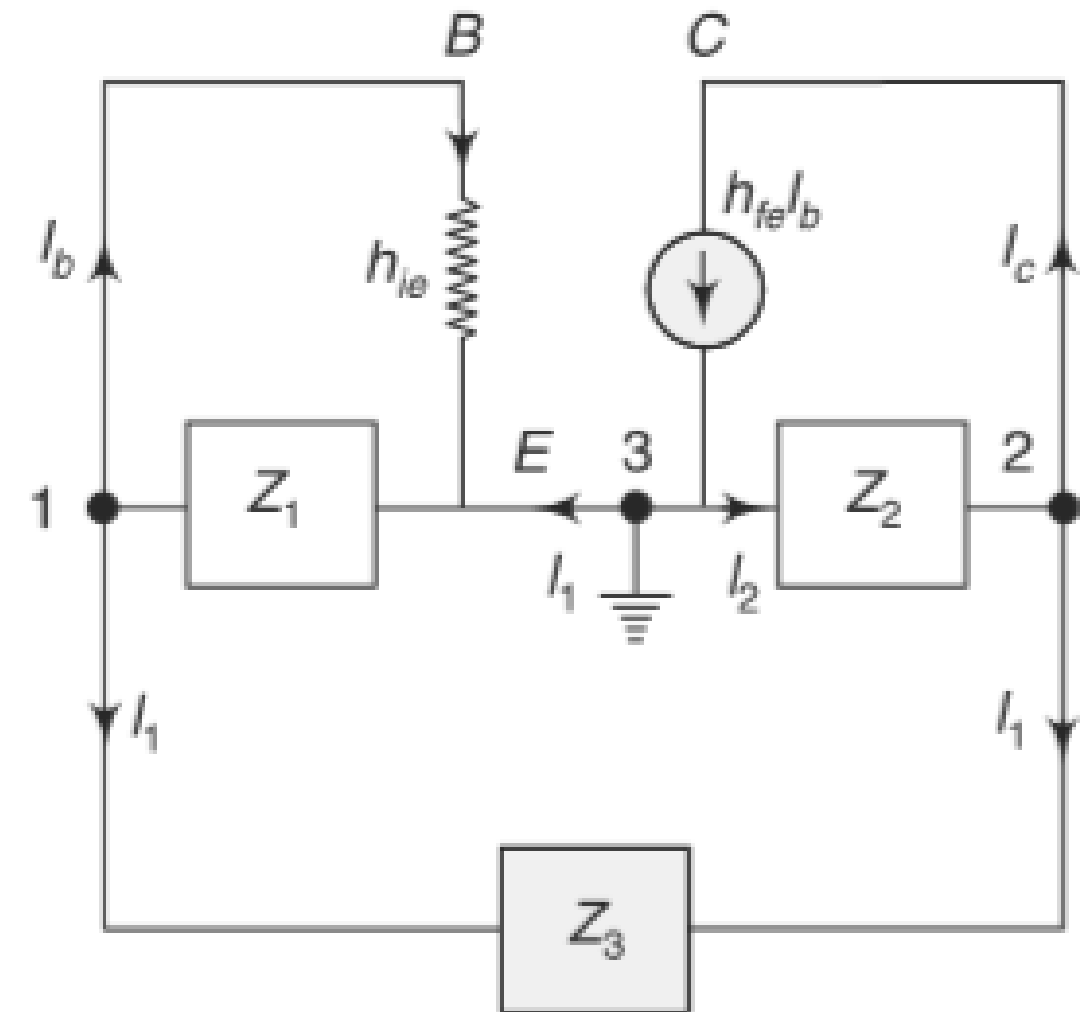
$$= -I_1 \left( \frac{h_{ie} (Z_1 + Z_3) + Z_1 Z_3}{Z_1 + h_{ie}} \right)$$





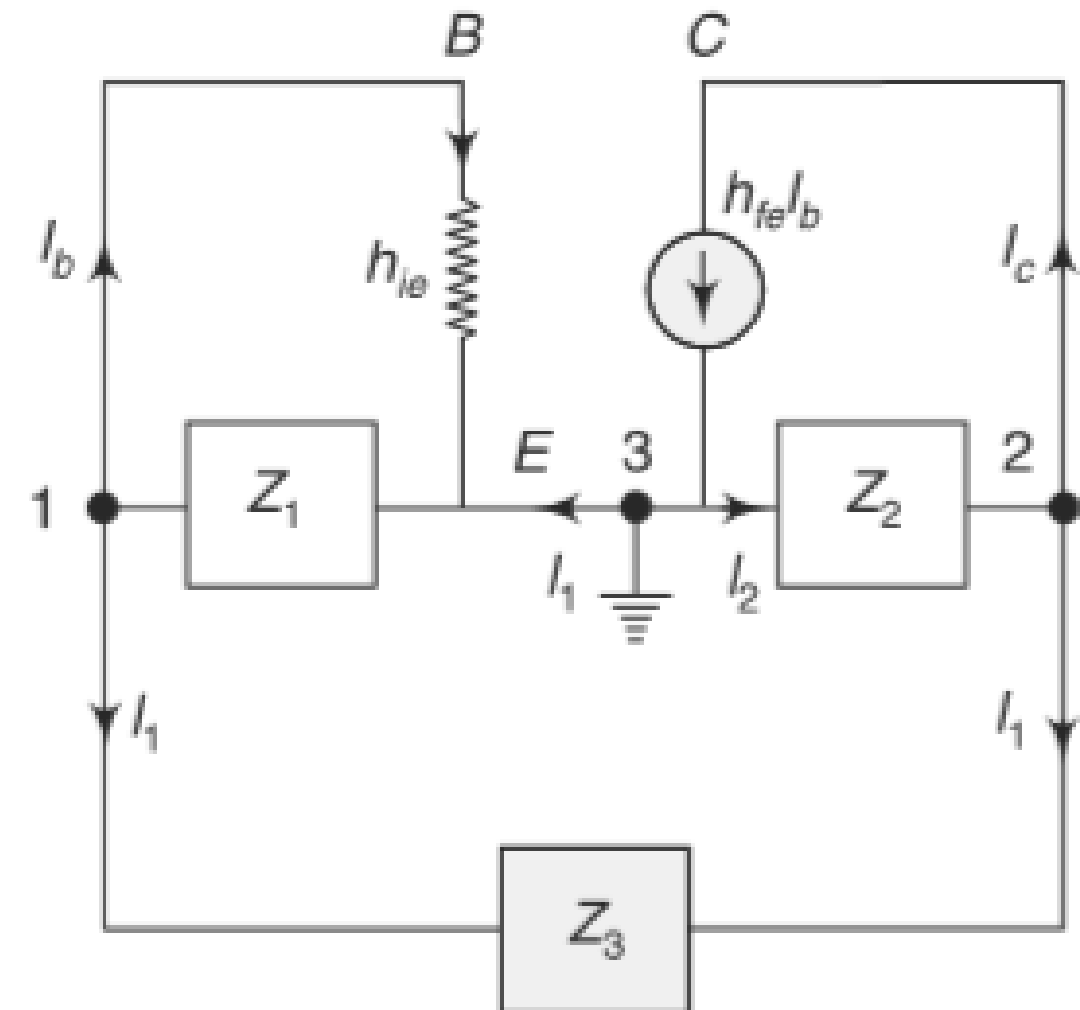
# Feedback Factor



$$\beta = \frac{V_{fb}}{V_o} = I_1 \left( \frac{Z_1 h_{ie}}{Z_1 + h_{ie}} \right) \left[ \frac{Z_1 + h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3} \right] \cdot \frac{1}{I_1}$$

$$\beta = \frac{Z_1 h_{ie}}{h_{ie}(Z_1 + Z_3) + Z_1 Z_3}$$





# Assessment 1 (Answer)



Derive the Equation of oscillator

Hints

$$A_{ve} \beta = 1$$



Answer

$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0$$



# References



Electronic Devices and Circuits By Salivahanan

**Thank You**