



SNS COLLEGE OF TECHNOLOGY

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

COURSE NAME : 19ECB201-ANALOG ELECTRONIC CIRCUITS

II YEAR /III SEMESTER

Unit 4- OSCILLATORS & MULTIVIBRATOR CIRCUITS

Topic 2 : Hartley Oscillator






Need for Oscillators



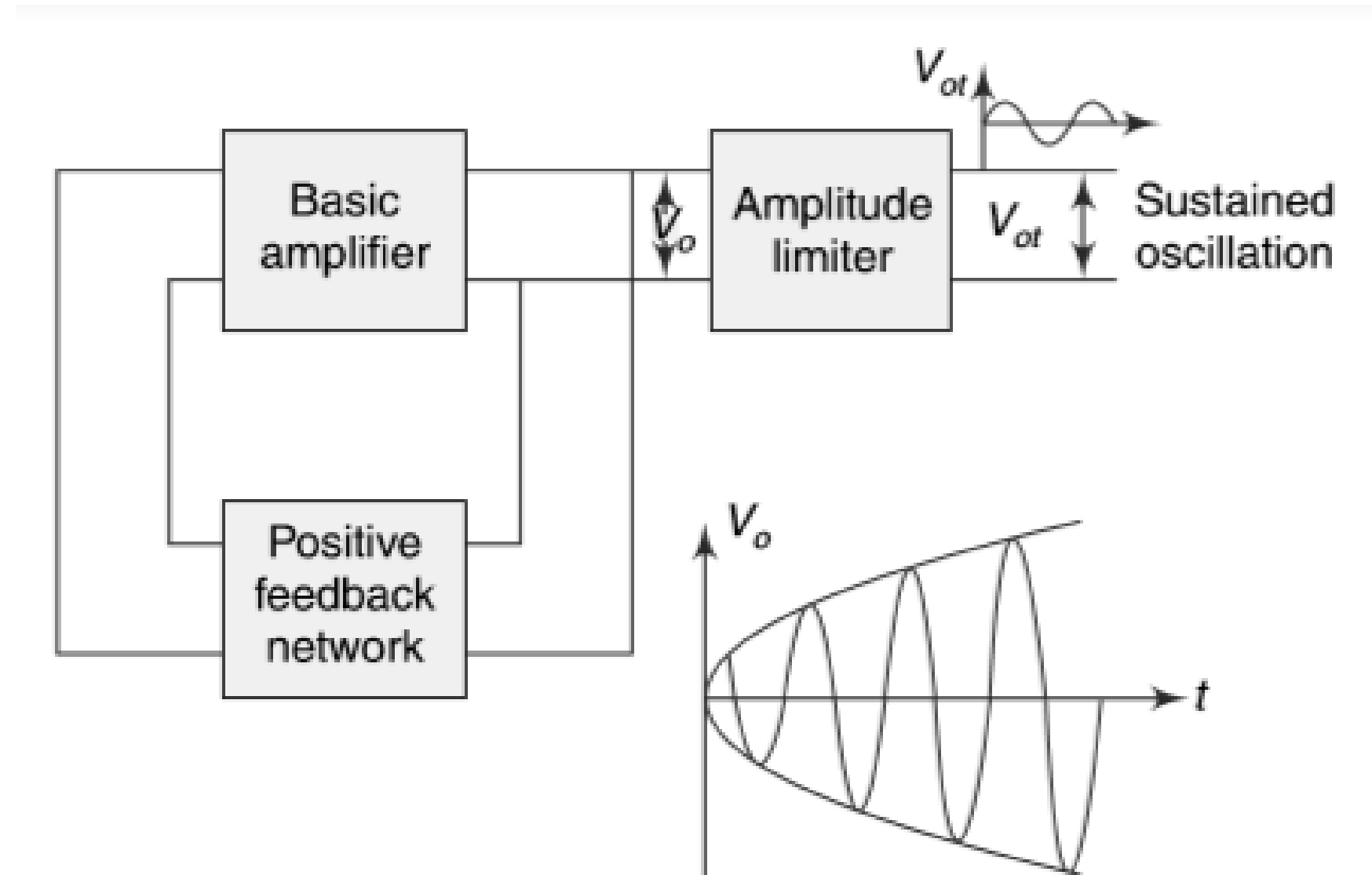- Communication Systems
- Control signals






Hybrid Oscillator Circuit




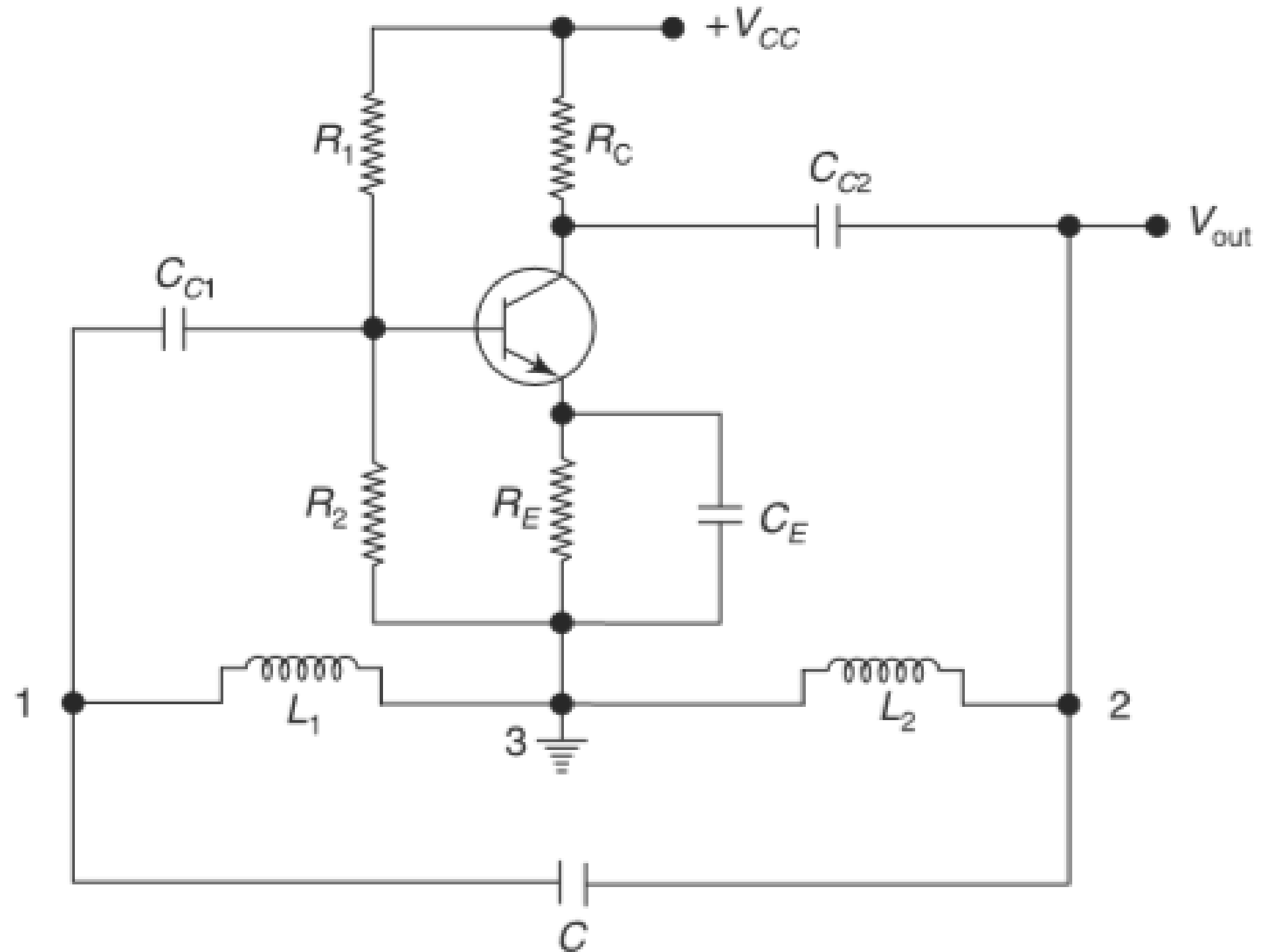- NPN transistor
- Conditions for oscillations
- Positive Feedback





Mechanism of Start of Oscillation

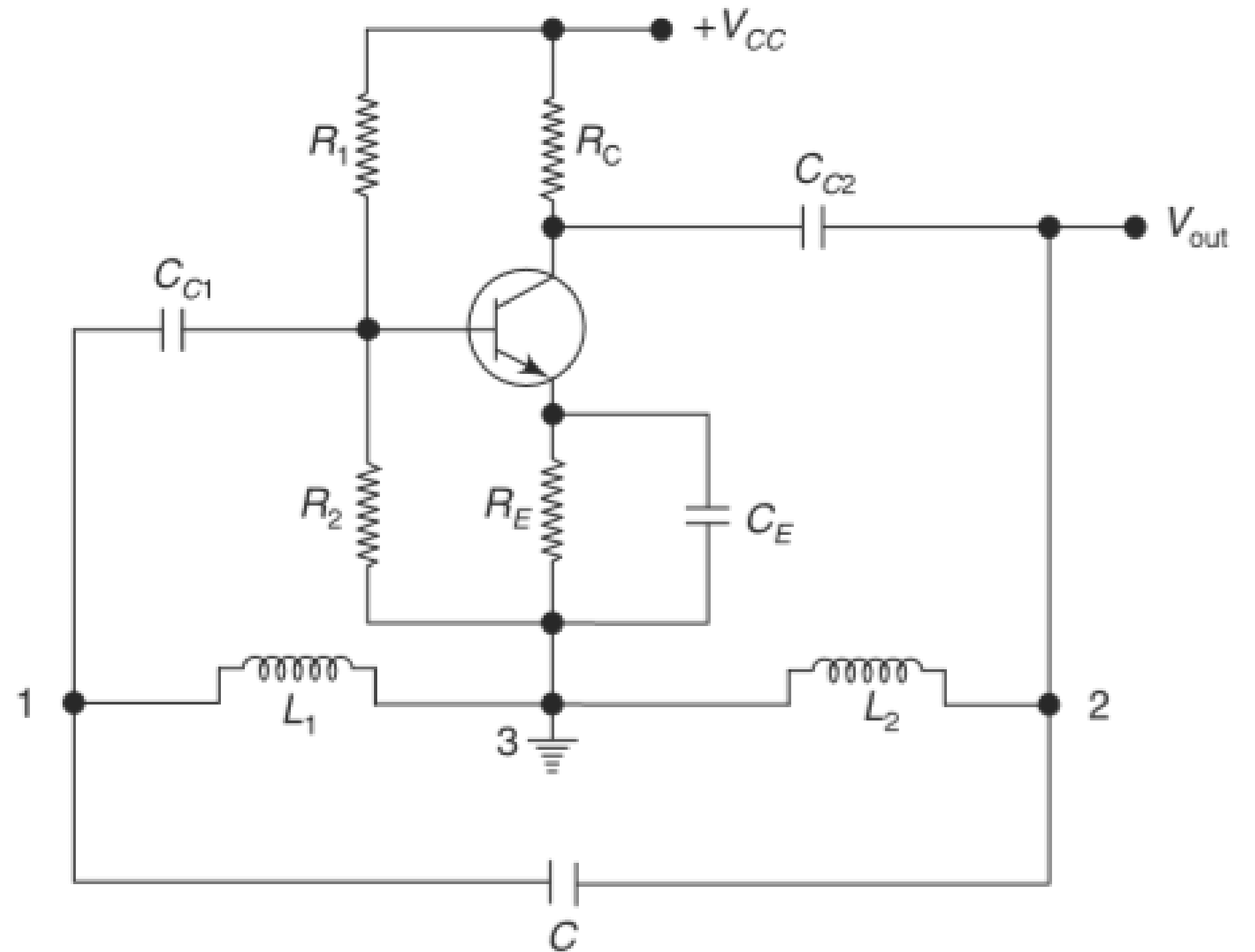




Stabilization of Amplitude



Amplitude Limiting

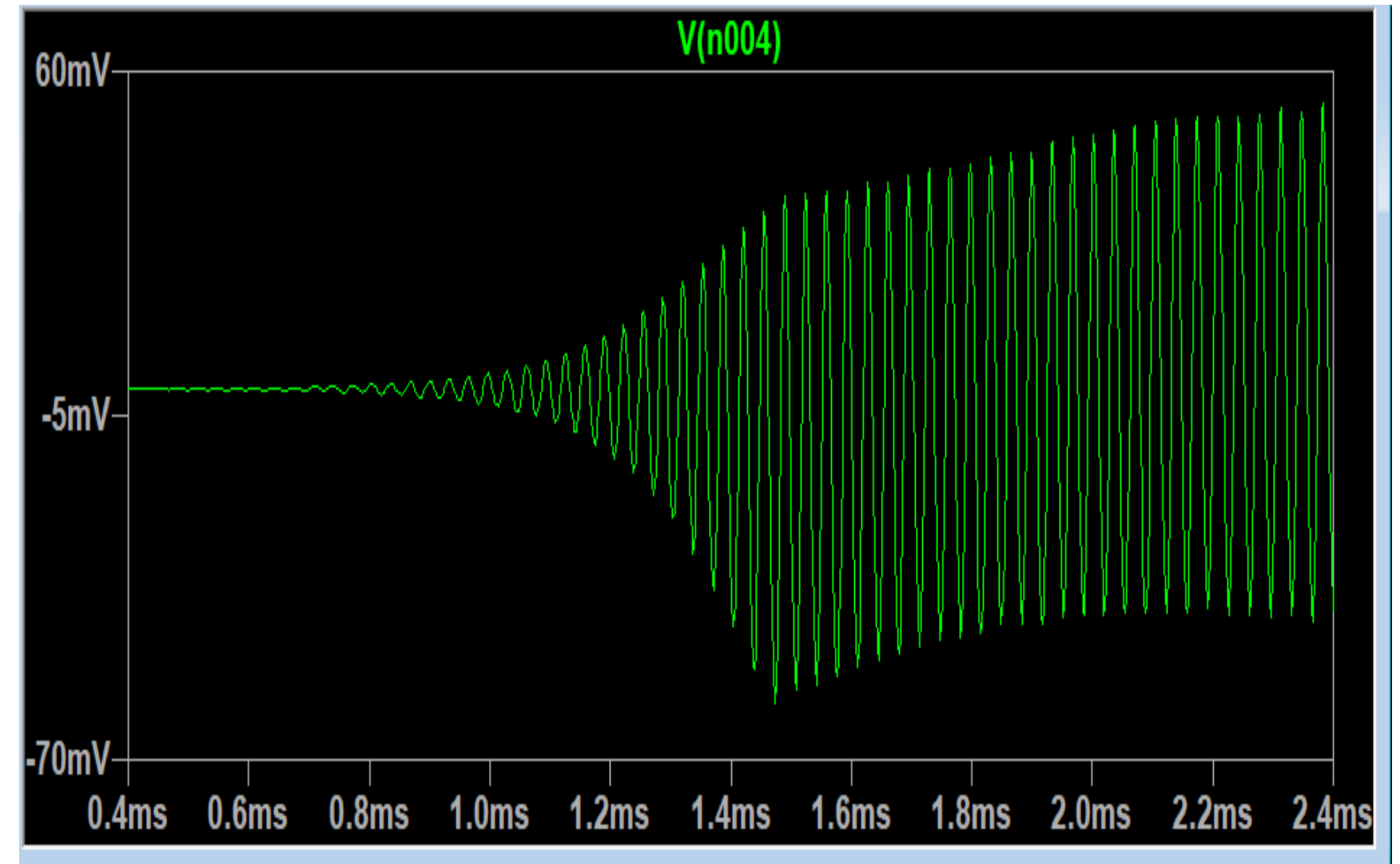




Frequency of Oscillation

$$Z_1 = j\omega L_1 + j\omega M$$

$$Z_2 = j\omega L_2 + j\omega M$$
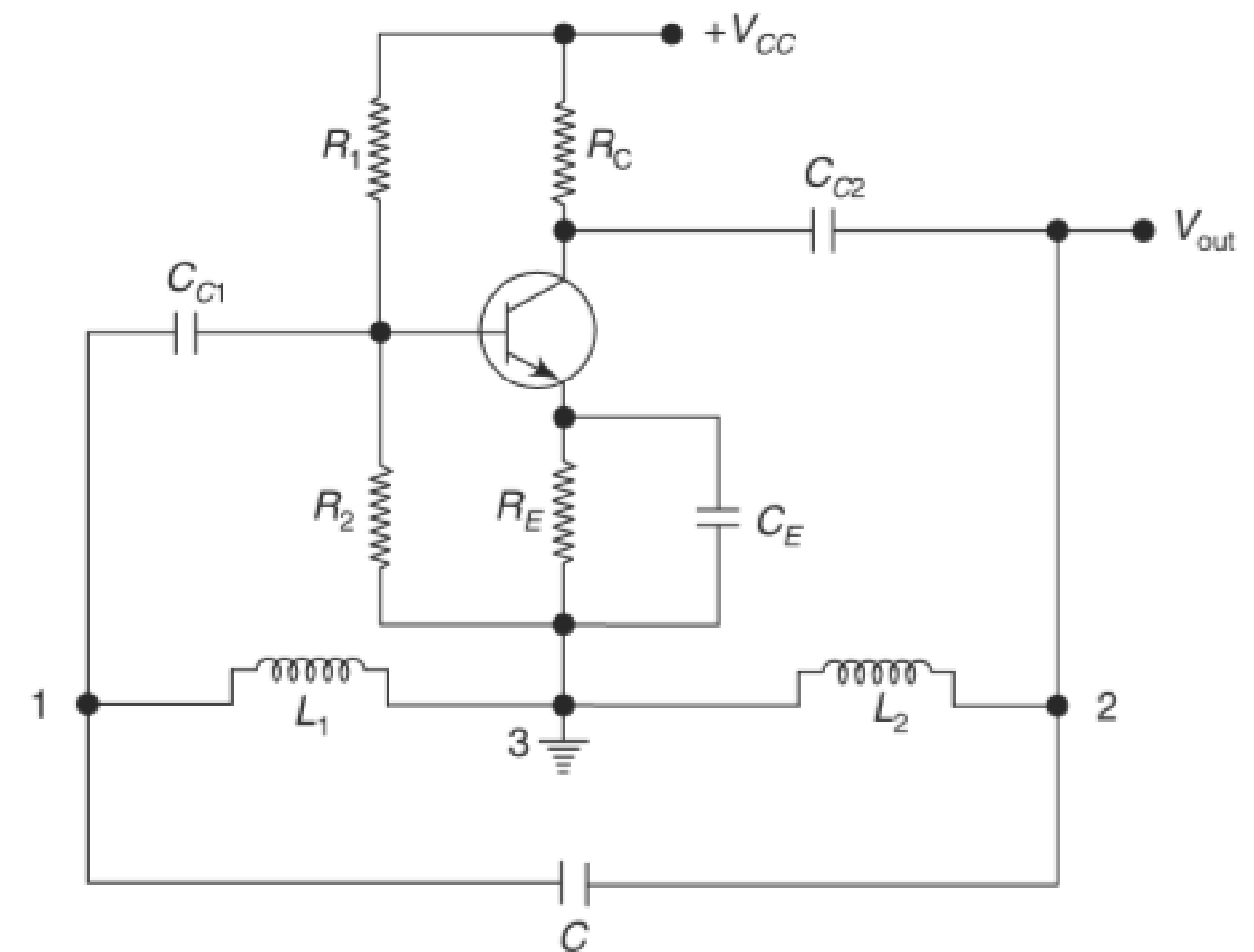
$$Z_3 = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$






Frequency of Oscillation

General Equation of Oscillation
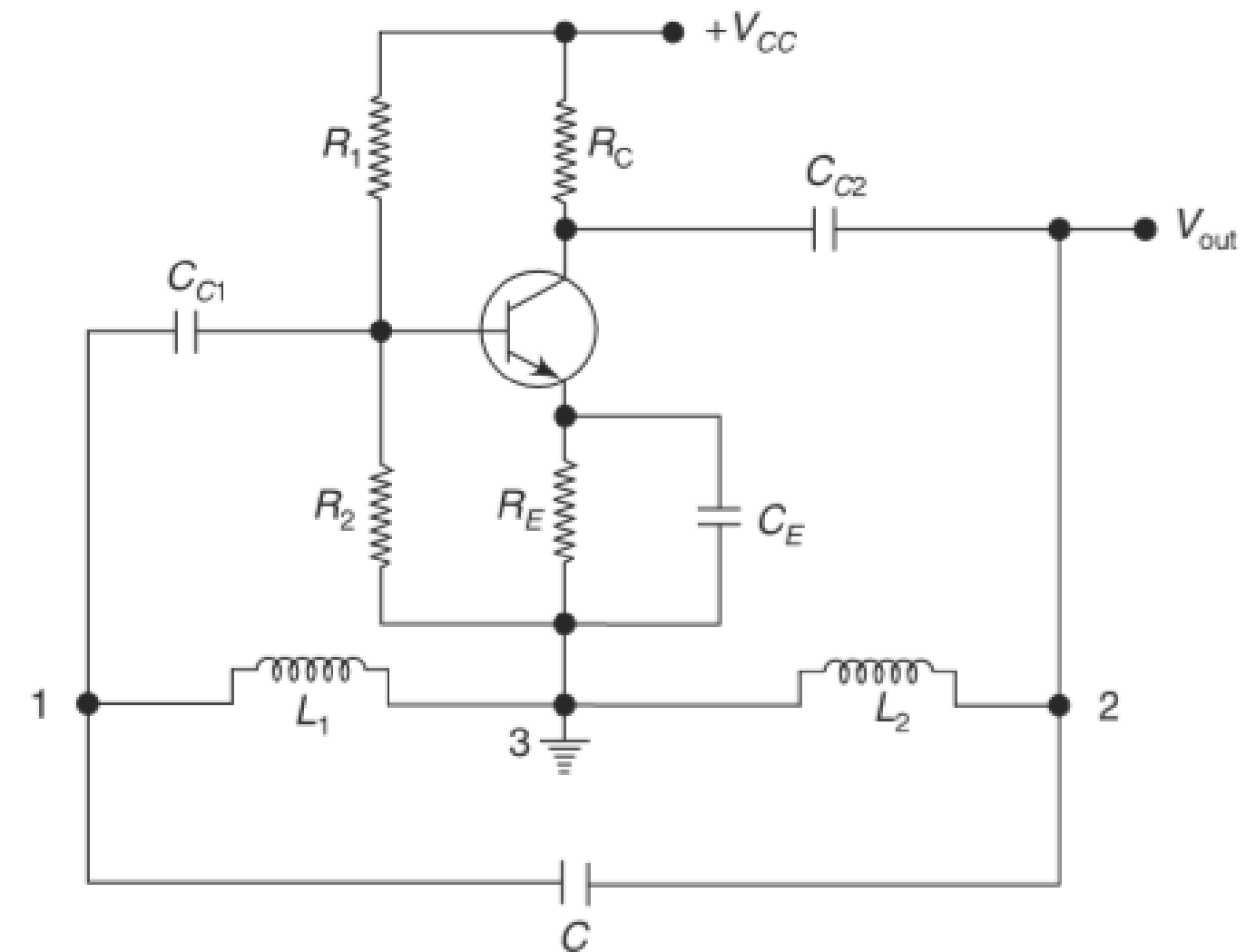
$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1Z_2(1 + h_{fe}) + Z_1Z_3 = 0$$





Frequency of Oscillation


$$j\omega h_{ie} \left[L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] - \omega^2 (L_1 + M) \left[(L_2 + M) (1 + h_{fe}) - \frac{1}{\omega^2 C} \right] = 0$$



Frequency of Oscillation



$$f_o = \frac{\omega_o}{2\pi}$$

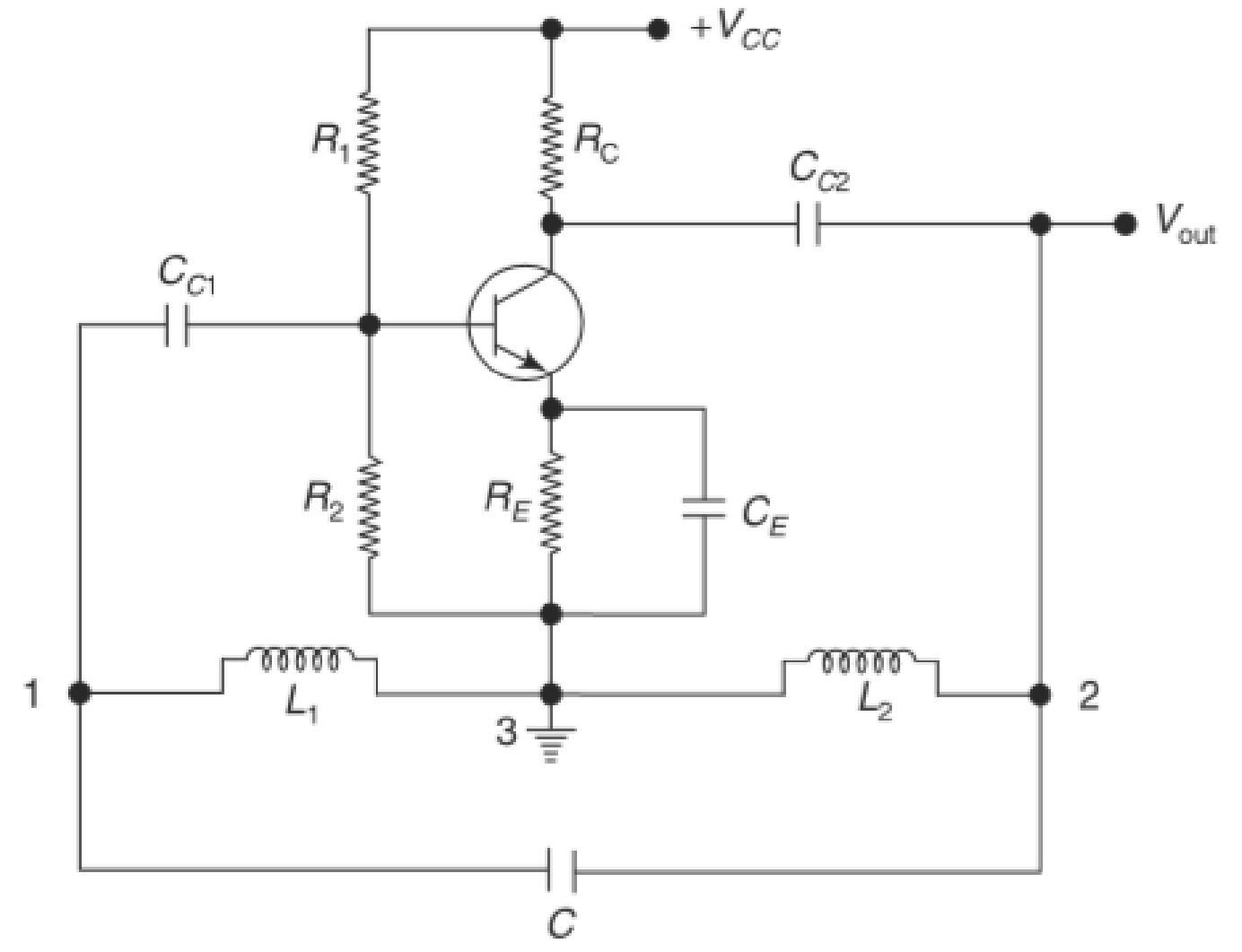




Frequency of Oscillation



For calculating the frequency of oscillation

Equate the imaginary part of the basic equation to zero
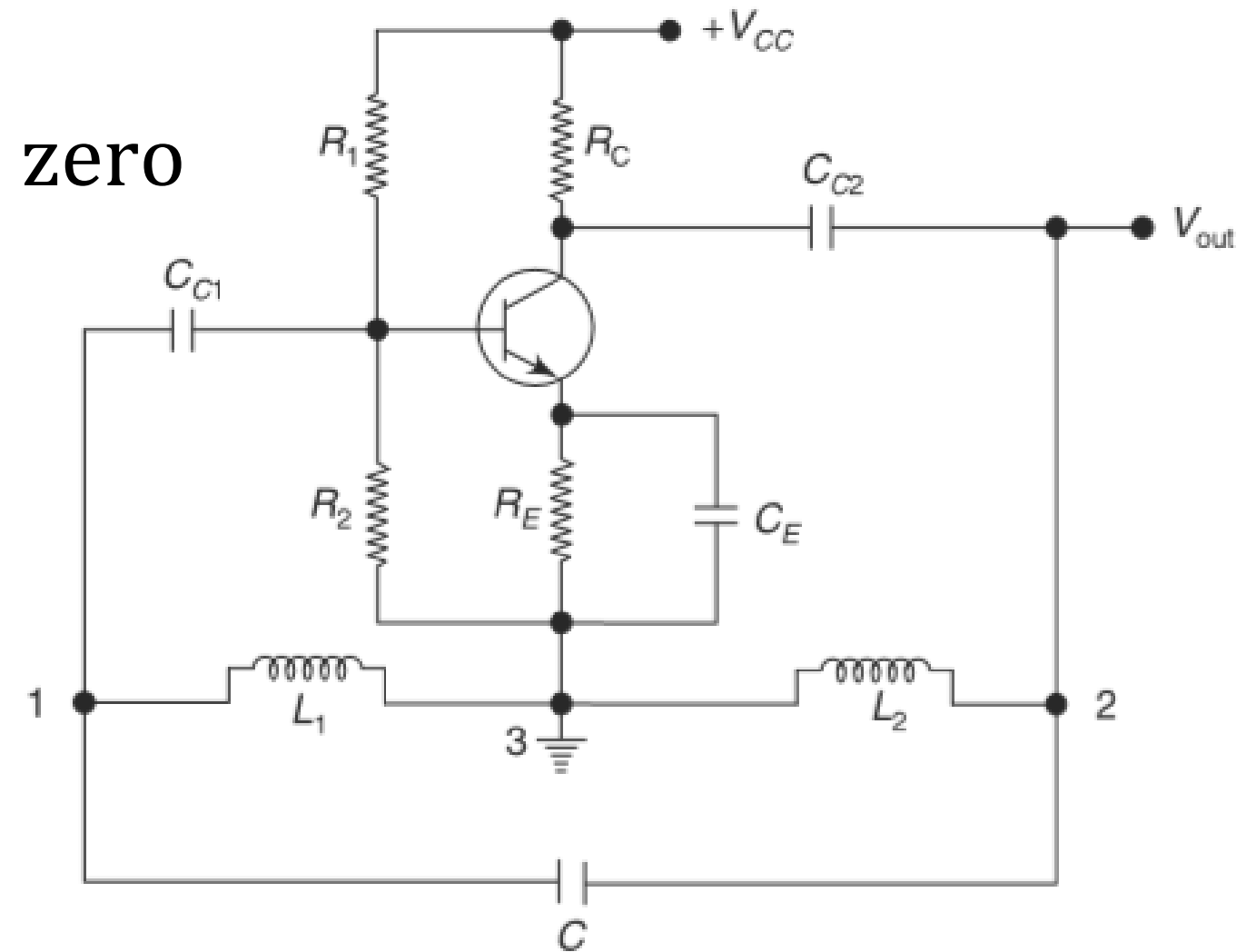
$$\left[L_1 + L_2 + 2M - \frac{1}{\omega_o^2 C} \right] = 0$$






Frequency of Oscillation


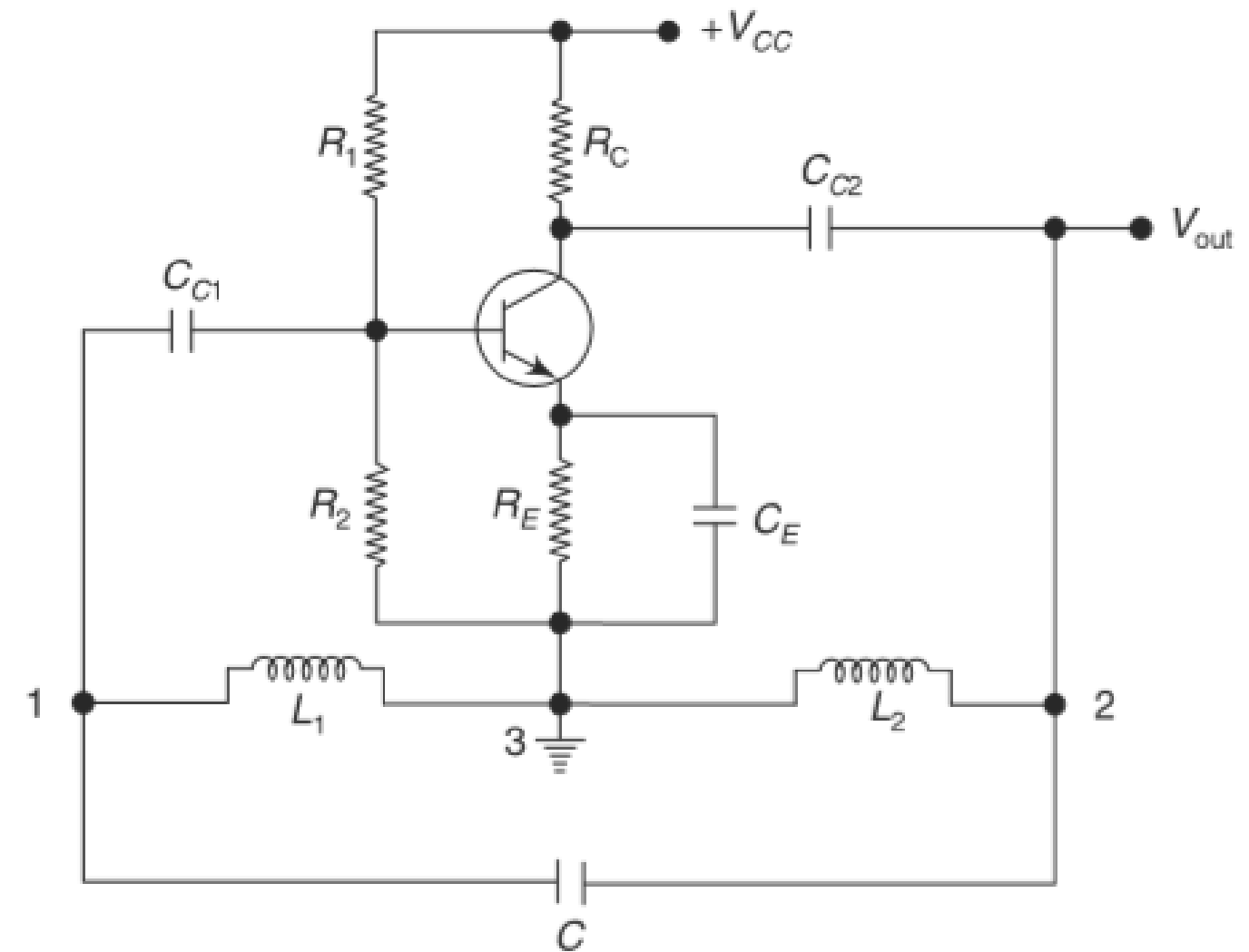
$$f_o = \frac{\omega_o}{2\pi} = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2M)C}}$$






Conditions for Maintenance of Oscillation



For obtaining the conditions for maintenance of oscillation equate the real part of the basic equation to zero
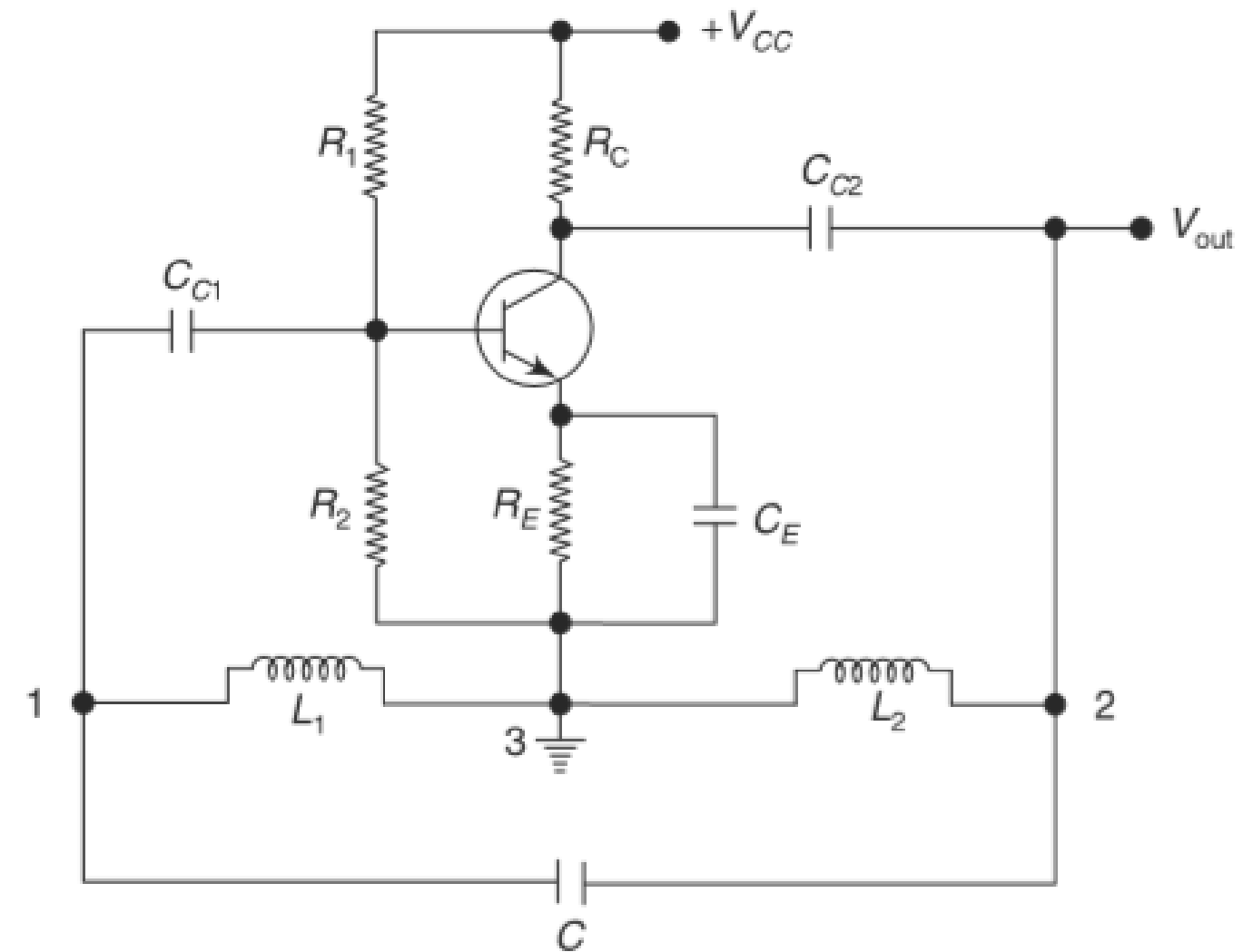
$$\left[(L_2 + M) (1 + h_{fe}) - \frac{1}{\omega_o^2 C} \right] = 0$$






Conditions for Maintenance of Oscillation



$$h_{fe} = \frac{L_1 + M}{L_2 + M}$$

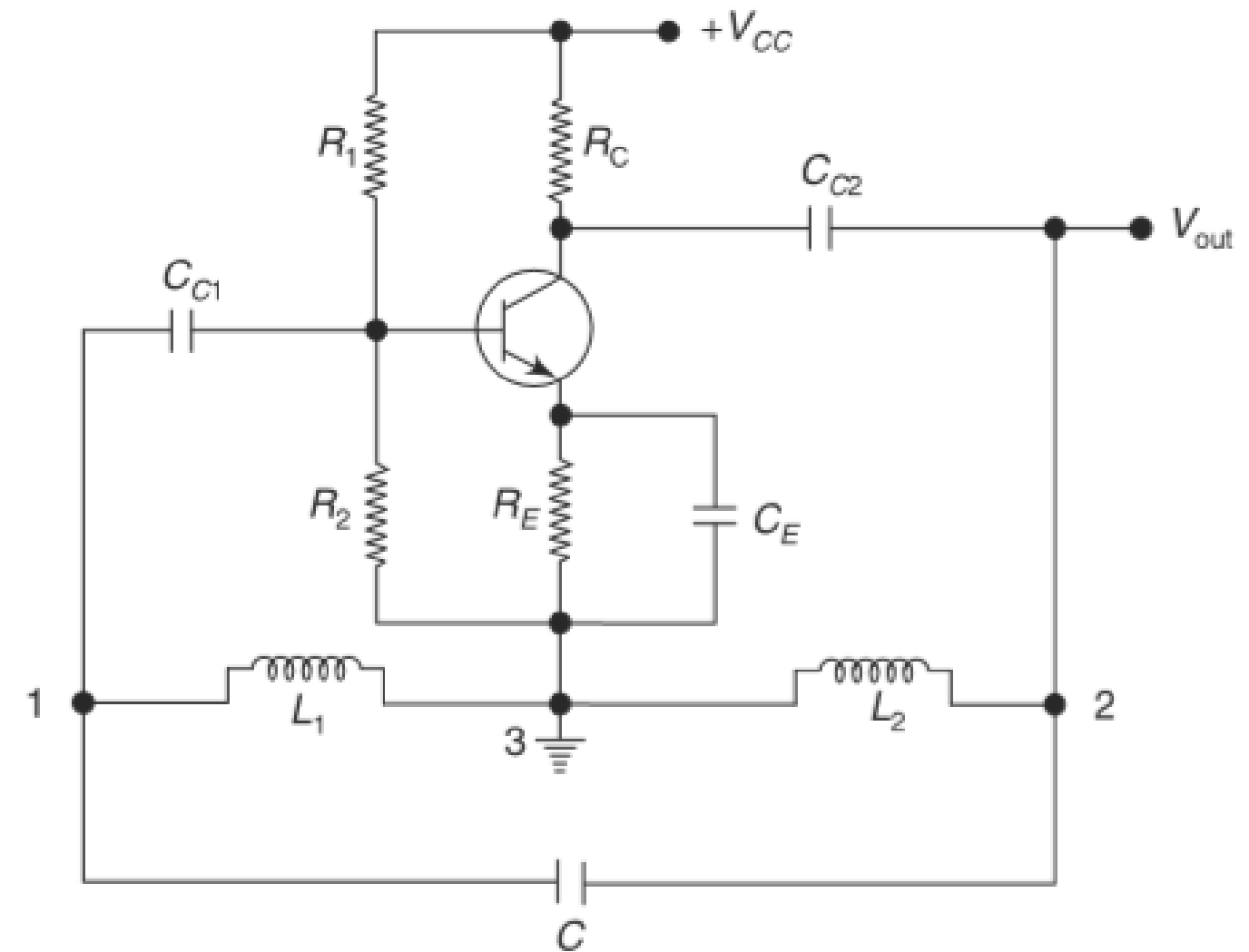



Derivation Basic eqn

$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0 \quad \text{--- (1)}$$
$$Z_1 = X_{L1} + X_{LM}$$
$$Z_1 = j\omega L_1 + j\omega M$$
$$Z_2 = j\omega L_2 + j\omega M$$
$$Z_3 = X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

Sub in (1)

$$h_{ie}(j\omega L_1 + j\omega M + j\omega L_2 + j\omega M - \frac{j}{\omega C}) + (j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M)(1 + h_{fe}) + (j\omega L_1 + j\omega M)(\frac{-j}{\omega C}) = 0$$
$$j\omega h_{ie}(L_1 + L_2 + 2M - \frac{1}{\omega^2 C}) + j\omega(L_1 + M)j\omega(L_2 + M)(1 + h_{fe}) + j\omega(L_1 + M)(\frac{-j}{\omega C}) = 0$$
$$j\omega h_{ie}(L_1 + L_2 + 2M - \frac{1}{\omega^2 C}) - \omega^2(L_1 + M)(L_2 + M)(1 + h_{fe}) + (L_1 + M)(\frac{1}{\omega^2 C}) = 0$$



Derivation



$$j\omega hie(L_1 + L_2 + 2M - \frac{1}{\omega^2 C}) - \omega^2(L_1 + M)(L_2 + M)(1 + hfe) + (L_1 + M)(\frac{1}{\omega^2 C}) = 0$$
$$j\omega hie[L_1 + L_2 + 2M - \frac{1}{\omega^2 C}] - \omega^2(L_1 + M)[(L_2 + M)(1 + hfe) - \frac{1}{\omega^2 C}] = 0$$

To cal. the freq. of operation
Equate the imag. term to zero

$$j\omega hie[L_1 + L_2 + 2M - \frac{1}{\omega^2 C}] = 0$$
$$L_1 + L_2 + 2M - \frac{1}{\omega^2 C} = 0$$
$$L_1 + L_2 + 2M = \frac{1}{\omega^2 C}$$
$$\omega^2 C = \frac{1}{L_1 + L_2 + 2M}$$
$$\omega^2 = \frac{1}{C[L_1 + L_2 + 2M]} \rightarrow \textcircled{1}$$

$\omega = 2\pi f$

$$f = \frac{1}{2\pi \sqrt{C[L_1 + L_2 + 2M]}}$$



Derivation



conditions for maintenance
of oscillation

Equate Real Part = 0

$$-\omega^2(L_1+M) \left[(L_2+M)(1+h_{fe}) - \frac{1}{\omega^2 C} \right] = 0$$
$$(L_2+M)(1+h_{fe}) = \frac{1}{\omega^2 C}$$
$$\omega^2 C = \frac{1}{(L_2+M)(1+h_{fe})} \rightarrow (2)$$

$$f = \frac{1}{2\pi \sqrt{C \left[(L_2+M)(1+h_{fe}) \right]}}$$

Sub (2) in (1).

$$\omega^2 C = \frac{1}{L_1 + L_2 + 2M}$$
$$\frac{1}{(L_2+M)(1+h_{fe})} = \frac{1}{L_1 + L_2 + 2M}$$



Derivation




$$\frac{(L_2 + M)(1 + hfe)}{[L_1 + L_2 + 2M]} = 1$$
$$\frac{(L_2 + M)(1 + hfe)}{[L_1 + M + L_2 + M]} = 1$$
$$\frac{[L_1 + M + L_2 + M]}{[L_2 + M][1 + hfe]} = 1$$
$$\frac{[L_1 + M] + [L_2 + M]}{[L_2 + M][1 + hfe]} = 1$$
$$\frac{[L_1 + M]}{[L_2 + M][1 + hfe]} + \frac{1}{[1 + hfe]} = 1$$
$$\frac{1}{(1 + hfe)} \left[\frac{L_1 + M}{L_2 + M} + 1 \right] = 1$$
$$\frac{L_1 + M}{L_2 + M} + 1 = 1 + hfe$$

$\frac{L_1 + M}{L_2 + M} = hfe$

 \rightarrow condition for maintenance of oscillation



Colpitts Oscillator

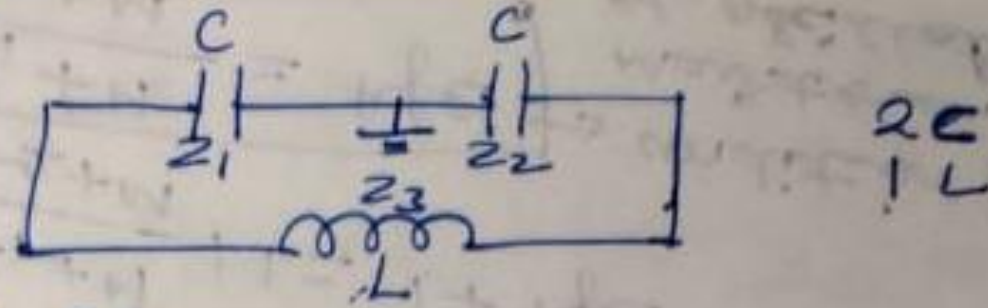

Basic equ

$$h_{ie}(Z_1 + Z_2 + Z_3) + (Z_1 Z_2)(1 + h_{fe}) + Z_1 Z_3 = 0$$

$$Z_1 = X_{C1} = \frac{1}{j\omega C_1} = \frac{-j}{\omega C_1}$$

$$Z_2 = X_{C2} = \frac{1}{j\omega C_2} = \frac{-j}{\omega C_2}$$

$$Z_3 = X_L = j\omega L$$

$$h_{ie} \left(\frac{-j}{\omega C_1} + \frac{-j}{\omega C_2} + j\omega L \right) + \left(\frac{-j}{\omega C_1} \right) \left(\frac{-j}{\omega C_2} \right) (1 + h_{fe})$$

$$+ \left(\frac{-j}{\omega C_1} \right) (j\omega L) = 0$$

$$j\omega h_{ie} \left(\frac{-1}{\omega^2 C_1} - \frac{1}{\omega^2 C_2} + L \right) - \frac{(1 + h_{fe})}{\omega^2 C_1 C_2}$$

$$+ \frac{L}{C_1} = 0$$



Derivation



$$\left[-j h_{ie} \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) + \left(\frac{(1+h_{fe})}{\omega^2 C_1 C_2} - \frac{L}{C_1} \right) \right] = 0$$

→ Equate imag part to zero

$$h_{ie} j \omega \left(-\frac{1}{\omega^2 C_1} - \frac{1}{\omega^2 C_2} + L \right) = 0$$
$$-\frac{1}{\omega^2 C_1} - \frac{1}{\omega^2 C_2} + L = 0$$
$$L = \frac{1}{\omega^2 C_1} + \frac{1}{\omega^2 C_2}$$
$$L = \frac{1}{\omega^2} \left[\frac{1}{C_1} + \frac{1}{C_2} \right]$$
$$\omega^2 = \frac{1}{L} \left[\frac{1}{C_1} + \frac{1}{C_2} \right] \rightarrow \text{①}$$

$\omega = 2\pi f$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left[\frac{1}{C_1} + \frac{1}{C_2} \right]}$$



Derivation



$$f = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{LC_1C_2}}$$

\rightarrow f depends only on C_1, C_2 & L , 3 elements belong to the circuit.
(e) f is not on the amplifier (e) transistor

conditions for maintenance of oscillation
Equate real part to zero

$$-\frac{(1+hfe)}{\omega^2 C_1 C_2} + \frac{L}{C_1} = 0$$
$$\frac{L}{C_1} = \frac{1+hfe}{\omega^2 C_1 C_2}$$
$$\omega^2 = \frac{(1+hfe)}{LC_2} \rightarrow \textcircled{2}$$
$$f = \frac{1}{2\pi} \sqrt{\frac{(1+hfe)}{LC_2}}$$



Derivation



Sub (3) in (1)

$$\frac{(1 + h_{fe})}{LC_2} = \frac{1}{L} \left[\frac{1}{C_1} + \frac{1}{C_2} \right]$$
$$\frac{1 + h_{fe}}{C_2} = \frac{C_1 + C_2}{C_1 C_2}$$
$$1 + h_{fe} = \frac{C_1 + C_2}{C_1}$$
$$1 + h_{fe} = 1 + \frac{C_2}{C_1}$$

$$h_{fe} = \frac{C_2}{C_1}$$

So, a circuit



Assessment 1



List the advantages and disadvantages of Hartley oscillator





References



Electronic Devices and Circuits By Salivahanan

Thank You