
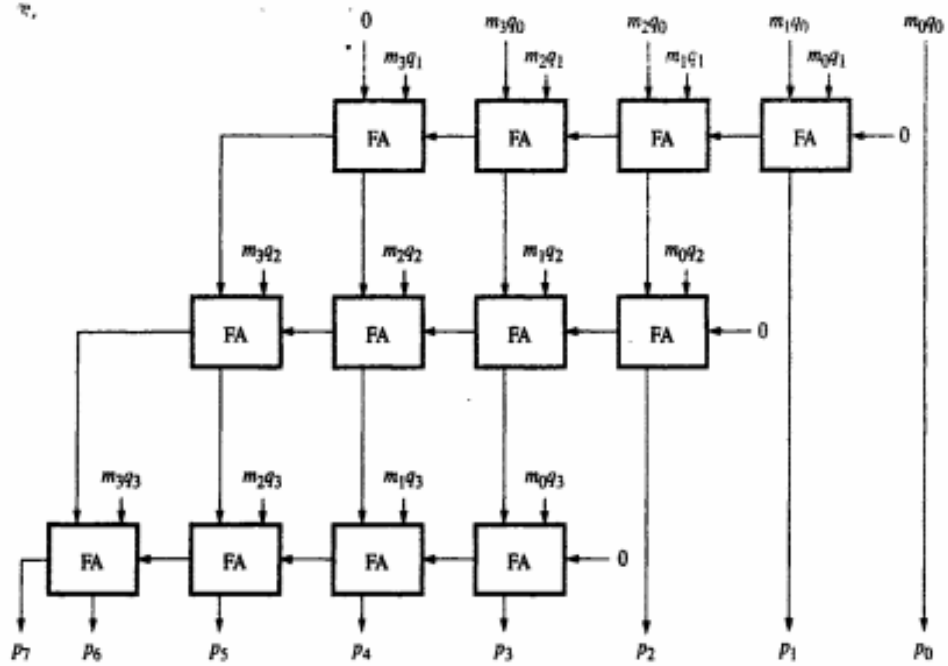


## Carry-Save Addition of Summands

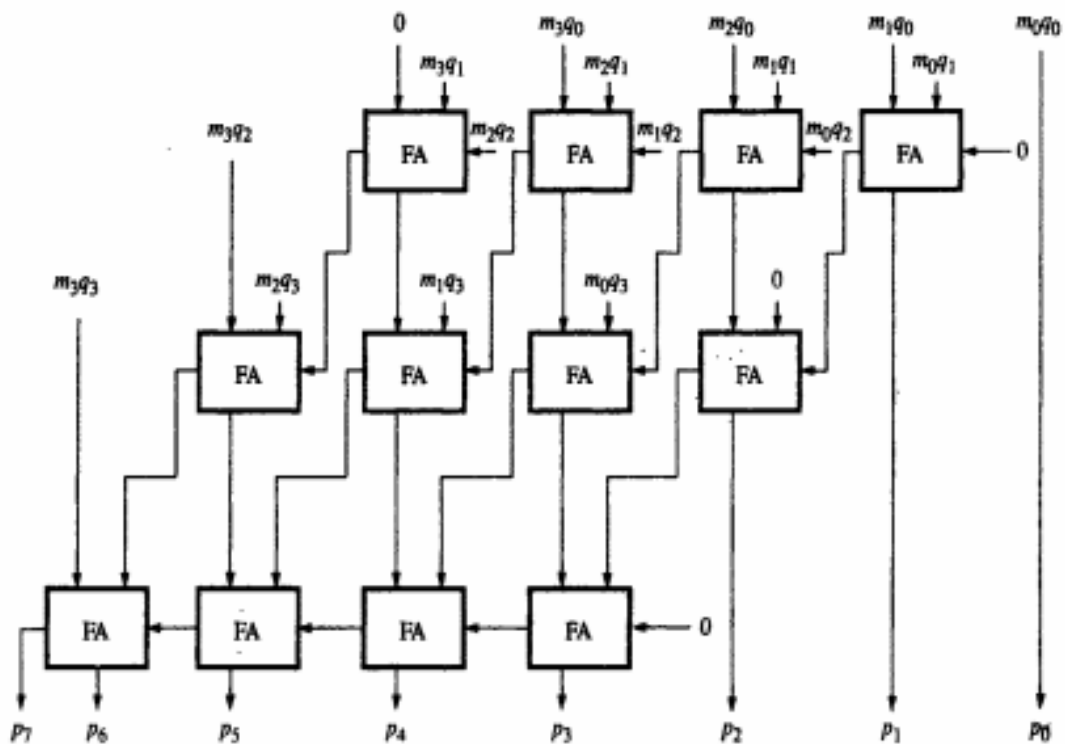

(a) Ripple-carry array (Figure 6.6 structure)




(b) Carry-save array

Figure 6.16 Ripple-carry and carry-save arrays for the multiplication operation  $M \times Q = P$  for 4-bit operands.

	1 0 1 1 0 1	(45)	M
x	1 1 1 1 1 1	(63)	Q
	1 0 1 1 0 1	A	
	1 0 1 1 0 1	B	
	1 0 1 1 0 1	C	
	1 0 1 1 0 1	D	
	1 0 1 1 0 1	E	
1 0 1 1 0	1	F	
1 0 1 1 0 0 0 1 0 0 1 1	(2,835)	Product	

**Figure 6.17** A multiplication example used to illustrate carry-save addition as shown in Figure 6.18.

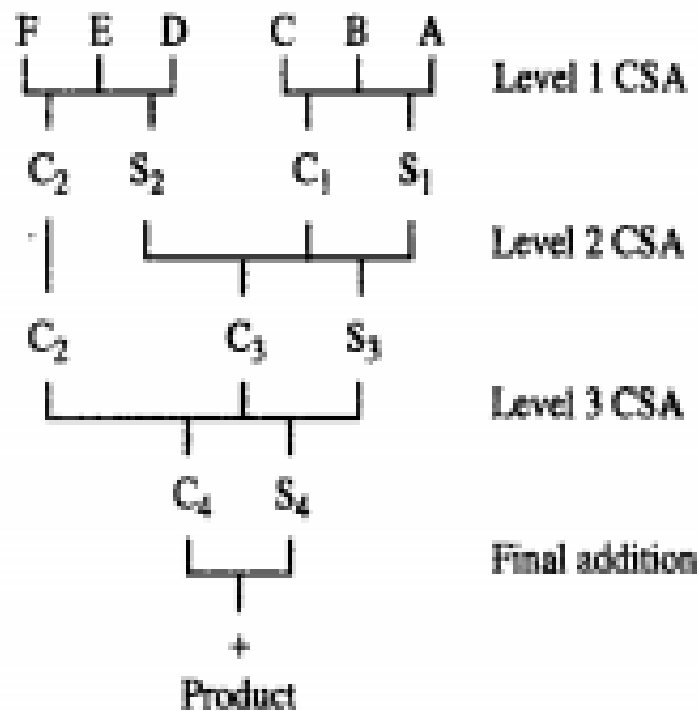

**Figure 6.19** Schematic representation of the carry-save addition operations in Figure 6.18.

