



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)



COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

COURSE NAME: 19EEB201 DC Machines and Transformers

II YEAR / III SEMESTER

Unit 3 – Testing of DC Motor

Topic 3: Swinburne's Test






What We'll Discuss

TOPIC OUTLINE




Swinburne's Test
Assessment

Swinburne's Test

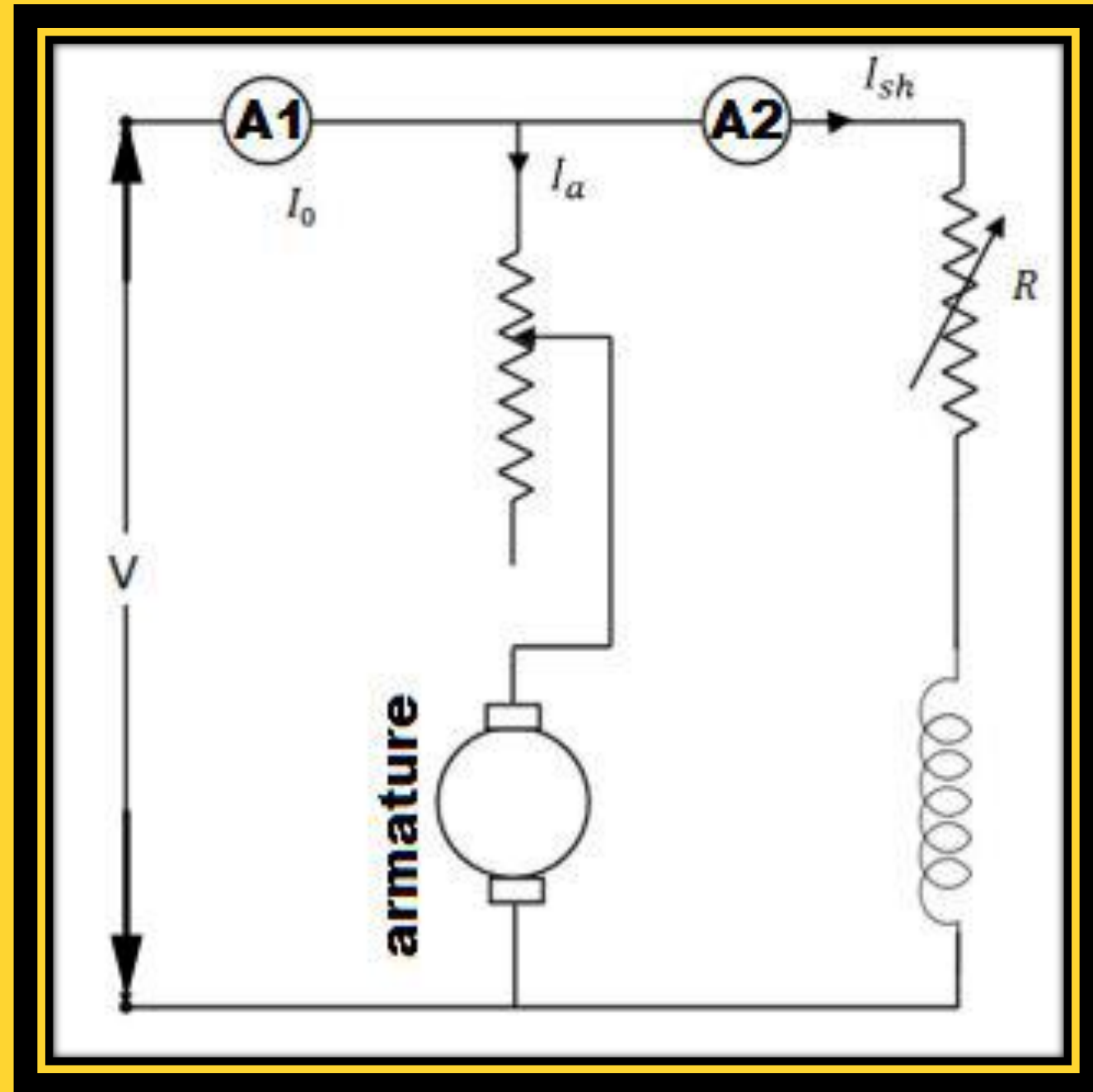

$$\text{Efficiency as a motor} = \frac{VI - (P_{cu} + W_c)}{VI}$$
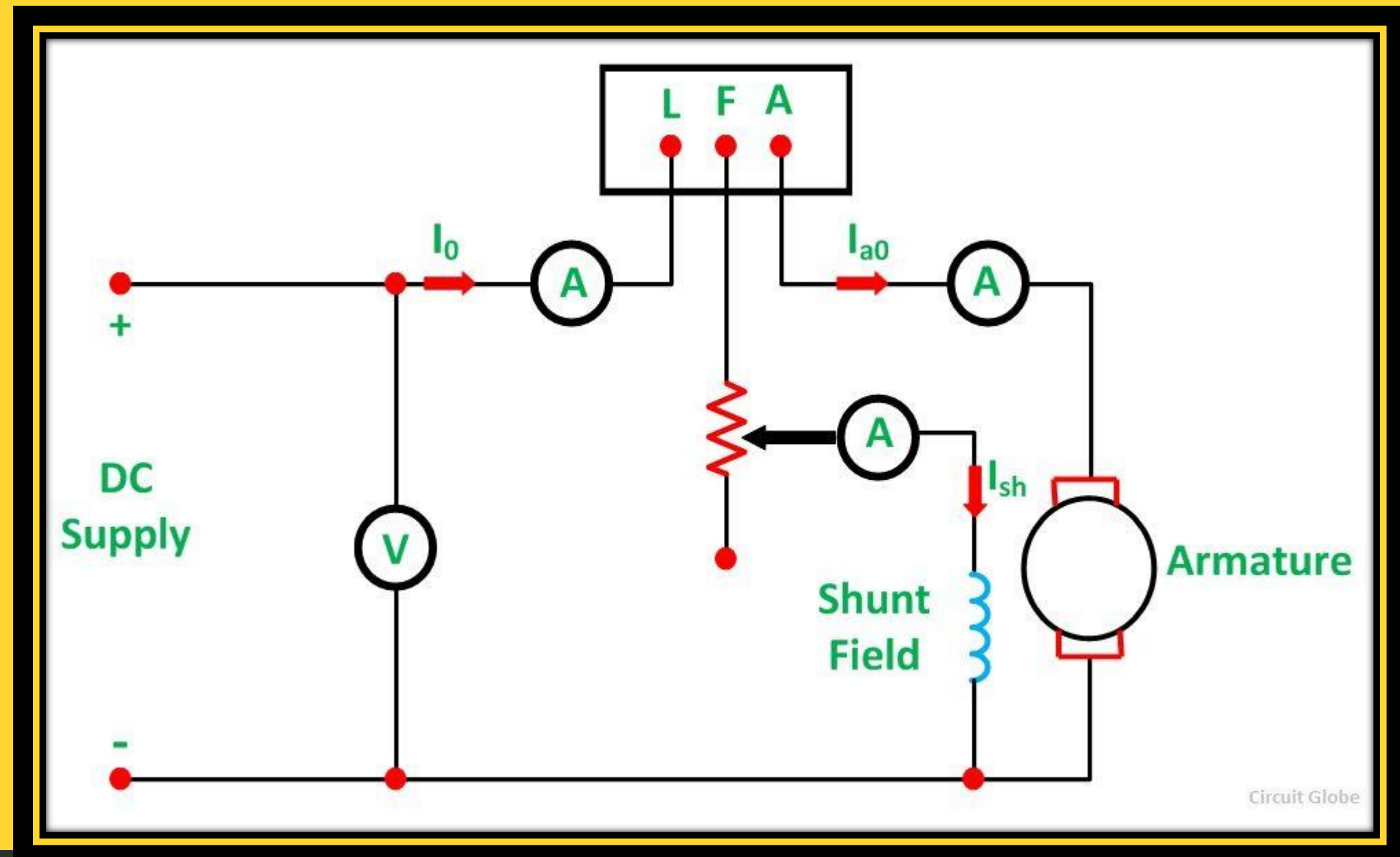
$$\text{Efficiency as a Generator} = \frac{VI - (P_{cu} + W_c)}{VI}$$





Swinburne's Test



The no-load current I_0 is measured by the ammeter A_1 whereas shunt field current I_{sh} is given by ammeter A_2 . The no-load armature current is $(I_0 - I_{sh})$ or I_{a0} .

Shunt regulator

Let, supply voltage = V no-load input = VI_0 watt

\therefore Power input to armature = $V(I_0 - I_{sh})$; Power input to shunt = VI_{sh}

No-load power input to armature supplies the following :

- (i) Iron losses in core
- (ii) friction loss
- (iii) windage loss and
- (iv) armature Cu loss, $(I_0 - I_{sh})^2 R_a$ or $I_{a0}^2 R_a$

In calculating armature Cu loss, 'hot' resistance of armature should be used. A stationary measurement of armature circuit resistance at the room-temperature of, say, 15°C is made by passing current through the armature from a low voltage d.c. supply [Fig. 31.5 (a)].

If we subtract from the total input the no-load armature Cu loss, then we get constant losses.

\therefore Constant losses $W_c = VI_0 - (I_0 - I_{sh})^2 R_a$

Knowing the constant losses of the machine, its efficiency at any other load can be determined as given below. Let I = load current at which efficiency is required.

Then, armature current is $I_a = I - I_{sh}$...if machine is motoring
 $= I + I_{sh}$...if machine is generating

Efficiency when running as a motor

Input = VI , Armature Cu loss = $I_a^2 R_a = (I - I_{sh})^2 R_a$
 Constant losses = W_c ...found above

\therefore Total losses = $(I - I_{sh})^2 R_a + W_c$; $\eta_m = \frac{\text{input} - \text{losses}}{\text{input}} = \frac{VI - (I - I_{sh})^2 R_a - W_c}{VI}$

Efficiency when running as a generator

Output = VI ; Armature, Cu loss = $(I + I_{sh})^2 R_a$; Constant loss = W_c ...found above

\therefore Total losses = $(I + I_{sh})^2 R_a + W_c$; $\eta_g = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{VI}{VI + (I + I_{sh})^2 R_a + W_c}$



Swinburne's Test



Advantages of Swinburne's test

- The biggest advantage is that the shunt machine is to be run as motor under no load condition requiring little power to be drawn from the supply.
- Based on the no load reading, efficiency can be predicted for any load current.

Disadvantages of Swinburne's test

- However, this test is not sufficient if we want to know more about its performance (effect of armature reaction, temperature rise, commutation etc.) when it is actually loaded.
- Secondly, one should have loads to absorb this power.



RECALL



1. Conduct a Swinburne's test in the laboratory and plot the results



THANK YOU