

## SNS COLLEGE OF TECHNOLOGY

## (An Autonomous Institution)

### **COIMBATORE-35**

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade **Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai** 

## **DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

## **COURSE NAME: 19EEB201 DC Machines and Transformers**

II YEAR / III SEMESTER

Unit 3 – Testing of DC Motor

Topic 4: Hopkinson's Test







# What We'll Discuss Topic outline

23.10.2022

19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE





## Hopkinson's Test Assessment





Hopkinson's Test is another useful method of testing the efficiency of a DC machine. It is a full load test and it requires two identical machines which are coupled to each other.

One of these two machines is operated as a generator to supply the mechanical power to the motor and the other is operated as a motor to drive the generator.

Hopkinson's test is also called back-to-back test or regenerative test.

23.10.2022

19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE







If there are no losses in the machine, then no external power supply would have needed. But due to the drop in the generator output voltage we need an extra voltage source to supply the proper input voltage to the motor.

Hence, the power drawn from the external supply is therefore used to overcome the internal losses of the motor-generator set. Hopkinson's test is also called regenerative test or back to back test or heat run test

The generator voltage is now made equal to the supply voltage by adjusting the shunt field resistance connected across the generator. This equality of these two voltages of generator and supply is indicated by the voltmeter as it gives a zero reading at this point connected across the switch. The machine can run at rated speed and at desired load by varying the field currents of the motor and the generator.

19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE







#### Calculation of Efficiency by Hopkinson's Test

Let, V = supply voltage of the machines. Then,

Motor input =  $V(I_1 + I_2)$ 

 $I_1$  = The current from the generator

 $I_2$  = The current from the external source

And, Generator output = VI<sub>1</sub>.....(1)

Let, both machines are operating at the same efficiency ' $\eta$ '.

Then, Output of motor =  $\eta \times input = \eta \times V(I_1 + I_2)$ 

> Input to generator = Output of the motor =  $\eta \times V(I_1 + I_2)$ *Output of generator* =  $\eta \times input = \eta \times [\eta \times V(I_1 + I_2)] = \eta^2$  $V(I_1 + I_2)$ .....(2)

From equation 1 an 2 we get,

$$VI_1 = \eta^2 V(I_1 + I_2) \text{ or } I_1 = \eta^2 (I_1 + I_2)$$

 $(I_1 + I_2 - I_4)^2 R_a$ 

I4 is the shunt field current of the motor. Shunt field copper loss in the motor will be =  $VI_4$  $(I_1 + I_3)^2 R_a$ 

I<sub>3</sub> is the shunt field current of the generator. Shunt field copper loss in the generator =  $VI_3$ Now, Power drawn from the external supply = VI<sub>2</sub> Therefore, the stray losses in both machines will be

Stray loss / machine = W/2

### 19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE

### 23.10.2022





or, 
$$\eta = \sqrt{\frac{l_1}{l_1 + l_2}}$$

Now, in case of motor, armature copper loss in the motor =

- R<sub>a</sub> is the armature resistance of both motor and generator.
- Next, in case of generator armature copper loss in generator =

  - $W = VI_2 (I_1 + I_2 I_4)^2 Ra + VI_4 + (I_1 + I_3)^2 R_a + VI_3$
- Let us assume that the stray losses will be same for both the machines. Then,



#### Efficiency of Generator

Total losses in the generator,

$$W_G = (I_1 + I_3)^2 R_a + V I_3 + rac{W}{2}$$

Generator output = VI<sub>1</sub> Then, efficiency of the generator,

$$\eta_{G} = \frac{output}{input} = \frac{output}{output + losses} = \frac{VI_{1}}{VI_{1} + W_{G}}$$

#### Efficiency of Motor

Total losses in the motor,

$$W_M = (I_1 + I_2 - I_4)^2 R_a + V I_4 + rac{W}{2}$$

Motor input = 
$$V(I_1 + I_2)$$

Then, efficiency of the motor,

$$\eta_M = \frac{output}{input} = \frac{input - losses}{input} = \frac{V(l_1 + l_2) - W_M}{V(l_1 + l_2)}$$

### 19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE

### 23.10.2022







## Advantages of Hopkinson's Test The merits of this test are...

- This test requires very small power compared to full-load power of the motor-generator coupled system. That is why it is economical. Large machines can be tested at rated load without much power consumption.
- Temperature rise and commutation can be observed and maintained in the limit because this test is done • under full load condition.
- Change in iron loss due to flux distortion can be taken into account due to the advantage of its full load ۲ condition.
- Efficiency at different loads can be determined. •

## **Disadvantages of Hopkinson's Test**

The demerits of this test are

- It is difficult to find two identical machines needed for Hopkinson's test. •
- Both machines cannot be loaded equally all the time.
- It is not possible to get separate iron losses for the two machines though they are different because of ullettheir excitations.
- It is difficult to operate the machines at rated speed because field currents vary widely. ٠

### 23.10.2022

### 19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE







## RECALL

## 1. Conduct a Hopkinsons test in the laboratory and plot the results

23.10.2022

19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE







19EEB201/DCMT/Dr.C.Ramakrishnan/ASP/EEE

23.10.2022



# THANK YOU