



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)



COIMBATORE-35

**Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai**

DEPARTMENT OF BIOMEDICAL ENGINEERING

COURSE NAME: 19EIB201/ ELECTRONIC DEVICES

II YEAR / III SEMESTER

Unit 3– Small Signal Amplifier



Topic 2: Transistor as Amplifier





DC Model and Parameters

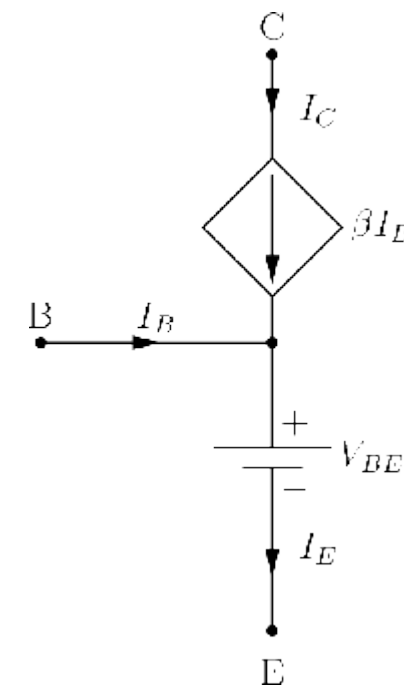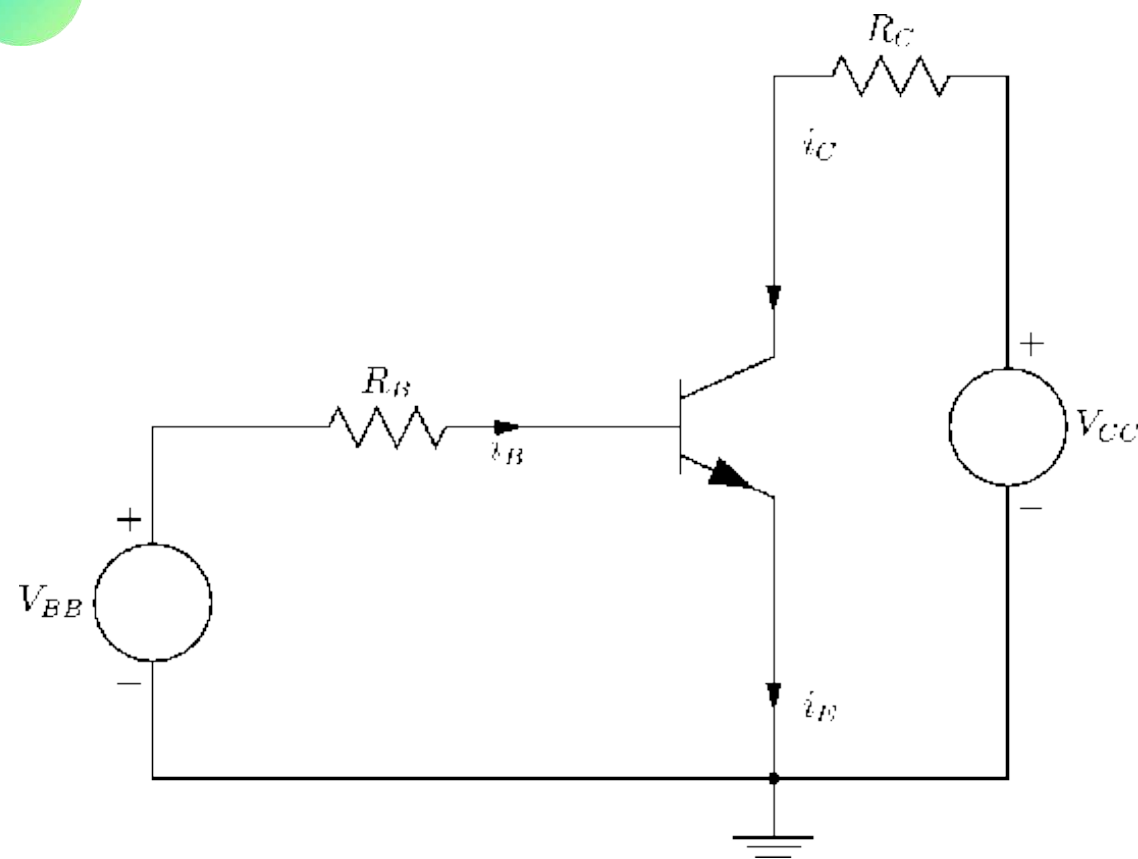- Consider the CE configuration of transistor for analysis.



$$\beta = \frac{I_C}{I_B}$$

$$\alpha = \frac{I_C}{I_E}$$


Common value would be around 0.99

$$\beta = \frac{\alpha}{1 - \alpha}$$

Common values would be around 20 to 400



AC Model Parameters

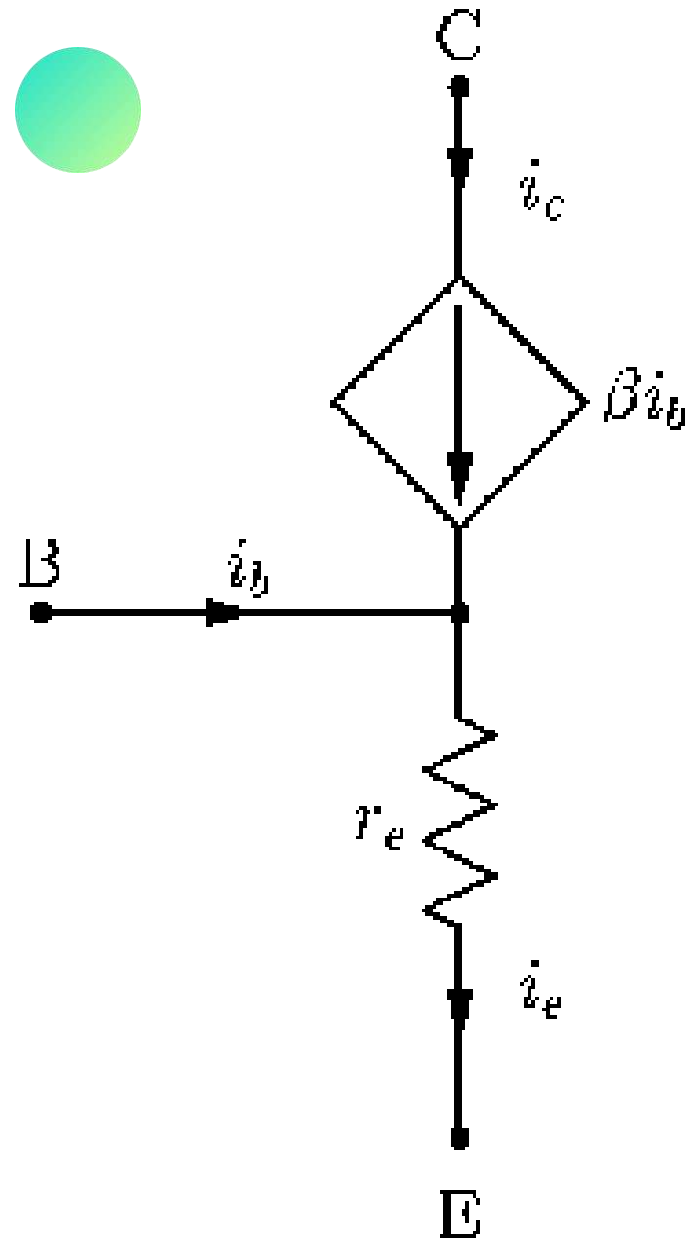


$$i_c = \beta i_b.$$

$$i_c = \alpha i_e.$$

$$i_e = i_b + i_c.$$

$$r_e = \frac{0.025}{I_E} \Omega$$

$$r_\pi = (\beta + 1)r_e$$

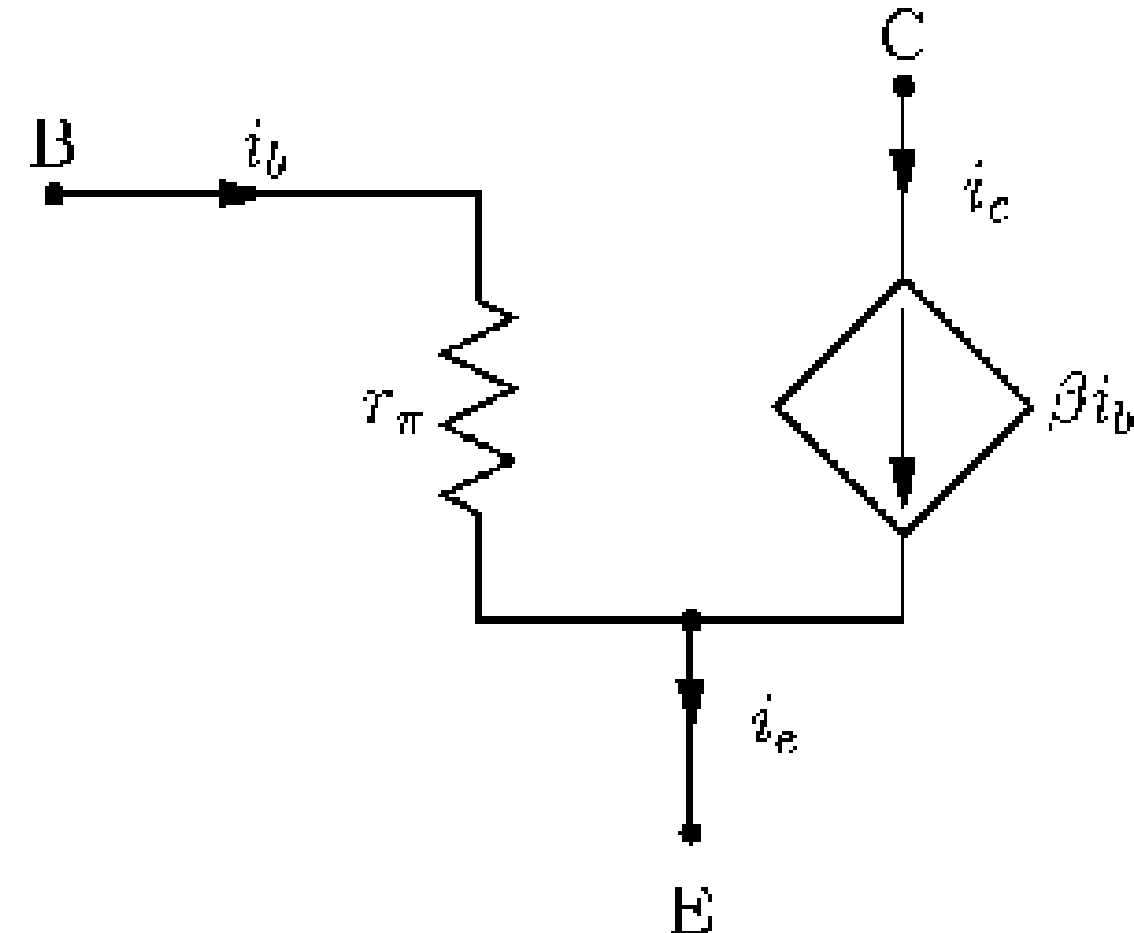



BJT Circuit – DC Analysis

$$V_{BE} = 0.7 \text{ V}, \quad I_C = \beta I_B, \quad I_E = I_B + I_C$$

The left part of the circuit gives, using KVL,


$$V_{BB} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{BB} - 0.7 \text{ V}}{R_B}$$

The right part of the circuit gives

$$V_{CC} = I_C R_C + V_{CE}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

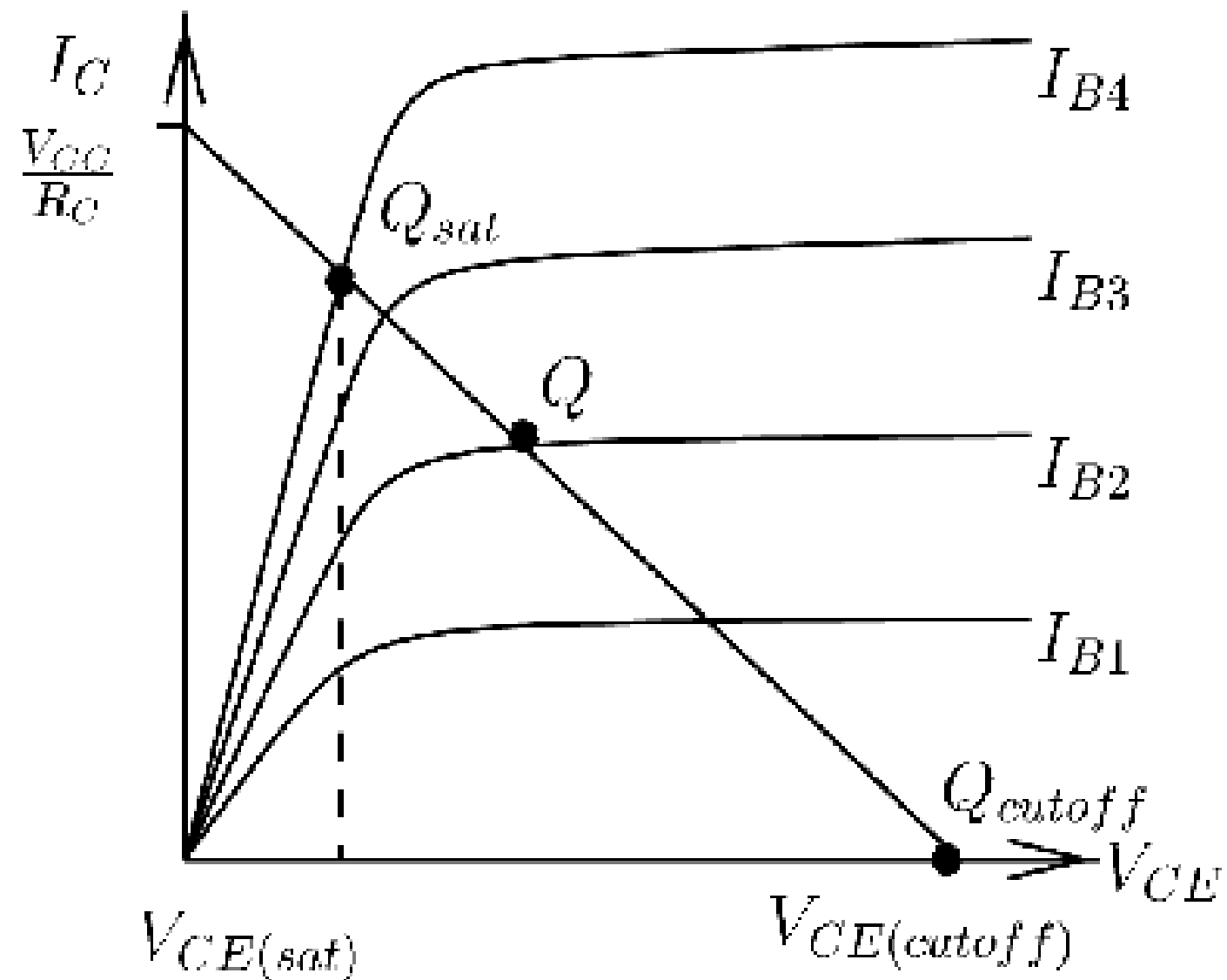


one can solve for V_{CE} to find the **quiescent** or **operating point** Q .



The Transistor as an Amplifier

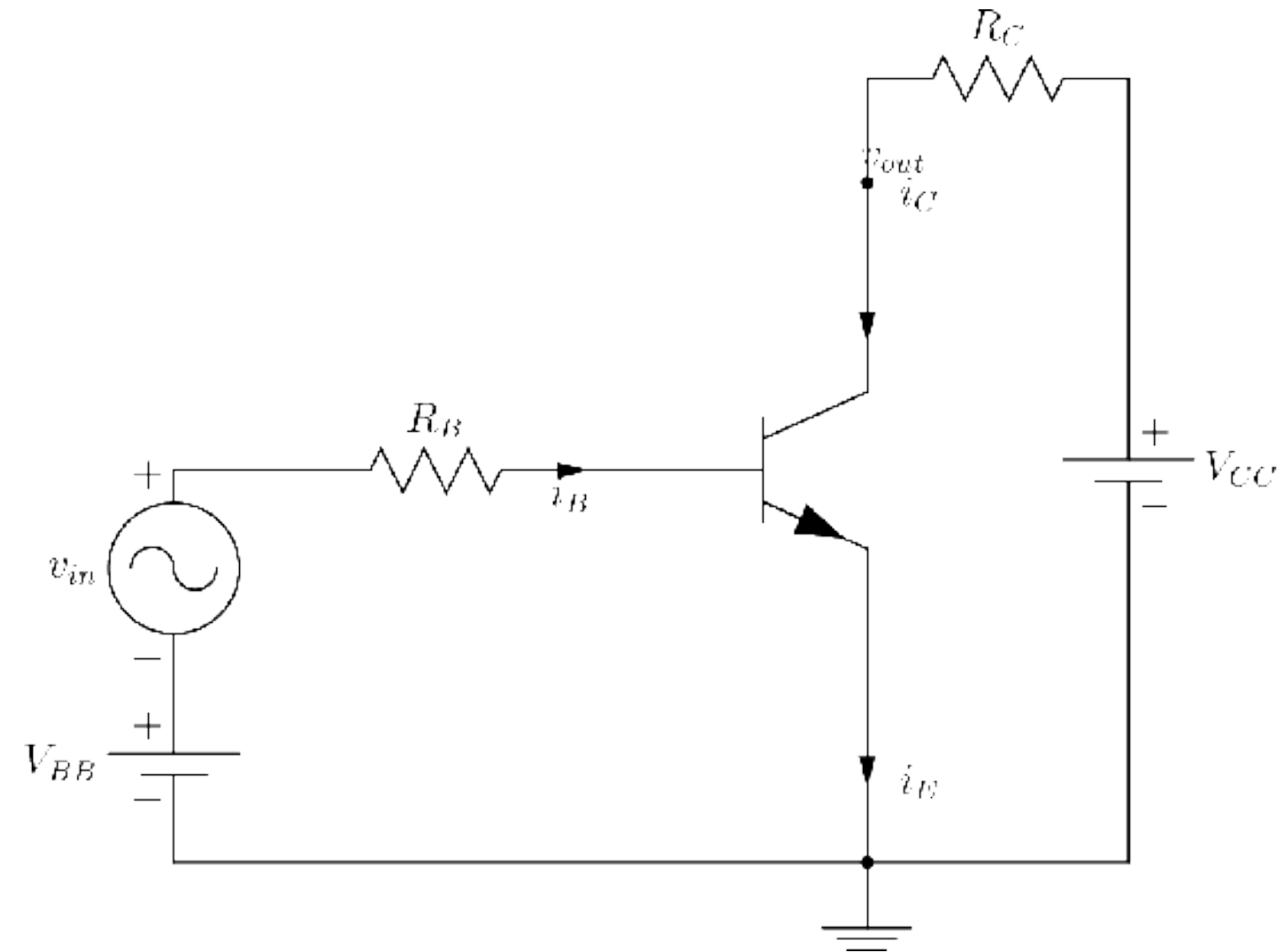
When the DC operating point Q is in the active region, the transistor can act as an amplifier to AC signals. For such purpose, Q should be set midway between Q_{sat} and Q_{cutoff} to allow for the maximum possible voltage excursions.





The Transistor as an Amplifier

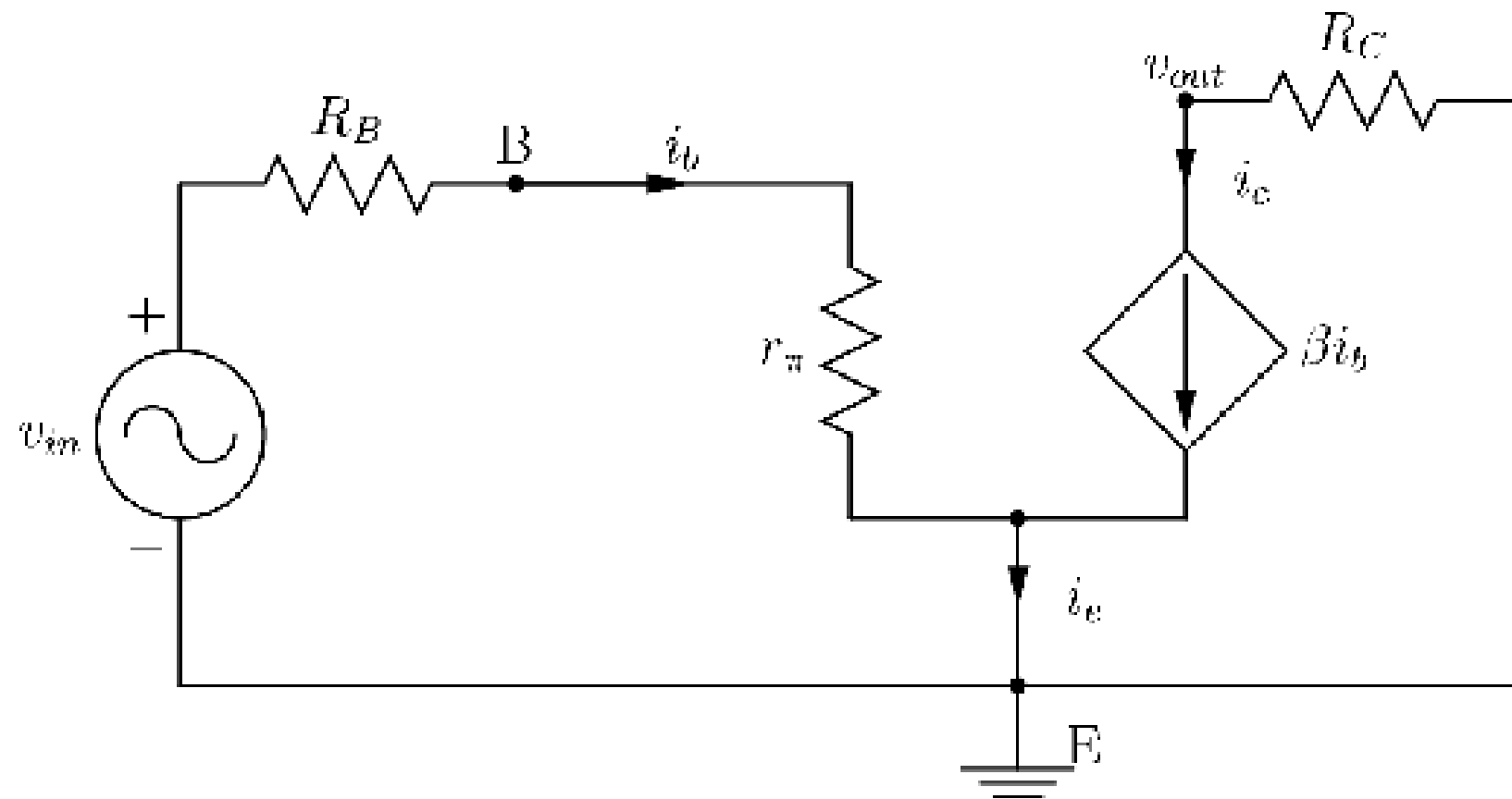It is convenient to re-draw the circuit showing only the AC signals. Here, the DC sources have been zeroed out; the AC component does not see them.



the input voltage v_{in} is amplified at the output (i.e. collector voltage v_c) by a gain factor

$$A = -\frac{\beta R_C}{R_B + (\beta + 1)r_e}$$

$$v_{in} = i_b(R_B + r_\pi)$$

$$i_b = \frac{v_{in}}{R_B + r_\pi} = \frac{v_{in}}{R_B + (\beta + 1)r_e}$$

$$v_c = -i_c R_C$$

$$v_c = -\beta R_C i_b$$

$$v_c = -\frac{\beta R_C}{R_B + (\beta + 1)r_e} v_{in}$$



SUMMARY



ASSESSMENT

Dear student,

Quiz is posted in your Google class room

Allotted time for quiz is 5 min

No of Questions is 10





sns
INSTITUTIONS

KEEP
LEARNING..
Thank u

SEE YOU IN NEXT CLASS

19EIB201/ED/Ms.B.Divya/AP/BME

09/09